

# **CG1111: Engineering Principles and Practice I**

## **Electrical Circuit Principles**



# What We'll Learn

Kirchhoff's Current Law (KCL)

Kirchhoff's Voltage Law (KVL)

Resistances in Series

Resistances in Parallel

Voltage Division Principle


Current Division Principle

# Kirchhoff's Current Law (KCL)

Sum of all currents entering a node  
=  
Sum of all currents leaving the node


- Based on **conservation of charges**
- Recall: current = rate of flow of charges
- Since charges cannot be created nor destroyed, the net flow of charges into or out of a node must be 0

$$i_1 = i_2 + i_3 + i_4$$

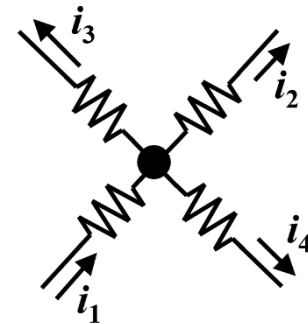
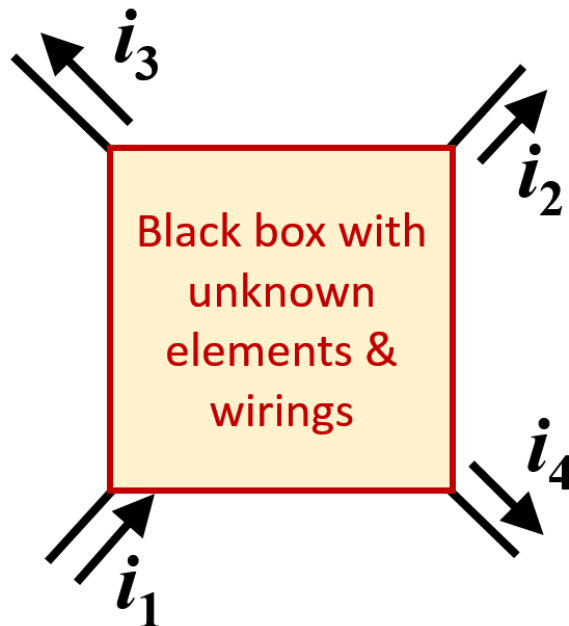
# Applying KCL to a “SuperNode”


- The “**supernode**” can be any enclosed portion of the circuit



$$i_1 = i_2 + i_3 + i_4$$

# KCL Example

- Find  $I_C$ :

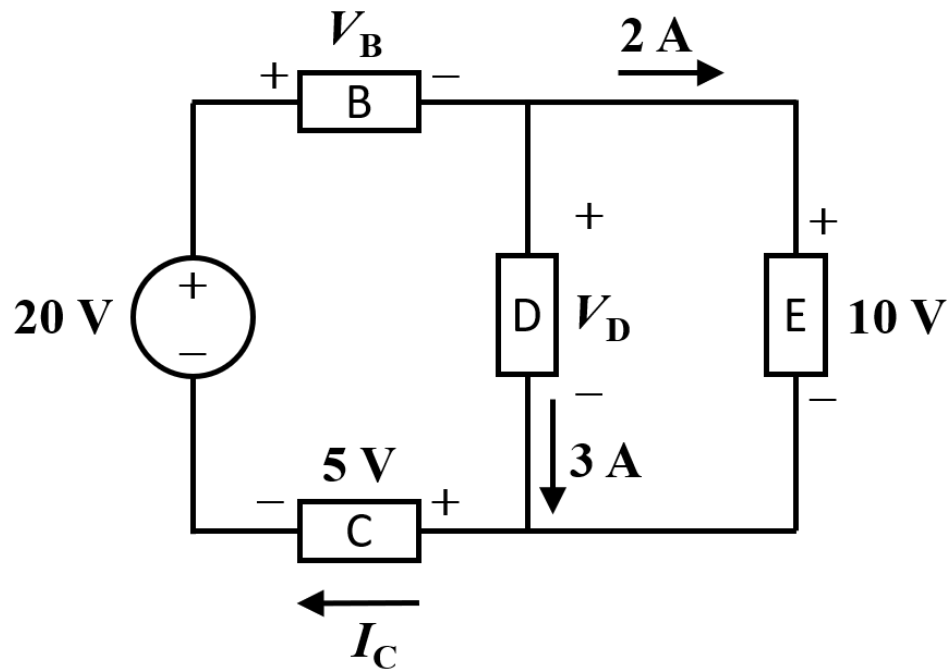


# Kirchhoff's Voltage Law (KVL)

Around any closed loop:

Sum of voltage rises  
=  
Sum of voltage falls


$$V_b = V_1 + V_2 + V_3$$

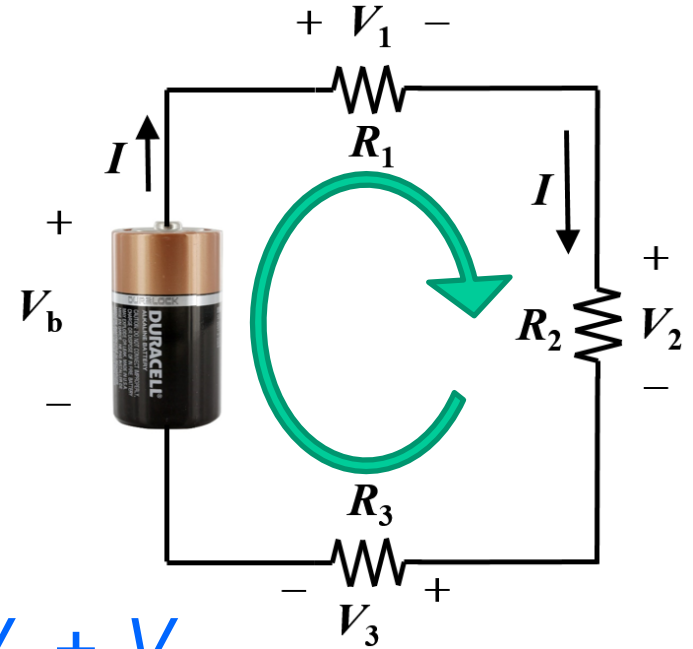

- Voltage rises when we go from negative polarity to positive polarity
- Voltage falls when we go from positive polarity to negative polarity

# KVL is Derived from the Principle of Conservation of Power


$$V_b = V_1 + V_2 + V_3$$

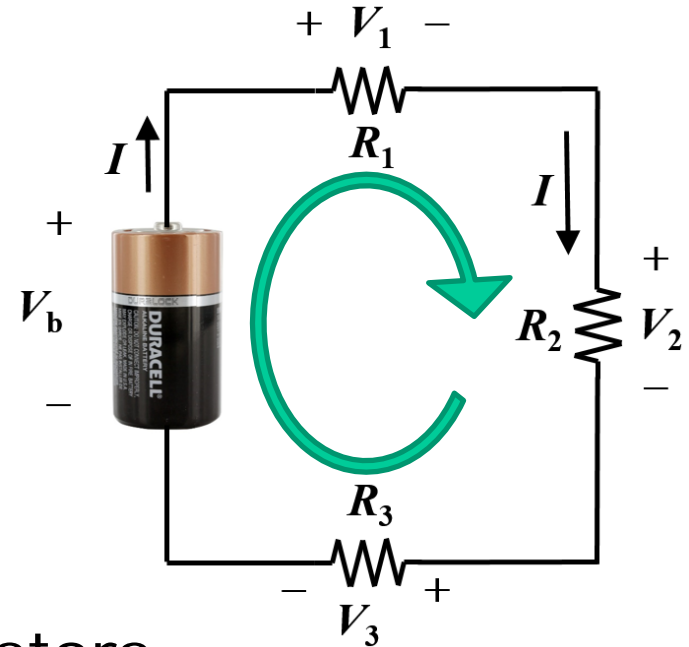

- Total power consumed by resistors  
 $= V_1 I + V_2 I + V_3 I = I (V_1 + V_2 + V_3)$
- Power supplied by battery  $= V_b I$
- By the principle of conservation of power,  
 $V_b I = I (V_1 + V_2 + V_3)$
- Hence,  $V_b = V_1 + V_2 + V_3$

# KVL Example

- Find  $V_B$  and  $V_D$ :

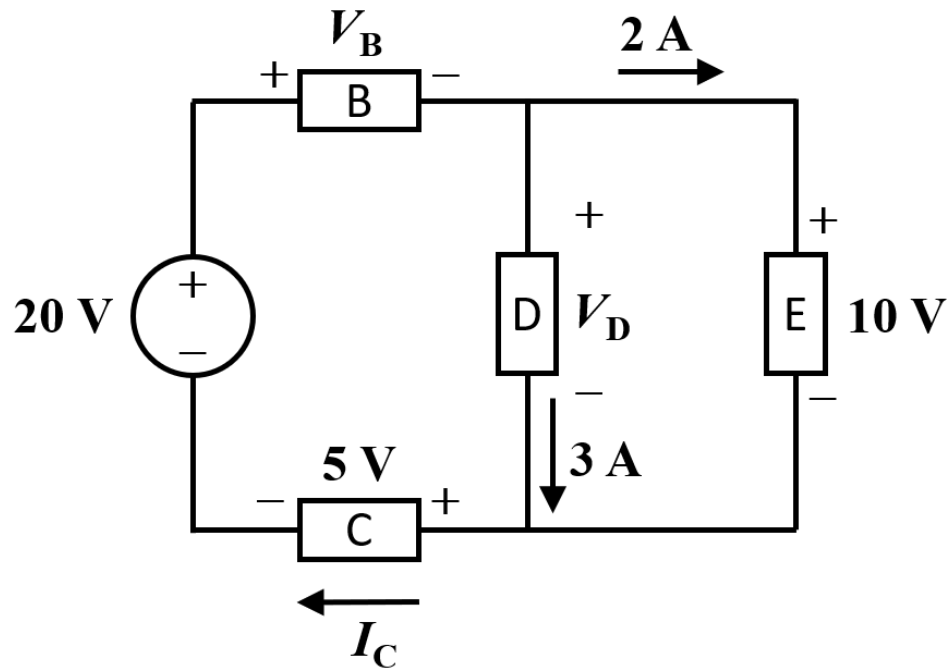



# Resistances in Series


- From KCL, we know that the **currents** in all the resistors in series will be **identical**

- From KVL & Ohm's Law,

$$\begin{aligned} V_b &= V_1 + V_2 + V_3 \\ &= R_1 I + R_2 I + R_3 I \\ &= (R_1 + R_2 + R_3) \times I \end{aligned}$$

- Since  $V_b$  is also given by  $R_{eq} \times I$ , therefore, the equivalent resistance is


$$R_{eq} = R_1 + R_2 + R_3$$

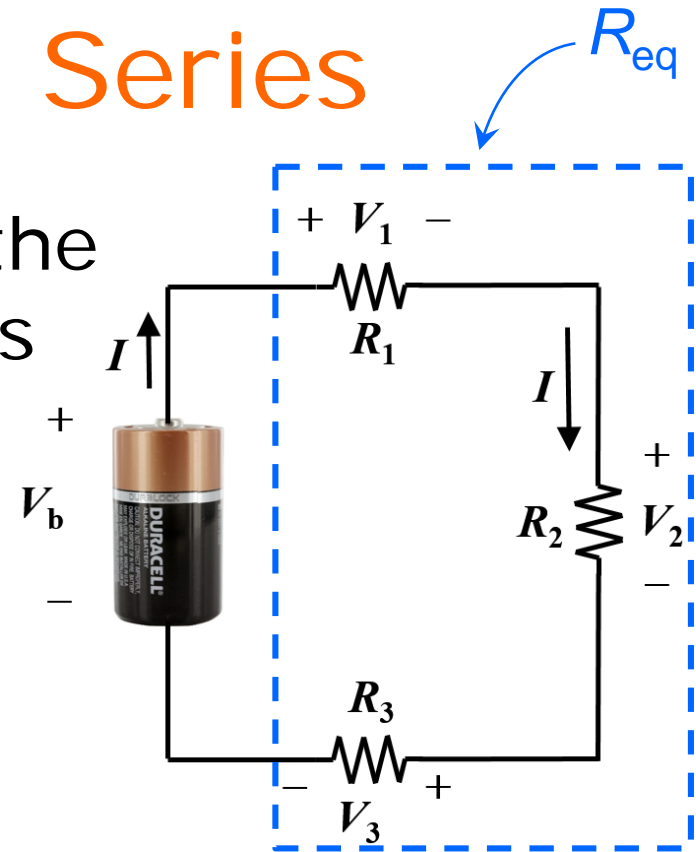

Resistances in **series** lead to **increased resistance**
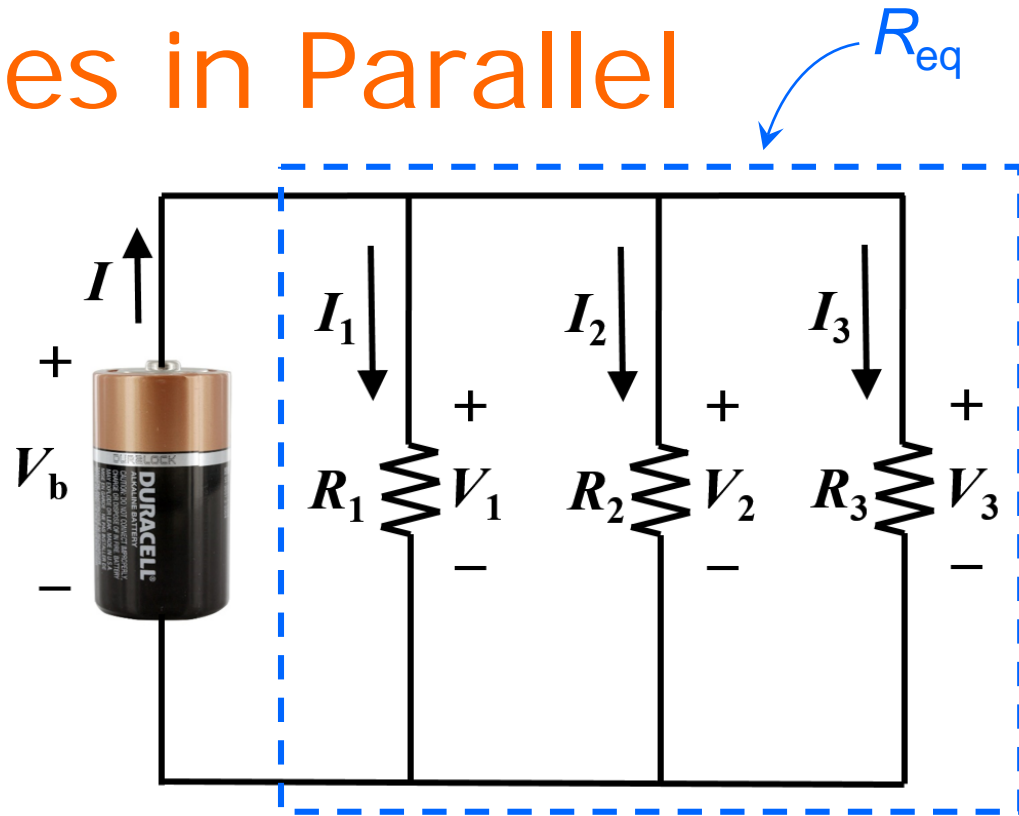
# Resistances in Parallel

- $V_1 = V_2 = V_3 = V_b$
- From KCL,  
$$I = I_1 + I_2 + I_3$$
$$= \frac{V_b}{R_1} + \frac{V_b}{R_2} + \frac{V_b}{R_3}$$
$$= V_b \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)$$



Since  $I = \frac{V_b}{R_{eq}}$ , we have  $\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$

Since  $\frac{1}{R_{eq}} > \frac{1}{R_i}$  for any  $i = 1, 2, 3$ ,  $\therefore R_{eq} < R_i$

Resistances in **parallel** lead to **reduced resistance**

# Resistances in Parallel: Special Cases

- Two resistances in parallel:

$$R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$$

- Two equal resistances in parallel:


$$R_{eq} = \frac{R}{2}$$

- $N$  equal resistances in parallel:


$$R_{eq} = \frac{R}{N}$$
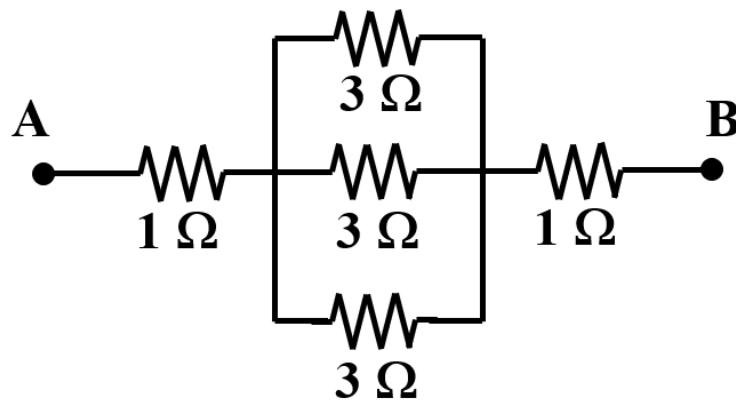
# Network Analysis Using Series & Parallel Equivalents

- A resistive circuit can be solved by repeated simplification through application of series & parallel equivalents
- Example:
  - Find equivalent resistance between A & B:



# Voltage Division Principle

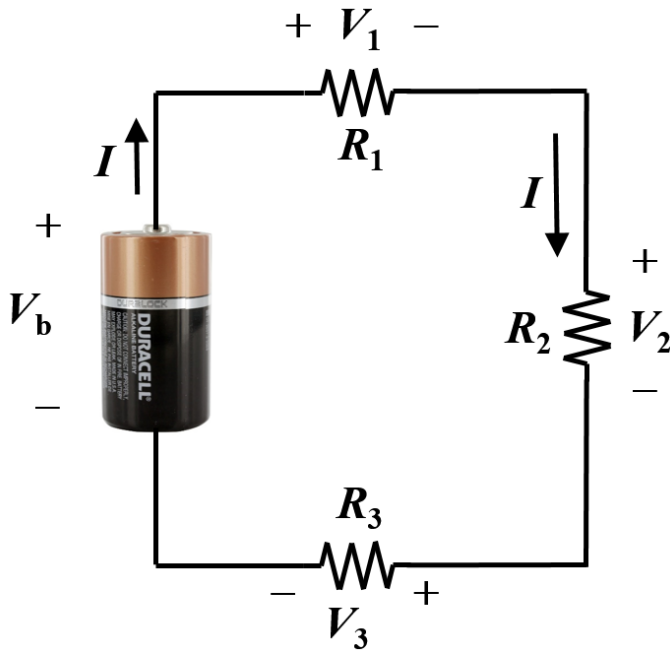

$$I = \frac{V_b}{R_1 + R_2 + R_3}$$

$$V_1 = I \times R_1 = \frac{R_1}{R_1 + R_2 + R_3} V_b$$


$$V_2 = I \times R_2 = \frac{R_2}{R_1 + R_2 + R_3} V_b$$

$$V_3 = I \times R_3 = \frac{R_3}{R_1 + R_2 + R_3} V_b$$


In series circuit, the voltage across each resistance is a **fraction** of the **total voltage**, equal to the **ratio** of the concerned resistance to the total resistance

# Example Using Voltage Division Principle

- Find voltage  $V_2$ :

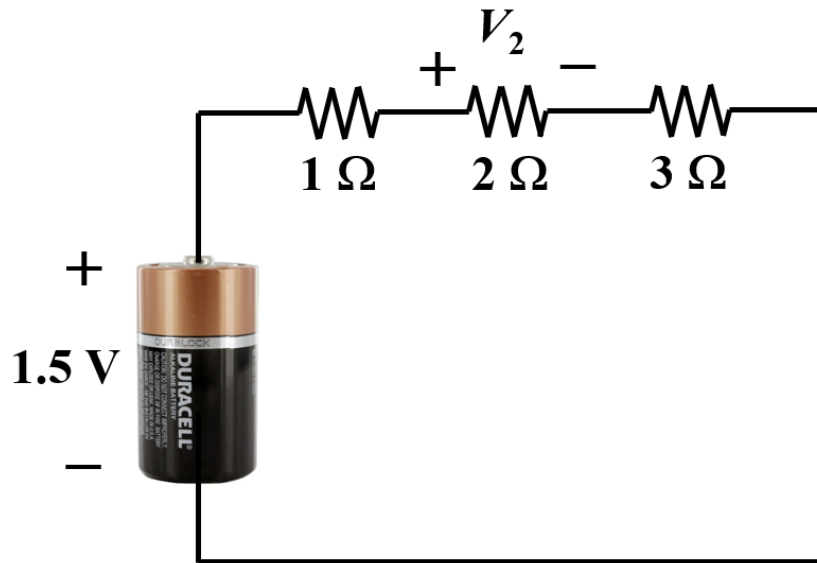

# Current Division Principle

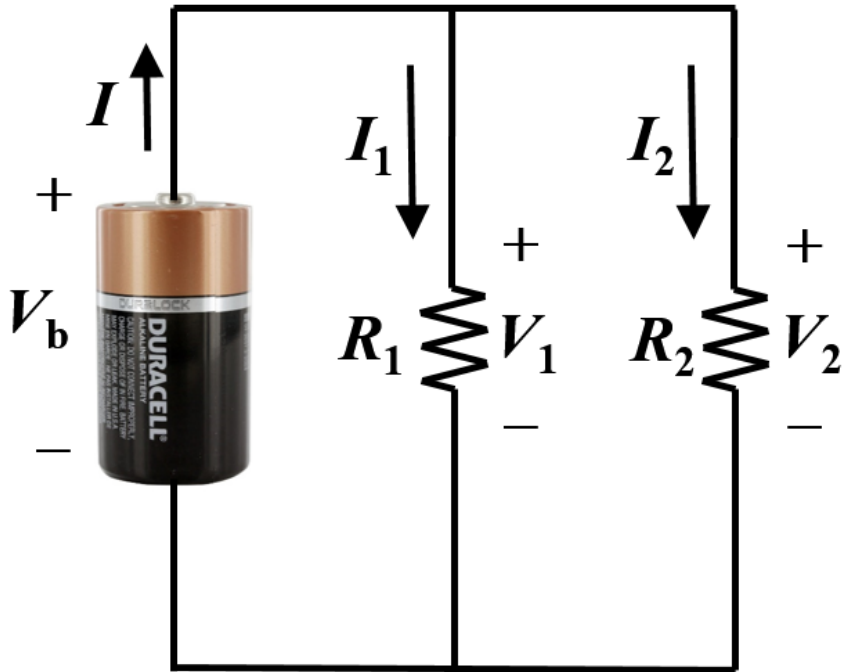

$$V_b = (R_1 \parallel R_2)I = \frac{R_1 R_2}{R_1 + R_2} I$$


$$I_1 = \frac{V_1}{R_1} = \frac{V_b}{R_1} = \frac{R_2}{R_1 + R_2} I$$

$$I_2 = \frac{V_2}{R_2} = \frac{V_b}{R_2} = \frac{R_1}{R_1 + R_2} I$$

For two resistances in parallel, the current flowing in each resistance is a fraction of the total current, equal to the ratio of the other resistance to the sum of both the resistances

# Example Using Current Division Principle

- Find current  $I_1$ :

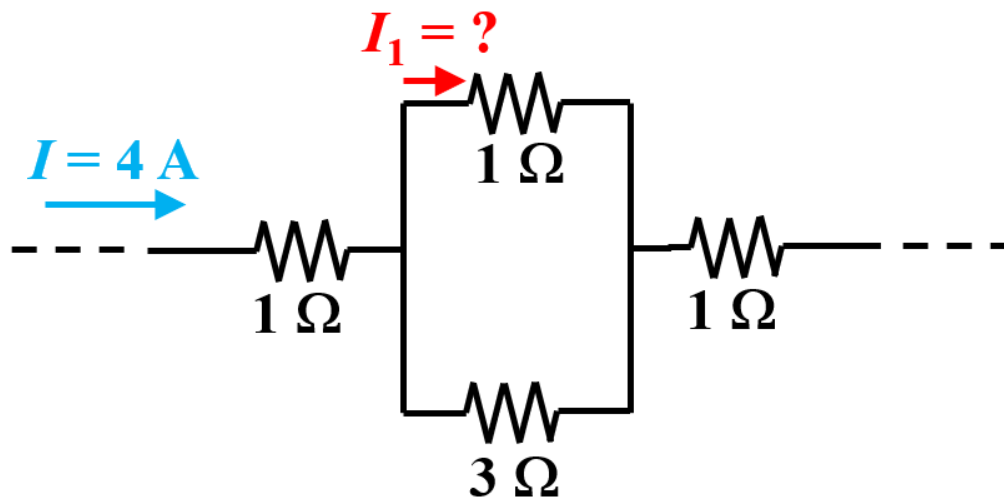



**THANK YOU**