


# **CG1111: Engineering Principles and Practice I**

Summary of Key Points  
for Week 6 to 11



# Principles of AC Circuits

Sinusoidal waveform

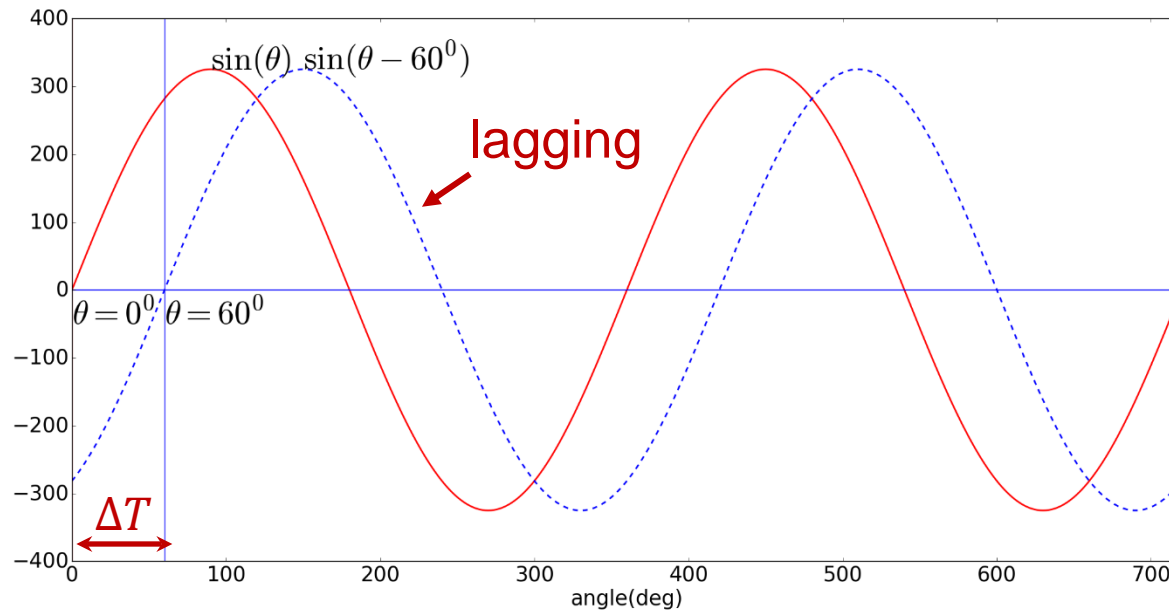

$$v(t) = V_m \cos(\omega t \pm \phi) \quad \phi = \frac{\Delta T}{T} \times 360^\circ$$

$V_m$ : Amplitude (or peak)

$\omega$ : Angular frequency in rad/s

$\phi$ : Phase angle

'+' if leading  
'-' if lagging

$$\omega = 2\pi f$$

$$T = \frac{1}{f}$$


# Root-Mean-Square (RMS)

- Significance of rms value:
  - They are the equivalent values of the DC voltage & current that would have the same average power dissipation in a resistive load
  - So that you can apply the same formula as DC!
  - Average power dissipation of resistive load in AC:


$$P = V_{rms} \times I_{rms} = I_{rms}^2 R = \frac{V_{rms}^2}{R}$$

$$V_{rms} = \frac{V_m}{\sqrt{2}}$$

$$I_{rms} = \frac{I_m}{\sqrt{2}}$$

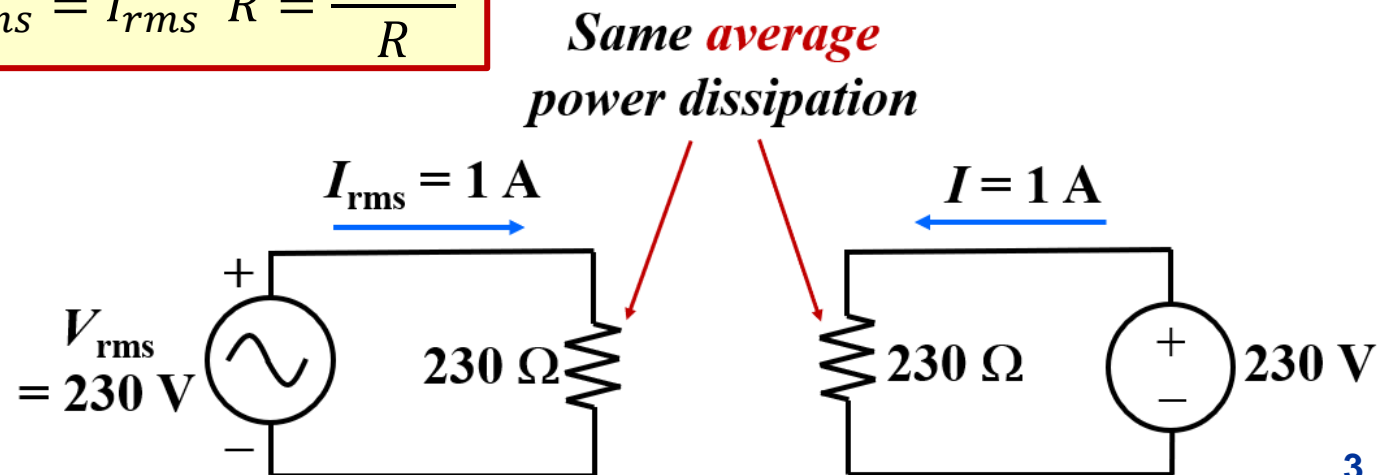

# AC Circuit Analysis in Time Domain?

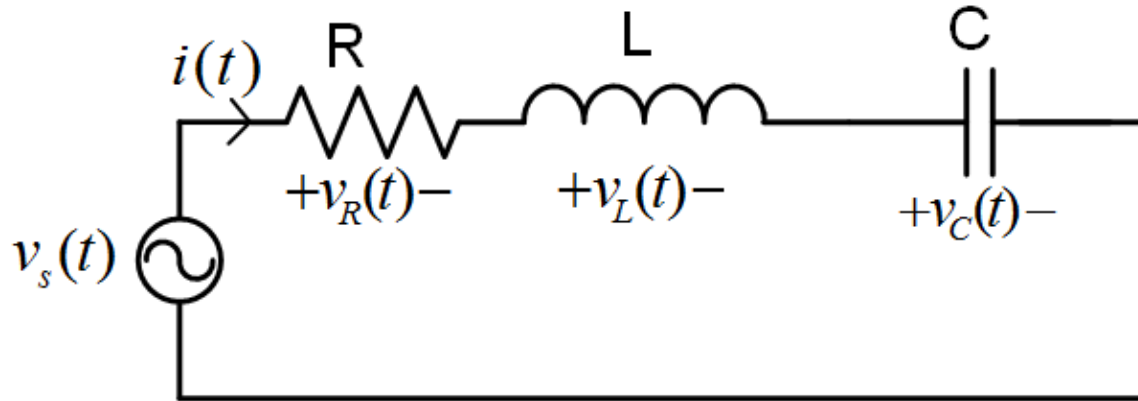


- In AC circuits, inductors/capacitors result in differential equations:

$$V_m \cos(\omega t) = v_R(t) + v_L(t) + v_C(t) = iR + L \frac{di}{dt} + \frac{\int i dt}{C}$$

→ difficult to solve in time-domain!

# AC Circuit Analysis

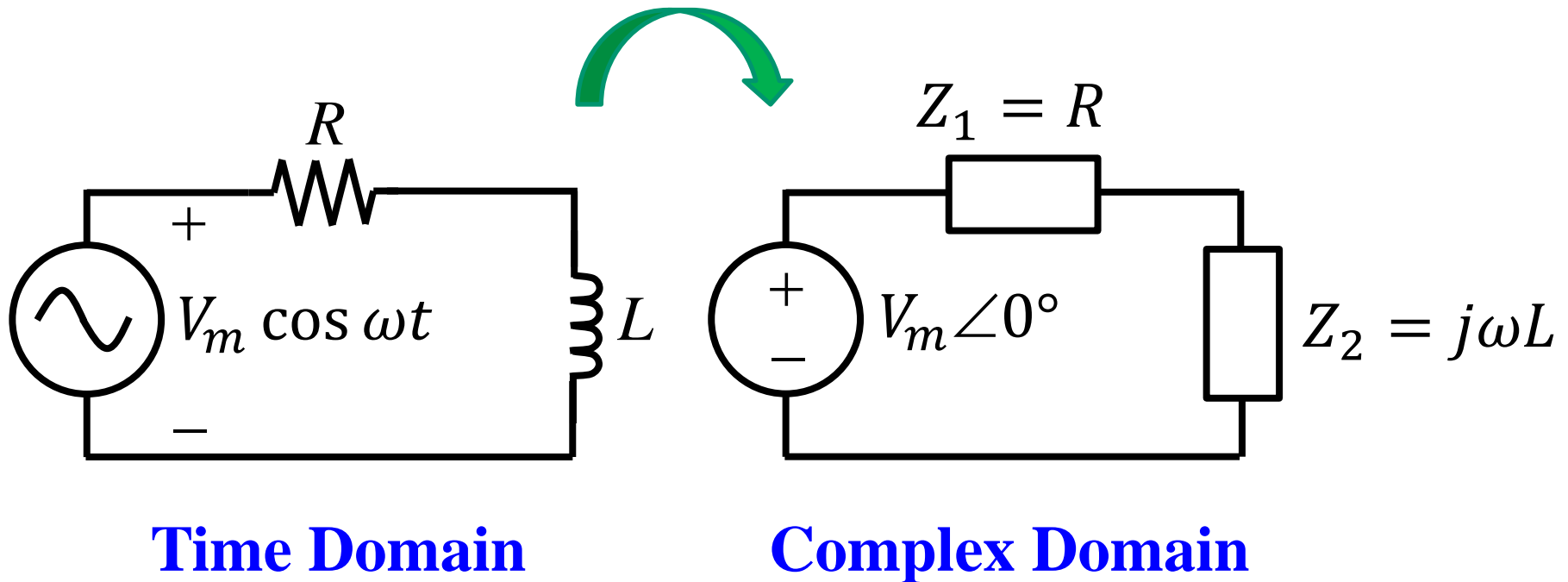

Can then solve using DC circuit analysis techniques:

- KVL, KCL, Ohm's Law, Potential divider principle, current division principle, Thevenin equivalent, NVA, series equivalent impedance, parallel equivalent impedance, etc.

# AC Circuit Analysis with Phasors & Impedances

We must work with KVL & KCL in **Phasor form**

Steps:

1. Replace **voltage sources** with their **phasors** (all must have same frequency)
2. Replace **R, L, C** elements with their **impedances**
3. Analyse circuit using **DC circuit analysis** techniques (work within **complex** domain)
4. Convert final results back to **time-domain**

# Phasors

- Sinusoidal voltage:

$$V_m \cos(\omega t + \theta)$$

- Phasor:

$$V_m \angle \theta$$


Note:

Another common practice is to represent phasors using the **RMS value** instead of the magnitude. In that case, the phasor will be written as  $\frac{V_m}{\sqrt{2}} \angle \theta$ .

Note:

- Phasor is just a definition. It leads to **mathematical convenience**, but has **no physical significance**

# Impedances

- For resistance:

$$R$$

- For inductor:

$$j\omega L = \omega L \angle 90^\circ$$

- For capacitor:

$$\frac{1}{j\omega C} = \frac{-j}{\omega C} = \frac{1}{\omega C} \angle -90^\circ$$




# Illustration: KVL Applies for Phasors


Voltage	Magnitude	Phase Angle	Real	Imaginary
$V_S$	7	$0^\circ$	7	0
$V_R$	4.95	$-45^\circ$	3.5	-3.5
$V_L$	4.95	$45^\circ$	3.5	3.5

In AC circuits with R, L, C elements, because of the phase differences, we can only apply KVL in complex domain:

$$V_S = V_R + V_L$$

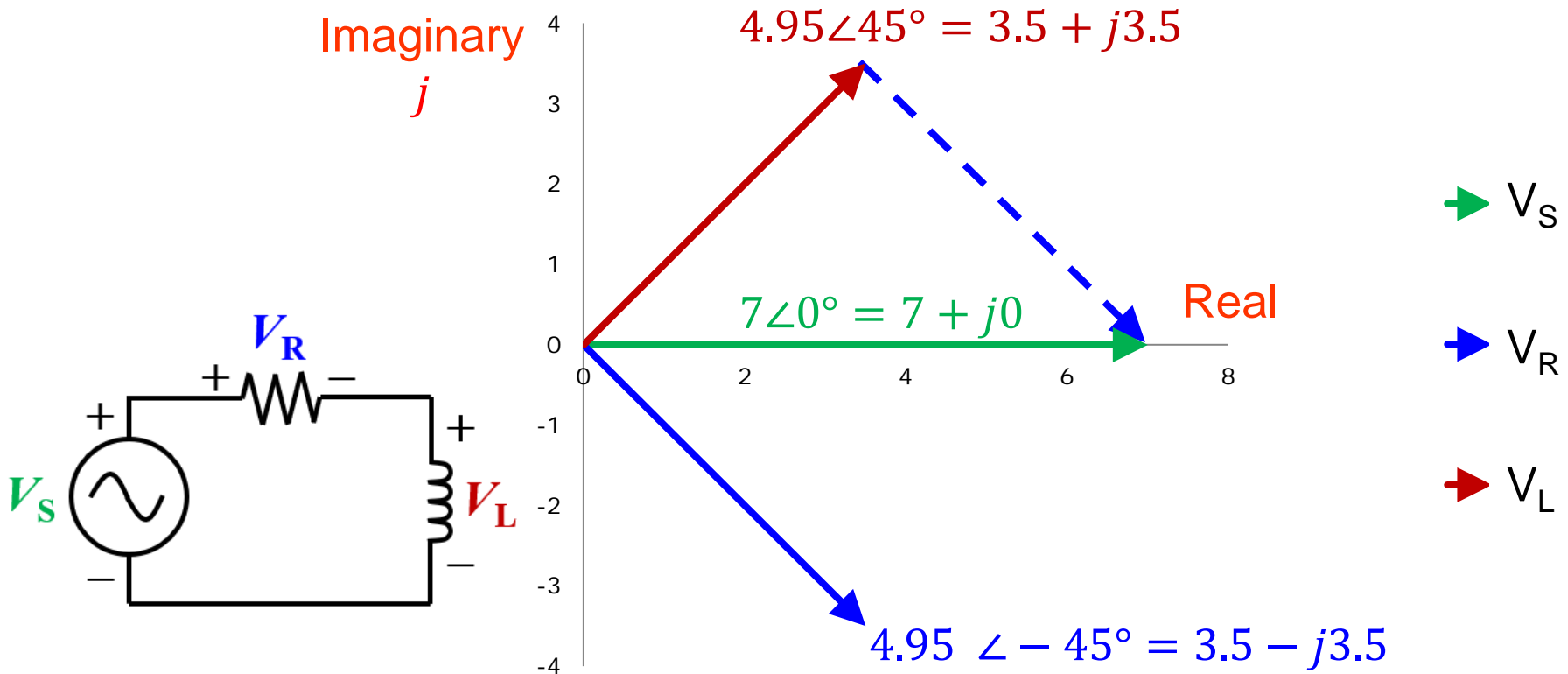
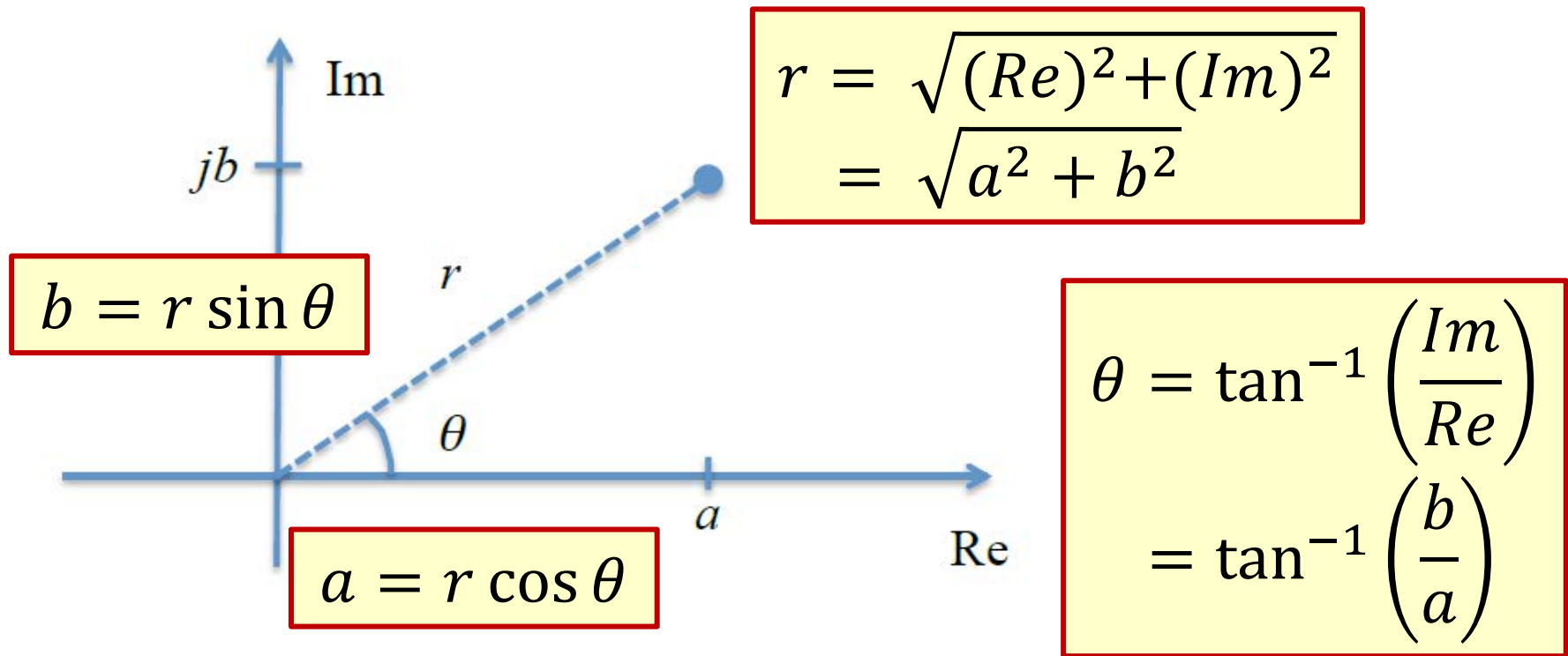
# Relationship Among Magnitude, Phase, Real & Imaginary Parts



# Phasor Division & Multiplication


- Division:

$$\frac{A \angle \theta_1}{B \angle \theta_2} = \frac{A}{B} \angle (\theta_1 - \theta_2)$$

- Multiplication:

$$A \angle \theta_1 \times B \angle \theta_2 = AB \angle (\theta_1 + \theta_2)$$


# Step-Up/Down Transformer

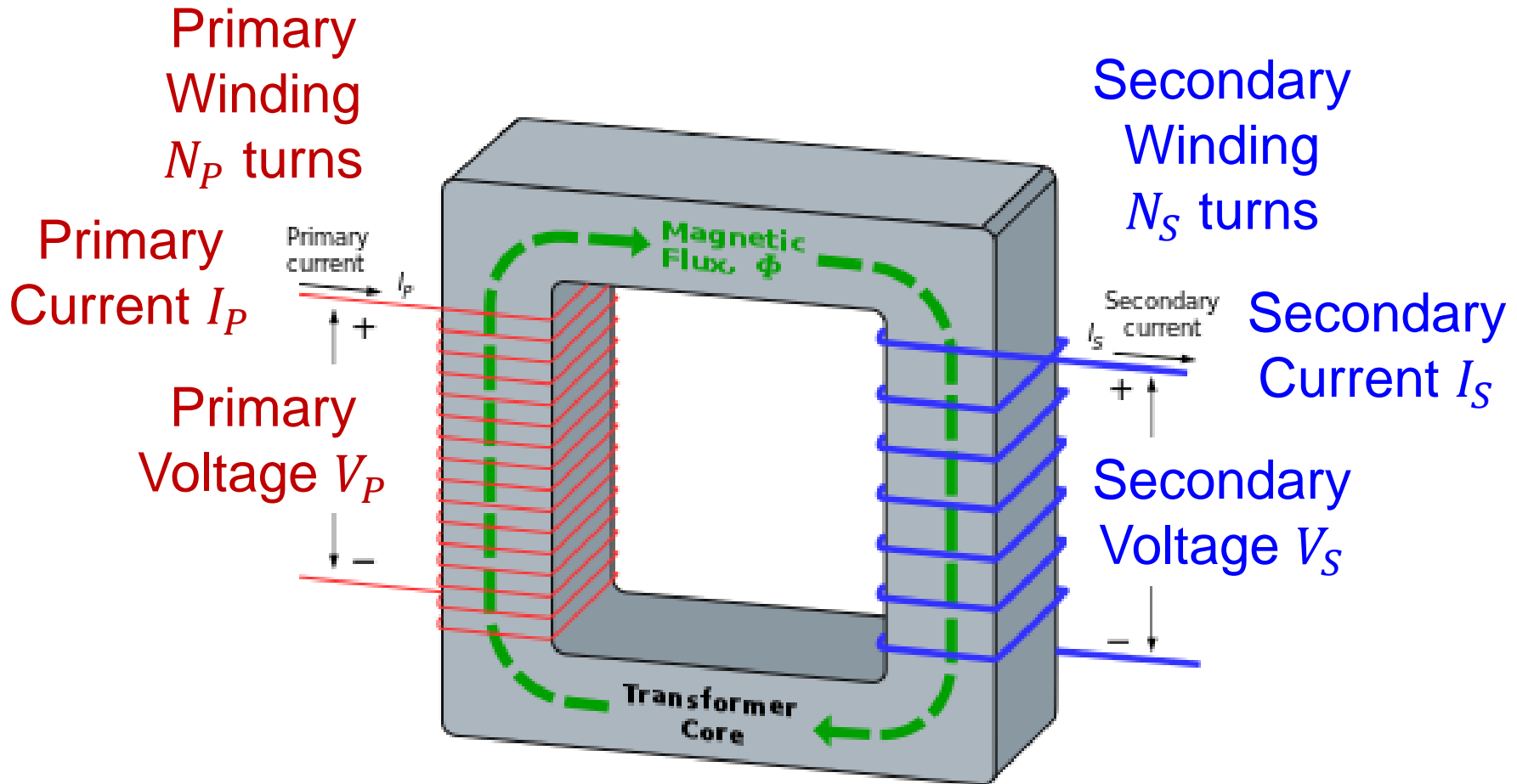



$$\frac{V_S}{V_P} = \frac{N_S}{N_P}$$

$$\frac{I_S}{I_P} = \frac{N_P}{N_S}$$


# Why Rectifier?

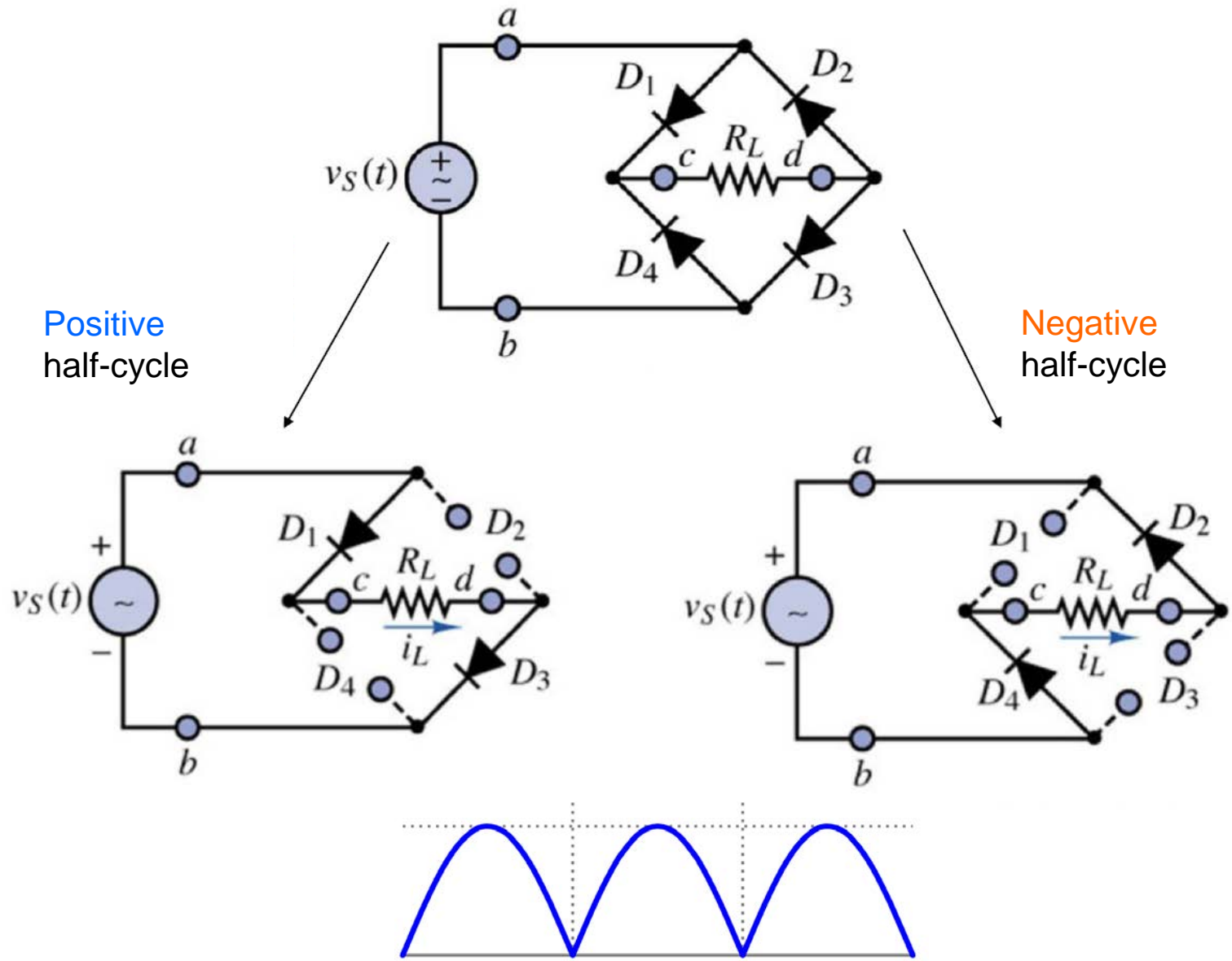

# Why Filter Capacitor?

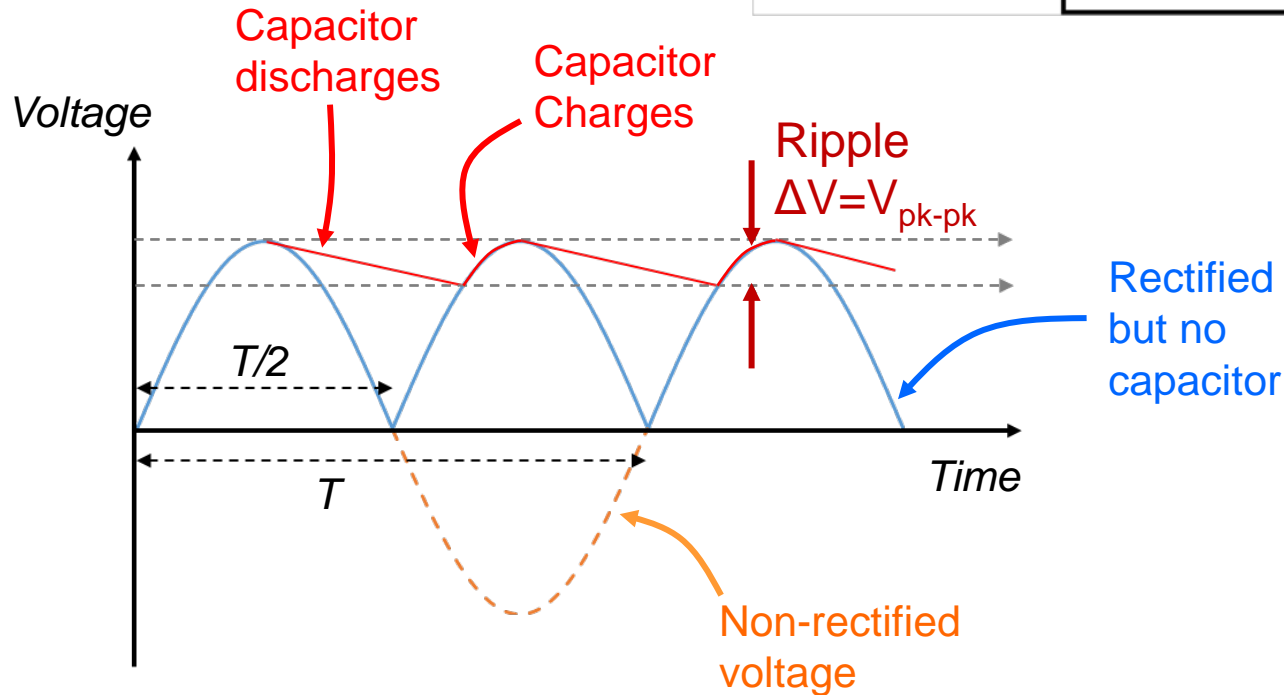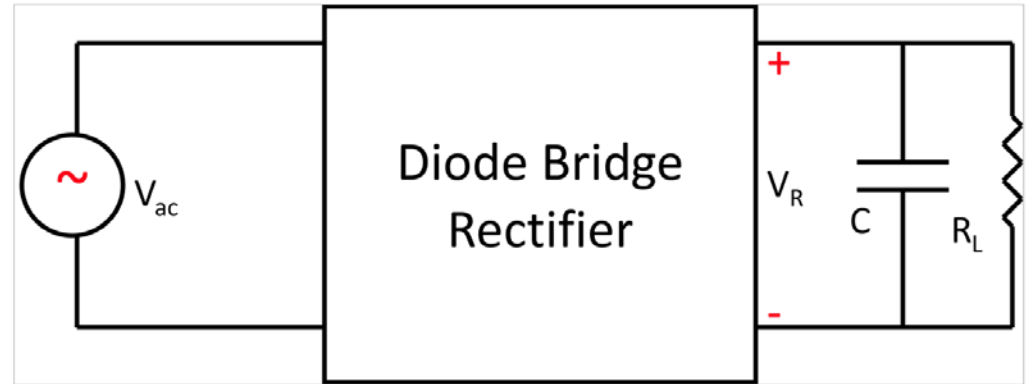

# Voltage Ripple

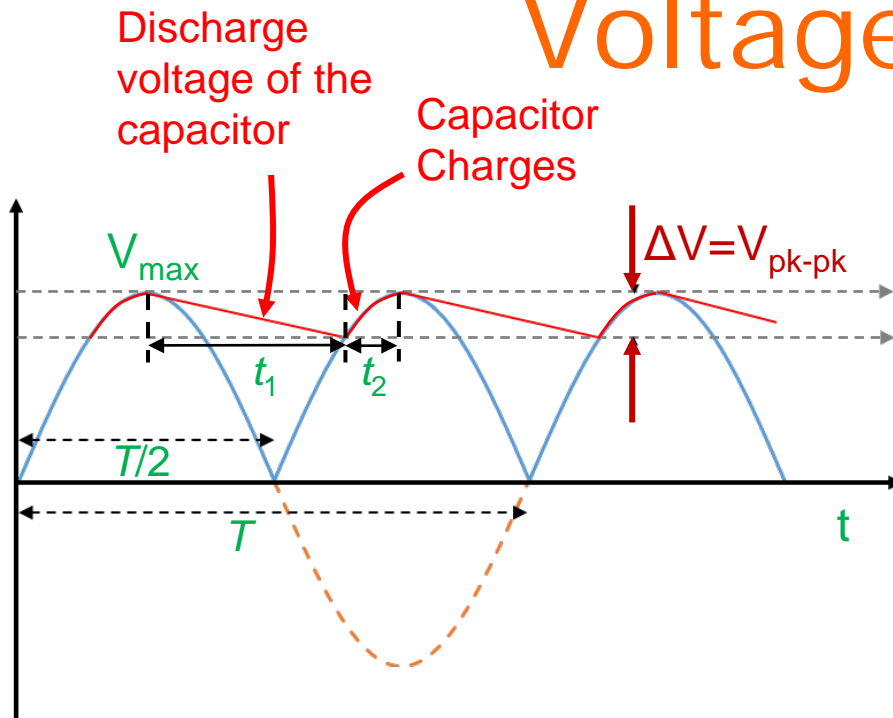

- Let  $V_{Load}$ : average load voltage
- Average load current is given by

$$I_L = \frac{V_{Load}}{R_L}$$

- Since it is a full-wave diode bridge rectifier, the pattern repeats **every  $T/2$**

- Let  $\Delta V$  be the peak-to-peak ripple voltage

- $\Delta V = \frac{\Delta Q}{C}$  (capacitance's definition)

- For small  $\Delta V$ ,  $t_1 \approx T/2$ . Since  $i(t) = \frac{dQ}{dt}$ , average current  $I_L \approx \frac{\Delta Q}{T/2}$ .

- Hence

$$\Delta V \approx \frac{I_L * T/2}{C} = \frac{V_{Load}}{R_L} * \frac{1}{2f_s} * \frac{1}{C}$$

# Characteristics of DC Motors

$$T_{\text{shaft}} = K_t I_m \text{ [N.m]}$$

$$E_b = K_e \omega \text{ [V]}$$

For PMDC motor:

$$K_t = K_e$$

Note:

$$\omega = 2\pi \times \frac{\text{RPM}}{60} \text{ [rad/s]}$$




# Power Conversion in Motors

- Mechanical power at motor shaft:


$$P_{\text{mech}} = T_{\text{shaft}} \omega \text{ [W]}$$

- Electrical power supplied to motor:

$$P_{\text{in}} = V_m I_m \text{ [W]}$$

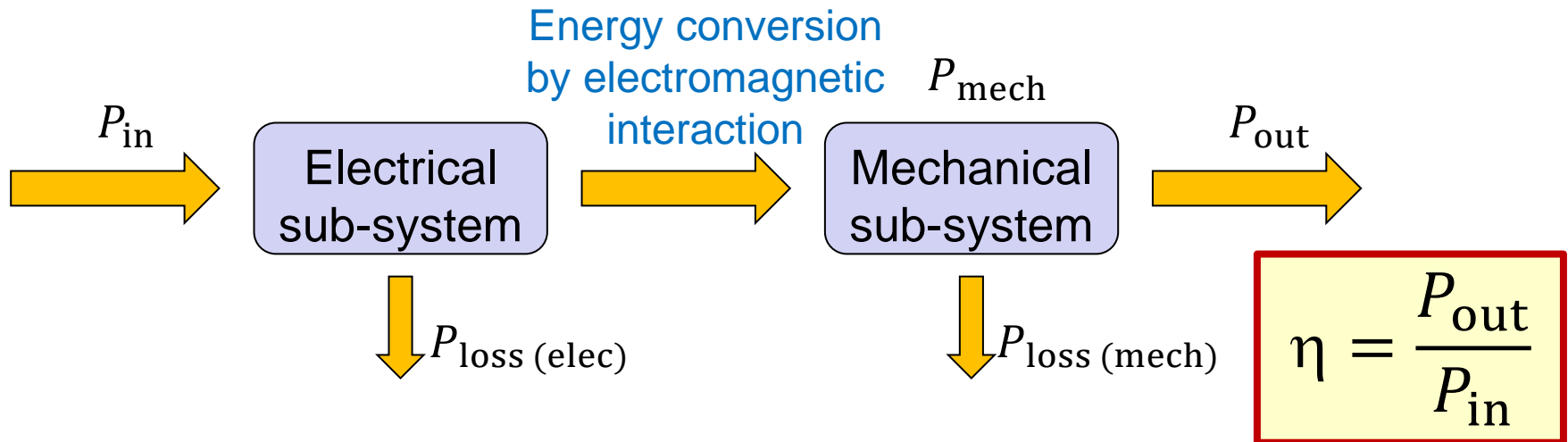

# Circuit Representation: PMDC Motor

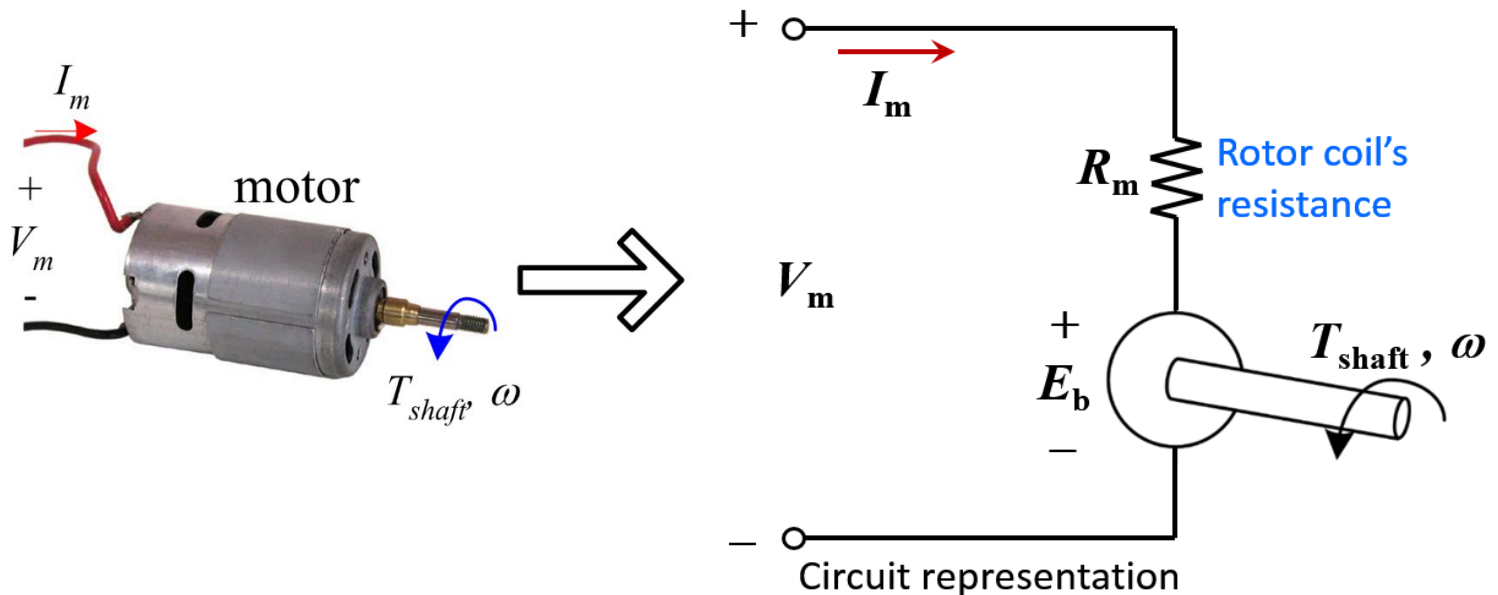

- From the circuit:

$$I_m = \frac{V_m - E_b}{R_m}$$

- Since  $E_b = K_e \omega$ , we have:

$$I_m = \frac{V_m}{R_m} - \frac{K_e \omega}{R_m}$$

# Basic Properties of PMDC Motor

Rearranging:

$$\omega = \frac{V_m}{K_e} - \frac{R_m I_m}{K_e}$$


- For a **fixed load** (i.e., **fixed**  $T_{\text{shaft}}$ , which implies **fixed**  $I_m$  since  $T_{\text{shaft}} = K_t I_m$ ):

Shaft speed  $\omega$  can be increased by increasing motor voltage  $V_m$


- For a **fixed voltage**, if  $T_{\text{shaft}}$  increases,  $I_m$  increases, and hence  $\omega$  decreases:

Shaft speed  $\omega$  decreases with increasing load  $T_{\text{shaft}}$

# Op-Amp Terminals

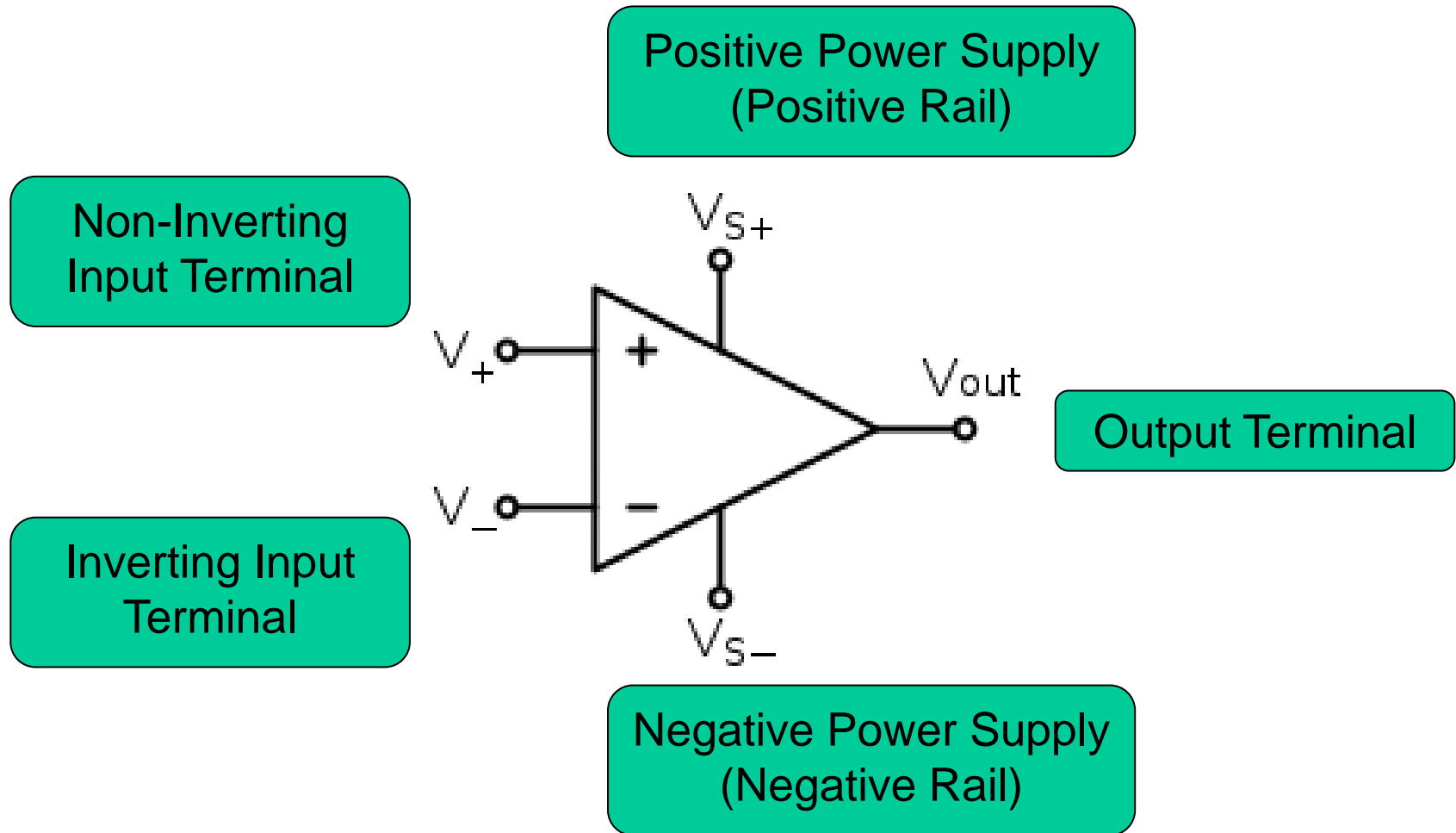

# Op-Amp Equivalent Circuit

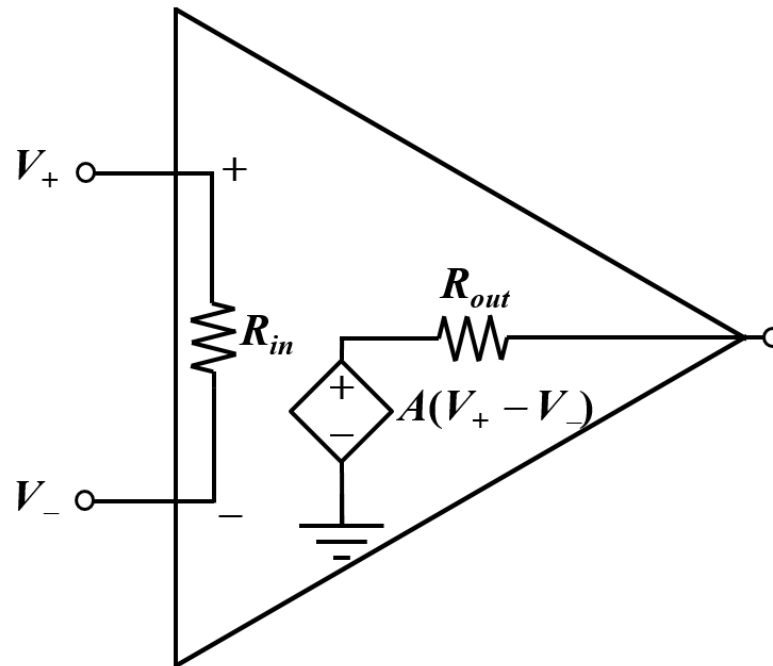

- $A$  is the open-loop voltage gain
  - It is very large, approaching infinity
- $R_{in}$  is the input impedance &  $R_{out}$  is the output impedance


# Typical Op Amp Parameters

Parameter	Variable	Typical Ranges	Ideal Values
Voltage Gain	$A$	$10^5$ to $10^8$	$\infty$
Input Impedance	$R_{in}$	$10^5$ to $10^8 \Omega$	$\infty \Omega$
Output Impedance	$R_{out}$	10 to $100 \Omega$	$0 \Omega$
Supply Voltage	$V_S$ $-V_S$	5 to 30 V -30 to 0 V	N/A N/A
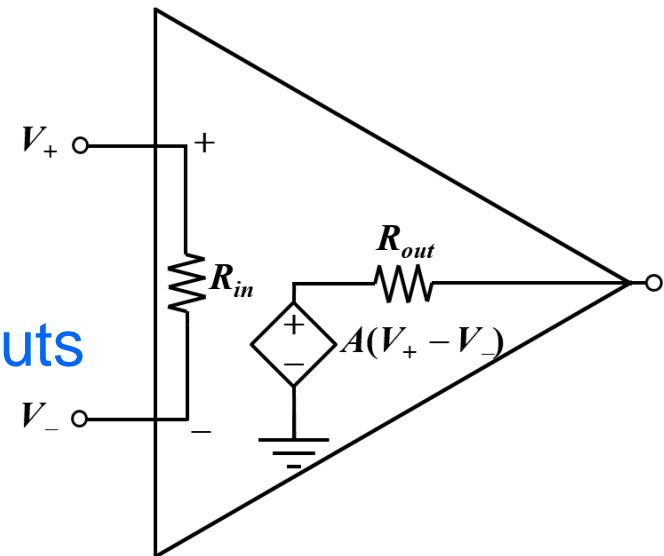
# Op-amp Golden Rules

- Rule 1: In a **closed loop**, the output attempts to do whatever is necessary to make the **voltage difference between the inputs zero**

- The voltage gain of a real op-amp is so high that a fraction of a mV difference between the  $V_+$  &  $V_-$  inputs will swing the output to saturation




- Rule 2: The inputs **draw no current**
  - The ideal op-amp has infinite input impedance ( $R_{in}$ ). Thus, the current drawn at the two terminals is zero
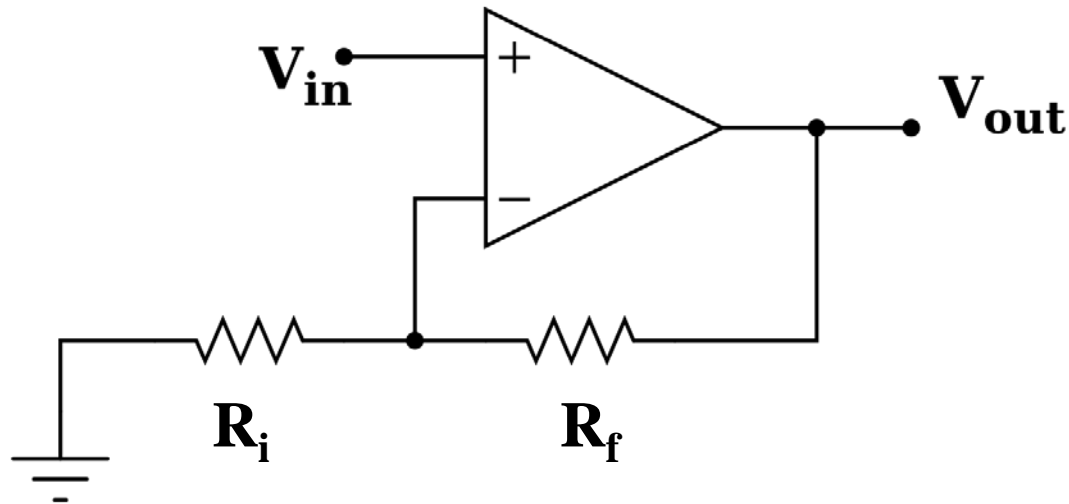
# Non-Inverting Amplifier

- For an ideal op-amp, the **non-inverting amplifier gain** is given simply by

$$\frac{V_{\text{out}}}{V_{\text{in}}} = 1 + \frac{R_f}{R_i}$$






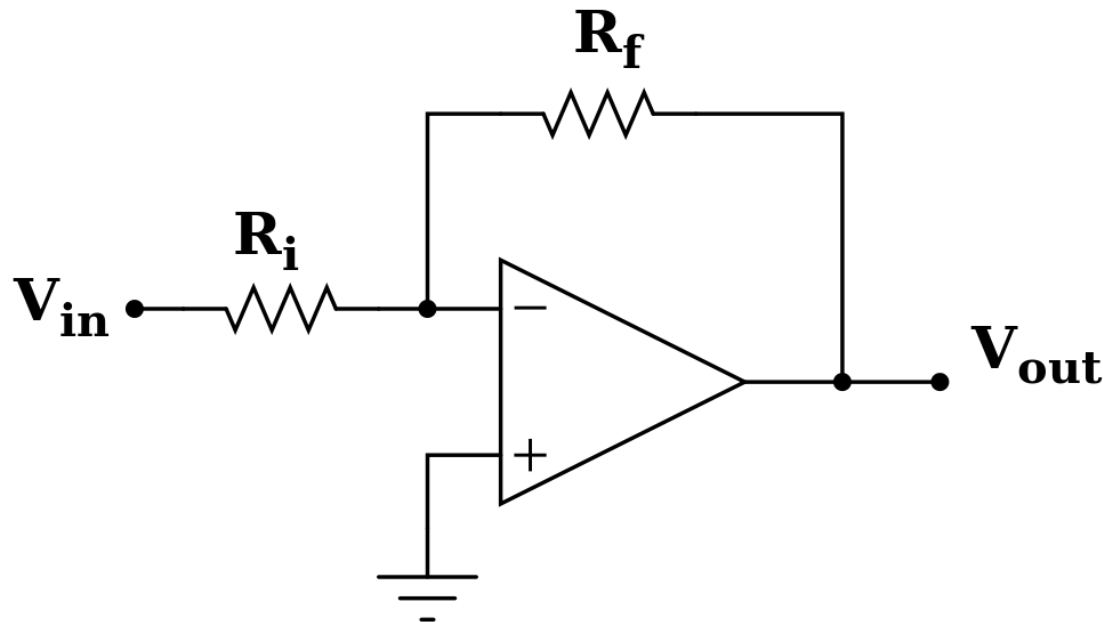
# Inverting Amplifier

- For an ideal op-amp, the **inverting amplifier gain** is given simply by

$$\frac{V_{\text{out}}}{V_{\text{in}}} = -\frac{R_f}{R_i}$$



# Comparator

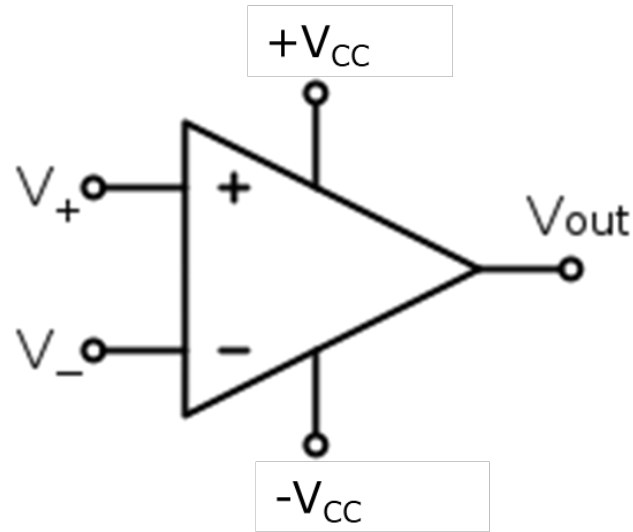


- The comparator is an electronic **decision-making** circuit that makes use of an op-amp's very high gain in its **open-loop state** (i.e., there is no feedback resistor)

# Op-Amp as a Comparator
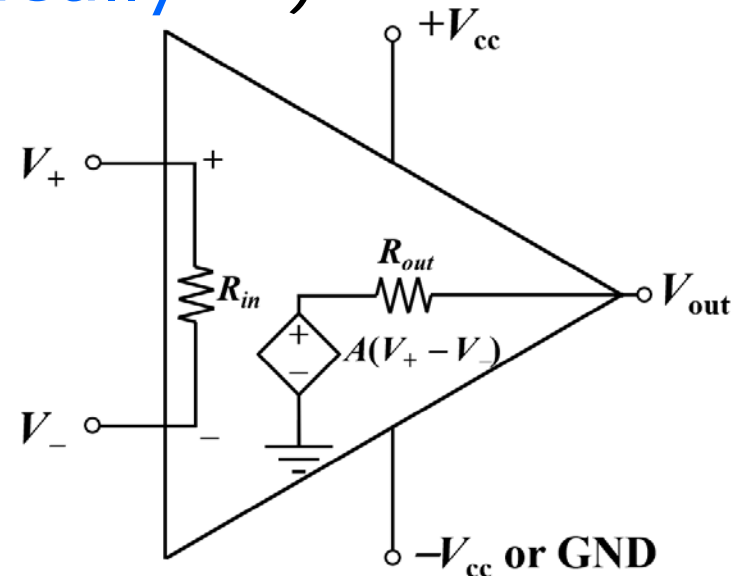
## – How It Works

Recall that for op-amp:

- The difference between the two inputs is amplified as ' $A(V_+ - V_-)$ ' at the output
- The **open-loop** voltage gain ('A') of the op-amp is very high (**ideally  $\infty$** )
- Even if there is a very small difference between the inputs, the high 'A' will pull the output to "**saturation**"



# Op-Amp as a Comparator


## – How It Works

- If  $V_+ > V_-$ :

$$V_{\text{out}} = +V_{\text{sat}}$$


- If  $V_- > V_+$ :
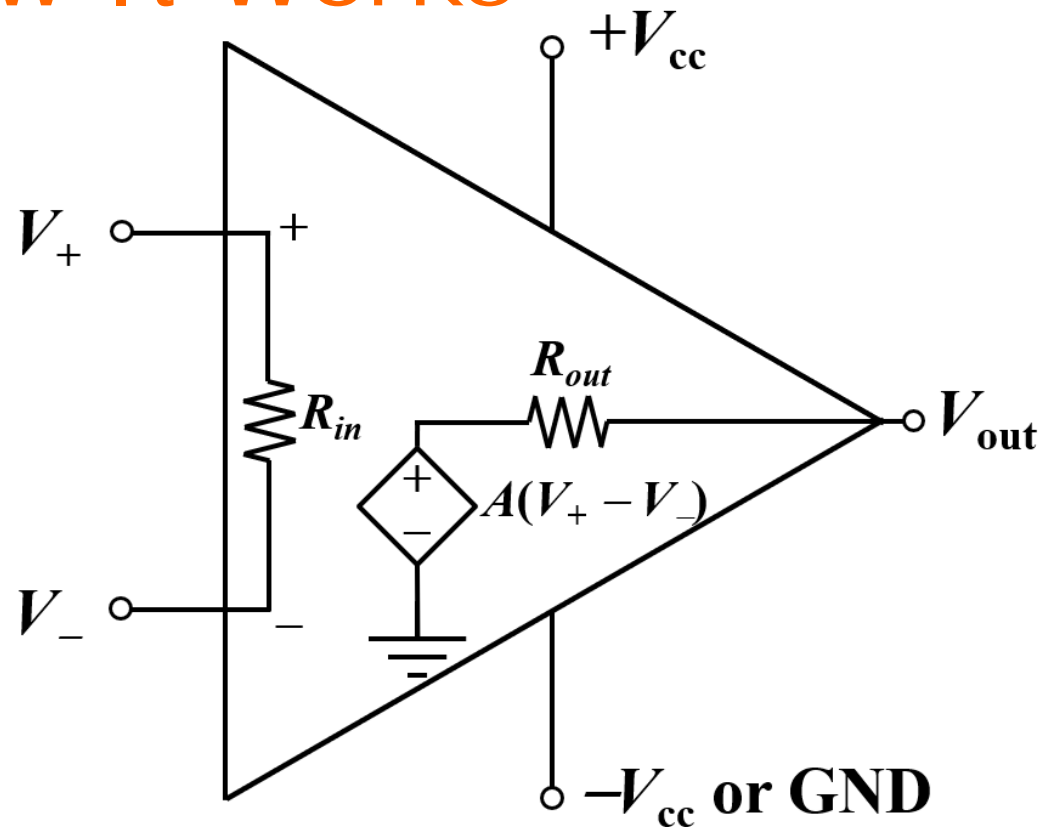
$$V_{\text{out}} = \begin{cases} -V_{\text{sat}} & \text{if dual power supply} \\ 0 & \text{if single power supply} \end{cases}$$


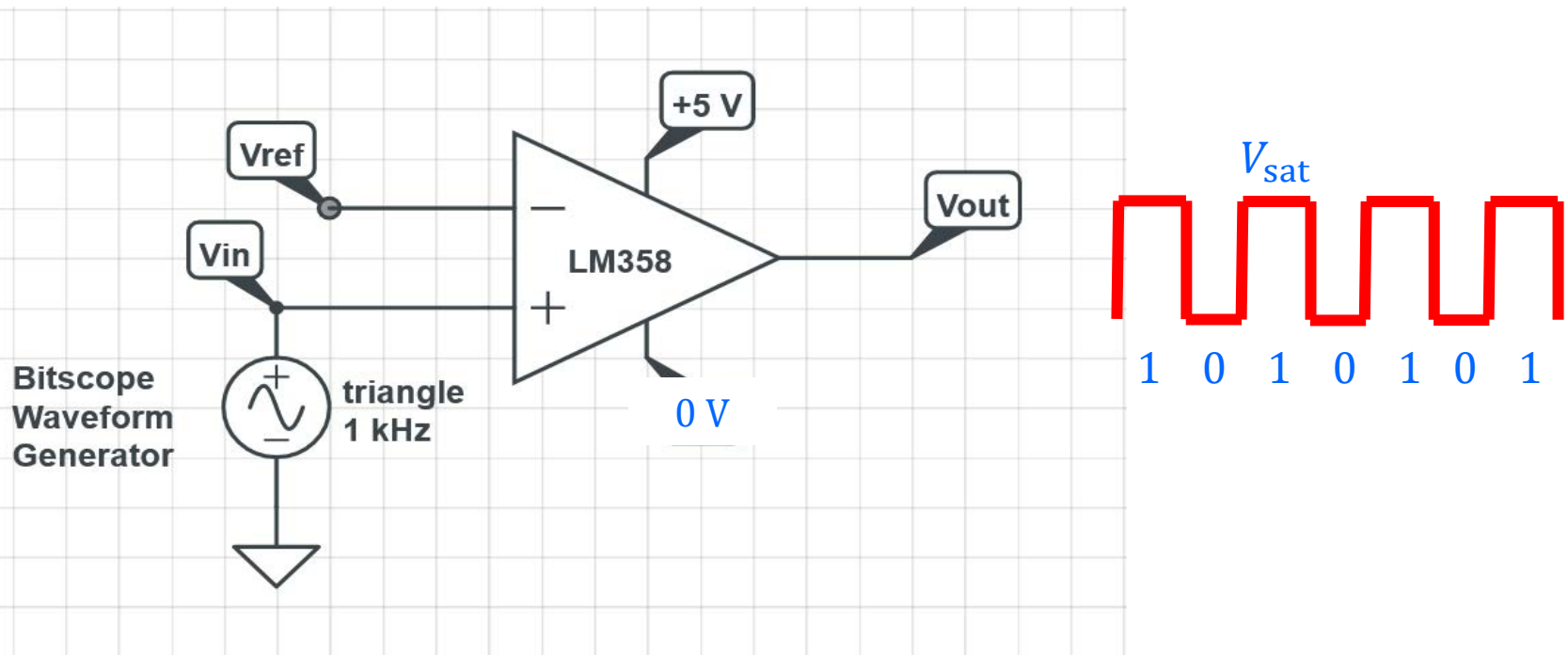
# Common Application of Comparator

- The comparator is ideal for converting analog signals to **digital signals** at certain threshold values




# Filter

- A filter is a device or process that removes some unwanted components or features from a signal
- Examples:
  - Removing the noise from measured ECG signal using a filter to help a doctor understand the heart better




- Removing some frequencies or frequency bands from an audio signal

# Passive Low-Pass Filter

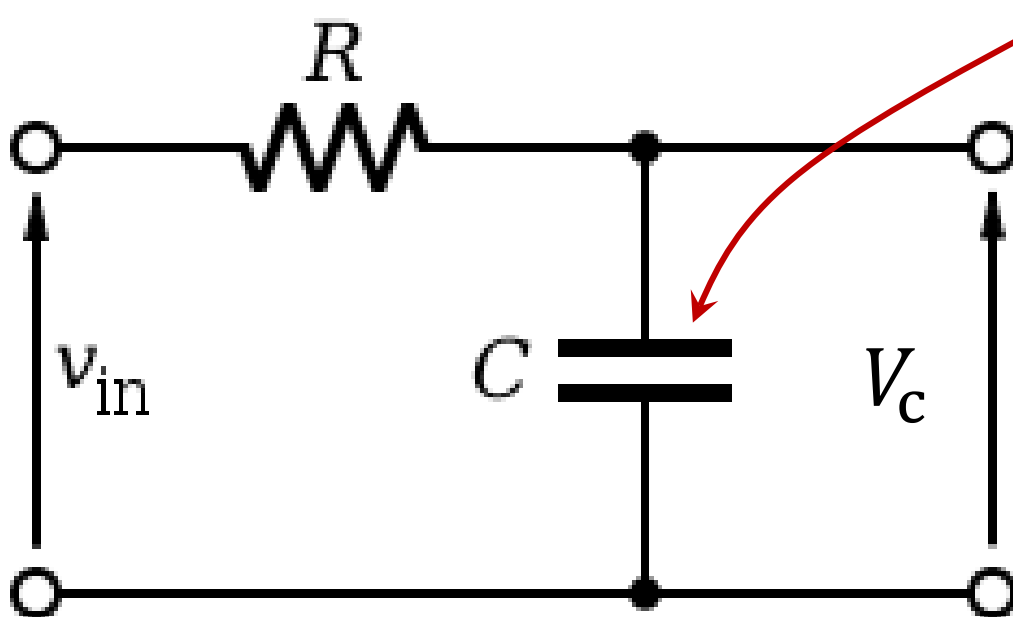

Voltage divider:  
The capacitor's impedance decreases as the frequency increases, hence  $V_c$  decreases

Gain  $\frac{V_c}{V_{in}}$  in dB

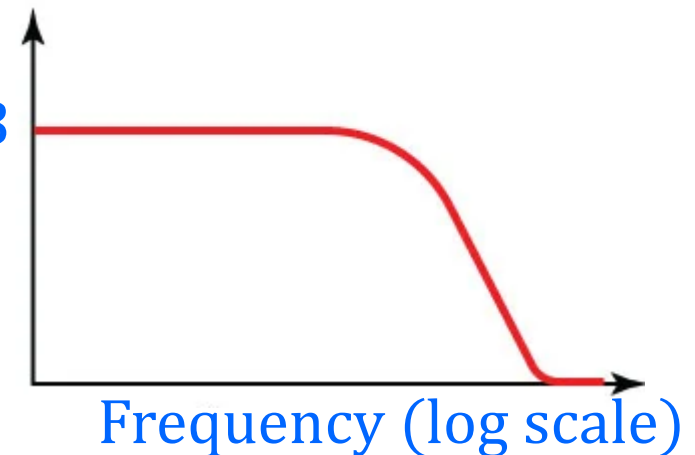

# Power Gain in decibels (dB)

- The **Voltage Amplification ( $A_v$ )** or **Gain** of a voltage amplifier/filter is given by:

$$A_v = \frac{V_{\text{out}}}{V_{\text{in}}}$$

- The voltage gain is commonly expressed in terms of the resulting **power gain** in **dB**:

$$\begin{aligned}\text{Power Gain (dB)} &= 10 \log_{10} \left( \frac{V_{\text{out}}}{V_{\text{in}}} \right)^2 \text{ dB} \\ &= 20 \log_{10} \left| \frac{V_{\text{out}}}{V_{\text{in}}} \right| \text{ dB}\end{aligned}$$



# Frequency Response

- It is the quantitative measure of the output spectrum of a system or device in response to a stimulus, and is used to characterize the dynamics of the system
  - Frequency in logarithmic Scale: horizontal x-axis




- Power Gain in decibels (dB): vertical y-axis
  - To describe a change in output power over the whole frequency range

$$\text{Power Gain in dB } (f) = 20 \log_{10} |A_v(f)|$$
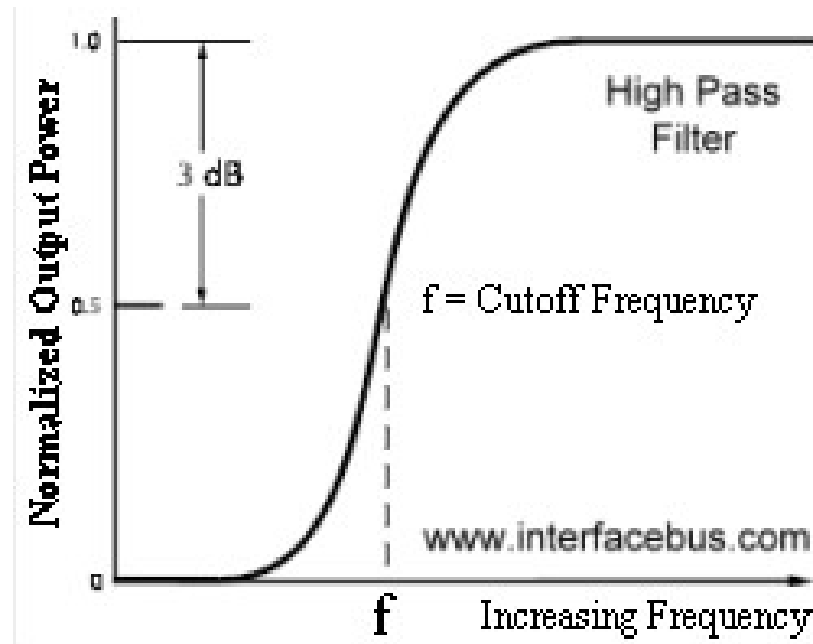
# Cut-off Frequency


- In filters, the cut-off frequency characterizes a **boundary** between a **passband** and a **stopband**
- The cut-off frequency is taken as the frequency at which the output of the circuit is **-3 dB** (corresponding to **half the power**) of the nominal passband value



# Cut-off Frequency: $-3$ dB Point (i.e., Half-power Point)
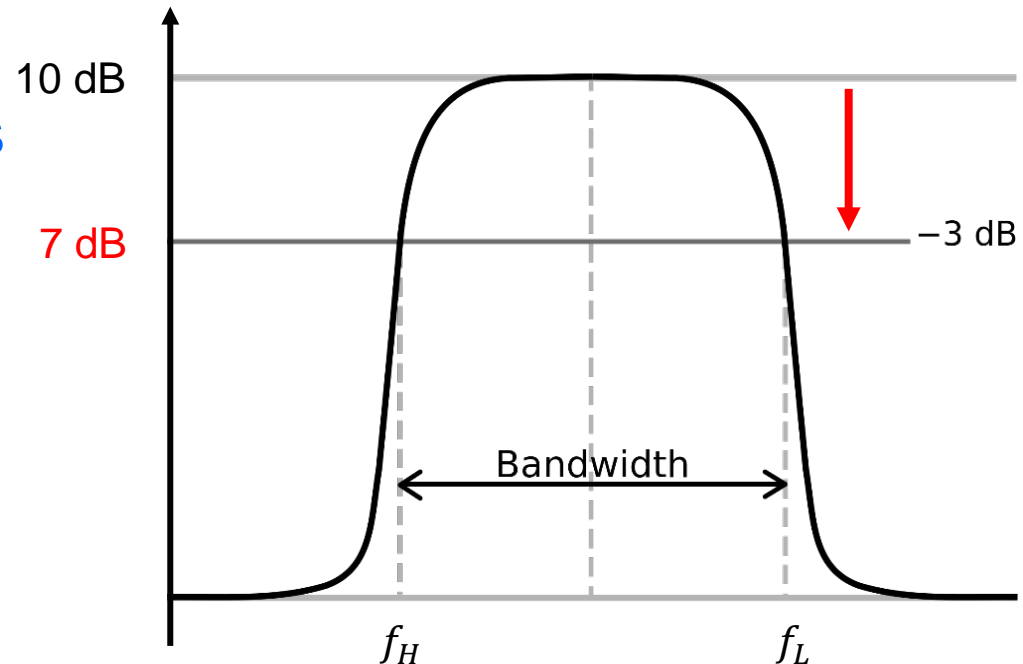
## ■ Graphical approach:

- Find the passband gain from the magnitude vs frequency plot
- Subtract 3 dB from the passband gain and draw a line on the plot
- The points where this line cuts the plot corresponds to the cut-off frequency(s)




# Cut-off Frequency: $-3$ dB Point (i.e., Half-power Point)

- Quantitative approach  
(for first-order filters):

$$f_H = \frac{1}{2\pi R_H C_H}, \quad f_L = \frac{1}{2\pi R_L C_L}$$
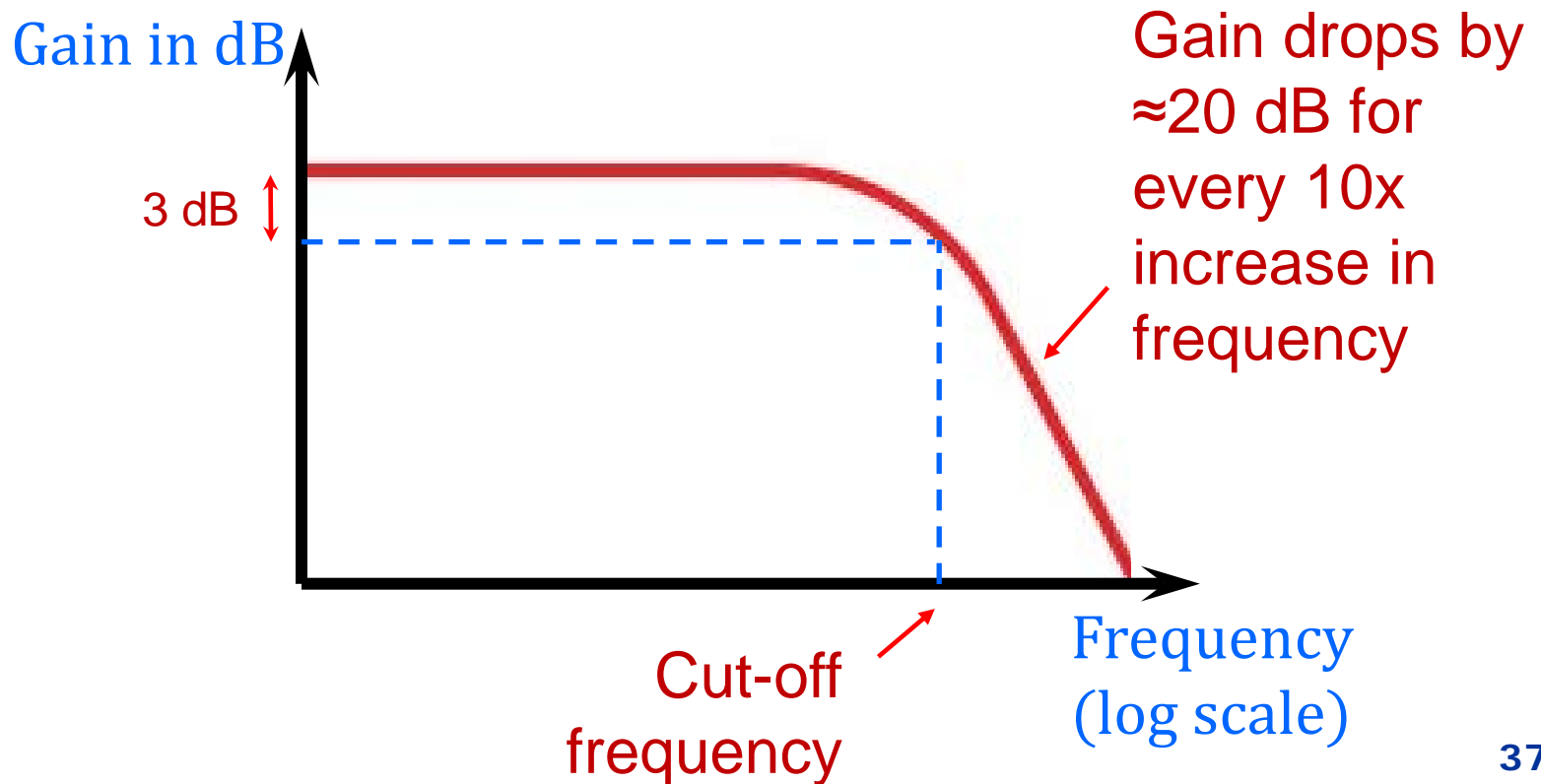
# First-order Low-Pass Filter


- Slope after cut-off frequency  
 $\approx -20 \text{ dB/decade}$


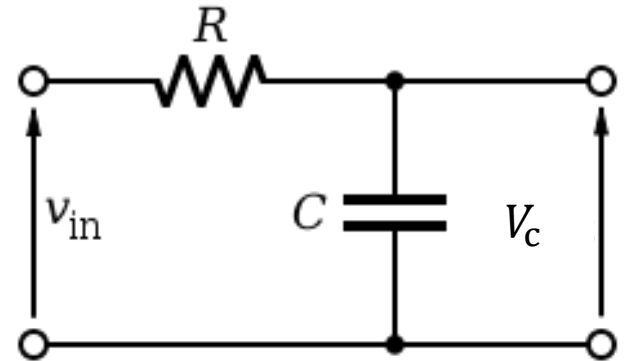
# Passive Low-Pass Filter

- We can use the voltage divider rule to find the voltage gain

$$\rightarrow V_c = \left[ \frac{\frac{1}{j\omega C}}{\frac{1}{j\omega C} + R} \right] V_{in}$$



$$\rightarrow \frac{V_c}{V_{in}} = \left[ \frac{\frac{1}{j\omega C}}{\frac{1}{j\omega C} + R} \right] = \left[ \frac{1}{1 + jR\omega C} \right] = \frac{1 \angle 0^\circ}{\sqrt{1^2 + (R\omega C)^2} \angle \theta^\circ}$$


$$\rightarrow \left| \frac{V_c}{V_{in}} \right| = \left[ \frac{1}{\sqrt{1 + (R\omega C)^2}} \right]$$

$$\text{Gain in dB} = \underbrace{20 \log_{10} 1}_{\text{Passband gain (= 0 dB)}} - \underbrace{20 \log_{10} \sqrt{1 + (\omega CR)^2}}_{\text{Change in gain with } \omega}$$
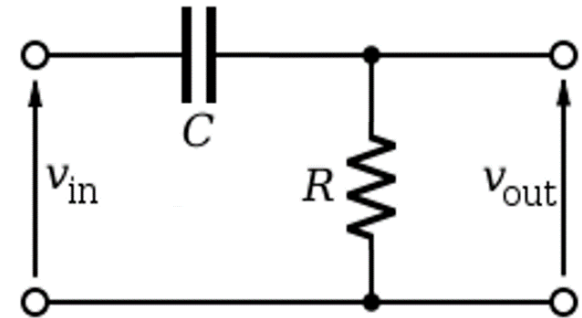
# Passive High-Pass Filter

- Using **voltage divider rule** to find the **voltage gain**:

$$\rightarrow V_{\text{out}} = \left[ \frac{R}{R + \frac{1}{j\omega C}} \right] V_{\text{in}}$$




$$\rightarrow \frac{V_{\text{out}}}{V_{\text{in}}} = \left[ \frac{R}{R + \frac{1}{j\omega C}} \right] = \left[ \frac{1}{1 - \frac{j}{\omega CR}} \right] = \frac{1 \angle 0^\circ}{\sqrt{1^2 + \left( \frac{1}{\omega CR} \right)^2} \angle \theta^\circ}$$

$$\rightarrow \left| \frac{V_{\text{out}}}{V_{\text{in}}} \right| = \left[ \frac{1}{\sqrt{1 + \left( \frac{1}{\omega CR} \right)^2}} \right] = \underbrace{20 \log_{10} 1}_{\text{Passband gain (= 0 dB)}} - \underbrace{20 \log_{10} \sqrt{1 + \left( \frac{1}{\omega CR} \right)^2}}_{\text{Change in gain with } \omega \text{ (-3 dB occurs at } f_H \text{)}} \text{ dB}$$

Magnitude

# Active Low-Pass Filter

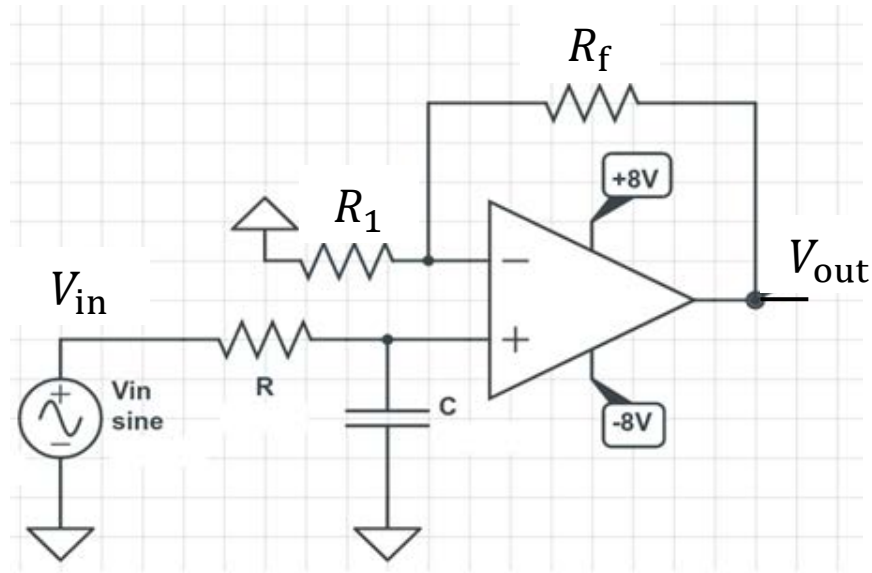

$$\frac{V_{out}}{V_{in}} = \frac{V_{out}}{V_{+}} \times \frac{V_{+}}{V_{in}} = \left(1 + \frac{R_f}{R_1}\right) \frac{V_{+}}{V_{in}}$$

Hence,

$$\left| \frac{V_{out}}{V_{in}} \right| = \left(1 + \frac{R_f}{R_1}\right) \frac{1}{\sqrt{1 + (R\omega C)^2}}$$




# The Need for Amplifying Signals


- Voltage output from sensors may be in the order of **mV**, e.g., microphone signals
- The sensor voltage output would need to be scaled before A-to-D conversion for more accurate measurements (e.g., using Arduino Uno)
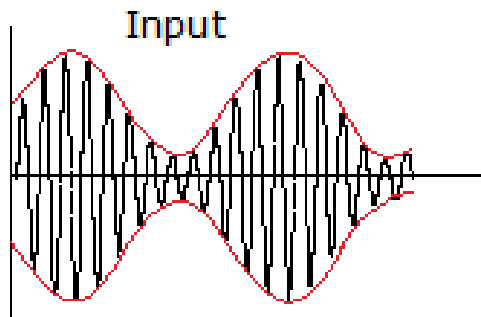
# Envelope Detector


- An envelope detector is an electronic circuit that takes a high-frequency signal as input (**sound**) and provides an output which is the envelope of the original signal
- The capacitor in the circuit stores up charge on the rising edge, and releases it slowly (through the load) when signal falls



(Sound Signal)

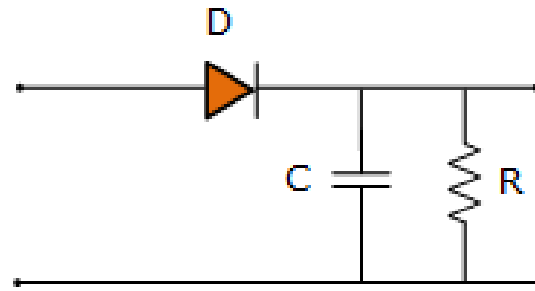


Envelope Detector

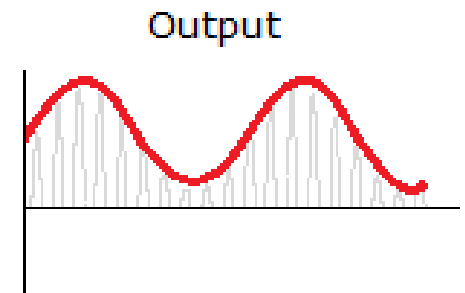


(Envelope of the Input)

# IR Proximity Sensor

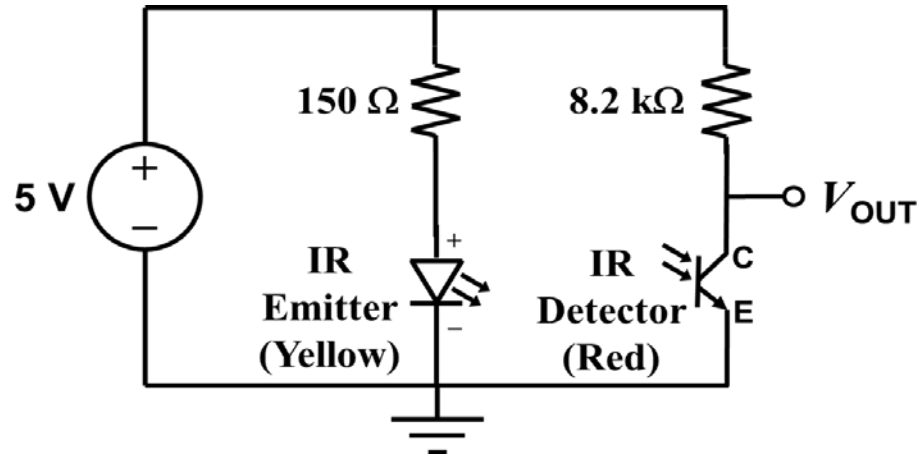

$V_{out}$  (V) vs Distance (cm)

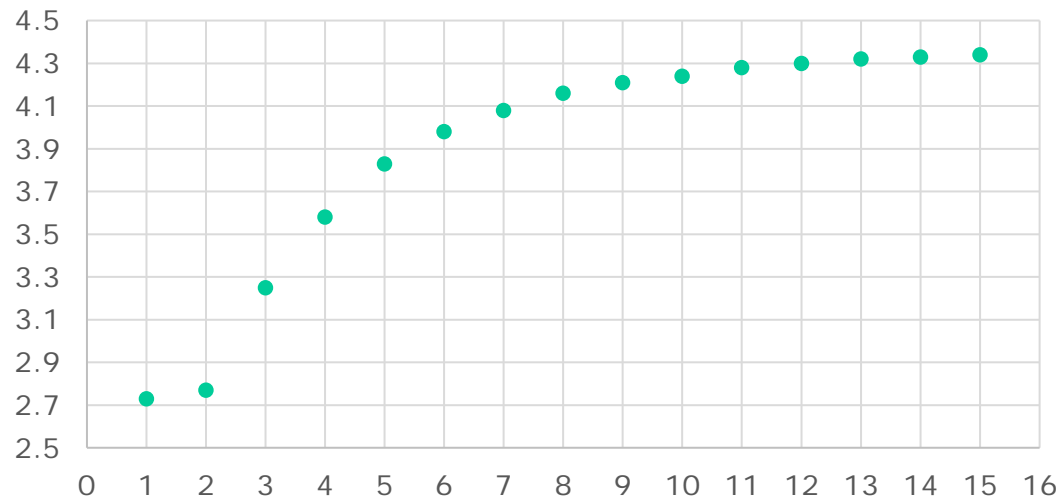


# Classification of Signals

- Continuous signals

- Independent variable is a continuous variable

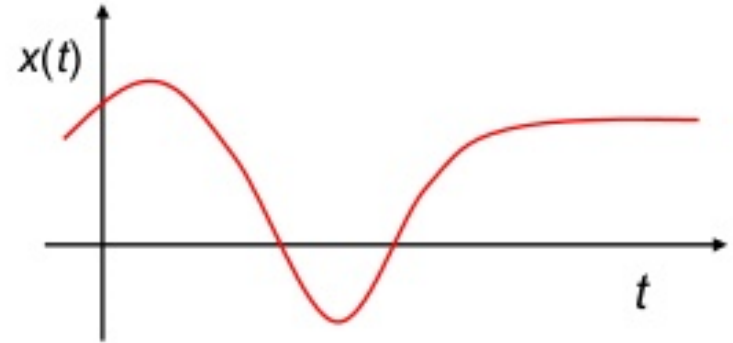- Examples

- ✓ Sine wave from a function generator
- ✓ Speech signal received from a microphone




- Discrete signals


- Independent variable takes on discrete values, e.g., integers

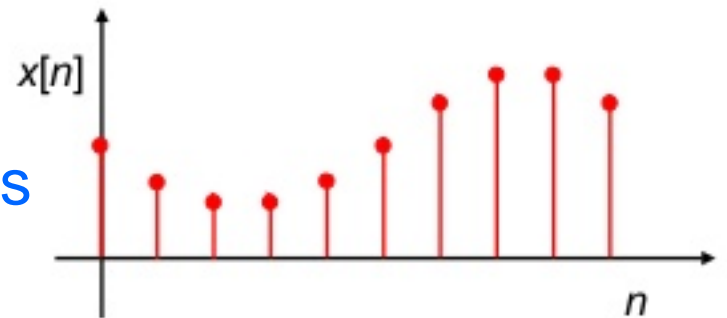- Examples


- ✓ Weekly stock market index
- ✓ Speech signal stored on a digital computer



# Continuous vs. Discrete Time Signals

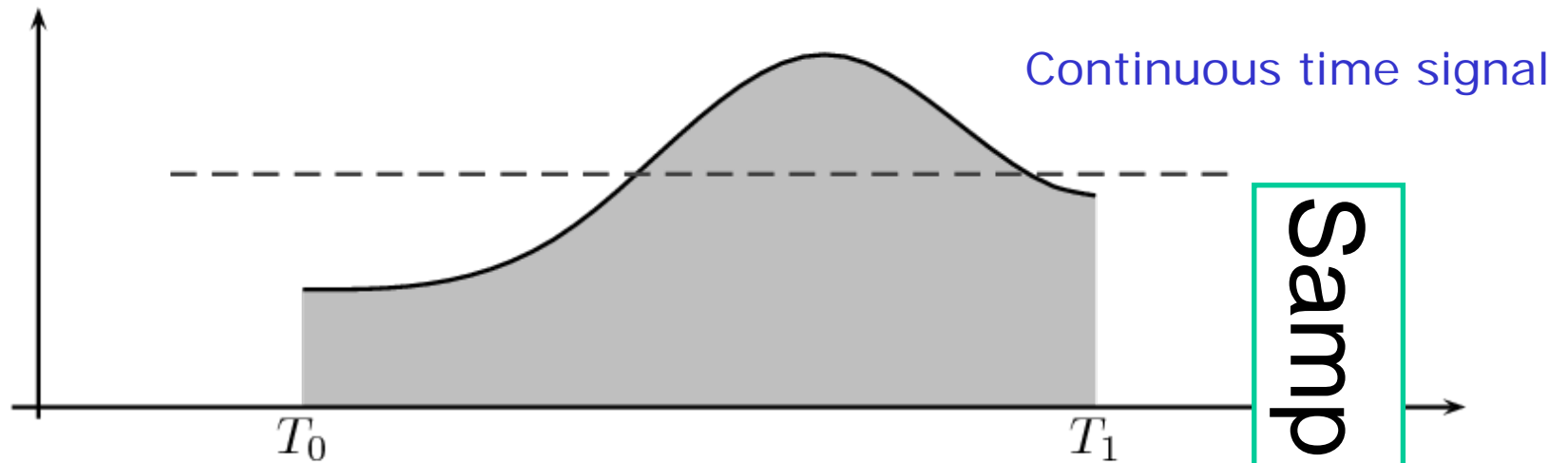

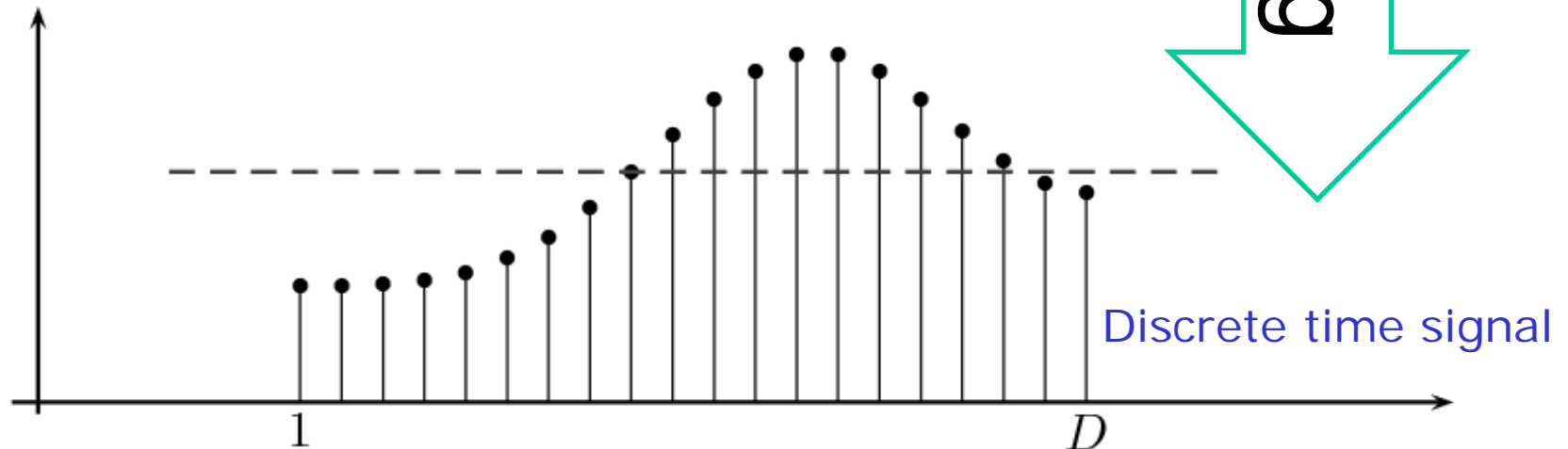The sampling rate or frequency is the number of times a signal is read per second



# Sampling Theorem

- How frequently should the signal be sampled to ensure that information contained in the signal is preserved?


$$f_s \geq 2 \times \text{max frequency component in the signal}$$

# Nyquist Rate & Nyquist Frequency

- The minimum sampling rate that is required to well represent a continuous time signal with highest frequency component  $f$  is given by  $2 \times f$  and this is known as the Nyquist rate
- For a given sampling rate  $f_s$ , perfect reconstruction is possible for a continuous signal whose highest frequency component is  $f_s/2$ , also known as the Nyquist frequency
  - For example, audio CDs use a sampling rate of 44.1 kHz. Therefore, the Nyquist frequency is 22.05 kHz
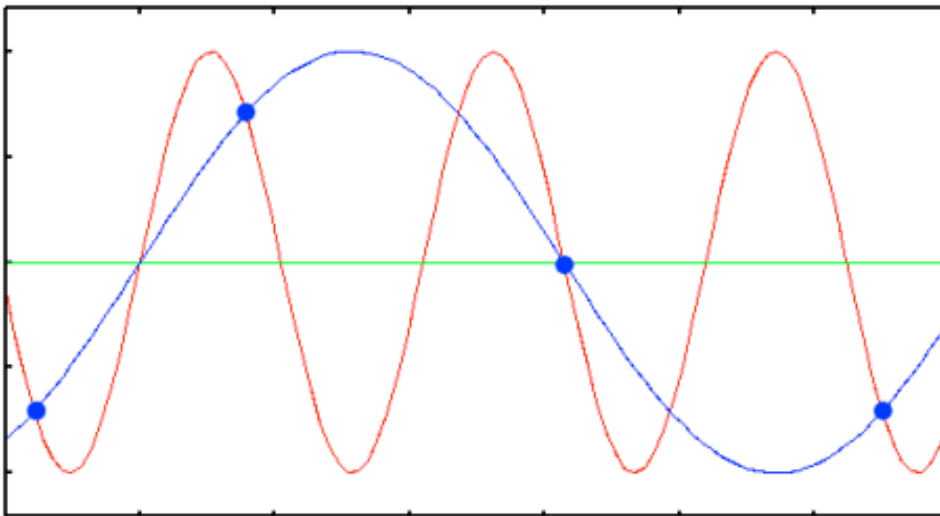
# Aliasing

- When the **sampling rate** is **lower** than the **Nyquist rate**, the signal reconstructed from samples (using DAC) is different from the original continuous signal
- This effect is known as **aliasing**



The red waveform represents the original continuous time signal


The blue dots represent samples obtained from the continuous signal with **sampling rate < Nyquist rate**



# Spectral Analysis


- Any function of time can be described as a **sum of sine waves**, each with **different amplitudes and frequencies**
- **Spectral analysis** investigates the distribution of a signal's **frequency components**
- The plot of a signal's **frequency components** and their corresponding **magnitudes** is called "**frequency spectrum**"

# Example of Frequency Spectrum

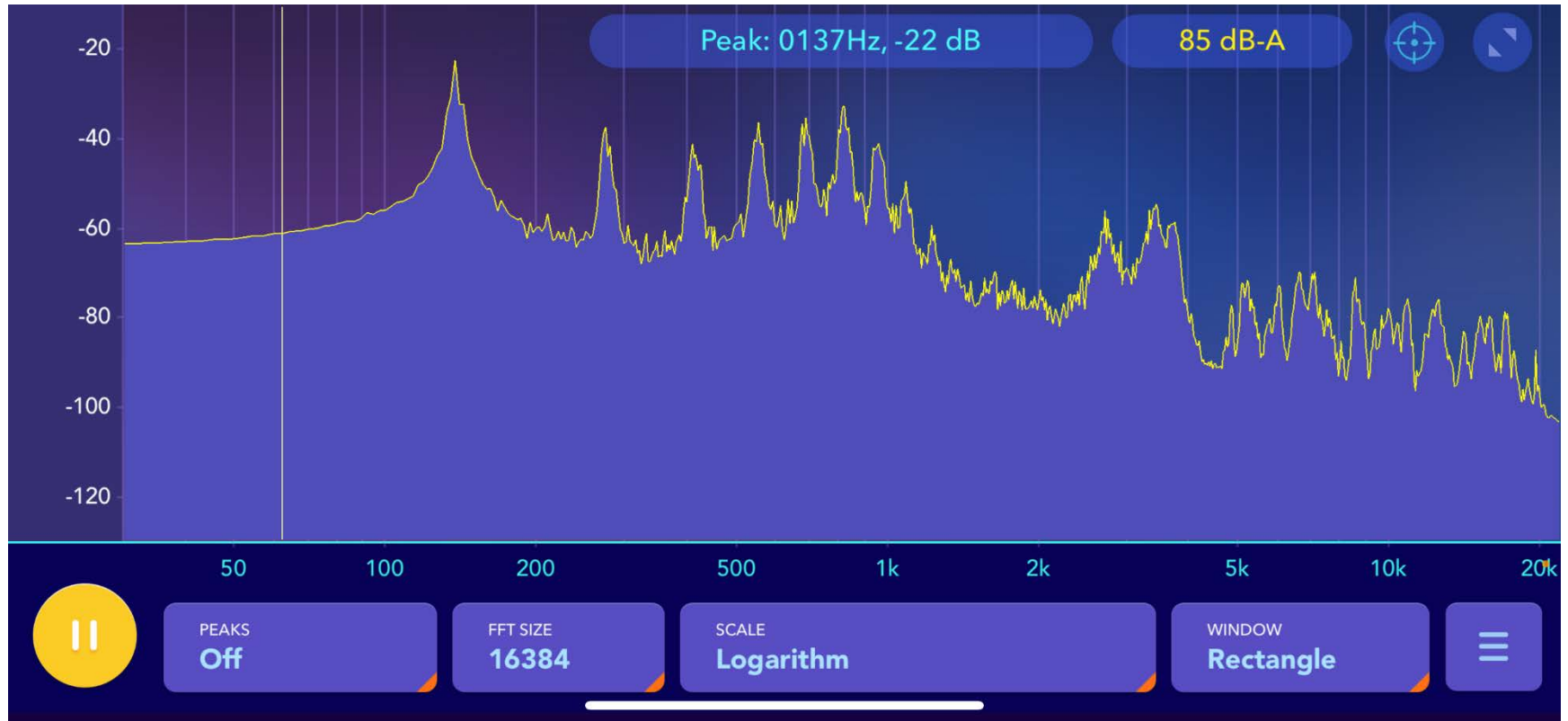

The frequency spectrum of a particular audio tone
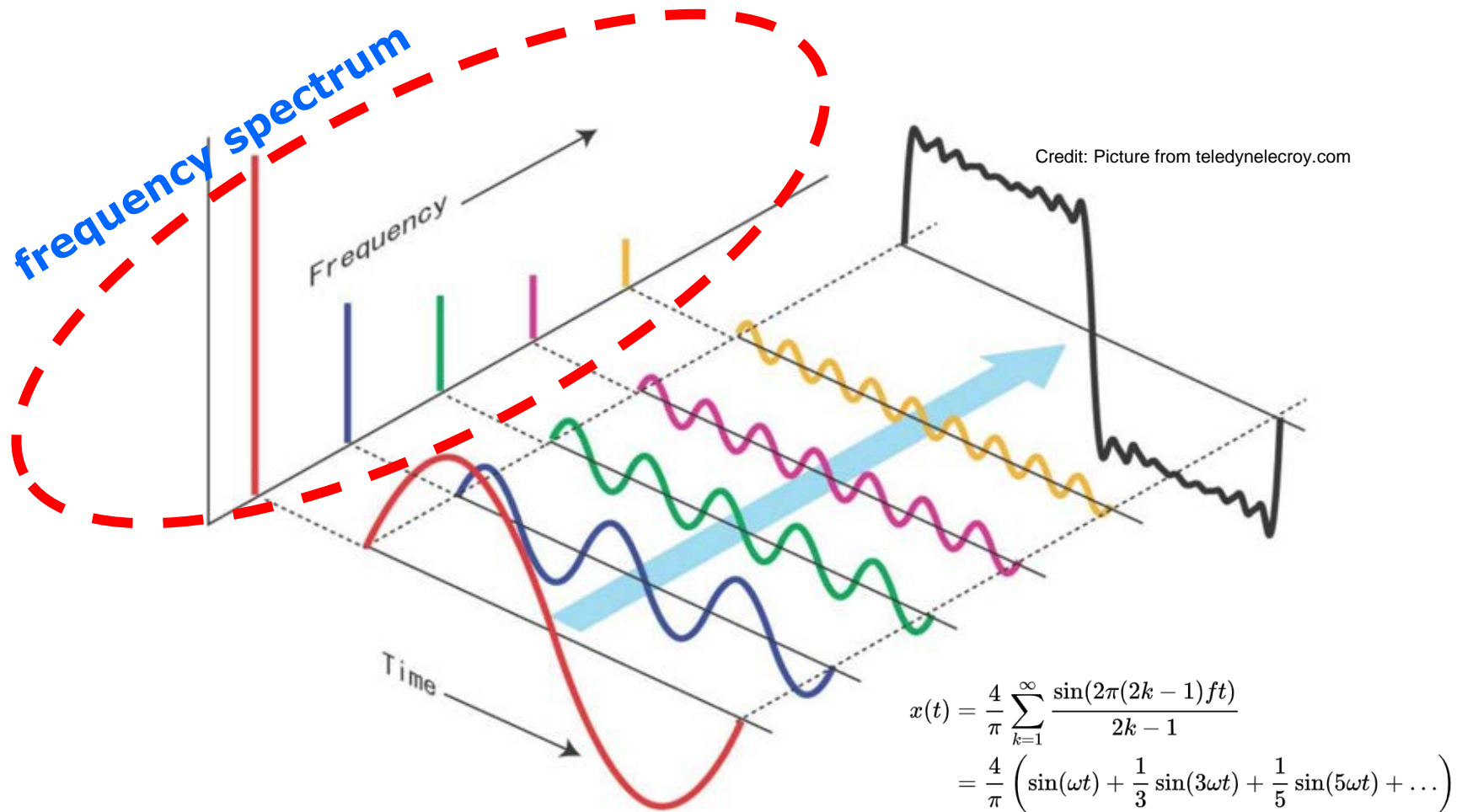
# Oscilloscope Can Help Us Perform Spectral Analysis



- A square wave (triangular waveform too) can be decomposed into an infinite sum of sinusoidal waves

# Filters Can Help Suppress (Attenuate) Undesirable Frequencies

