

CG1111: Engineering Principles and Practice I

Principles & DC Transient of Inductors




Learning Outcomes

Inductors:

- Be aware of some of their applications
- Appreciate their basic principles
- Appreciate their energy storage capability

Application: Traffic Sensor

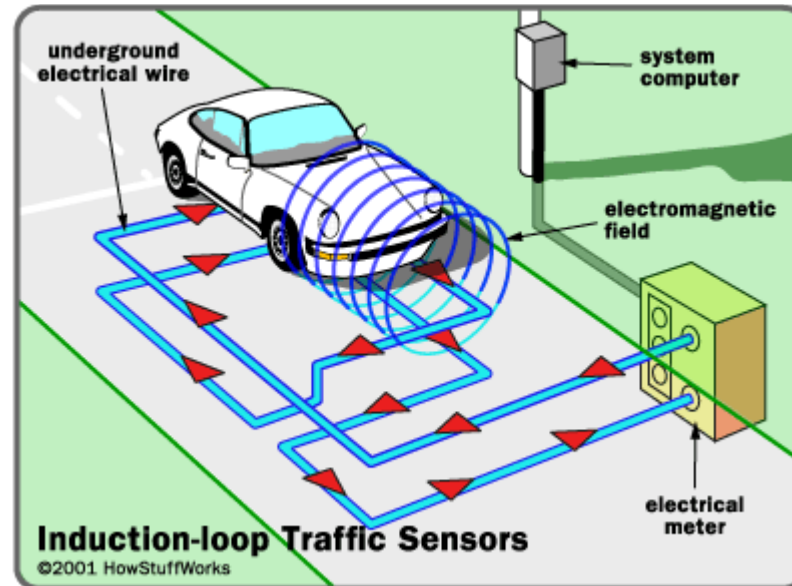


Credit: Picture from HowStuffWorks.com

- Many traffic junctions have wire coil sensors embedded underneath the roads
- When a vehicle is above the coil, its inductance increases due to the car's steel
- The change in inductance is detected by a circuit


Application: Ignition System for Spark Plugs

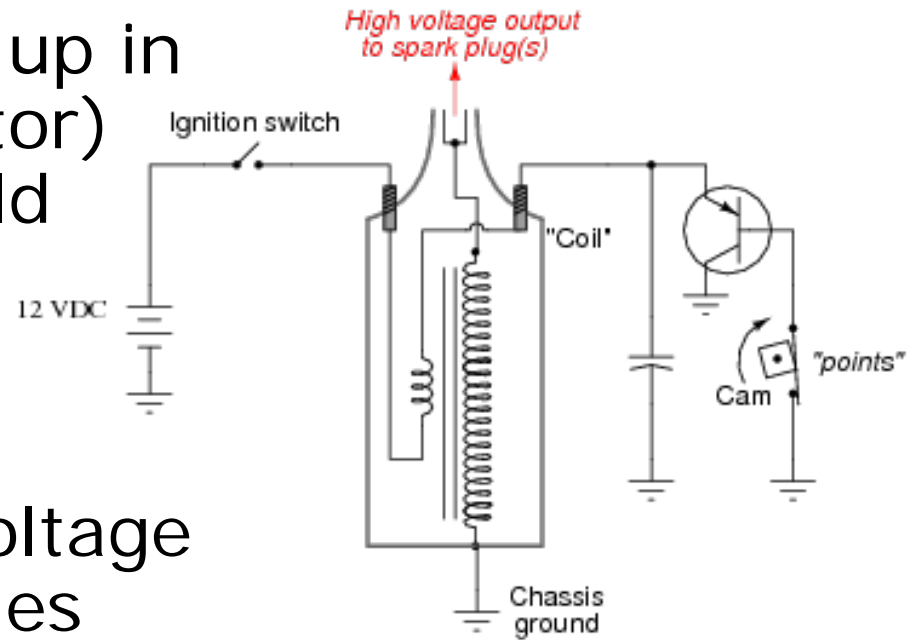- Allows current is built up in ignition coil (an inductor) → stores magnetic field energy
- When current is interrupted, a large voltage occurs across electrodes
- Fuel-air mixture becomes ionized & an electrically conductive channel develops → spark!



Generates a spark to ignite fuel-air mixture in petrol car's engine


Examples of Inductors

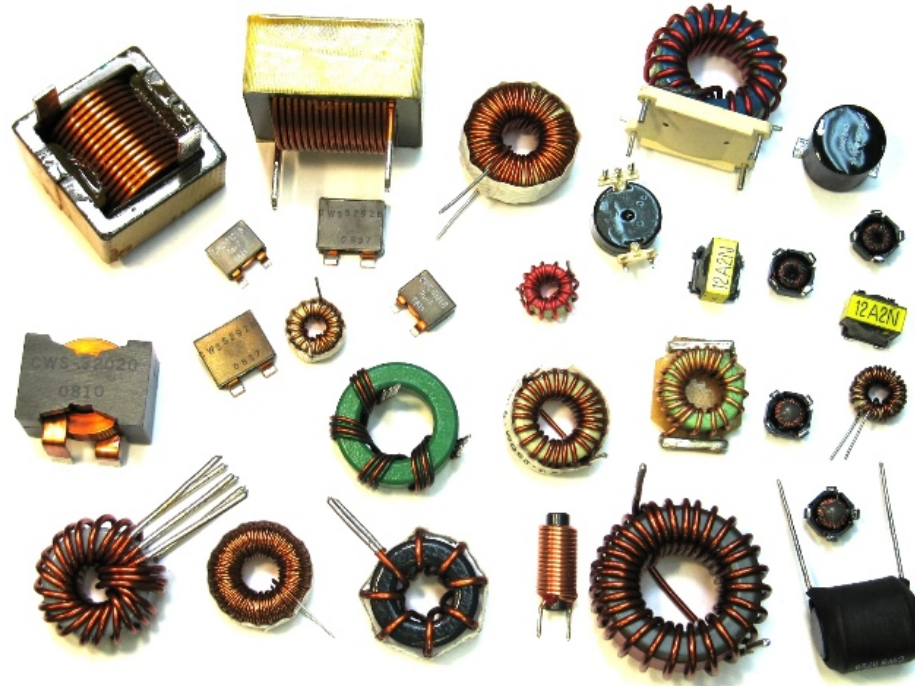

Credit: Picture from Autodesk.com

Principle Construction of Inductor

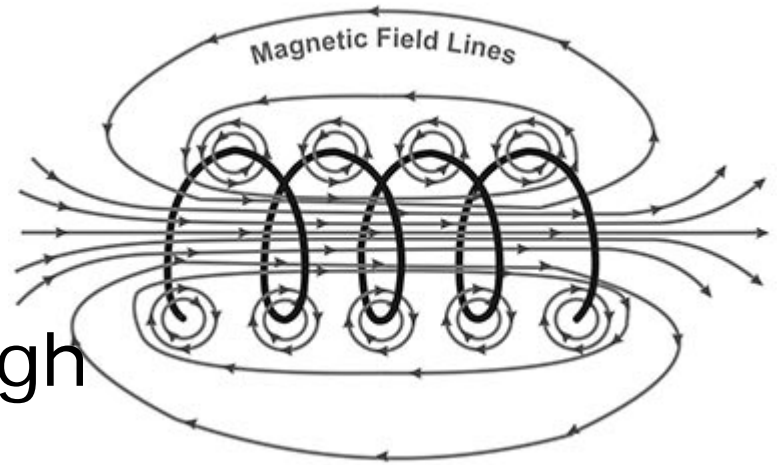- Constructed by coiling a wire in some form
- A current flowing through the coil produces a **magnetic flux Φ** that is proportional to this current
- The proportionality constant is called the "**Inductance**": **$\Phi = Li$**



Credit: Picture from Autodesk.com

Faraday's Law

- A voltage is induced in a coil when the magnetic flux varies with time

$$v = \frac{d\Phi}{dt} = \frac{d(Li)}{dt}$$

- Since L is assumed to be a constant:

$$v = L \frac{di}{dt}$$

Steady-state Voltage

- From $v = L \frac{di}{dt}$ we see that inductor has voltage only when its current is changing
- At steady state, when the current is stable, its voltage will be 0


Hence, inductors in DC circuits behave as
short-circuit in steady state

Formula for Inductance

- A coil's inductance can be determined using


$$L = \frac{\mu_r \mu_0 N^2 A}{l}, \text{ where}$$

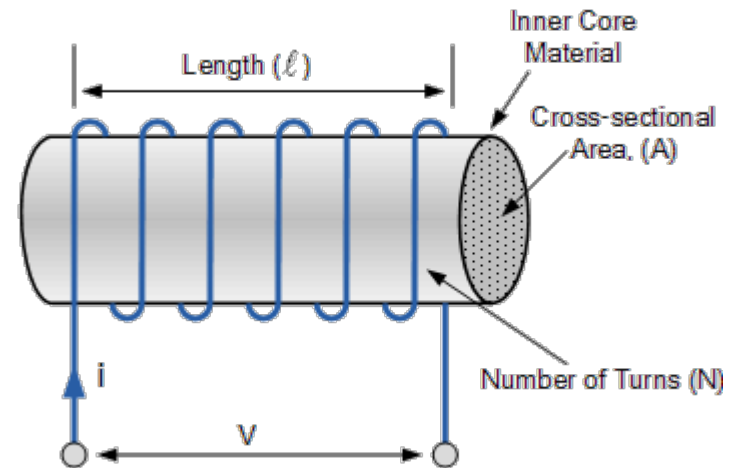- μ_r : Relative permeability of core material
- μ_0 : Permeability of free space ($4\pi \times 10^{-7}$ Wb.A/m)
- N : Number of turns in the coil
- A : Cross-sectional area of core
- l : Length of the core



Material	μ_r
Vacuum	1
Carbon steel	100
Iron	5000

Inductances in Series


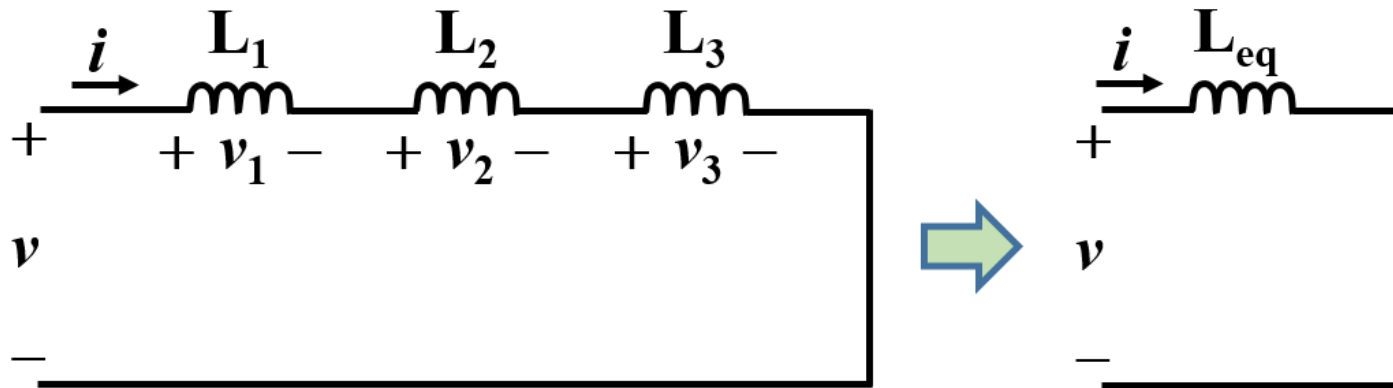


- Current is the **same** for all three inductors, but **voltage different**
- From KVL: $v = v_1 + v_2 + v_3$

$$\Rightarrow L_{eq} \frac{di}{dt} = L_1 \frac{di}{dt} + L_2 \frac{di}{dt} + L_3 \frac{di}{dt}$$

Hence, $L_{eq} = L_1 + L_2 + L_3$

Inductances in Parallel

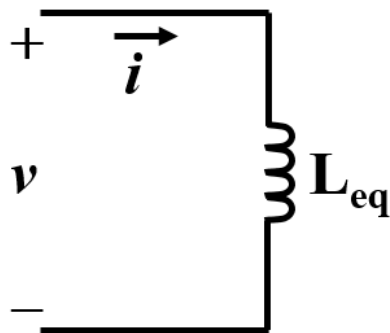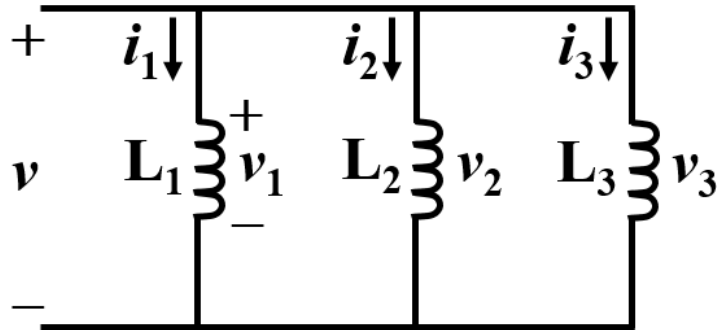

- Voltage is the same for all three inductors, but current different
- Since $v_n = L_n \frac{di_n}{dt}$
$$\Rightarrow \frac{di_n}{dt} = \frac{v_n}{L_n} = \frac{v}{L_n}$$
- From KCL: $i = i_1 + i_2 + i_3$
Hence, $\frac{di}{dt} = \frac{di_1}{dt} + \frac{di_2}{dt} + \frac{di_3}{dt}$
- $\therefore \frac{v}{L_{eq}} = \frac{v}{L_1} + \frac{v}{L_2} + \frac{v}{L_3}$

Hence,
$$\frac{1}{L_{eq}} = \frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3}$$

Energy Storage

- When current passes through an inductor, energy is stored in its magnetic field
- The stored energy can be expressed in terms of the **work done in establishing the magnetic field**
- Instantaneous power $P = iv = iL \frac{di}{dt}$
- Hence, work done is

$$W = \int_0^T P dt = \int_0^T iL \frac{di}{dt} dt = L \int_0^I i di = \boxed{\frac{1}{2} LI^2}$$

Inductor's Current Cannot Change Instantaneously!

- From earlier slide, $v(t) = L \frac{di(t)}{dt}$
- If current changes instantaneously from i_1 to i_2 (i.e., in zero time duration), then $\frac{di(t)}{dt} = \infty$


→ Impossible because it requires $v(t) = \infty$

Hence, inductor current **cannot change instantaneously**, and must be continuous

- This reluctance to change is because of the energy stored in the inductor's magnetic field

What Happens if We Try to Break Inductor's Current?

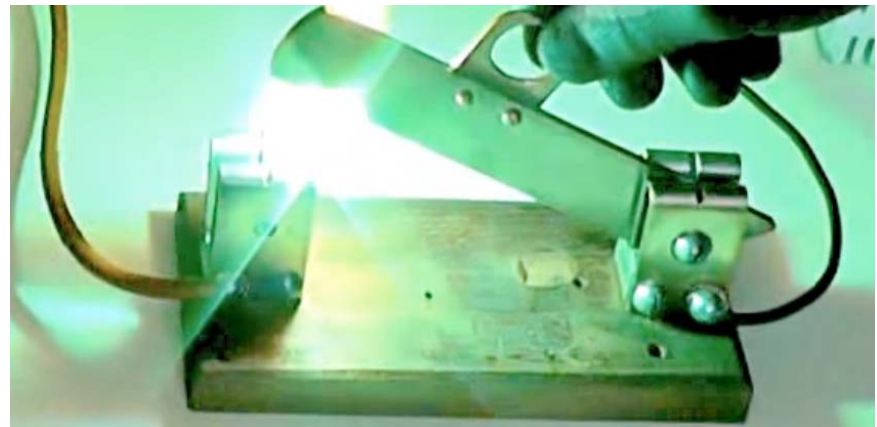- Not possible to open a switch in 0 time in real life
- The inductor's voltage becomes extremely large, but not ∞ (e.g., how spark plug works)
- The air around can breakdown causing a **flash arc** (see <https://www.youtube.com/watch?v=Zez2r1RPpWY>)



Inductor's Transient Current in a Series RL Circuit

- Following the same procedure as transient voltage analysis for capacitors, we can also derive an inductor's current when it is in a series RL circuit:

$$i_L(t) = i_L(0)e^{-\frac{t}{\tau}} + i_L(\infty)[1 - e^{-\frac{t}{\tau}}], \tau = \frac{L}{R}$$

THANK YOU