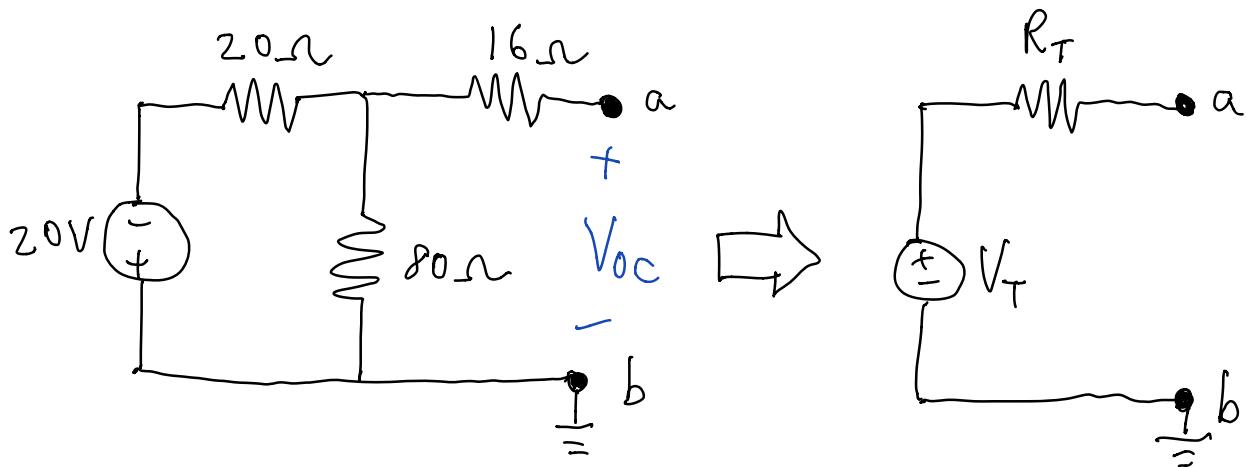



Additional Practice Questions for Thevenin Equivalent Circuits

① Find the Thevenin equivalent circuit across a & b :




$$V_T = V_{OC} = \frac{80}{20+80} \times (-20) = -16V$$

To find R_T , put source to 0 :

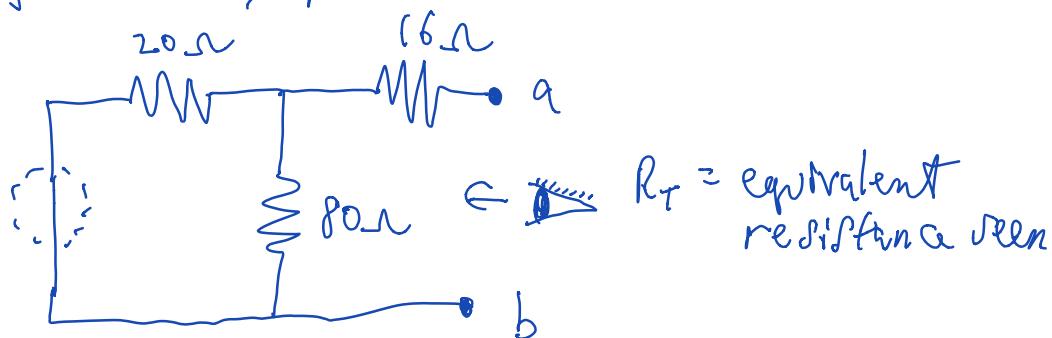


$$\therefore R_T = (20//80) + 16 = 32\Omega$$


Thevenin circuit :

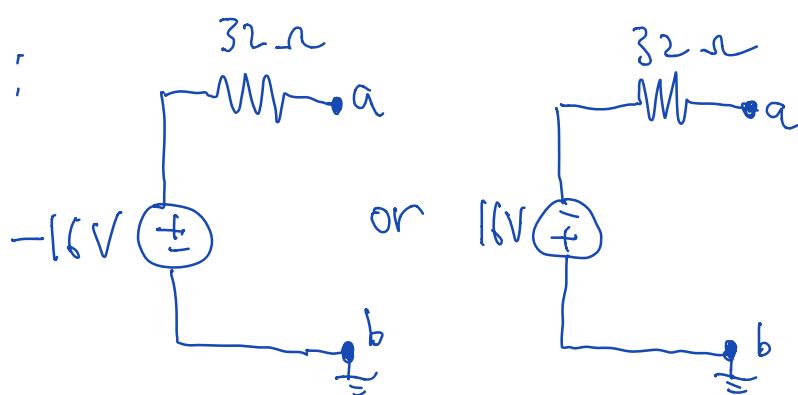

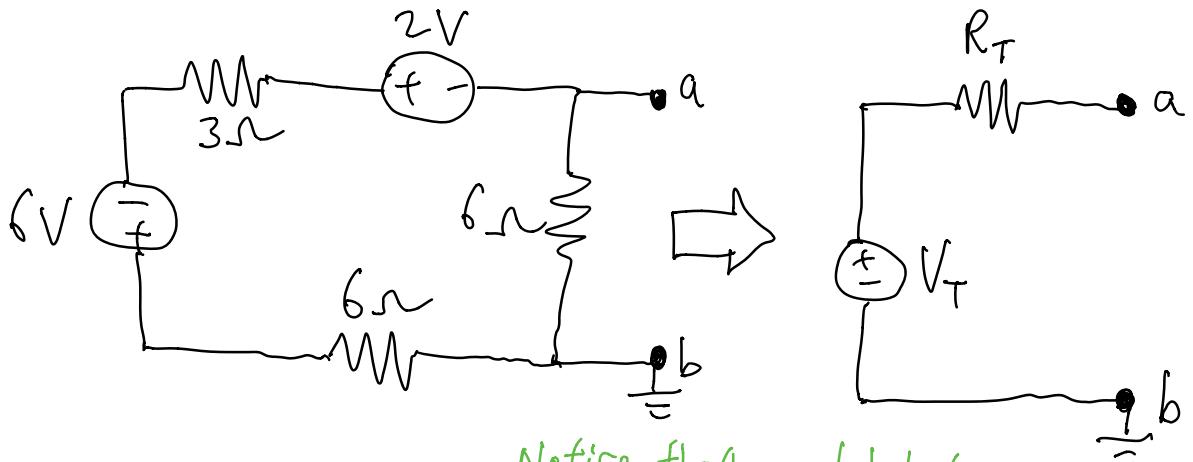
② Find the Thevenin equivalent circuit across a & b :



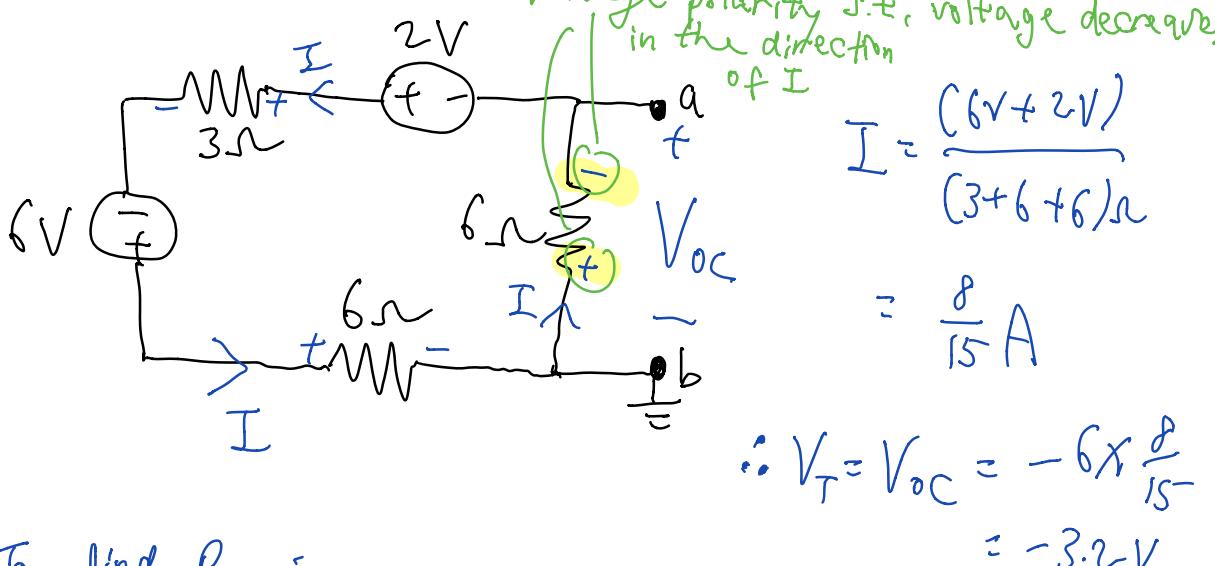Notice that we label the voltage polarity s.t. voltage decreases in the direction of I




To find R_T :


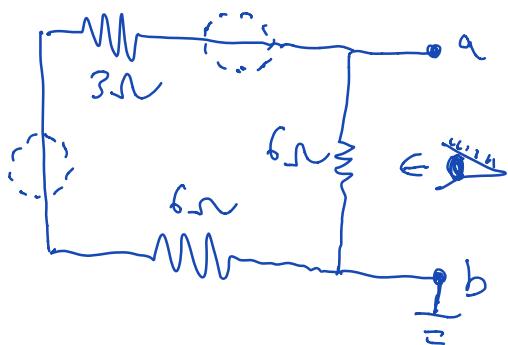


$$R_T = (3+6) \parallel 6 = 3.6 \Omega$$

Therefore,


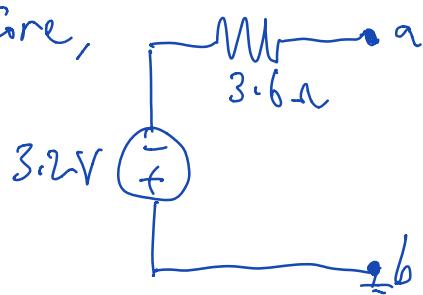


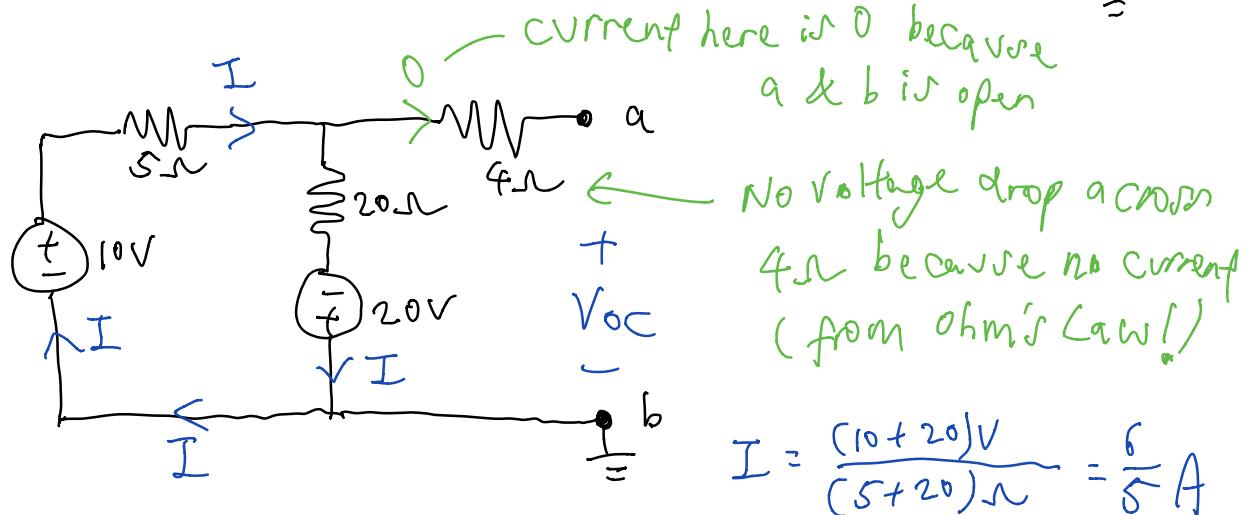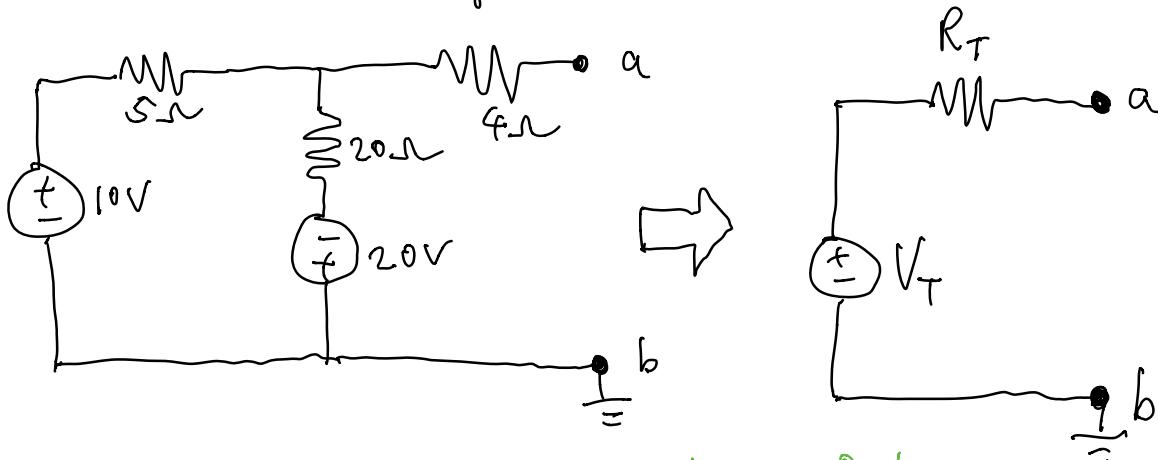③ Find the Thevenin equivalent circuit across a & b :




$$\therefore V_T = V_{OC} = (20 \times \frac{6}{5}) - 20 = 4V$$


Finding R_T :

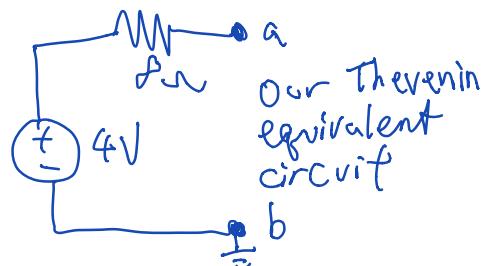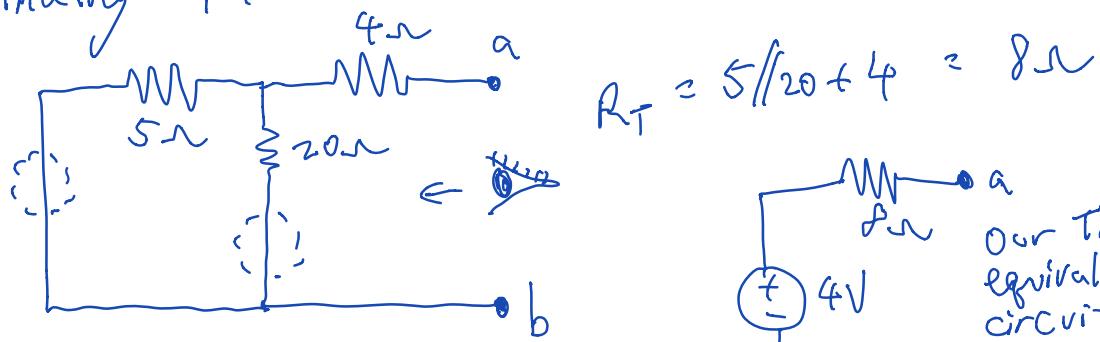

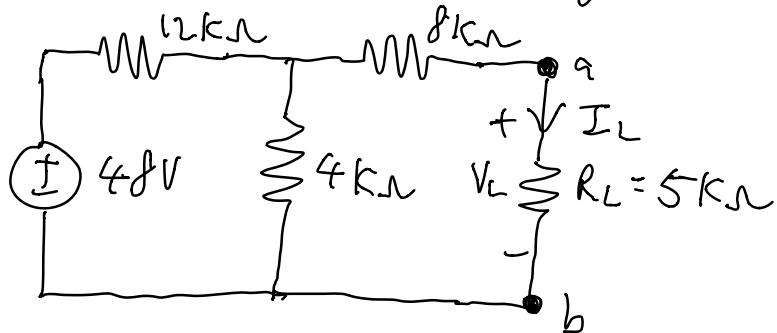- (4) In the following circuit, R_L is the load.
 Find the Thvenin equivalent circuit as seen by R_L ,
 and also the load voltage V_L and load current I_L .



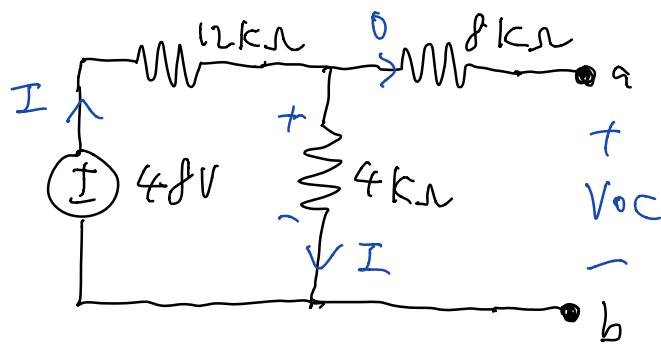
To find the Thvenin equivalent circuit seen by the load,
we must first remove the load.



$$I = \frac{48V}{(12k + 4k)\Omega} = 3mA$$


$$\begin{aligned} \therefore V_T &= V_{oc} \\ &= 4k\Omega \times 3mA \\ &= 12V \end{aligned}$$

Finding R_T :

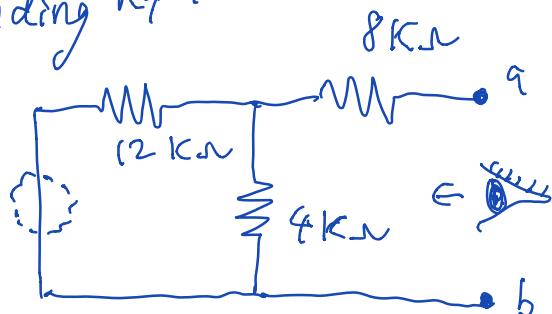


$$\begin{aligned} R_T &= (12k \parallel 4k) + 8k \\ &= 11k\Omega \end{aligned}$$

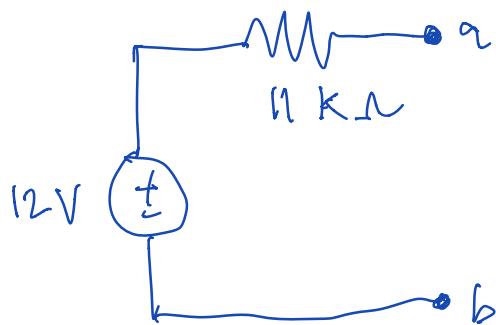; The Thvenin equivalent circuit seen by the load is :




The circuit with the load is thus :

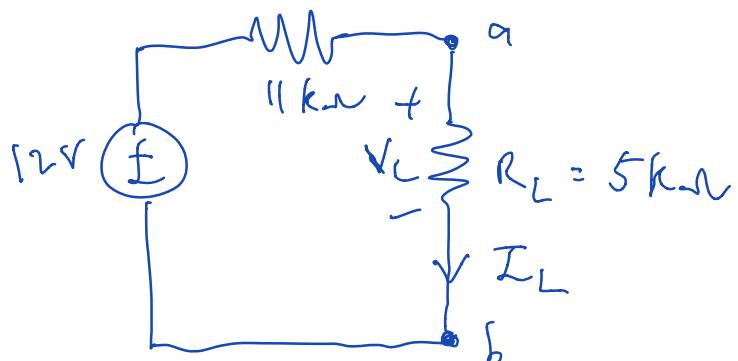


$$\therefore I_L = \frac{12\text{ V}}{(11\text{ k} + 5\text{ k})\text{ }\Omega} = 0.75\text{ mA}$$

$$\therefore V_L = \frac{5\text{ k}}{11\text{ k} + 5\text{ k}} \times 12\text{ V} = 3.75\text{ V}$$

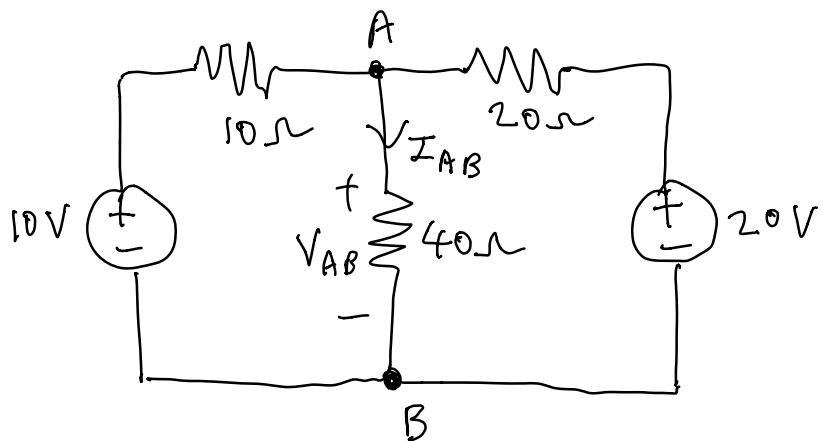- ⑤ In the following circuit, the 40Ω is the load.
 Use Thévenin equivalent circuit to solve
 for V_{AB} & I_{AB} .



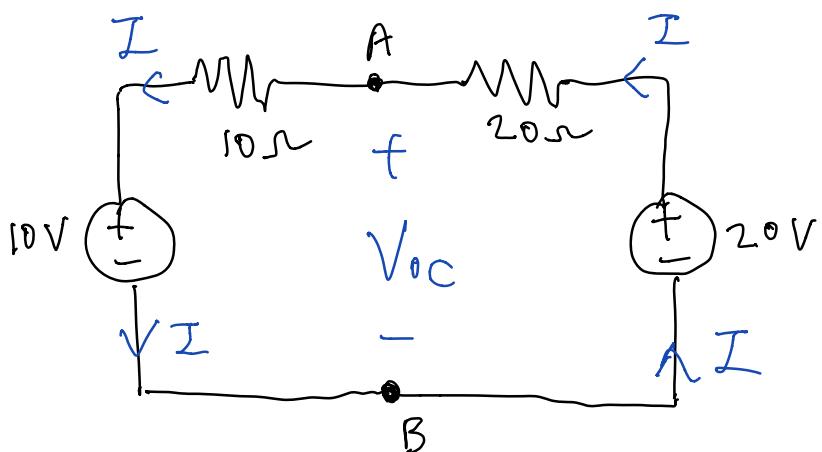
To find Thévenin equivalent circuit as seen by the load, we must first remove the load.



If you can see it directly by inspection,

$$I = \frac{(20 - 10)V}{10\Omega + 20\Omega} = \frac{1}{3}A$$

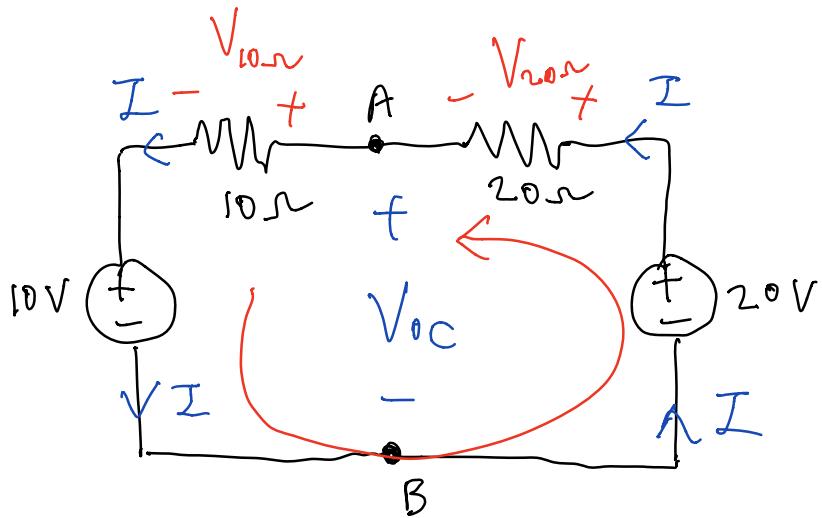If you cannot see it by inspection, you can always go to the basics by applying KVL & Ohm's Law:



Sum of voltage rise = Sum of voltage fall


$$20V = V_{10\Omega} + V_{20\Omega} + 10V$$

$$(20 - 10) = 10I + 20I$$

$$\therefore I = \frac{20 - 10}{(10 + 20)} = \frac{1}{3} A$$


$$\begin{aligned}\therefore V_T &= V_{OC} = 20 - V_{20\Omega} \\ &= 20 - 20 \times I \\ &= 13 \frac{1}{3} V\end{aligned}$$

To find R_T :

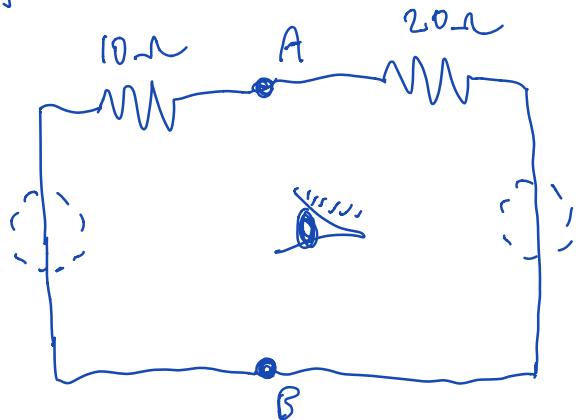

$$R_T = \text{Equivalent resistance seen across } A \& B \\ = 10 \parallel 20 = 6\frac{2}{3} \Omega$$

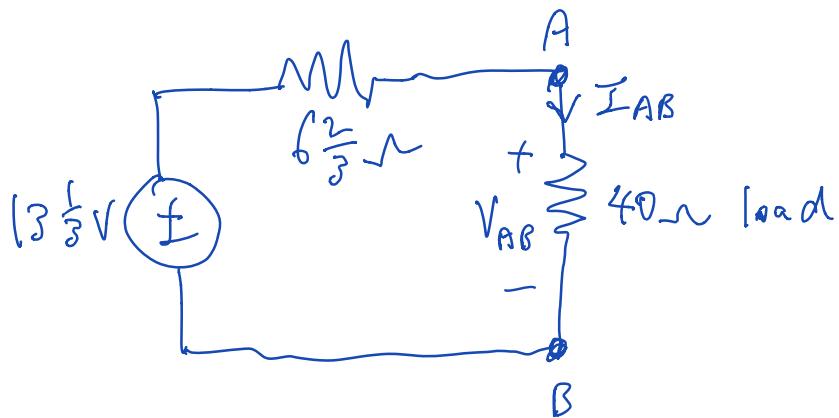∴ Our Thevenin equivalent circuit + load
is as follows:



$$\therefore V_{AB} = \frac{40}{40 + 6\frac{2}{3}} \times 13\frac{1}{3} = 11.4 \text{ V}$$

$$I_{AB} = \frac{13\frac{1}{3}}{40 + 6\frac{2}{3}} = 0.286 \text{ A}$$