


CG1111: Engineering Principles and Practice I

Fundamentals of Electricity



What We'll Learn

- Basic electrical quantities

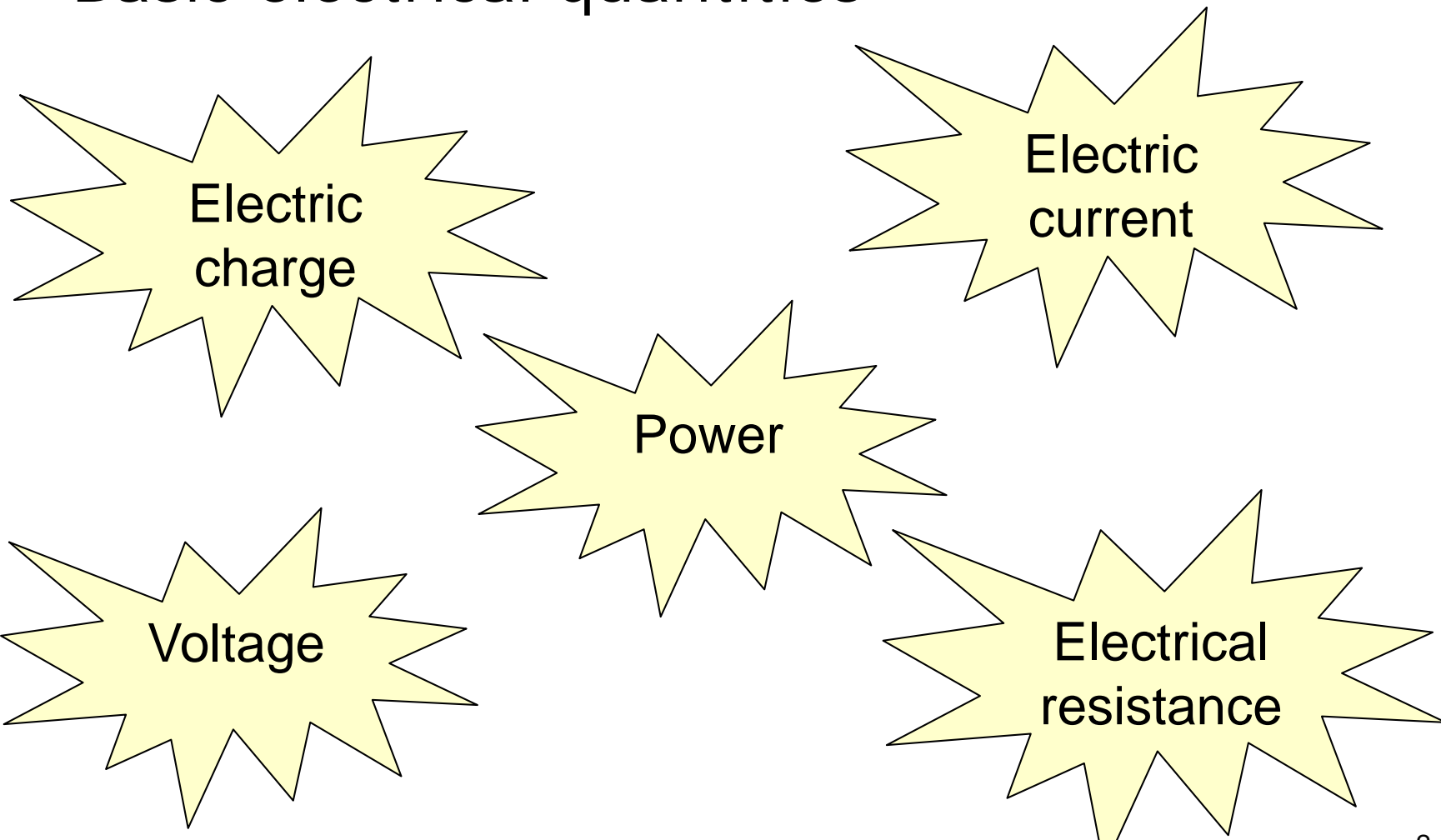

Electric
charge

Electric
current


Power

Voltage


Electrical
resistance

What is Electric Charge?

- Electric charge is the physical property of matter that causes it to experience a force when placed in an electromagnetic field
- Smallest charge that exists:
 - Charge carried by an electron: $q_e = -1.602 \times 10^{-19} \text{ C}$
 - The SI derived unit of electric charge is coulomb (C)
- In a conductor, when under the influence of an electric field, electrons will move, giving rise to an electric current

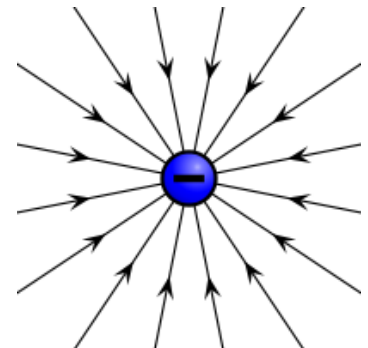

Voltage: The Pressure of Electricity

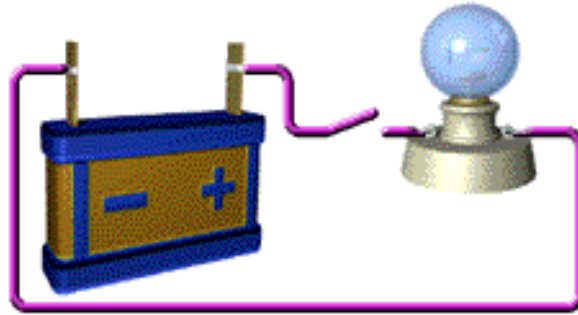

Credit: Picture from Intel

- There is something about the battery that pushes the electricity...

Voltage: The Pressure of Electricity




- Voltage: the amount of electrical pressure
- Unit of voltage: Volt (V)
- Also called electromotive force (EMF)

Voltage: A More Formal Definition

- It is a measure of the **energy transferred per unit charge** when the charge is moved from **one point to another point**
 - Unit: Volt (V), equivalent to Joules/Coulomb (J/C)
 - Voltage is always **measured across two ends** of an element with labeled polarities
 - The '+' terminal is at a higher energy level than the '-' terminal




Active Element (Source)

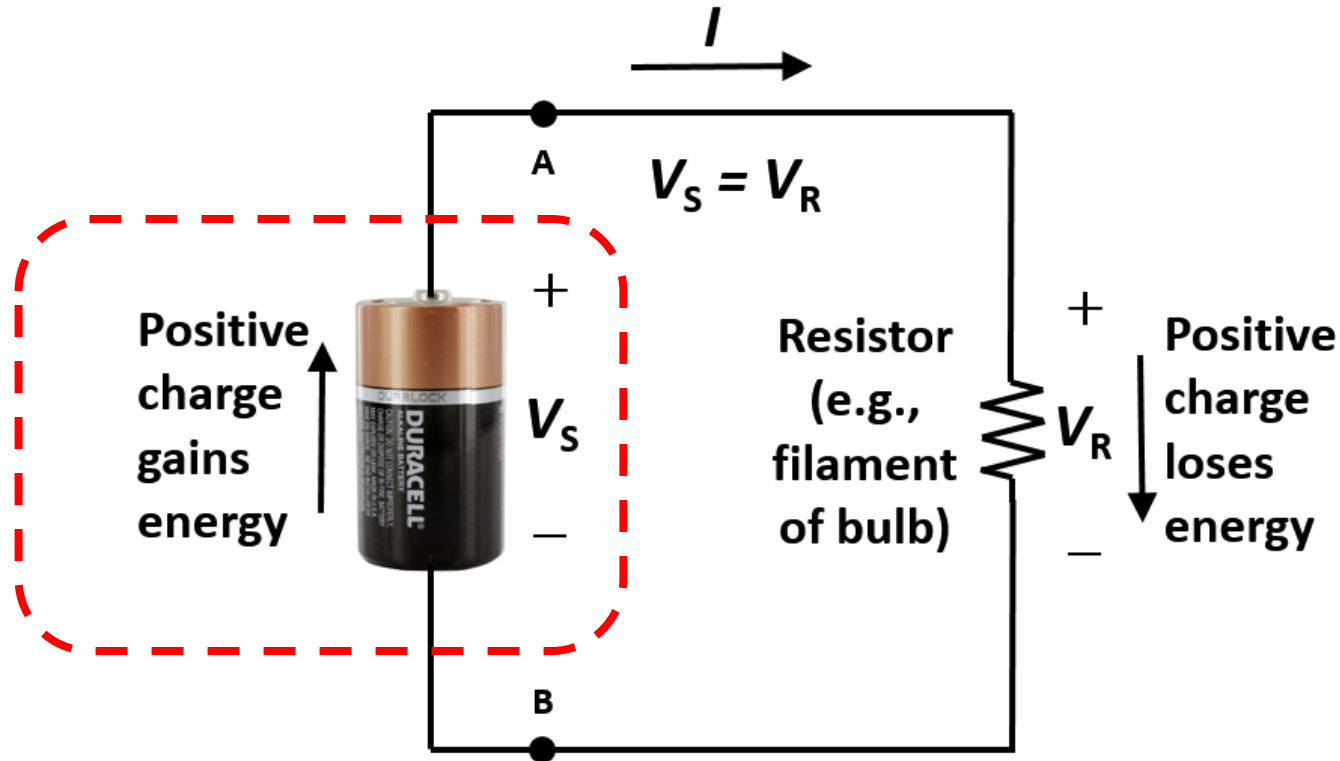

- If positive charge **enters** the **negative** polarity & **exits** the **positive** polarity of an element
 - The charge gains energy from the element
 - The element is a “**source**” (**active element**)


Passive Element (Load)

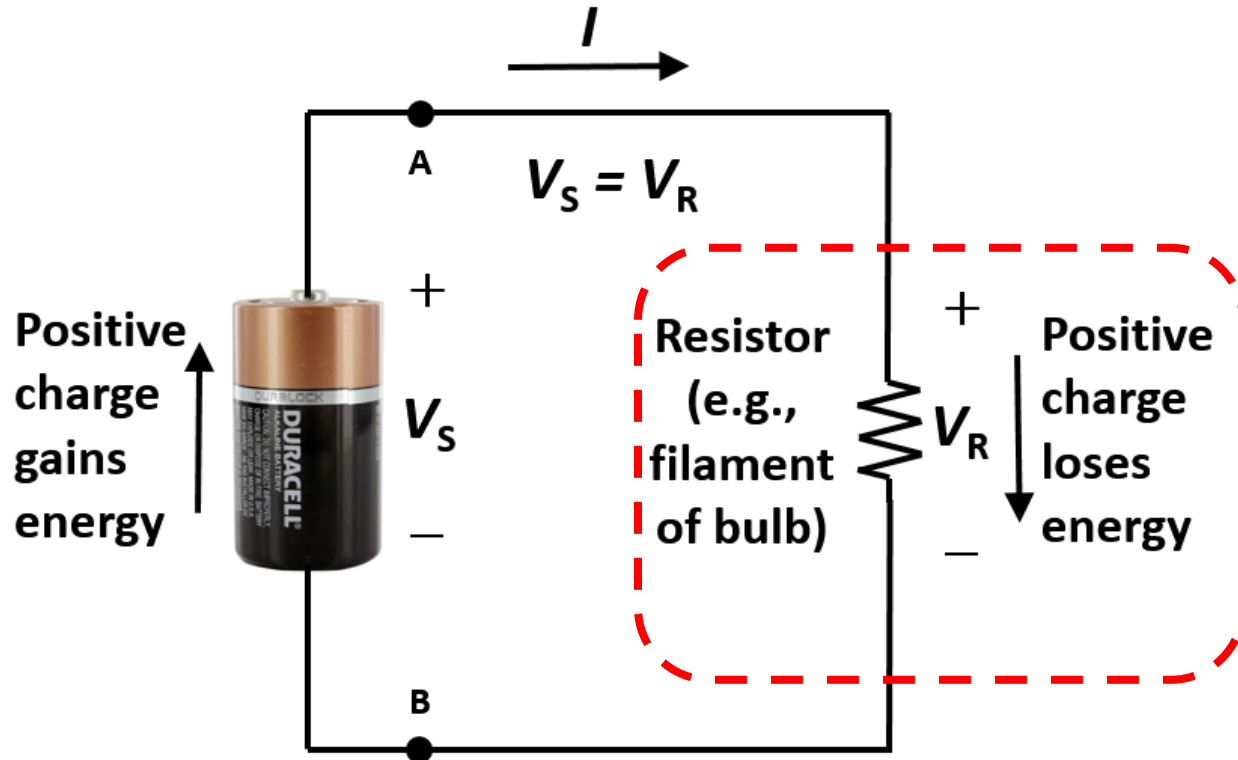

- If positive charge **enters** the **positive** polarity & **exits** the **negative** polarity of an element
 - The charge loses energy in the element
 - The element is a “load” (passive element)

Electric Current


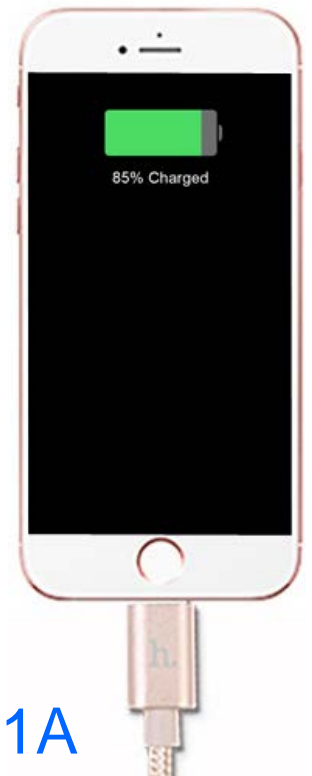
- Electric current = **time rate** of flow of electrical charges through an element
- Unit: Ampere (A)
- 1 Ampere = 1 Coulomb / second



iPhone's charging current: ~1A

Electric Current Has Direction

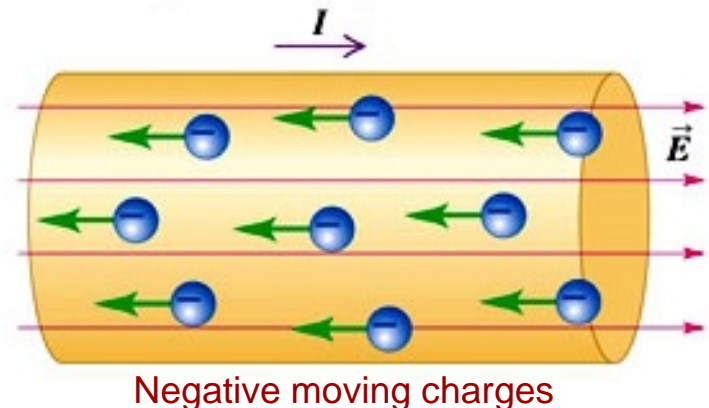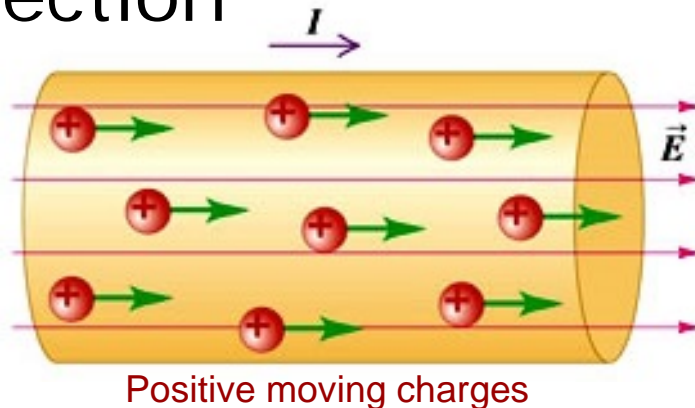- Direction of positive current = direction of flow of positive charges
 - Regardless of whether the free charges in the conductor are positive, negative, or both
- For the case of **negative** moving charges (e.g., electrons in metals), the **current** is defined to be **positive** in the **opposite** direction



Electric Power

- Recall that
 - Voltage = Energy transferred per unit charge
 - Current = Charge per unit time
- Voltage x Current = Rate of energy transfer
= Power
- Examining their units, we have
 $V \times A = (J/C) \times (C/s) = J/s = W \text{ (Watts)}$

$$P = V \times I$$

Resistance & Ohm's Law

- When electric current flows through a wire or other circuit elements, it encounters some opposition
- Ohm's Law states that the voltage across an ideal resistor is proportional to the current through it
- The constant of proportionality is called "Resistance" (unit: Ohm)

Ohm's Law:


$$V = I \times R$$

Point to Note About Ohm's Law

- Ohm's Law is an empirical relationship, i.e., observed through experiments
- It is only an approximation
 - It does not hold at very high voltage & current values, as well as very low voltage & current values

Resistance

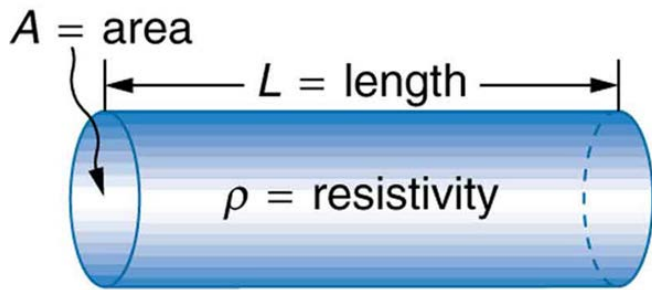- Resistance depends on the **material** as well as the **geometry** of the element




$$R = \rho \frac{L}{A}$$

Material	Resistivity ρ (Ωm)
Silver	1.629×10^{-8}
Copper	1.725×10^{-8}
Gold	2.271×10^{-8}
Aluminium	2.733×10^{-8}
Iron	9.98×10^{-8}

Practical Resistors

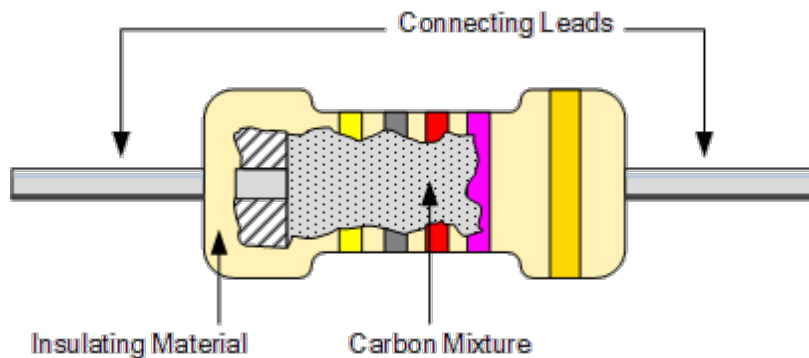- Useful in electrical circuits because you can use them to control the behaviour in other parts of the circuit



- For example, a resistor can be used to limit the current flowing through an LED:
 - To control the desired brightness
 - To prevent it from burning out

What Happens When Current Flows Through Resistance?

- Charge particles lose energy to the element → voltage drop
- Besides voltage drop, the energy loss also heats up the element
- Power loss $P_L = V \times I = (I \times R) \times I = I^2 \times R$
- Hence, $P_L \propto I^2$!!!
- Commonly used resistors in the lab → rated at 0.25 W


Practical Voltage Source

- In practice, voltage sources like batteries have internal resistance
 - There will be a voltage drop across this internal resistance (in series) when current is drawn
 - The higher the load current, the higher the voltage drop, & the higher the power loss

$$V_{AB} = V_{oc} - I_L R_{in}$$



≡

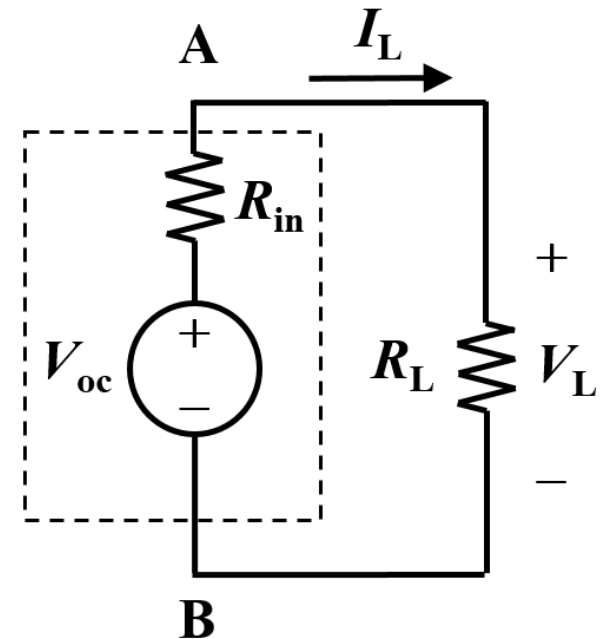

Wires Must Have Sufficient Cross-Sectional Area!

- Recall that $R = \frac{\rho L}{A}$
- If $A \uparrow$, $R \downarrow$, and hence $P_L \downarrow$ for the same I
- Hence, the appropriate A for wires depend on the max current expected
 - Notice that jumper cables used for jump-starting cars are thick because of the high current
 - Otherwise wires start to melt!



THANK YOU