

# **CG1111: Engineering Principles and Practice I**

## **DC Transient Behaviour of Capacitors**




# DC Transients

What are “Transients”?

- The **time-varying voltages and currents** resulting from the **adding or removing** of a **power source** to circuits containing energy storage elements (e.g., capacitors/inductors)

# RC Circuit with a DC Source

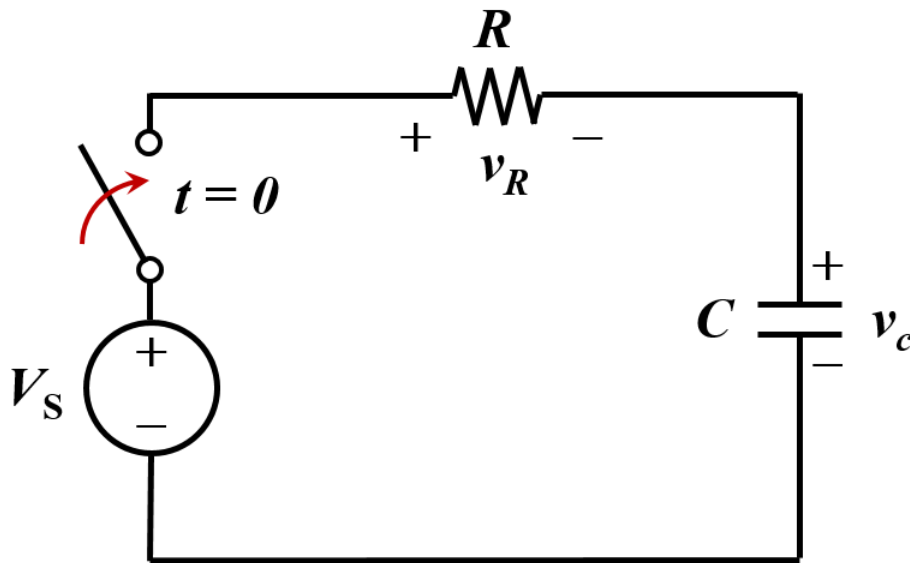

- From KVL:

$$V_S = v_R + v_c$$

- Recall:

$$i = C \frac{dv_c}{dt} \text{ and } v_R = iR$$

- Hence,

$$V_S = RC \frac{dv_c}{dt} + v_c$$

First-order differential equation

# First-order Differential Equation's Solution

- First-order differential equation:

$$\tau \frac{dx}{dt} + x = K, \text{ where } \tau \text{ \& } K \text{ are constants}$$

- Solution has the following form:

$$x(t) = x(0)e^{-\frac{t}{\tau}} + K[1 - e^{-\frac{t}{\tau}}]$$

- $\tau$  is called the "time constant"

# Capacitor's Charging Voltage in a Series RC Circuit

- From Slide 3:

$$V_S = RC \frac{dv_c}{dt} + v_c$$

- Compare with 1<sup>st</sup> order differential equation from Slide 4:


$$K = \tau \frac{dx}{dt} + x$$

- Hence, the solution is

$$v_c(t) = v_c(0)e^{-\frac{t}{\tau}} + V_S[1 - e^{-\frac{t}{\tau}}], \tau = RC$$

Note that  $V_S$  is actually  $v_c(\infty)$

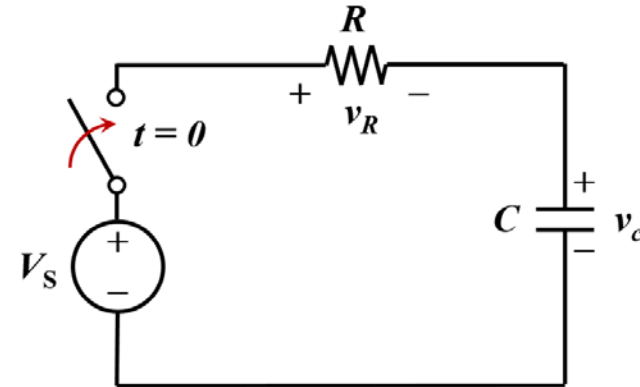- If  $v_c(0) = 0$ , then  $v_c(t) = V_S[1 - e^{-\frac{t}{\tau}}], \tau = RC$



# Capacitor's Discharging Voltage in a Series RC Circuit

- Following the same procedure, we can derive a capacitor's voltage when it is discharging through a resistor connected in series:

$$v_c(t) = v_c(0)e^{-\frac{t}{\tau}}, \text{ where } \tau = RC$$


- Hence, a more general form of a capacitor's transient voltage in a **series RC circuit** can be expressed as

$$v_c(t) = v_c(0)e^{-\frac{t}{\tau}} + v_c(\infty)[1 - e^{-\frac{t}{\tau}}], \tau = RC$$

# Shape of First-order Transient

Charging:  $v_c(t) = V_S[1 - e^{-\frac{t}{\tau}}]$       Discharging:  $v_c(t) = v_c(0)e^{-\frac{t}{\tau}}$

$t$	$e^{-\frac{t}{\tau}}$	$1 - e^{-\frac{t}{\tau}}$
$\tau$	0.368	0.632
$2\tau$	0.135	0.865
$3\tau$	0.050	0.950
$4\tau$	0.018	0.982
$5\tau$	0.007	0.993

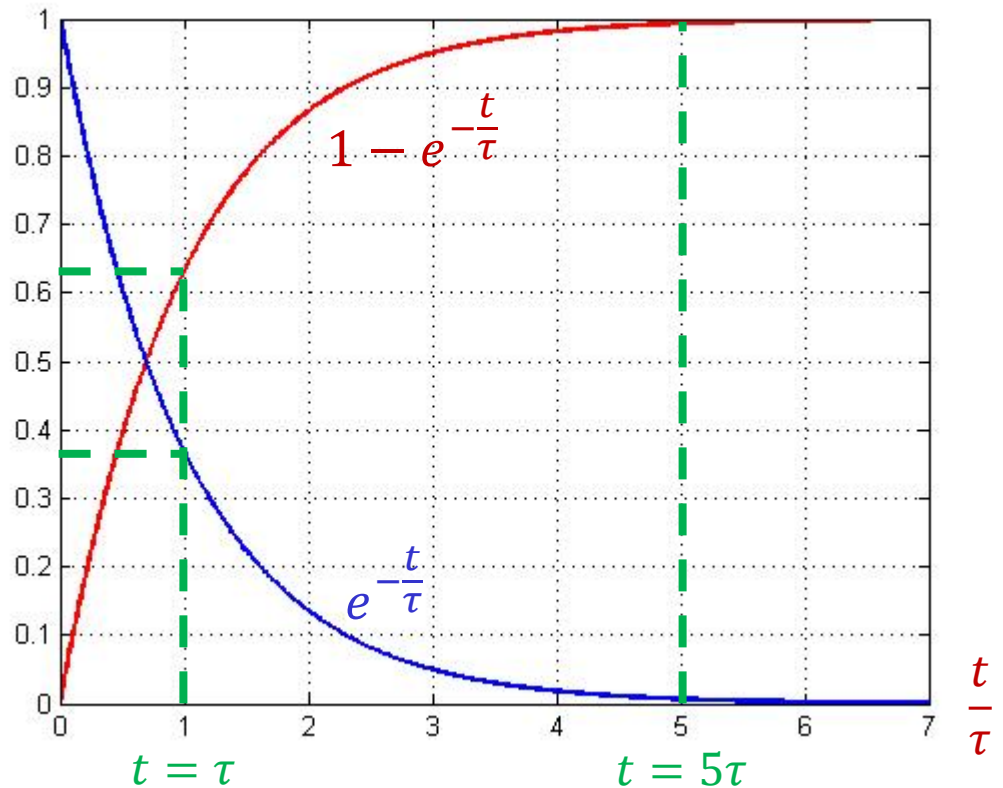

# Steps for Solving $v_c(t)$ Transient in General RC Circuits

- Use DC **steady-state analysis** of the circuit before the transient starts to find the initial values:

$$v_c(0^-) = v_c(0^+)$$

- And also the **final steady-state** values:

$$v_c(\infty)$$

- Use **Thevenin equivalent** to reduce the circuit to the standard **series RC circuit**
- Use the general form of the solution:

$$v_c(t) = v_c(0)e^{-\frac{t}{\tau}} + v_c(\infty)[1 - e^{-\frac{t}{\tau}}], \tau = RC$$



**THANK YOU**