

# **CG1111: Engineering Principles and Practice I**

## **Principles of AC Circuits**



# Learning Outcomes

- Familiarize with the common power supply distribution at home/office
- Understand the properties of sinusoidal signals:
  - Amplitude, RMS, frequency, angular frequency, and phase
- Understand AC circuit analysis technique using phasor and impedance
  - Transformation to complex domain

# 3-Pin Power Plug

Parts of Plug	Image
<p>Terminal hole marking</p> <ul style="list-style-type: none"><li>• L ('Live', also known as 'Phase')</li><li>• N ('Neutral')</li><li>• E ('Earth', also known as 'Protective')</li></ul> <p>Core colour of flexible cable</p> <ul style="list-style-type: none"><li>• L: Brown</li><li>• N: Blue</li><li>• E: Green and yellow</li></ul> <p>Fuses</p> <ul style="list-style-type: none"><li>• A 13 Ampere plug should be fitted with a 13 Ampere fuse</li></ul>	

- Between the Live (L) and Neutral (N), there is a voltage source whose value is a sine/cosine function of time
- Frequency: 50 Hz
- Some appliances may transform it internally to DC

# Sinusoidal Waveform


General expression of sinusoidal voltage:

$$v(t) = V_m \cos(\omega t + \phi)$$

$V_m$ : Peak voltage

$\omega$ : Angular frequency  
in rad/s

$\phi$ : Phase angle

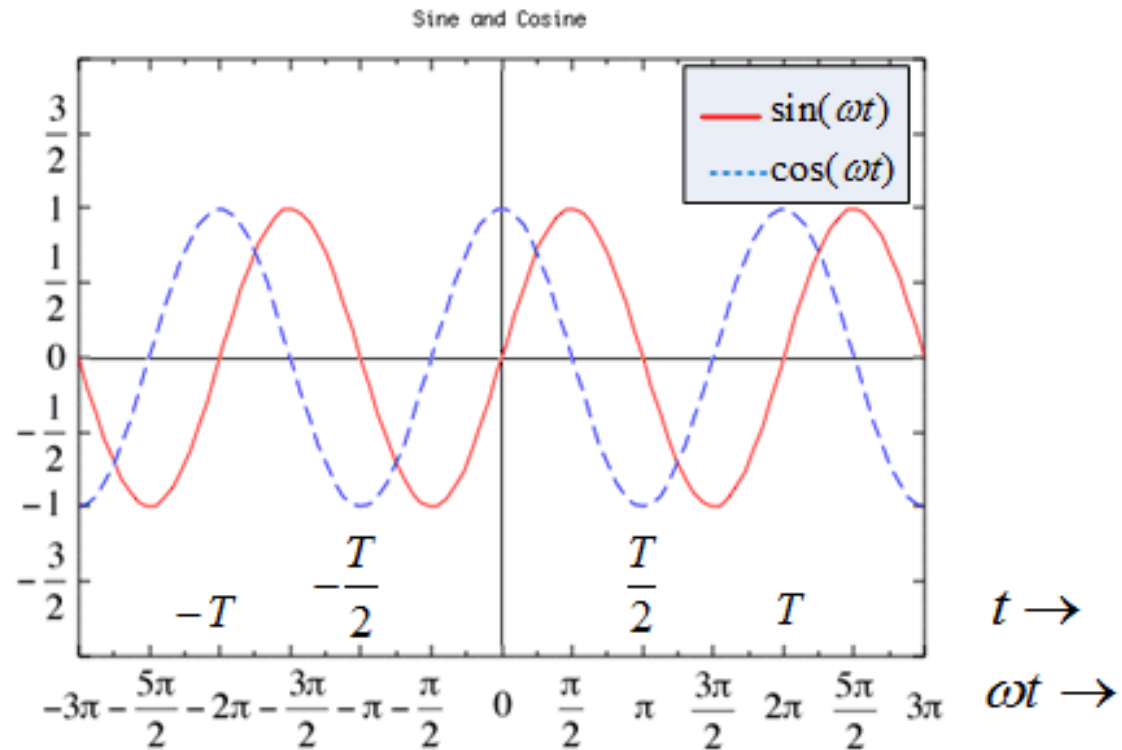

Note:

- $\omega = 2\pi f$ , where  $f$  is the frequency in Hz, i.e., number of cycles per sec
- $T = \frac{1}{f}$  is the time period which the waveform repeats itself

# Root Mean Square (RMS)

- The RMS values of AC voltage and current, are the **equivalent values** of the **DC voltage & current** that would have the **same average power dissipation** in a **resistive load**

- Average power dissipation of **resistive load** in AC:

$$P = V_{rms} \times I_{rms} = I_{rms}^2 R = \frac{V_{rms}^2}{R}$$


- Singapore's mains electricity: 230 V rms

- Definition of RMS:  $x_{rms} = \sqrt{\frac{1}{T} \int_0^T x^2(t) dt}$

- For sinusoidal waveform,  $v(t) = V_m \cos(\omega t + \phi)$ , the relationship between  $V_{rms}$  and  $V_m$  is


$$V_{rms} = \frac{V_m}{\sqrt{2}}$$
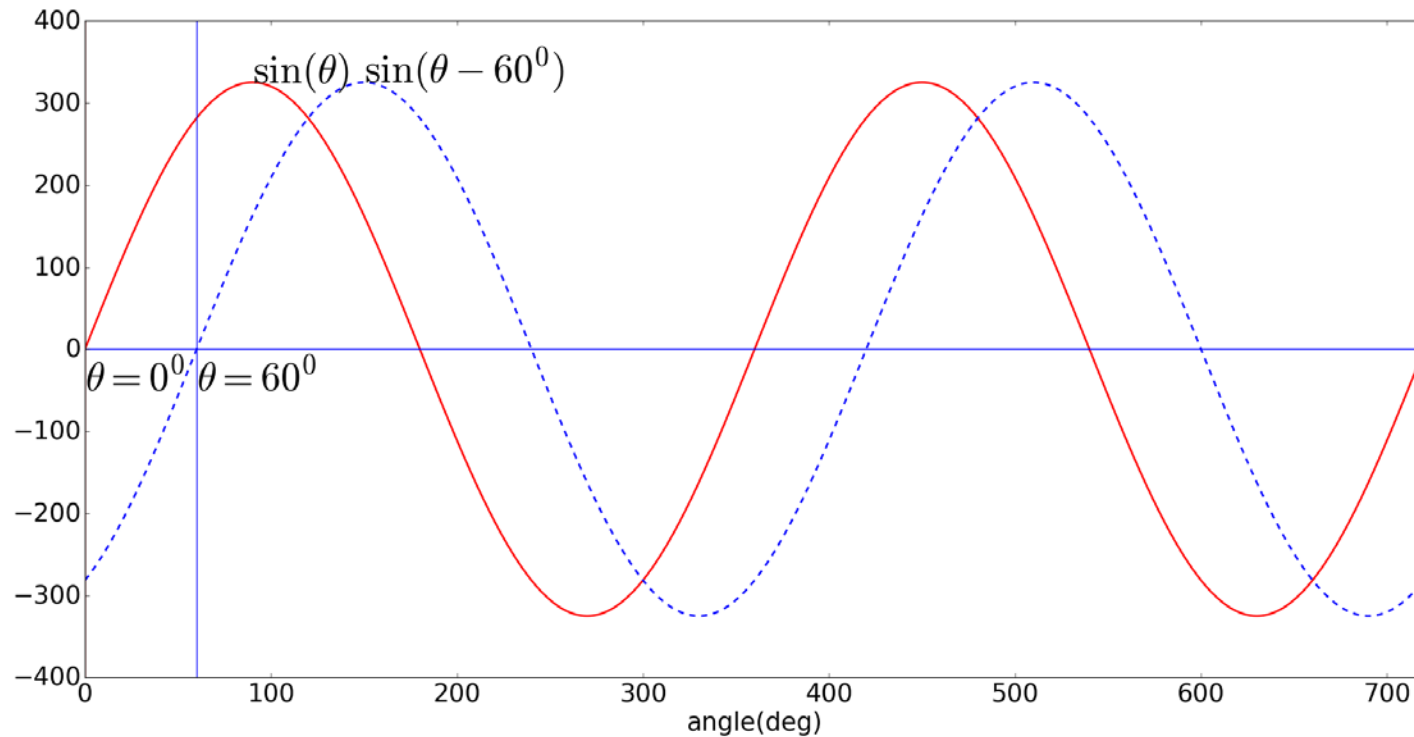
# Phase Difference Between Signals of the Same Frequency



- For signals with the same frequency, the relative position in their cycle is a measure of their phase difference
- In the above example, the blue (dotted) signal is **lagging** (behind) the red (solid) signal by  $60^\circ$

# AC Circuit Analysis in Time Domain?

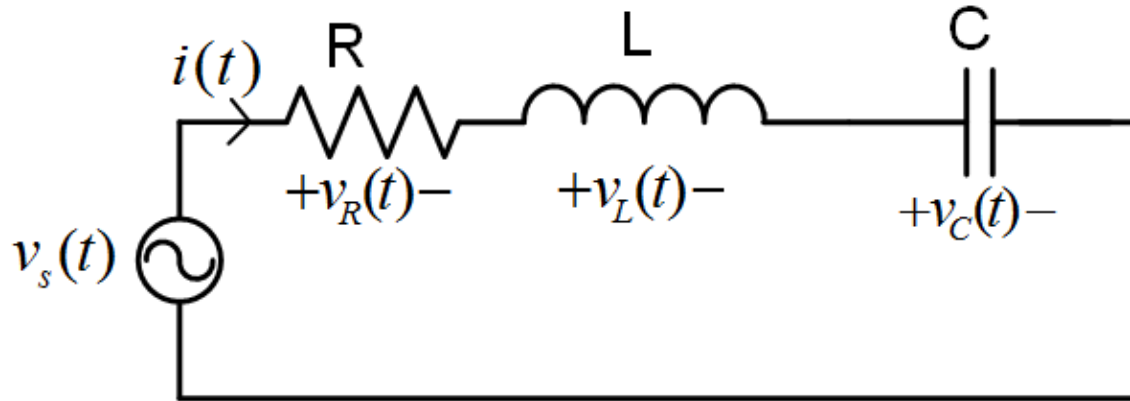

- In DC circuits, inductors/capacitors are treated as short/open at steady state → result in resistive circuits
- In AC circuits, however, they will result in differential equations:

$$V_m \cos(\omega t) = v_R(t) + v_L(t) + v_C(t) = iR + L \frac{di}{dt} + \frac{\int i dt}{C}$$

→ difficult to solve in time-domain!

# AC Circuit Analysis in Complex Domain

- Transform differential equations in time-domain into algebraic equations in **complex-domain!**
- Two mathematical terms:
  - **Phasor:** Voltage & Current sinusoids are represented by complex numbers called “Phasors”
  - **Impedance:** R-L-C are represented by their complex resistances called “Impedances”
- This converts the AC circuit to an equivalent resistive circuit with DC sources
  - Can then use DC circuit analysis techniques!



# Phasors

- Sinusoidal voltage:

$$V_m \cos(\omega t + \theta)$$

- Phasor:

$$V_m \angle \theta$$


Note:

Another common practice is to represent phasors using the **RMS value** instead of the magnitude. In that case, the phasor will be written as  $\frac{V_m}{\sqrt{2}} \angle \theta$ .

Note:

- Phasor is just a definition. It leads to **mathematical convenience**, but has **no physical significance**

# Phasor Examples


- $325 \cos(300t + 45^\circ) \rightarrow 325 \angle 45^\circ$
- $10 \cos(300t - 60^\circ) \rightarrow 10 \angle -60^\circ$
- $20 \sin(300t + 75^\circ) \rightarrow 20 \cos(300t + 75^\circ - 90^\circ)$   
 $\rightarrow 20 \angle -15^\circ$
- All signals must have the **same frequency**
- All must be converted to sine or cosine (**consistent**) before taking phase angle

# Phasor (Polar $\leftrightarrow$ Rectangular Form)

$$r\angle\theta = x + jy$$

where
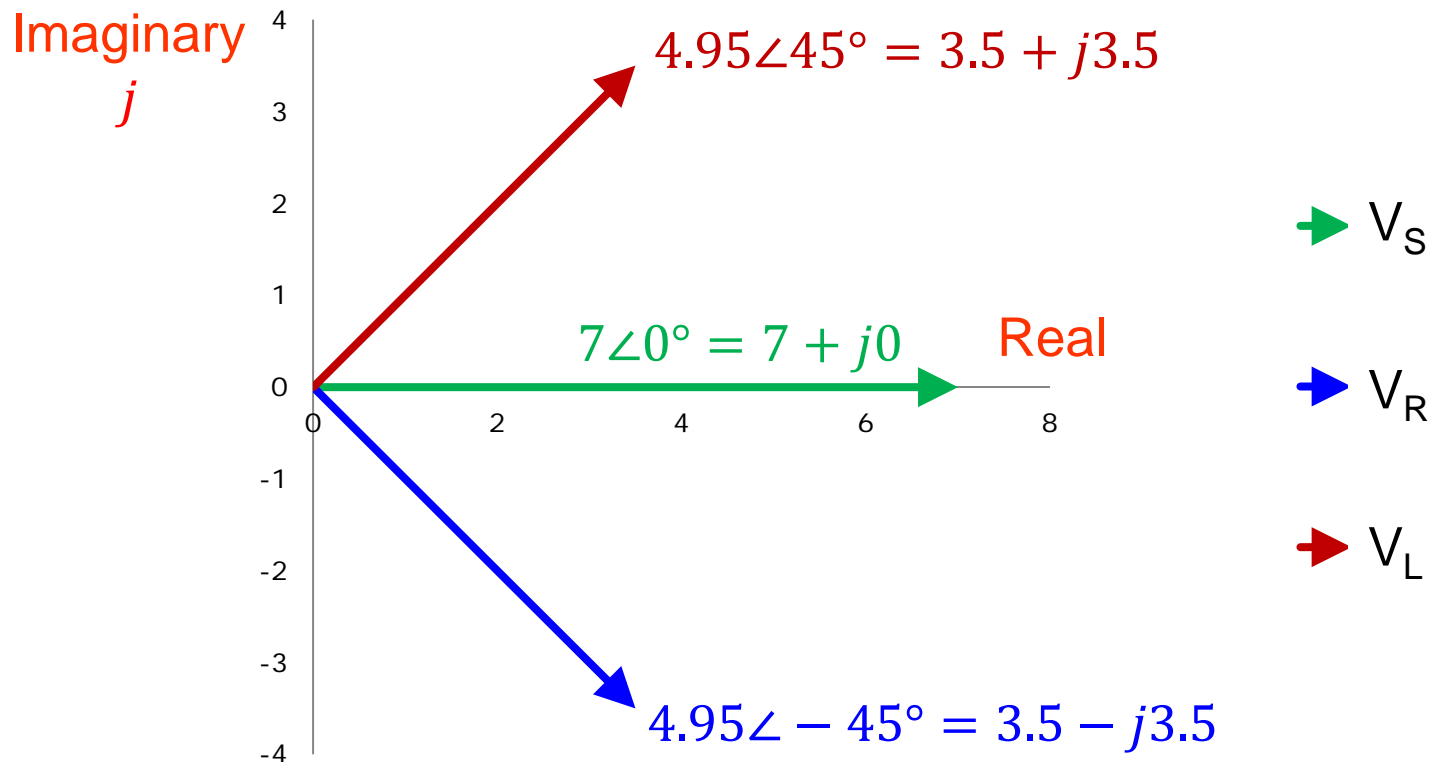
$$x = r \cos \theta$$
$$y = r \sin \theta$$



# Impedance of Inductor

- Suppose inductor current is

$$i(t) = I_m \cos(\omega t) \\ \rightarrow I_m \angle 0^\circ \text{ (Phasor)}$$

- Then its voltage is

$$v(t) = L \frac{di}{dt} = -\omega L I_m \sin(\omega t) = \omega L I_m \cos(\omega t + 90^\circ) \\ \rightarrow \omega L I_m \angle 90^\circ \text{ (Phasor)}$$

- Impedance of inductor is

$$Z_L = \frac{\text{voltage phasor}}{\text{current phasor}} = \frac{\omega L I_m \angle 90^\circ}{I_m \angle 0^\circ} = \omega L \angle 90^\circ = \boxed{j\omega L}$$

# Impedance of Capacitor

- Suppose capacitor voltage applied is

$$v(t) = V_m \cos(\omega t) \\ \rightarrow V_m \angle 0^\circ \text{ (Phasor)}$$

- Then its current is

$$i(t) = C \frac{dv}{dt} = -\omega C V_m \sin(\omega t) = \omega C V_m \cos(\omega t + 90^\circ) \\ \rightarrow \omega C V_m \angle 90^\circ \text{ (Phasor)}$$

- Impedance of capacitor is

$$Z_C = \frac{\text{voltage phasor}}{\text{current phasor}} = \frac{V_m \angle 0^\circ}{\omega C V_m \angle 90^\circ} = \frac{1}{\omega C \angle 90^\circ} = \boxed{\frac{1}{j\omega C} = \frac{-j}{\omega C}}$$

Also equal to  $\frac{1}{\omega C} \angle -90^\circ$

# Impedance of Resistor

- Suppose resistor current is

$$i(t) = I_m \cos(\omega t) \\ \rightarrow I_m \angle 0^\circ \text{ (Phasor)}$$

- Then its voltage is

$$v(t) = Ri = RI_m \cos(\omega t) \\ \rightarrow RI_m \angle 0^\circ \text{ (Phasor)}$$

- Impedance of resistor is

$$Z_R = \frac{\text{voltage phasor}}{\text{current phasor}} = \frac{RI_m \angle 0^\circ}{I_m \angle 0^\circ} = R \angle 0^\circ = \boxed{R}$$


# AC Circuit Analysis with Phasors & Impedances

Must work with KVL & KCL in **Phasor form**

Steps:

1. Replace **voltage sources** with their **phasors** (all must have same frequency)
2. Replace **R, L, C** elements with their **impedances**
3. Analyse circuit using **DC circuit analysis** techniques (work within **complex** domain)
4. Convert final results back to **time-domain**

# AC Circuit Analysis Example

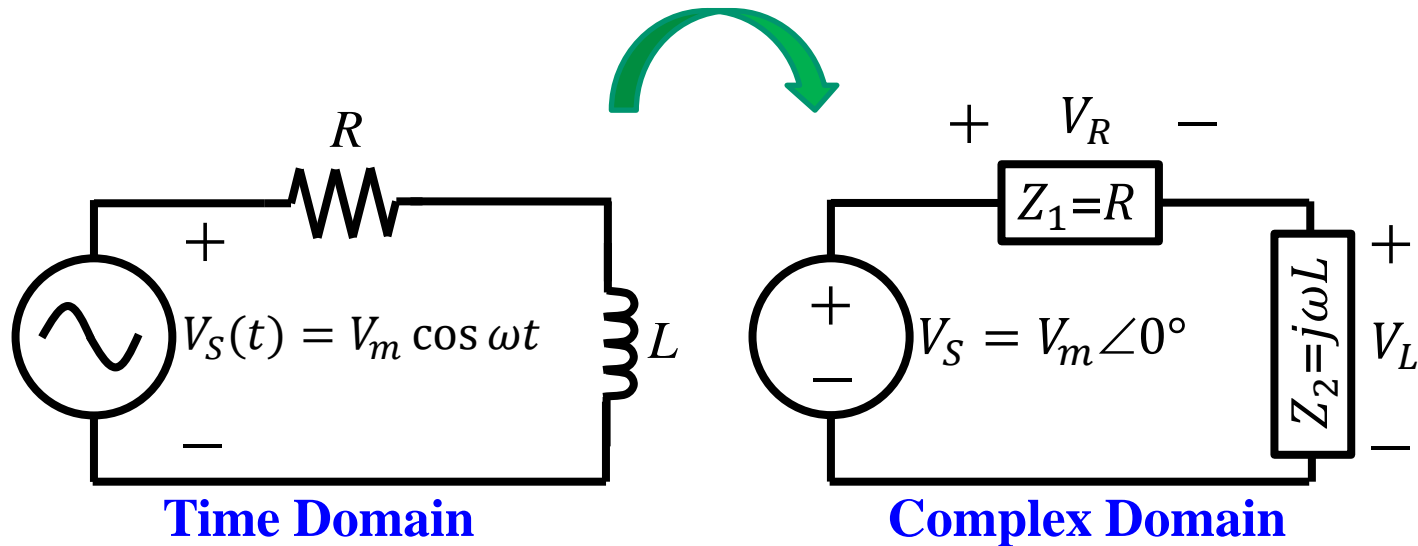

$$\begin{aligned}
 V_L &= \frac{Z_2}{Z_1 + Z_2} V_m \angle 0^\circ = \frac{j\omega L}{R + j\omega L} V_m \angle 0^\circ = \frac{\omega L \angle 90^\circ \times V_m \angle 0^\circ}{\sqrt{R^2 + \omega^2 L^2} \angle \tan^{-1}(\frac{\omega L}{R})} \\
 &= \frac{\omega L V_m}{\sqrt{R^2 + \omega^2 L^2}} \angle [90^\circ - \tan^{-1}(\frac{\omega L}{R})]
 \end{aligned}$$

Therefore, the inductor's voltage in time domain is:

$$V_L(t) = \frac{\omega L V_m}{\sqrt{R^2 + \omega^2 L^2}} \cos[\omega t + 90^\circ - \tan^{-1}(\frac{\omega L}{R})]$$



# Illustration: KVL Applies for Phasors


Voltage	Magnitude	Phase Angle	Real	Imaginary
$V_S$	7	$0^\circ$	7	0
$V_R$	4.95	$-45^\circ$	3.5	-3.5
$V_L$	4.95	$45^\circ$	3.5	3.5

In AC circuits with R, L, C elements, because of the phase differences, we can only apply KVL in complex domain:

$$V_S = V_R + V_L$$

Assumptions made for the variables in previous slide:

- $V_m = 7$
- $\omega L = R$

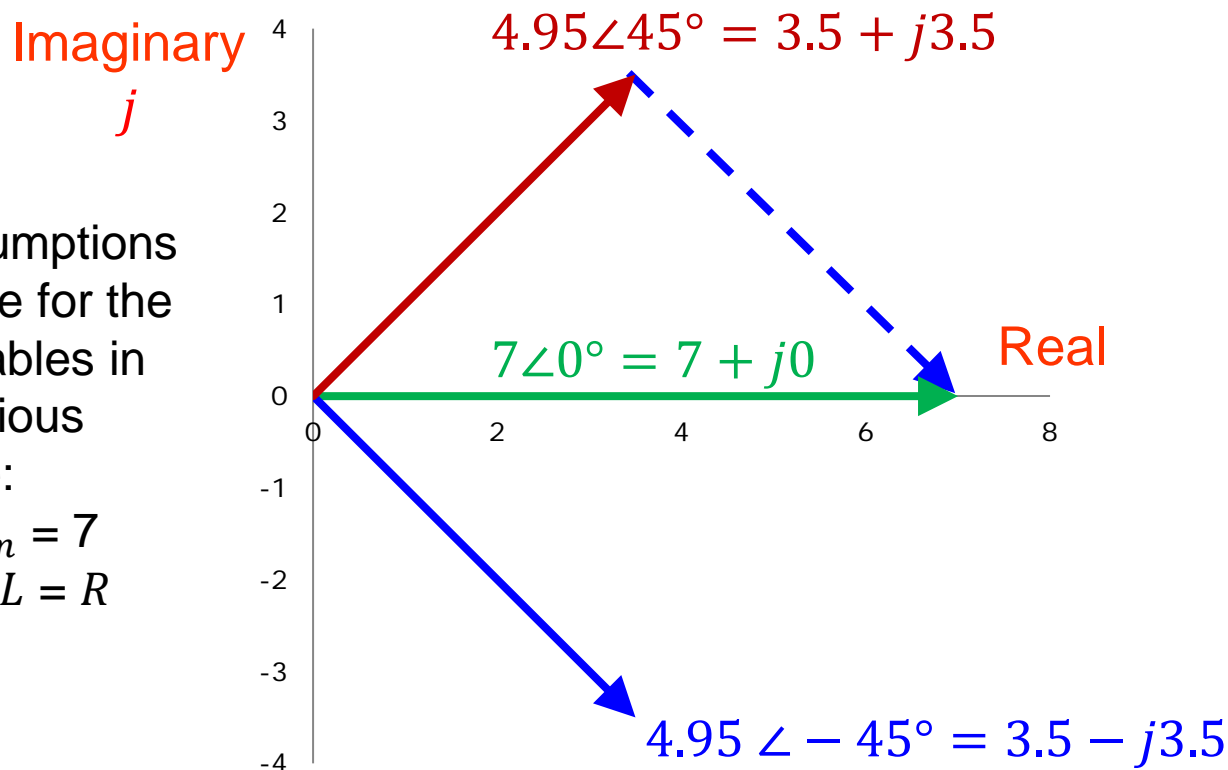

→  $V_S$

→  $V_R$

→  $V_L$

**THANK YOU**