

CG1111: Engineering Principles and Practice I

Debrief and Tutorial for Week 8



Characteristics of DC Motors

Torque of shaft:

$$T_{\text{shaft}} = K_t I_m \text{ [N.m]}$$

Back emf:

$$E_b = K_e \omega \text{ [V]}$$

For PMDC motor:

$$K_t = K_e$$

Note:

$$\omega = 2\pi \times \frac{\text{RPM}}{60} \text{ [rad/s]}$$


Power

- Mechanical power at motor shaft:


$$P_{\text{out}} = T_{\text{shaft}} \omega \text{ [W]}$$

- Electrical power supplied to motor:

$$P_{\text{in}} = V_m I_m \text{ [W]}$$

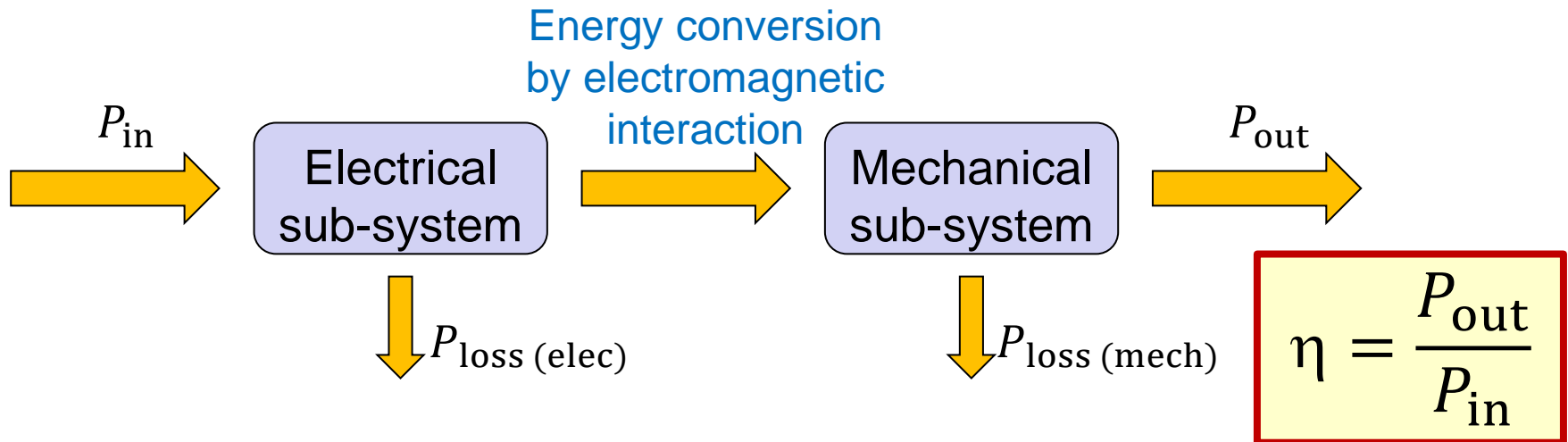

Circuit Representation: PMDC Motor

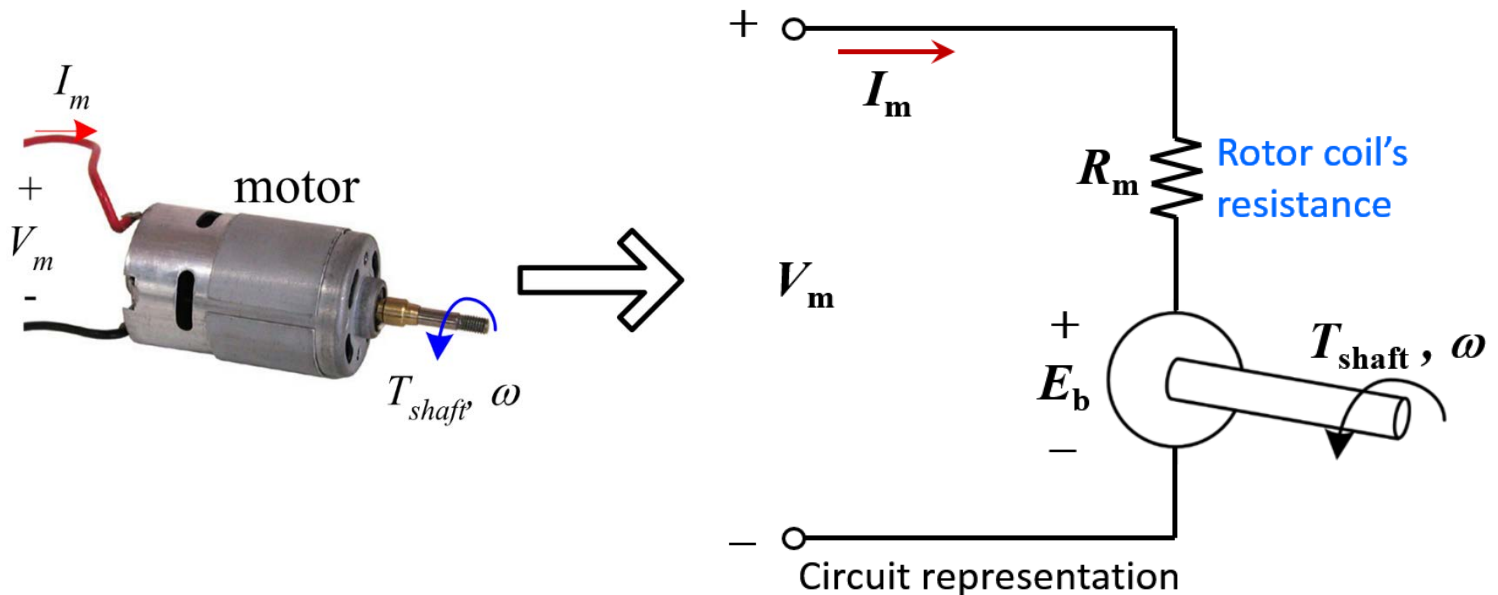

- From the circuit:

$$I_m = \frac{V_m - E_b}{R_m}$$

- Since $E_b = K_e \omega$, we have:

$$I_m = \frac{V_m}{R_m} - \frac{K_e \omega}{R_m}$$

Basic Properties of PMDC Motor

Rearranging:

$$\omega = \frac{V_m}{K_e} - \frac{R_m I_m}{K_e}$$


- For a **fixed load** (i.e., **fixed** T_{shaft} , which implies **fixed** I_m since $T_{\text{shaft}} = K_t I_m$):

Shaft speed ω can be increased by increasing motor voltage V_m


- For a **fixed voltage**, if T_{shaft} increases, I_m increases, and hence ω decreases:

Shaft speed ω decreases with increasing load T_{shaft}

Op-Amp Terminals

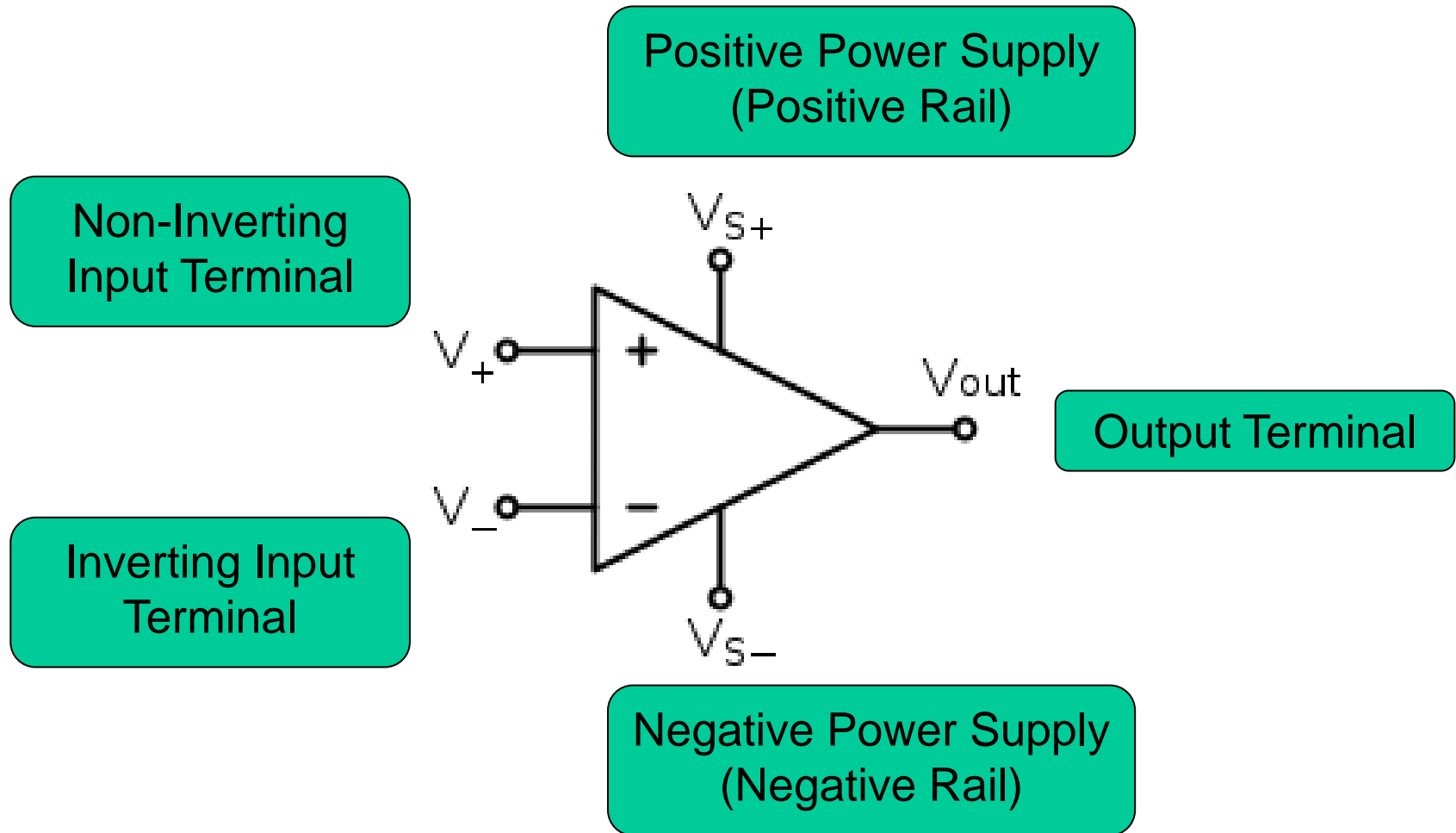

Op-Amp Equivalent Circuit

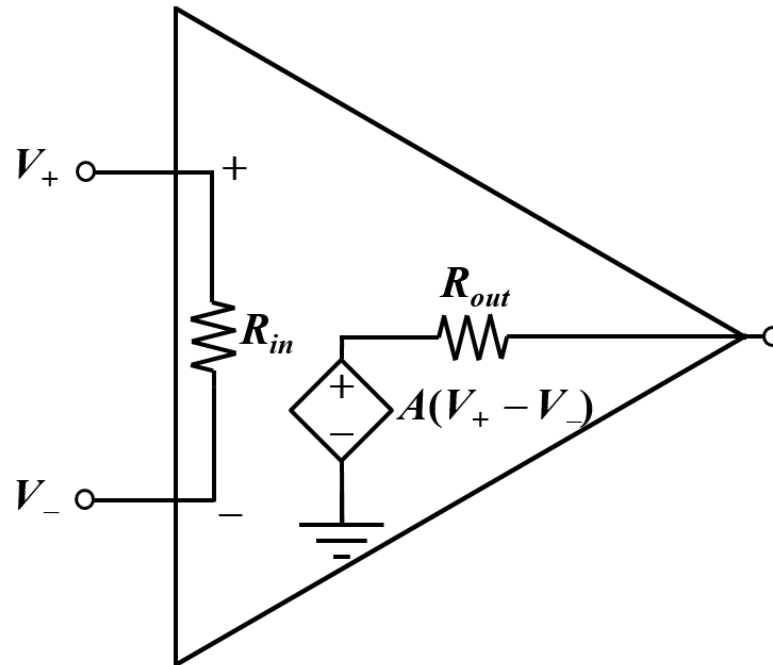

- A is the open-loop voltage gain
 - It is very large, approaching infinity
- R_{in} is the input impedance & R_{out} is the output impedance


Typical Op Amp Parameters

Parameter	Variable	Typical Ranges	Ideal Values
Voltage Gain	A	10^5 to 10^8	∞
Input Impedance	R_{in}	10^5 to $10^8 \Omega$	$\infty \Omega$
Output Impedance	R_{out}	10 to 100Ω	0Ω
Supply Voltage	V_{S+} or V_{CC} V_{S-} or V_{EE} or $-V_{CC}$	5 to 30 V -30 to 0 V	N/A N/A

Op-amp Golden Rules

- Rule 1: **In a closed loop**, the output attempts to do whatever is necessary to make the voltage difference between the inputs zero

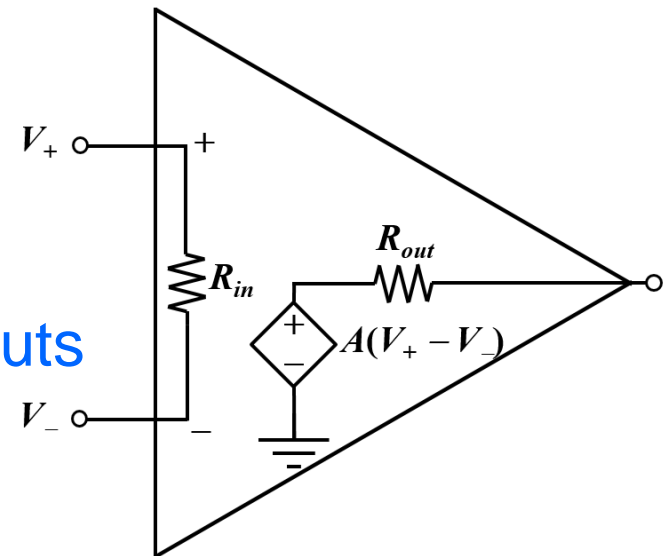- The voltage gain of a real op-amp is so high that a fraction of a mV difference between the V_+ & V_- inputs will swing the output to saturation




- Rule 2: The inputs draw no current
 - The ideal op-amp has infinite input impedance (R_{in}). Thus, the current drawn at the two input terminals ~ 0 .

Non-Inverting Amplifier

- For an ideal op-amp, the **non-inverting amplifier gain** is given simply by

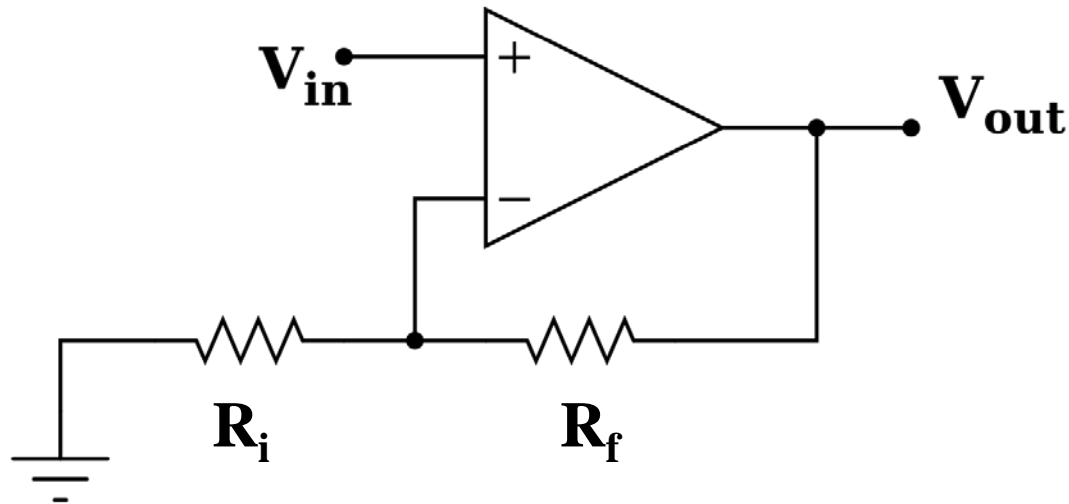
$$\frac{V_{\text{out}}}{V_{\text{in}}} = 1 + \frac{R_f}{R_i}$$



Inverting Amplifier

- For an ideal op-amp, the **inverting amplifier gain** is given simply by
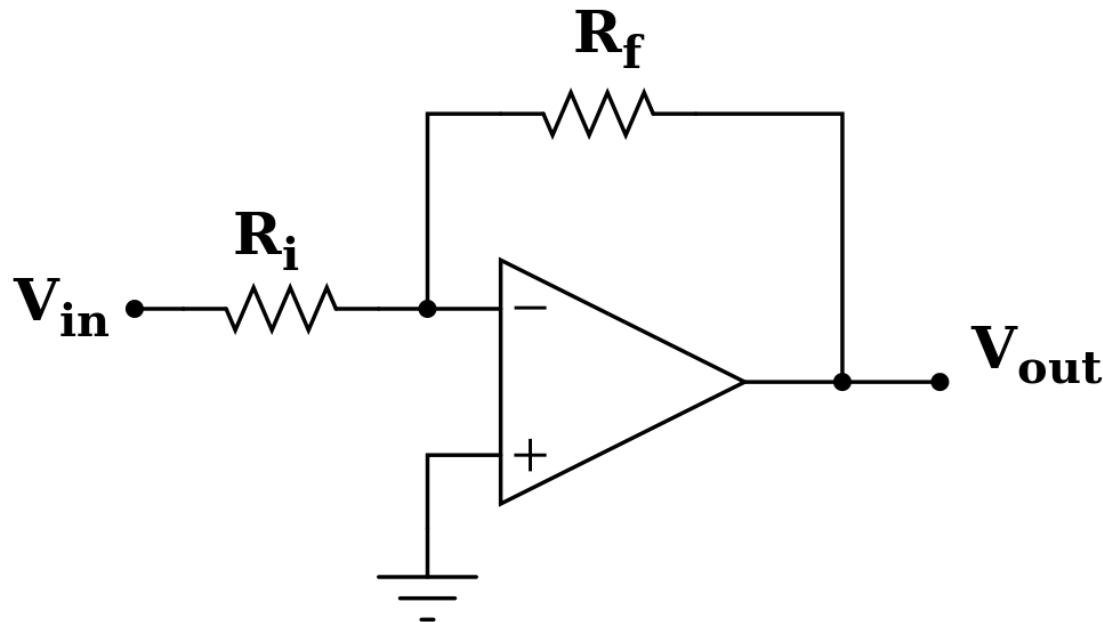
$$\frac{V_{\text{out}}}{V_{\text{in}}} = -\frac{R_f}{R_i}$$



Power Gain in decibels (dB)

- The **Voltage Amplification (A_v)** or **Gain** of a voltage amplifier/filter is given by:

$$A_v = \frac{V_{\text{out}}}{V_{\text{in}}}$$

- The voltage gain is commonly expressed in terms of the resulting **power gain** in **dB**:

$$\begin{aligned}\text{Power Gain (dB)} &= 10 \log_{10} \left(\frac{V_{\text{out}}}{V_{\text{in}}} \right)^2 \text{ dB} \\ &= 20 \log_{10} \left| \frac{V_{\text{out}}}{V_{\text{in}}} \right| \text{ dB}\end{aligned}$$

Question 1

- PMDC motor, 12 V source
- No-load speed = 3800 RPM
- Stall torque = 30 mNm
- If now running at 2500 RPM, find
 - a) I_m
 - b) T_{shaft}
 - c) E_b
 - d) Electrical power consumed
 - e) Shaft power
 - f) Power loss in rotor coil

Solution to Q1

- First, find all **unknown motor parameters**

- 3800 RPM $\rightarrow \omega_{\text{no-load}} = 398 \text{ rad/s}$

- Recall that:

$$I_m = \frac{V_m}{R_m} - \frac{K_e \omega}{R_m}$$

- At **no-load**, $I_m \approx 0$ since $T_{\text{shaft}} \approx 0$

- Hence, $V_m \approx K_e \omega_{\text{no-load}} \rightarrow K_e \approx \frac{12}{398} = 30 \frac{\text{mV}}{\text{rad/s}}$

- For PMDC motor, $K_t = K_e = 30 \frac{\text{mNm}}{\text{A}}$

- At **stall condition**, $T_{\text{stall}} = 30 \text{ mNm}$

- $I_{\text{stall}} = \frac{T_{\text{stall}}}{K_t} = 1 \text{ A}$

- Since $\omega_{\text{stall}} = 0$, $I_{\text{stall}} = \frac{V_m}{R_m} \rightarrow R_m = \frac{12 \text{ V}}{1 \text{ A}} = 12 \Omega$

Solution to Q1

At 2500 RPM:

a) Find $I_{2500 \text{ RPM}}$ and b) $T_{2500 \text{ RPM}}$

$$\omega_{2500 \text{ RPM}} = 261.8 \text{ rad/s}$$

$$\begin{aligned} I_{2500 \text{ RPM}} &= \frac{V_m}{R_m} - \frac{K_e \omega_{2500 \text{ RPM}}}{R_m} \\ &= \frac{12}{12} - \frac{0.03 \times 261.8}{12} = 0.346 \text{ A} \end{aligned}$$

$$\begin{aligned} \text{Therefore, } T_{2500 \text{ RPM}} &= K_t I_{2500 \text{ RPM}} \\ &= 10.4 \text{ mNm} \end{aligned}$$

Solution to Q1

c) Find back emf $E_{2500 \text{ RPM}}$

$$E_{2500 \text{ RPM}} = K_e \omega_{2500 \text{ RPM}} = 7.85 \text{ V}$$

d) Find total electrical power consumed P_e

$$P_e = V_m \times I_{2500 \text{ RPM}} = 4.15 \text{ W}$$

Solution to Q1

e) Find shaft power P_{shaft}

$$P_{\text{shaft}} = T_{2500 \text{ RPM}} \times \omega_{2500 \text{ RPM}} = 2.72 \text{ W}$$

f) Find power loss in rotor coil

$$P_{\text{loss}} = R_m \times (I_{2500 \text{ RPM}})^2 = 1.44 \text{ W}$$

Question 2

- Same motor as Q1
- Load condition unchanged
 - (i.e., same torque as $T_{2500 \text{ RPM}}$ previously)
- New desired speed = 1500 RPM
- Find:
 - a) Rotor current I_m and the required V_m
 - b) PWM duty cycle if DC source still 12 V
 - c) T_{on} and T_{off} if PWM frequency = 5 kHz
 - d) Electrical power consumed
 - e) Power loss in rotor coil

Solution to Q2

a) Find current I_m and the required V_m


Same load means **same torque** as $T_{2500 \text{ RPM}}$ previously, hence **current remains unchanged** at

$$I_m = 0.346 \text{ A}$$

$$\omega_{1500 \text{ RPM}} = 157.1 \text{ rad/s}$$

$$E_b = K_e \omega = 4.71 \text{ V}$$

$$V_m = R_m I_m + E_b = 8.86 \text{ V}$$

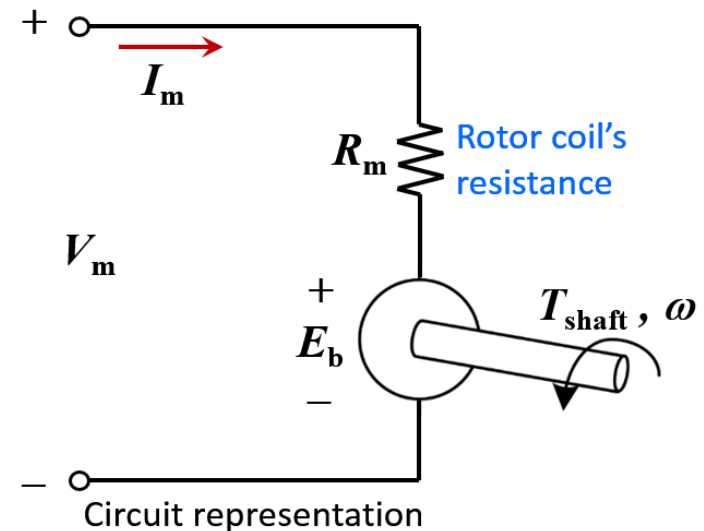

Solution to Q2

b) Find PWM duty cycle if DC source is 12 V

$$\text{Duty Cycle} = \frac{8.86}{12} = 73.8\%$$

c) T_{on} and T_{off} if PWM frequency = 5 kHz

$$T_p = \frac{1}{5000} = 200 \mu\text{s}$$

$$T_{\text{on}} = 0.738 \times 200 \mu\text{s} = 147.6 \mu\text{s}$$

$$T_{\text{off}} = T_p - T_{\text{on}} = 52.4 \mu\text{s}$$

Solution to Q2

d) Find total electrical power consumed

$$P_e = V_m \times I_m = 8.86 \times 0.346 = 3.07 \text{ W}$$

e) Find power loss in rotor coil

$$P_{\text{loss}} = R_m \times (I_m)^2 = 1.44 \text{ W}$$

(same as Q1!)

Question 3

- PMDC motor with fan
- Fan's load torque $T_L = 0.05\omega + 0.001\omega^2$
- $K_t = 2.42 \text{ Nm/A}$
- $R_m = 0.2 \Omega$
- 50 V DC power supply

- Find:
Speed of fan

Solution to Q3

Recall that:

$$T_{\text{shaft}} = K_t I_m$$

$$I_m = \frac{V_m}{R_m} - \frac{K_e \omega}{R_m}$$

For PMDC motor:

$$K_t = K_e$$

Therefore:

$$T_{\text{shaft}} = 2.42 \times \left(\frac{50}{0.2} - \frac{2.42}{0.2} \omega \right) = 605 - 29.3\omega$$

Solution to Q3

Since $T_{\text{shaft}} = T_L = 0.05\omega + 0.001\omega^2$

$$605 - 29.3\omega = 0.05\omega + 0.001\omega^2$$

$$\omega^2 + 29350\omega - 605000 = 0$$

Solution of quadratic equation:


$$\omega = +20.6 \text{ or } -29371$$

Keeping the positive value, we have

$$\omega = 20.6 \text{ rad/s} \rightarrow 197 \text{ RPM}$$

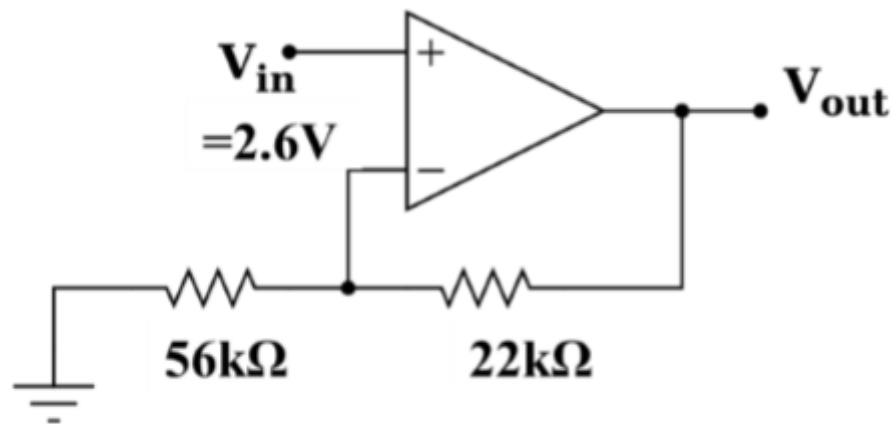
Question 4

- Calculate all **voltage drops** and **currents** in this circuit, and label the currents' **directions** & voltage **polarities**
- Calculate the overall voltage gain of this amplifier circuit (A_v), both as a ratio and as a figure in units of decibels (dB)



Solution to Q4

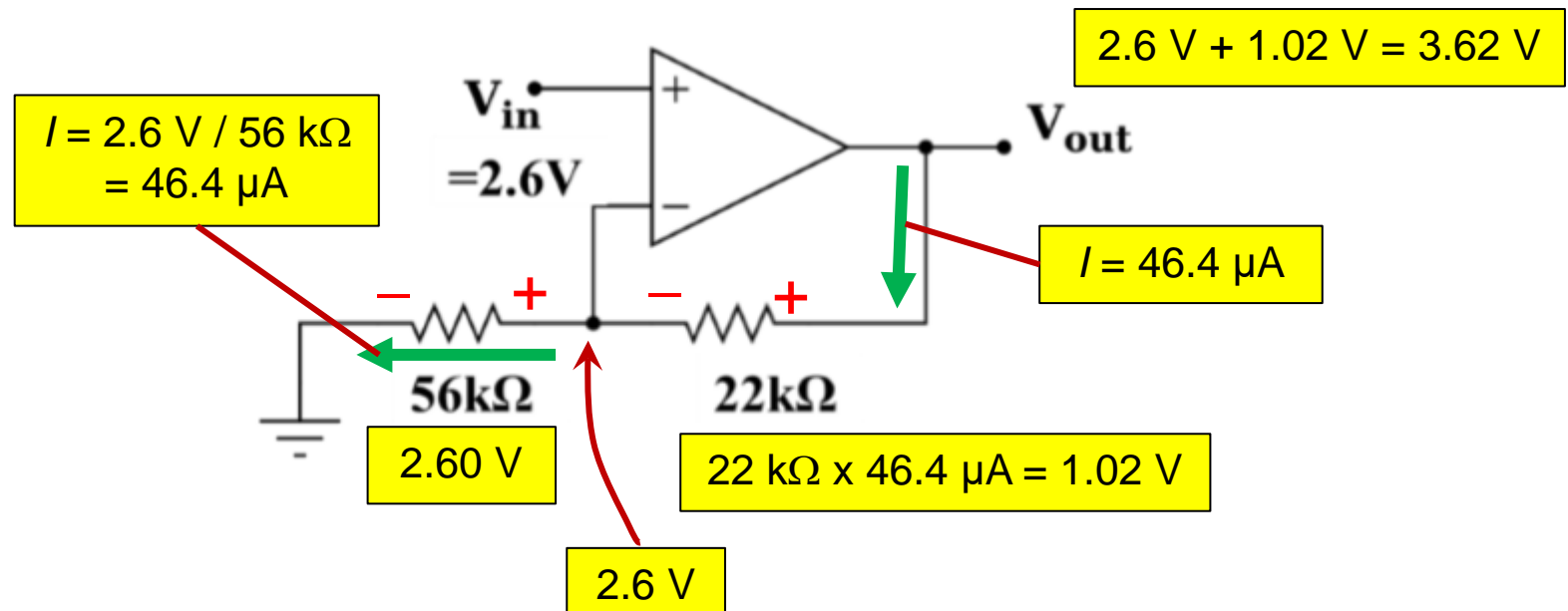
- Opamp's golden rule: $V_+ \approx V_-$
- No current entering '+' & '-' inputs



- Gain $= \frac{V_{out}}{V_{in}} = \frac{3.62}{2.6} = 1.39\text{ V/V (Volt per Volt)}$
- Gain in dB $= 20 \log_{10} (1.39) = 2.86\text{ dB}$

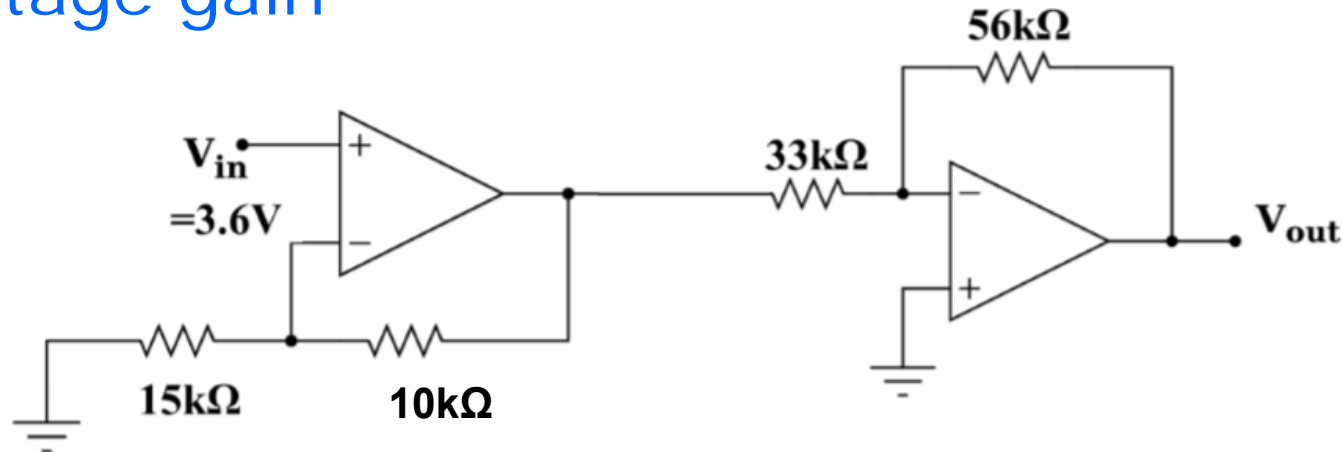
Question 5

- Calculate all **voltage drops** and **currents** in this circuit, and label the currents' **directions** & voltage **polarities**
- Calculate the **voltage gain** for **each stage** of this amplifier circuit (both as a ratio and in units of decibels), then calculate the **overall voltage gain**




Solution to Q5

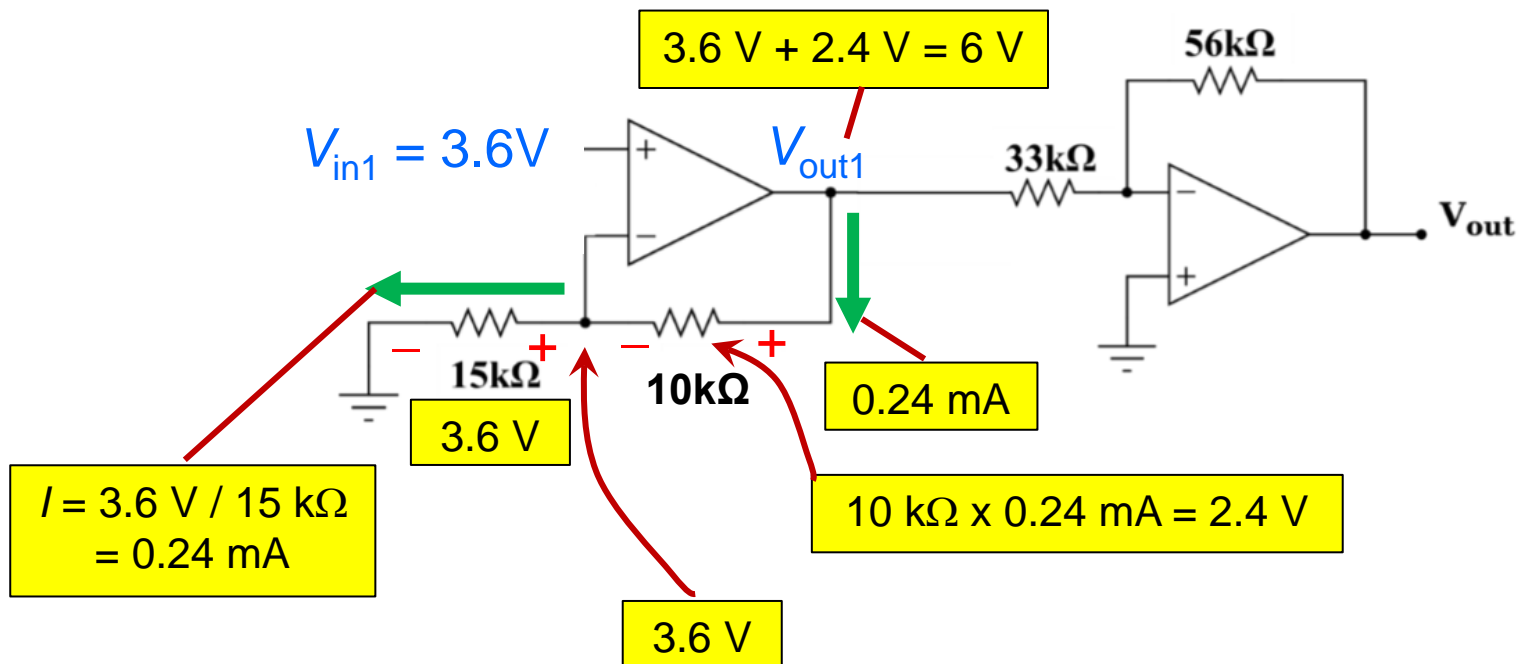- Gain of 1st stage = $\frac{V_{out1}}{V_{in1}} = \frac{6}{3.6} = 1.67 \text{ V/V}$
- Gain in dB = $20 \log_{10} (1.67) = 4.45 \text{ dB}$



Solution to Q5

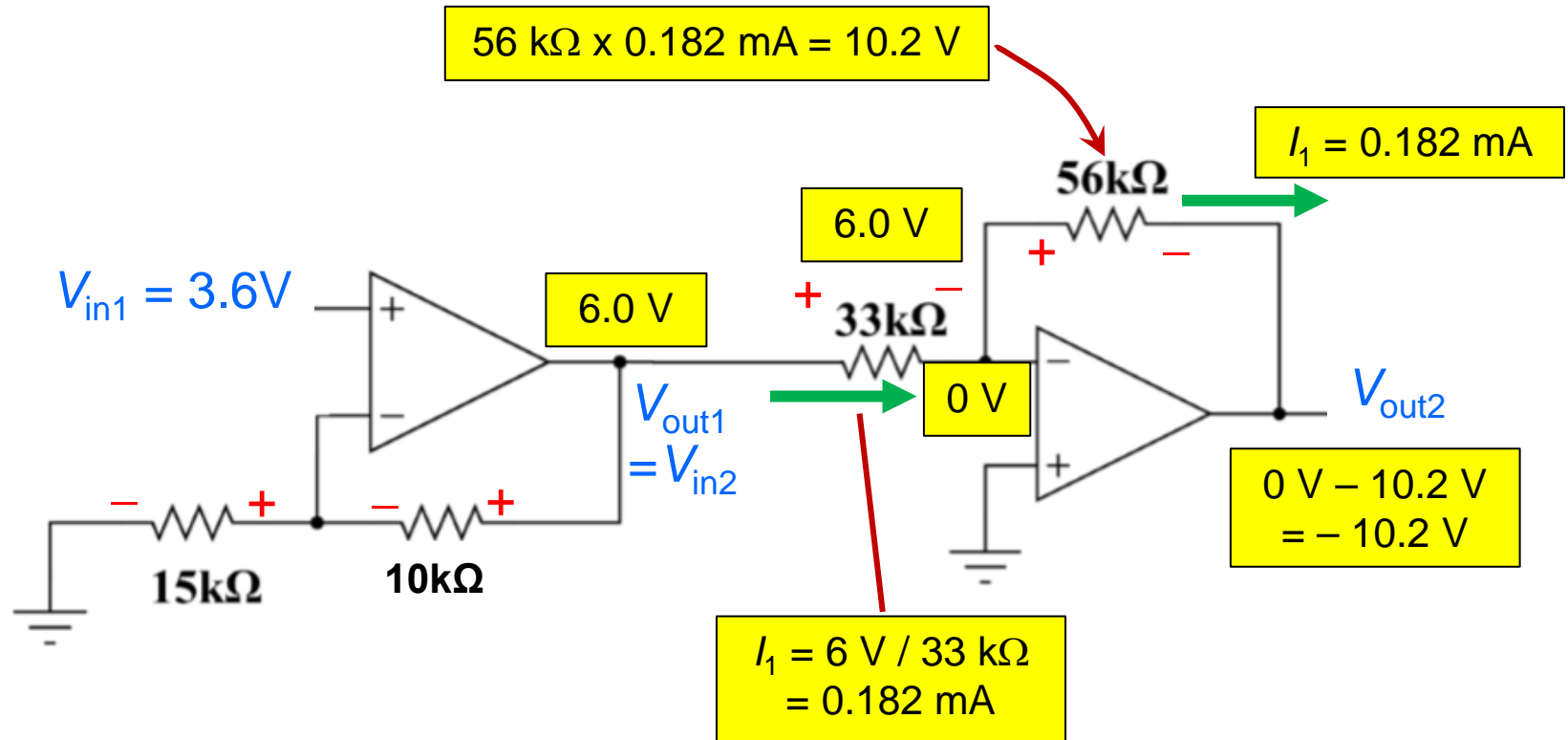

- Gain of 2nd stage = $\frac{V_{out2}}{V_{in2}} = -\frac{10.2}{6} = -1.7 \text{ V/V}$
- Gain in dB = $20 \log_{10} (|-1.7|) = 4.61 \text{ dB}$
- Overall voltage gain = $1.67 \times (-1.7) = -2.84 \text{ V/V} = 9.07 \text{ dB}$