

**NATIONAL UNIVERSITY OF SINGAPORE**

**CG1111 – ENGINEERING PRINCIPLES AND PRACTICE I**

**QUIZ #1**

**06 OCTOBER 2018**


---

**INSTRUCTIONS:**

1. This paper contains **20** multiple-choice questions (MCQs), with only a **SINGLE** correct answer each.
  2. Answer **ALL** questions.
  3. Use only **2B pencils** to shade the bubble sheet.
  4. This is an **OPEN-BOOK** test.
  5. There is no restriction on the use of programmable calculators.
  6. There is **no penalty (i.e., no negative marks) for wrong answers**. Please attempt all questions.
  7. You are **NOT ALLOWED** to use your **mobile phone, tablet or computer** during the test.
  8. **DO NOT READ** the questions until you are told to do so.
  9. Time allowed: **90 MINUTES**
-

1. An appliance consists of 3 subsystems working in parallel with the following power efficiencies:  $\eta_1 = 96\%$ ,  $\eta_2 = 83\%$ ,  $\eta_3 = 91\%$ . What is the minimum input power required by the appliance if each subsystem's output power is 600 W?  
  
(A) 828 W  
  
(B) 2008 W  
  
(C) 670 W  
  
(D) 2483 W
  
2. What is the discharge current of a 12600 mWh battery operating at 3.6 V and 0.2C?  
  
(A) 2.52 A  
  
(B) 7 A  
  
(C) 0.016 A  
  
(D) 0.7 A
  
3. Calculate the number of batteries in series and the number of parallel branches required in a battery pack for a remote surveillance system consisting of Lithium Ion batteries, to last a period of 6 hours. The mid-point voltage per battery for the required maximum instantaneous C rate of 2C is 3.6 V. Single battery capacity at the maximum allowable 70% depth of discharge (same as end of discharge) is 6000 mAh. There are 4 subsystems working in series and the required operating voltage is 17 V. The subsystem efficiencies are 85%, 83%, 90%, and 78%, respectively, and the output power required is 80 W.  
  
(A) 5 batteries in series, 9 parallel branches  
  
(B) 5 batteries in series, 10 parallel branches  
  
(C) 4 batteries in series, 9 parallel branches  
  
(D) 4 batteries in series, 10 parallel branches


4.

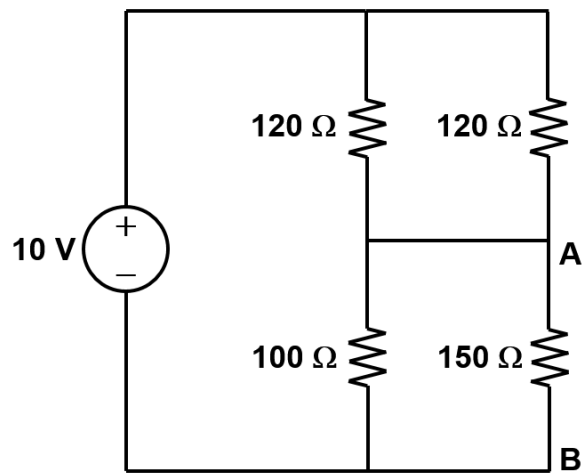

The voltage difference  $V_{AB}$  (given by  $V_A - V_B$ ) is

- (A) 4.55 V
- (B) 5.00 V
- (C) 5.05 V
- (D) 5.56 V


5.

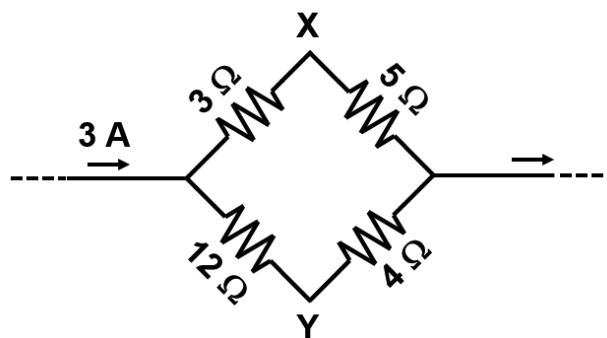

A current of 3 A flows through a resistor network as shown in the figure above. The voltage difference  $V_{XY}$  (given by  $V_X - V_Y$ ) is

- (A) -21.00 V
- (B) -6.00 V
- (C) 6.00 V
- (D) 21.00 V


6.

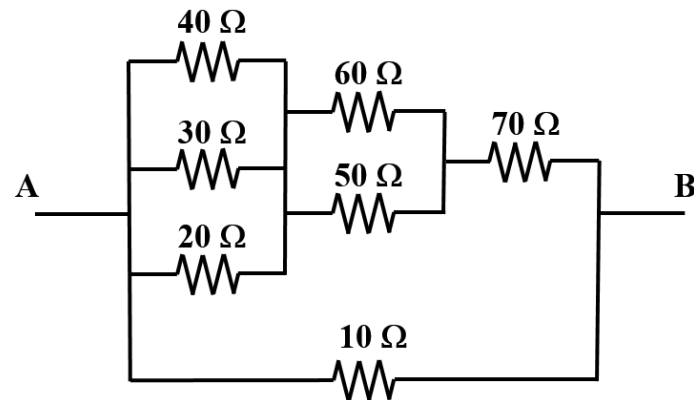

For the resistor network shown in the figure above, what is the equivalent resistance  $R_{AB}$  between the terminals A and B?

- (A)  $9.14\ \Omega$
- (B)  $10.94\ \Omega$
- (C)  $106.5\ \Omega$
- (D)  $116.5\ \Omega$


7.

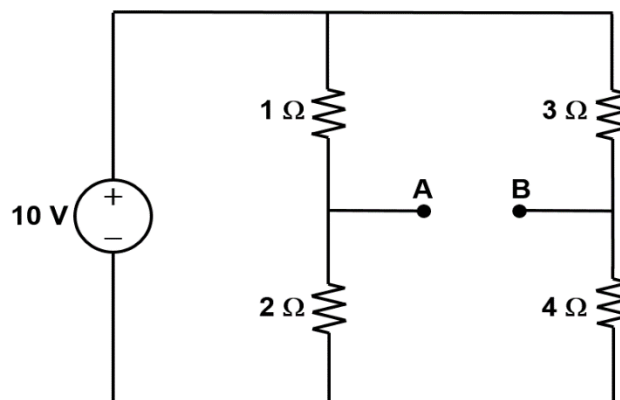

What is the Thevenin resistance of the Thevenin equivalent circuit seen across nodes **A** and **B**?

- (A)  $2.38\ \Omega$
- (B)  $2.08\ \Omega$
- (C)  $0.48\ \Omega$
- (D)  $10\ \Omega$


8.

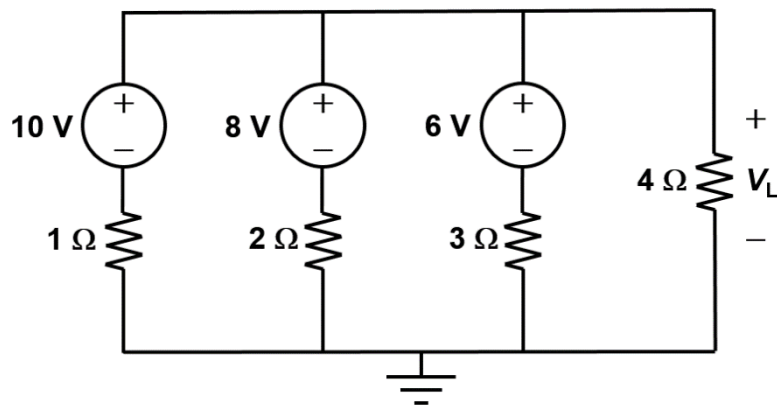

For the circuit shown in the figure above, what is the voltage  $V_L$ ?  
(Hint: Use Node Voltage Analysis method)

- (A) 3.43 V
- (B) 5.33 V
- (C) 8 V
- (D) 7.68 V


9.

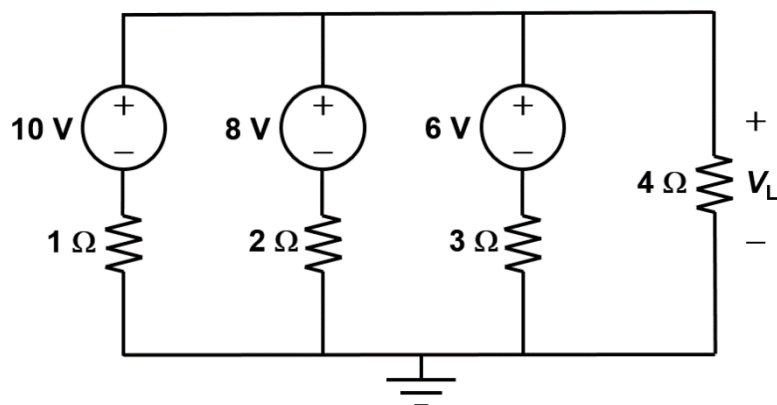

For the circuit shown in the figure above, the 6 V voltage source is

- (A) not supplying, nor consuming power.
- (B) supplying a power of 5.14 W.
- (C) consuming a power of 3.36 W.
- (D) consuming a power of 0.94 W.


10.

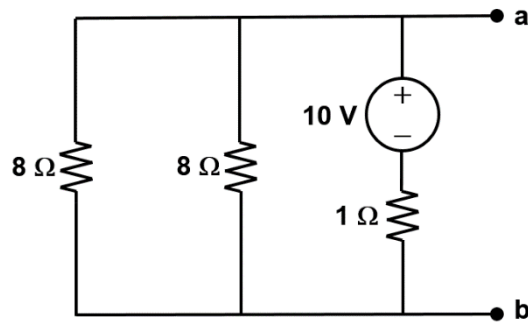

Suppose a load resistance  $R_L$  is to be placed across the nodes **a** and **b** in the circuit above, so as to draw maximum power. What is this maximum power that can be utilized by the load  $R_L$ ?

- (A) 10 W
- (B) 20 W
- (C) 40 W
- (D) 80 W


11.

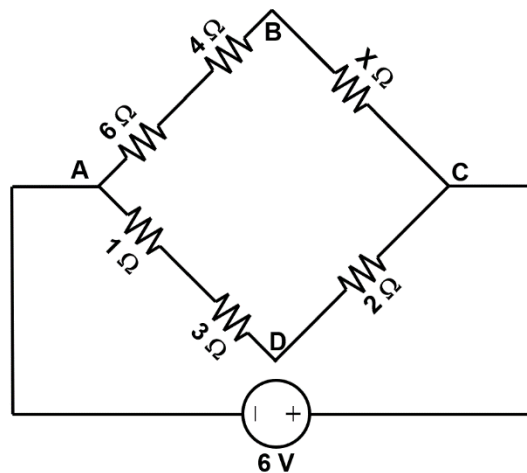

For the circuit shown in the figure above, if the voltage difference  $V_{BD}$  (given by  $V_B - V_D$ ) is 1 V, what is the value of resistance X?

- (A) 0.5 Ω
- (B) 1 Ω
- (C) 2 Ω
- (D) 4 Ω


12.

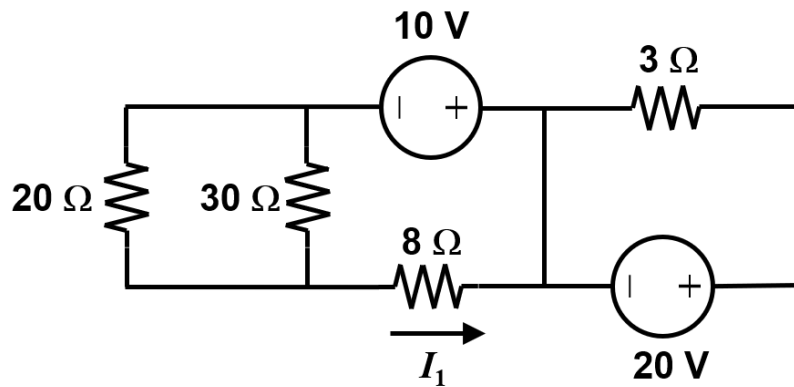

For the circuit shown in the figure above, what is the value of current  $I_1$ ?

- (A) 0.5 A
- (B) -0.26 A
- (C) 0.32 A
- (D) -0.5 A


13.

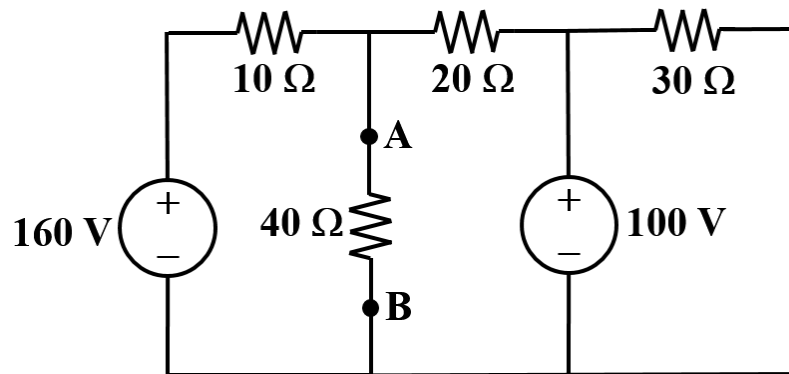

For the circuit shown in the figure above, what is the Thevenin equivalent circuit as seen by the 40 Ω resistor (i.e., between nodes A and B)?

- (A)  $V_T = 120 \text{ V}$ ,  $R_T = 6.67 \text{ Ω}$
- (B)  $V_T = 140 \text{ V}$ ,  $R_T = 6.67 \text{ Ω}$
- (C)  $V_T = 120 \text{ V}$ ,  $R_T = 5.45 \text{ Ω}$
- (D)  $V_T = 140 \text{ V}$ ,  $R_T = 5.45 \text{ Ω}$


14.

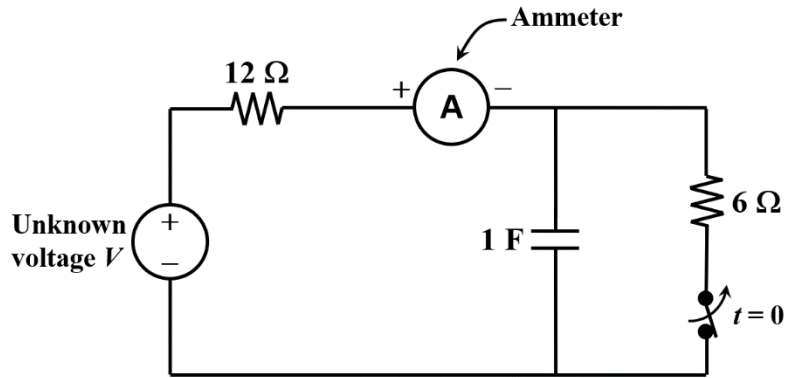

For the circuit shown in the figure above, the switch has been closed for a long time, and the current measured by the ammeter was 1 A before time  $t = 0$ . At time  $t = 0$ , the switch is opened. What would be the current reading on the ammeter at time  $t = 0^+$  s?

- (A) Very large current
- (B) 1.5 A
- (C) 1 A
- (D) 0.5 A

15.

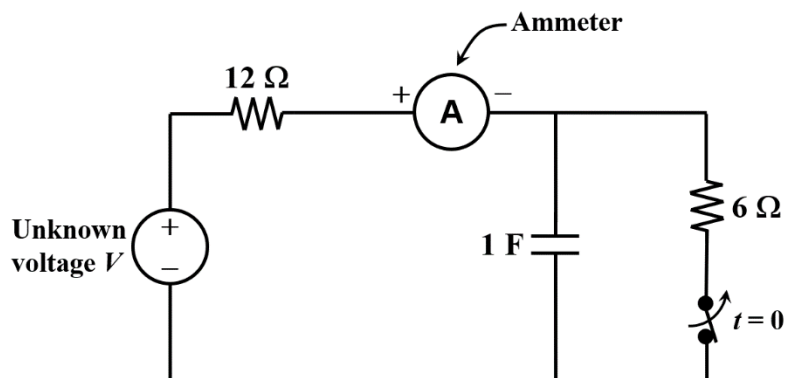


For the circuit shown in the figure above, the switch has been closed for a long time, and the current measured by the ammeter was 1 A before time  $t = 0$ . At time  $t = 0$ , the switch is opened. What would be the current reading on the ammeter at time  $t = 12$  s?

- (A) 0.37 A
- (B) 0.55 A
- (C) 0.87 A
- (D) 1.18 A




16.

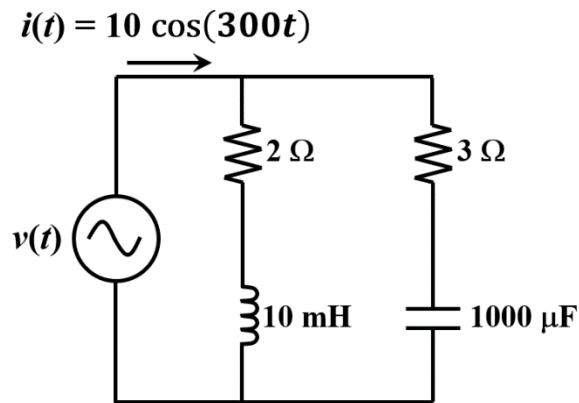

In the circuit shown in the figure above, the voltage  $v(t)$  is

- (A)  $12.3 \cos(300t + 38.1^\circ) \text{ V}$
- (B)  $44.8 \cos(300t - 48.0^\circ) \text{ V}$
- (C)  $36.1 \cos(300t + 56.3^\circ) \text{ V}$
- (D)  $32.3 \cos(300t + 12.1^\circ) \text{ V}$


17.

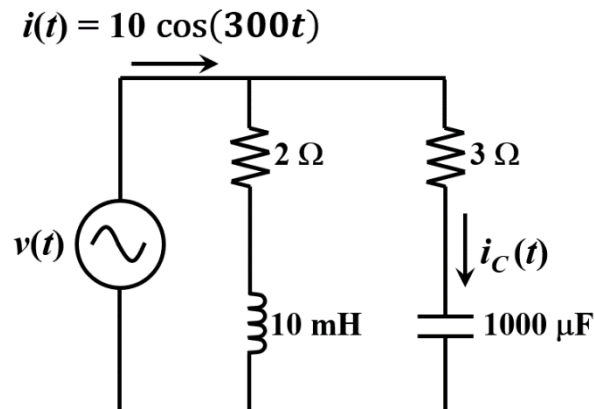

In the circuit shown in the figure above, the current  $i_c(t)$  is

- (A)  $7.2 \cos(300t + 60.1^\circ) \text{ A}$
- (B)  $7.2 \cos(300t - 60.1^\circ) \text{ A}$
- (C)  $8.9 \cos(300t - 44.2^\circ) \text{ A}$
- (D)  $8.9 \cos(300t + 44.2^\circ) \text{ A}$


18.

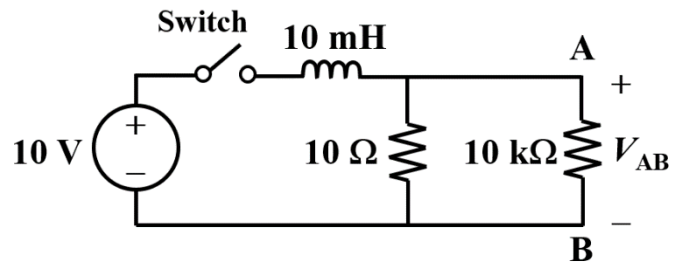

In the circuit shown in the figure above, the switch was initially OPEN for a long time. At time  $t = 0$ , the switch is closed. What is the voltage  $V_{AB}$  at time  $t = 0^+$  (i.e., immediately after the switch is closed)?

- (A) 10.00 V
- (B) 9.99 V
- (C) 0.01 V
- (D) 0 V


19.

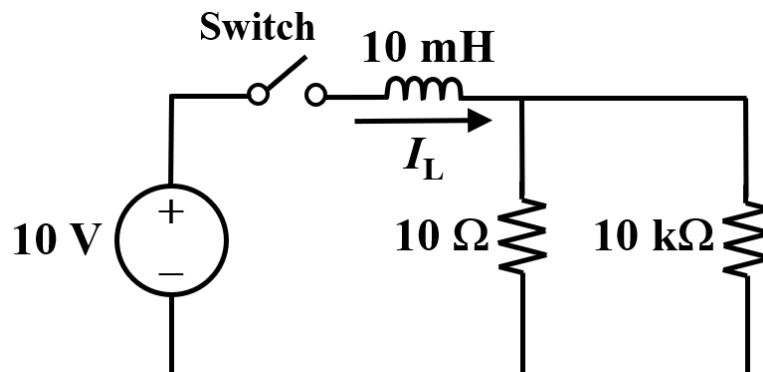

In the circuit shown in the figure above, the switch was initially OPEN for a long time. At time  $t = 0$ , the switch is closed. What is the inductor current  $I_L$  at time  $t = 1$  ms?

- (A) 0.368 A
- (B) 0.632 A
- (C) 1.001 A
- (D) 0.001 A

20.

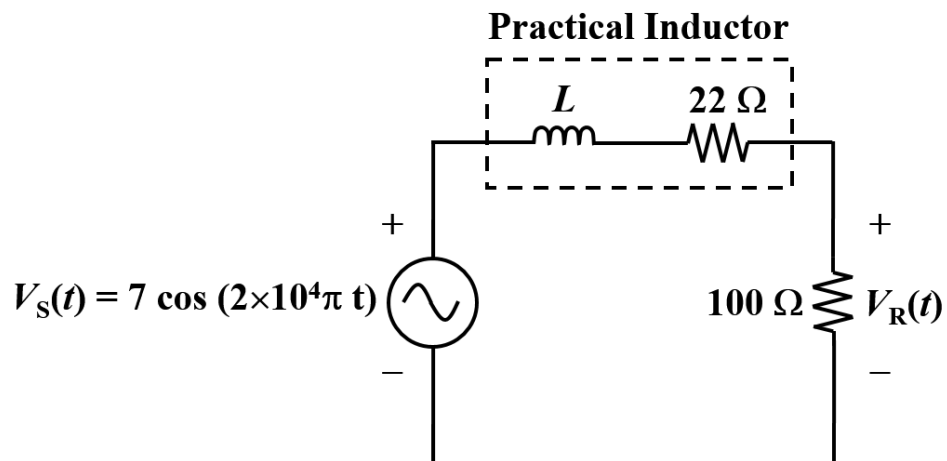

In the circuit shown in the figure above, a  $100 \Omega$  resistor is connected in series with a practical inductor. The practical inductor has a resistance of  $22 \Omega$ , and an unknown inductance  $L$ . Suppose the phase angle of the voltage  $V_R(t)$  is found to be  $-67^\circ$  with respect to the source voltage  $V_s(t)$ , the inductance  $L$  can be obtained as:

- (A)  $0.825 \text{ mH}$
- (B)  $3.75 \text{ mH}$
- (C)  $4.57 \text{ mH}$
- (D)  $5.88 \text{ mH}$

**END OF PAPER**