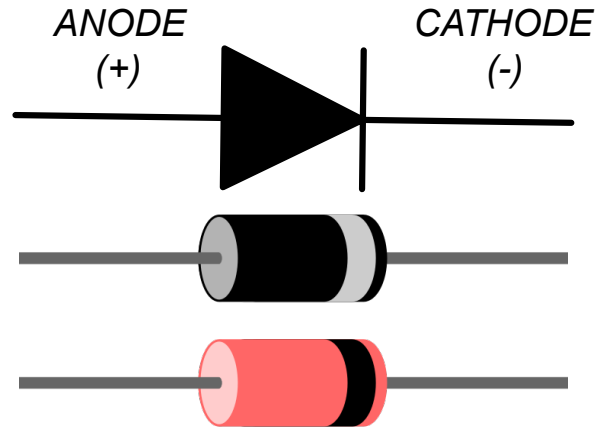


CG1111: Engineering Principles and Practice I

Preparation for Week 7, Studio 1
Diode and Diode Bridge Rectifiers







Diode




- A diode is a polarized device that allows current to flow only in one direction.
- The positive side "+" is called the anode where the current enters, and the negative side "-" is called the cathode where the current leaves.

Note: The symbolic diagram of a diode consists of a triangle and a line. The triangle in the symbol points to the forward direction in which the current flows.

Different Types of Diodes

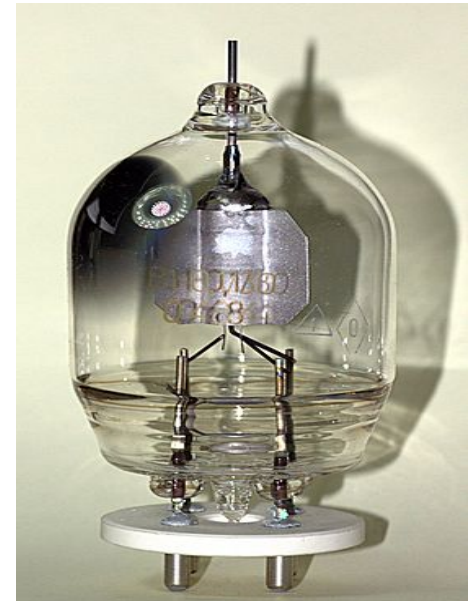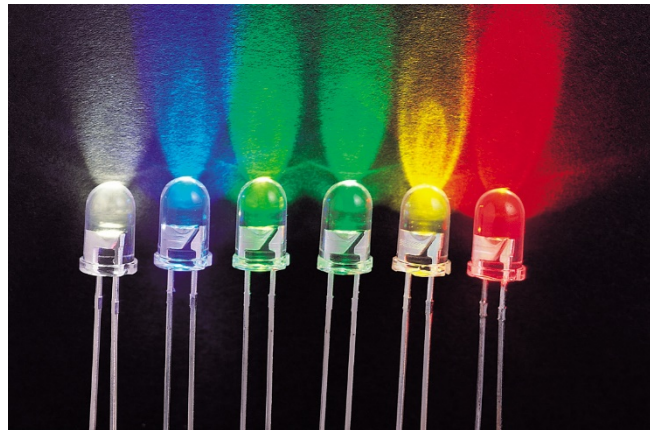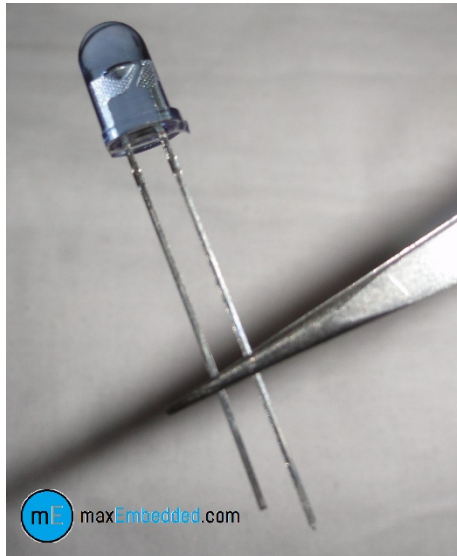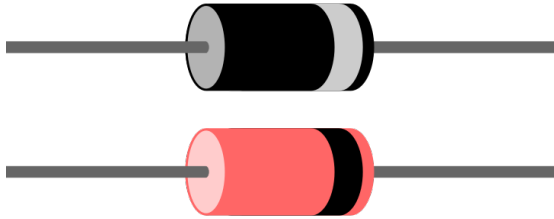


Diode : Forward Biased

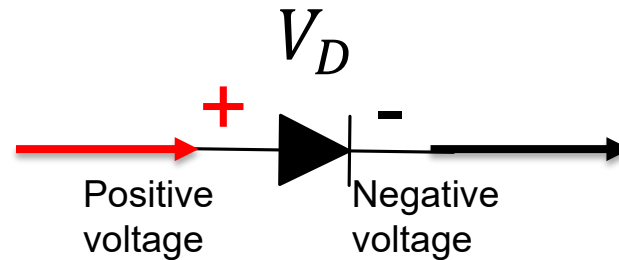


- Diode is “forward-biased” when a positive voltage is applied across the diode i.e the anode is at a higher voltage compared to the cathode
- Only when the applied voltage exceeds a threshold, the diode starts to conduct current
- Current grows exponentially with increment voltage beyond this threshold

Diode: Reverse Biased

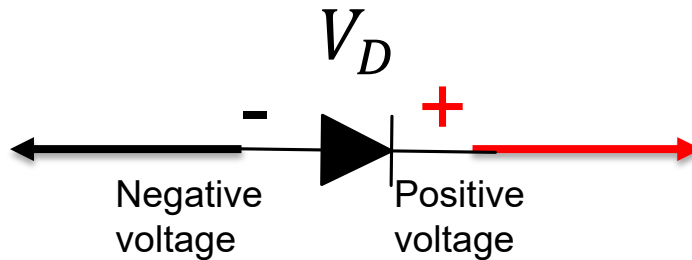


- When a negative voltage is applied across the diode (anode has a lower voltage than the cathode), the diode is “reverse-biased”
- Negligible current flows through the diode in this state
- When the reverse-biased voltage is beyond a limit, the diode breaks down
- This limit is called the breakdown voltage

Diode I-V Characteristics


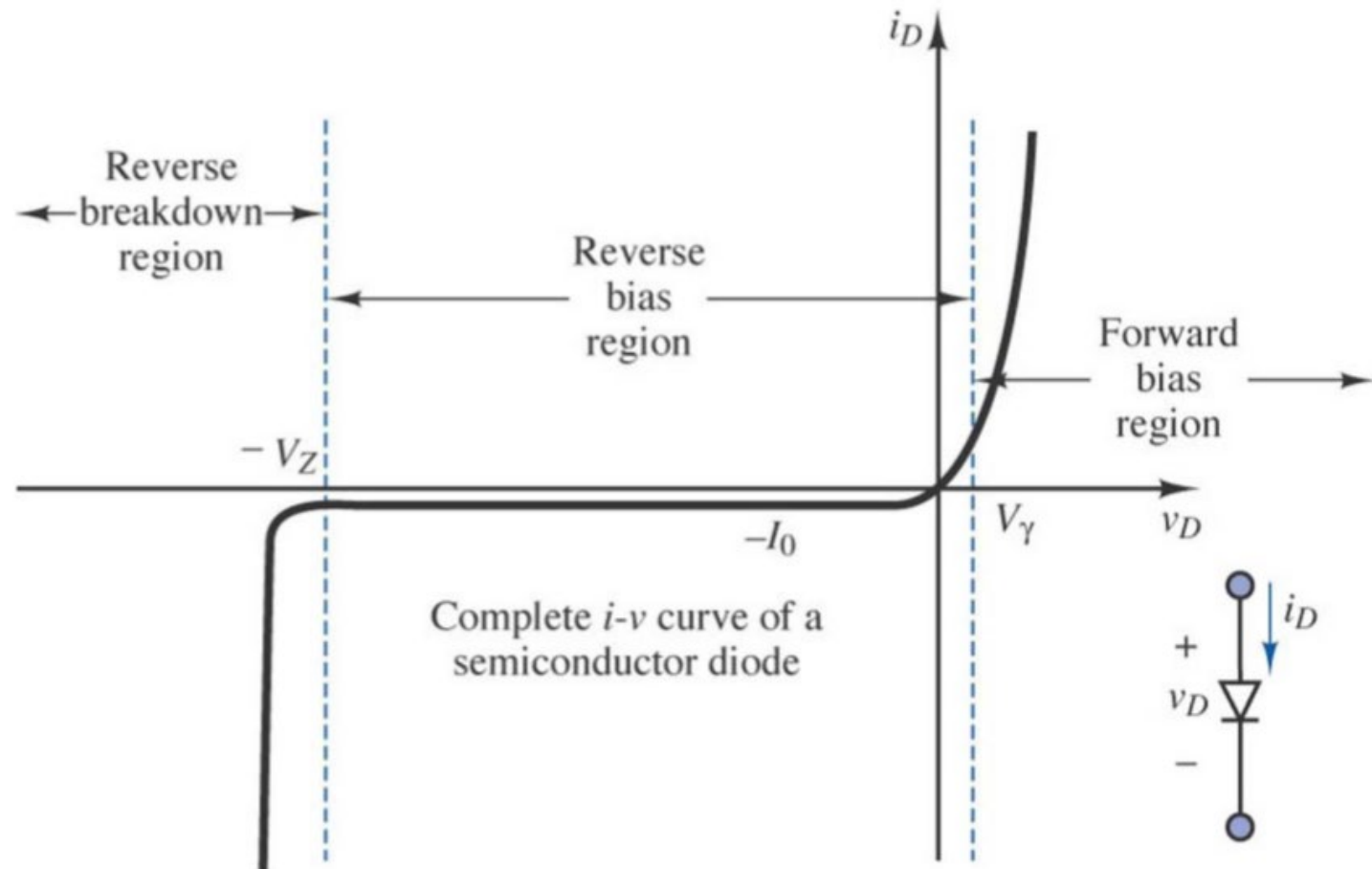


Rectifier


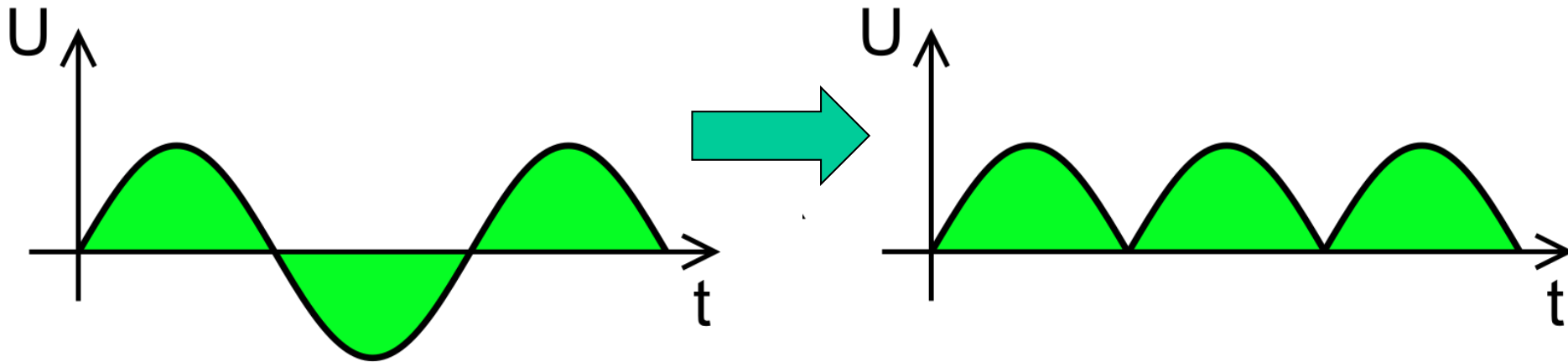
- A rectifier is a circuit which converts alternating current (AC) to direct current (DC)





Diode bridge rectifier

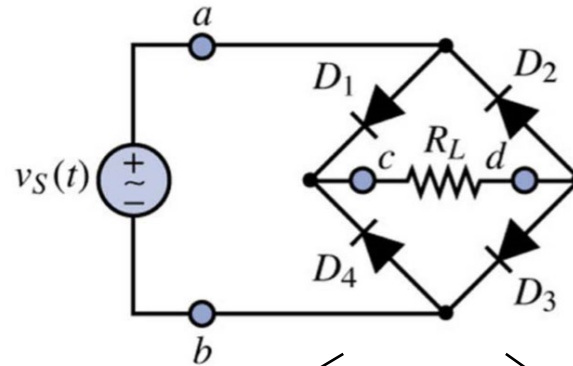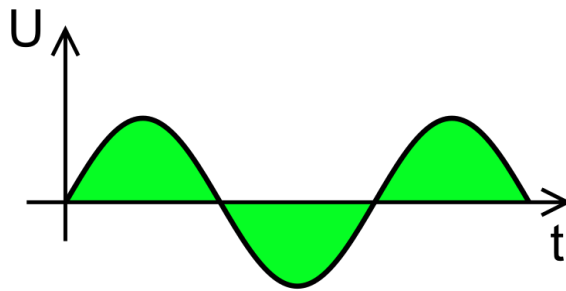

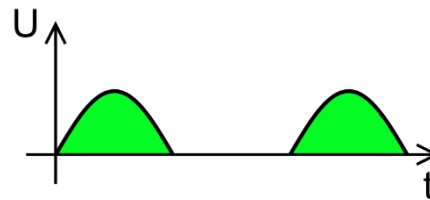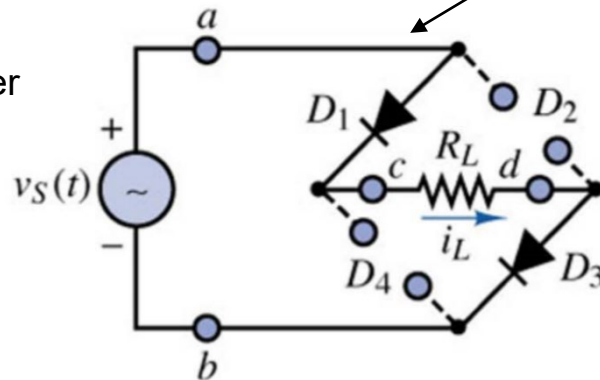During the **positive** half cycle, the rectifier circuit simplifies to




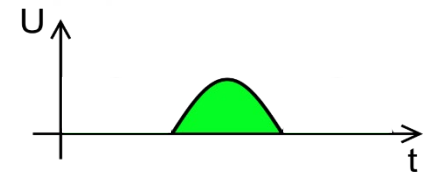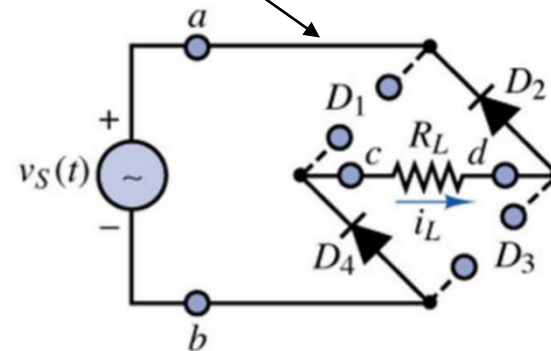During the **negative** half cycle, the rectifier circuit simplifies to



+

||

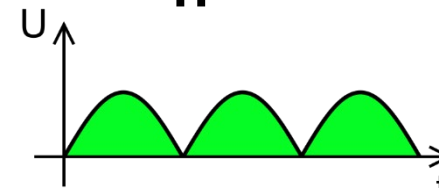

The rectifier output during the two half cycles combine to give the full rectified DC

THANK YOU