


CG1111: Engineering Principles and Practice I

Debrief and Tutorial for Week 7



Principles of AC Circuits

Sinusoidal waveform

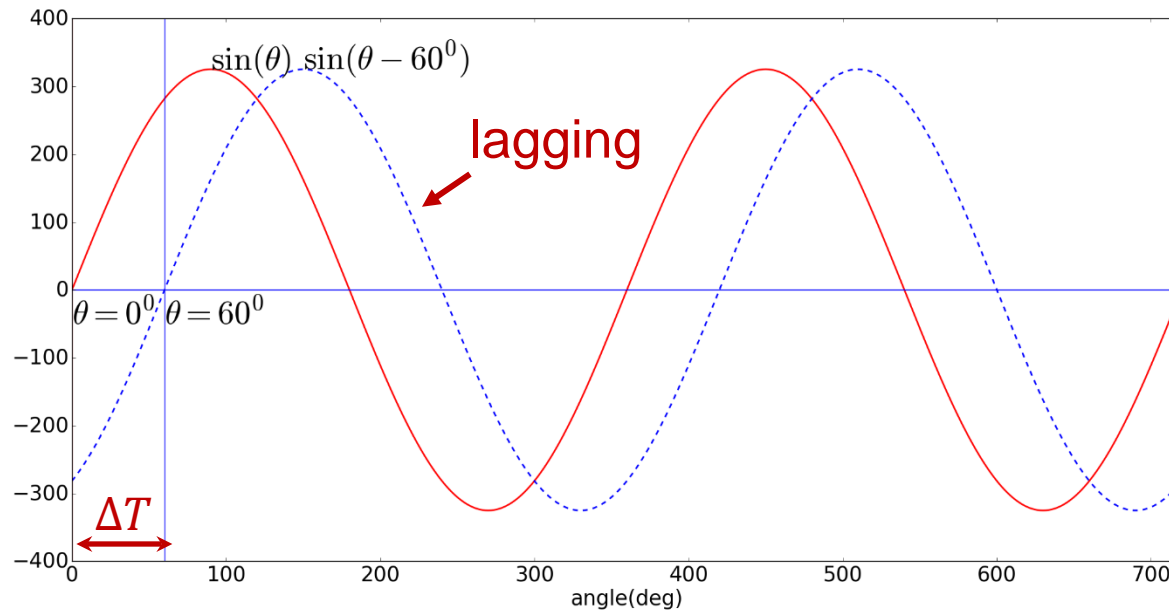

$$v(t) = V_m \cos(\omega t \pm \phi)$$

$$\phi = \frac{\Delta T}{T} \times 360^\circ$$

V_m : Amplitude (or peak)

ω : Angular frequency in rad/s

ϕ : Phase angle

'+' if leading

'-' if lagging

$$\omega = 2\pi f$$

$$T = \frac{1}{f}$$


Root-Mean-Square (RMS)

- Significance of rms value:
 - They are the equivalent values of the DC voltage & current that would have the same average power dissipation in a resistive load
 - So that you can apply the same formula as DC!
 - Average power dissipation of resistive load in AC:


$$P = V_{rms} \times I_{rms} = I_{rms}^2 R = \frac{V_{rms}^2}{R}$$

$$V_{rms} = \frac{V_m}{\sqrt{2}}$$

$$I_{rms} = \frac{I_m}{\sqrt{2}}$$

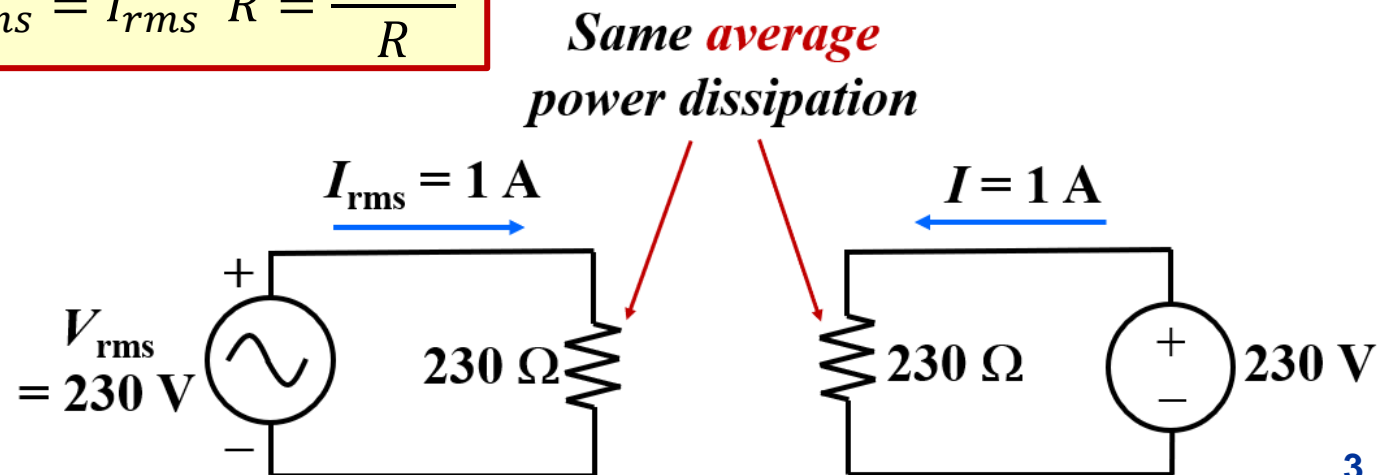

AC Circuit Analysis in Time Domain?

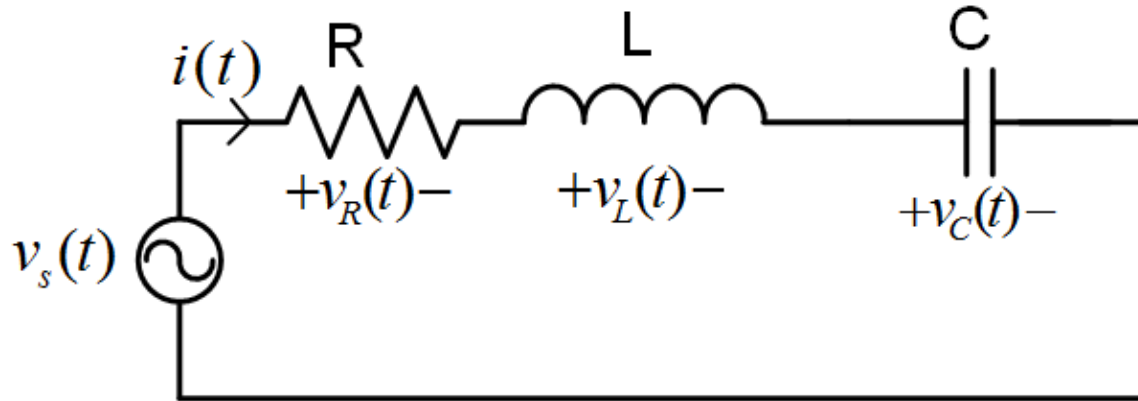


- In AC circuits, inductors/capacitors result in differential equations:

$$V_m \cos(\omega t) = v_R(t) + v_L(t) + v_C(t) = iR + L \frac{di}{dt} + \frac{\int i dt}{C}$$

→ difficult to solve in time-domain!

AC Circuit Analysis

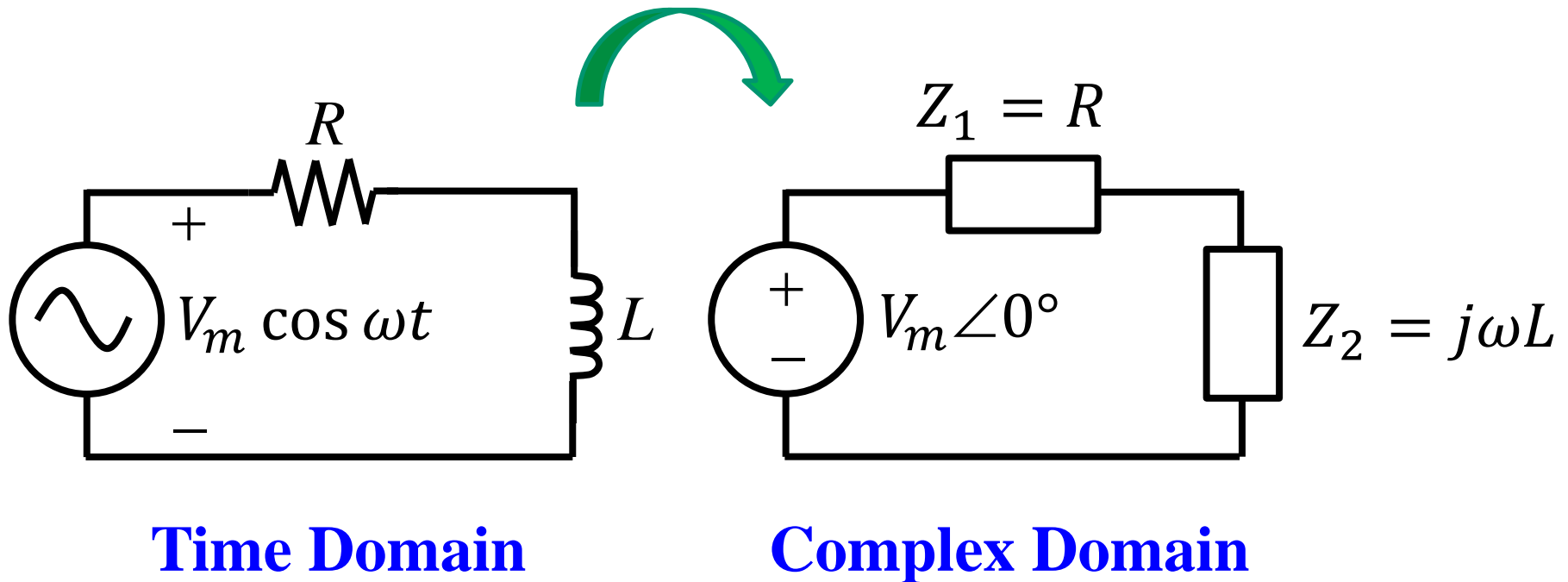

Can then solve using DC circuit analysis techniques:

- KVL, KCL, Ohm's Law, Potential divider principle, current division principle, Thevenin equivalent, NVA, series equivalent impedance, parallel equivalent impedance, etc.

AC Circuit Analysis with Phasors & Impedances

We must work with KVL & KCL in **Phasor form**

Steps:

1. Replace **voltage sources** with their **phasors** (all must have same frequency)
2. Replace **R, L, C** elements with their **impedances**
3. Analyse circuit using **DC circuit analysis** techniques (work within **complex** domain)
4. Convert final results back to **time-domain**

Phasors

- Sinusoidal voltage:

$$V_m \cos(\omega t + \theta)$$

- Phasor:

$$V_m \angle \theta$$

Note:

Another common practice is to represent phasors using the **RMS value** instead of the magnitude. In that case, the phasor will be written as $\frac{V_m}{\sqrt{2}} \angle \theta$.

Note:

- Phasor is just a definition. It leads to **mathematical convenience**, but has **no physical significance**

Impedances

- For resistance:

$$R$$

- For inductor:

$$j\omega L = \omega L \angle 90^\circ$$

- For capacitor:

$$\frac{1}{j\omega C} = \frac{-j}{\omega C} = \frac{1}{\omega C} \angle -90^\circ$$



Illustration: KVL Applies for Phasors

Voltage	Magnitude	Phase Angle	Real	Imaginary
V_S	7	0°	7	0
V_R	4.95	-45°	3.5	-3.5
V_L	4.95	45°	3.5	3.5

In AC circuits with R, L, C elements, because of the phase differences, we can only apply KVL in complex domain:

$$V_S = V_R + V_L$$

Imaginary
 j

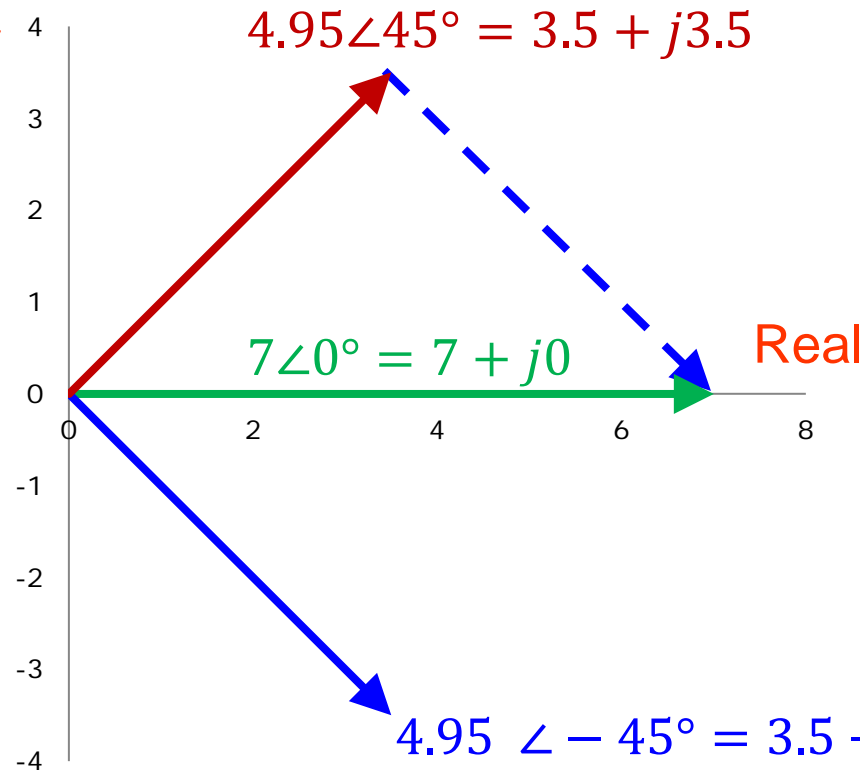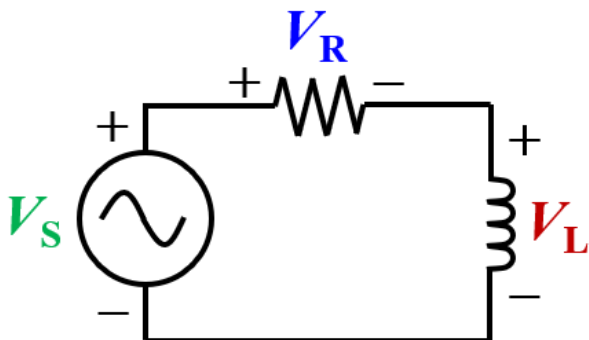


→ V_S

→ V_R

→ V_L

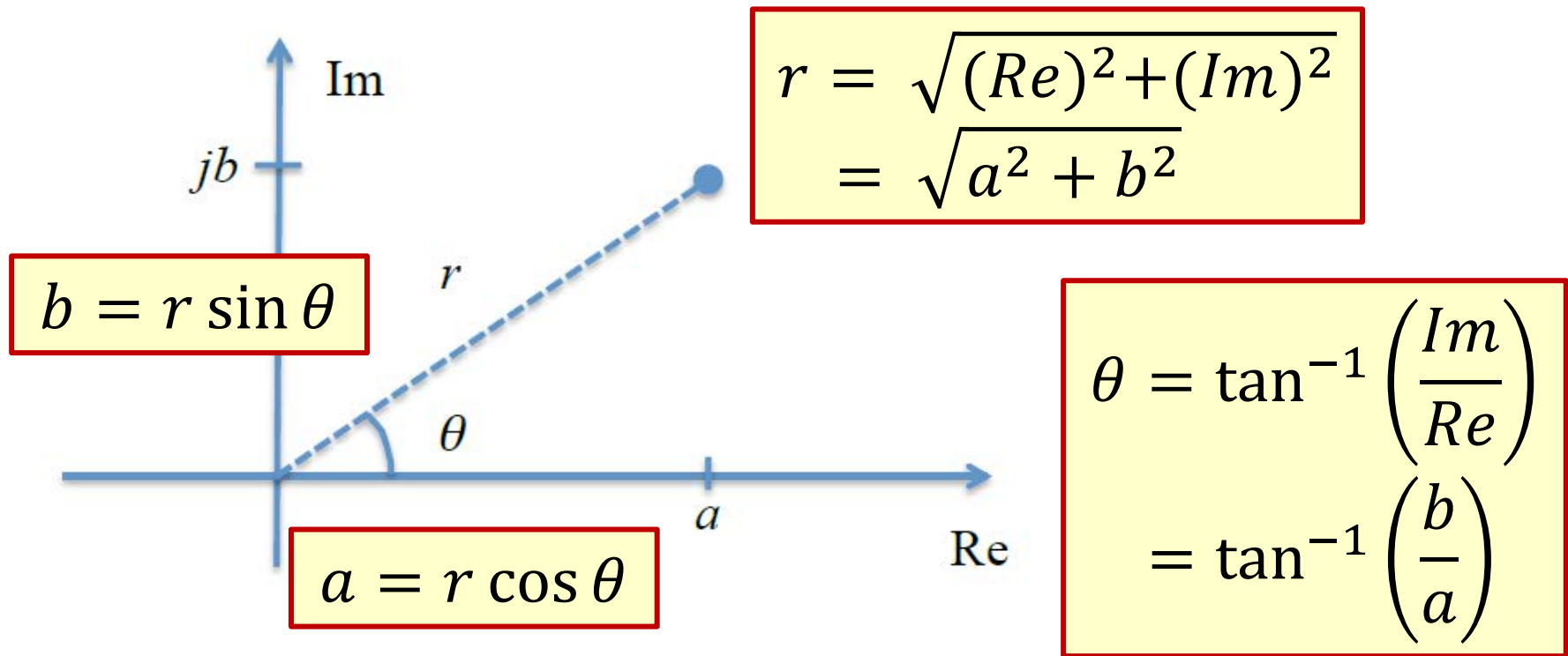Relationship Among Magnitude, Phase, Real & Imaginary Parts



Phasor Division & Multiplication


- Division:

$$\frac{A\angle\theta_1}{B\angle\theta_2} = \frac{A}{B}\angle(\theta_1 - \theta_2)$$

- Multiplication:

$$A\angle\theta_1 \times B\angle\theta_2 = AB\angle(\theta_1 + \theta_2)$$


Step-Up/Down Transformer

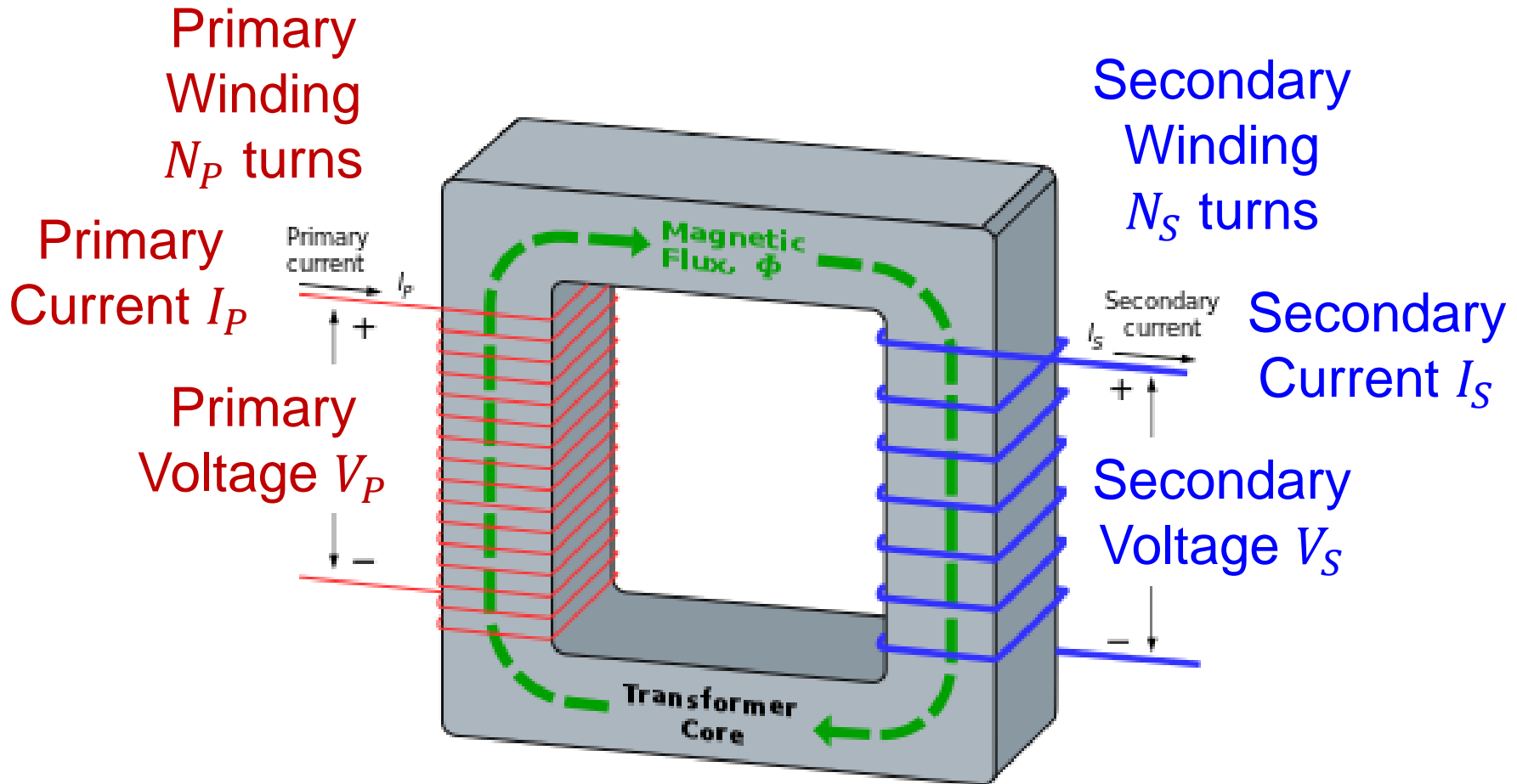



$$\frac{V_S}{V_P} = \frac{N_S}{N_P}$$

$$\frac{I_S}{I_P} = \frac{N_P}{N_S}$$

Why Rectifier?

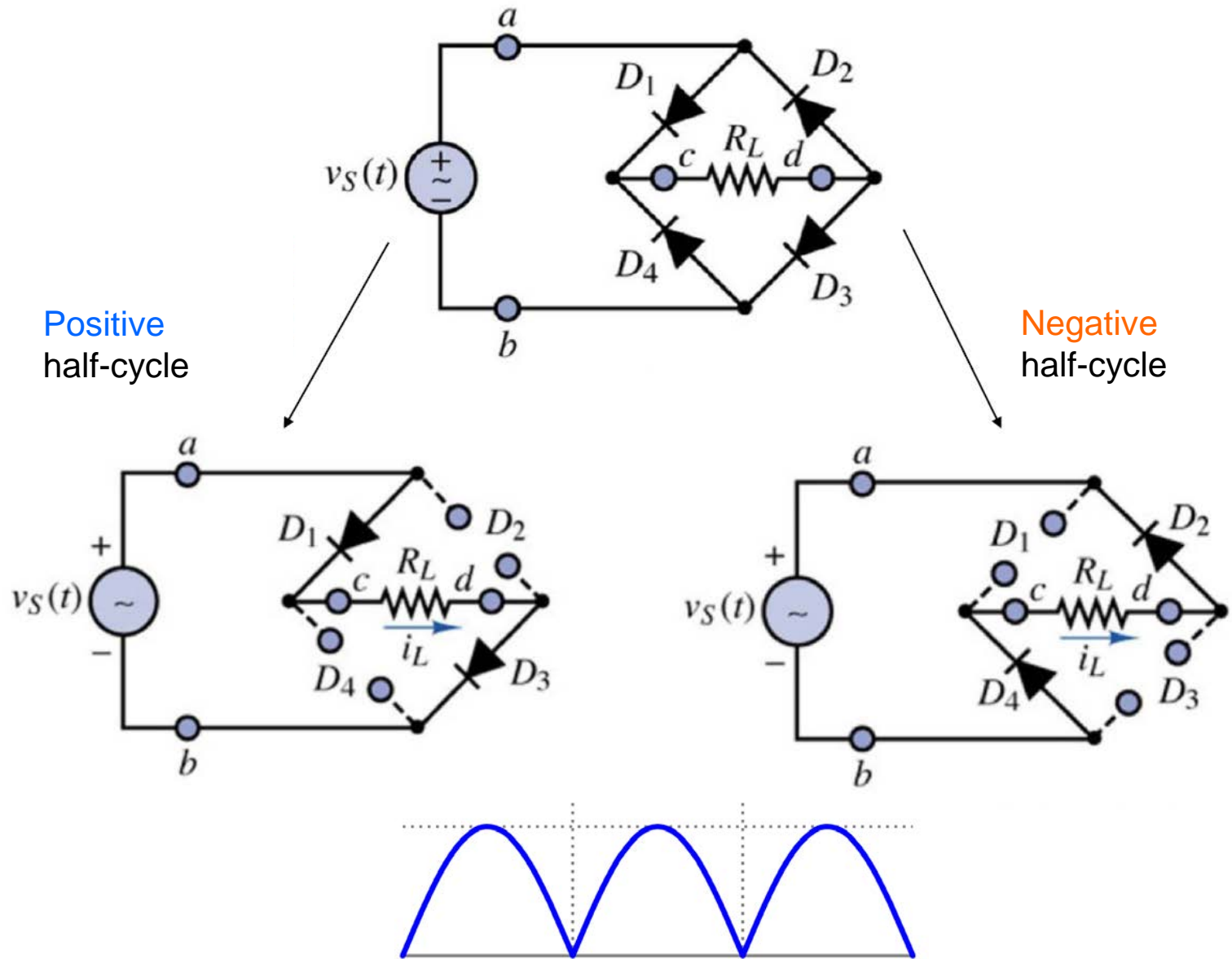


Why Filter Capacitor?

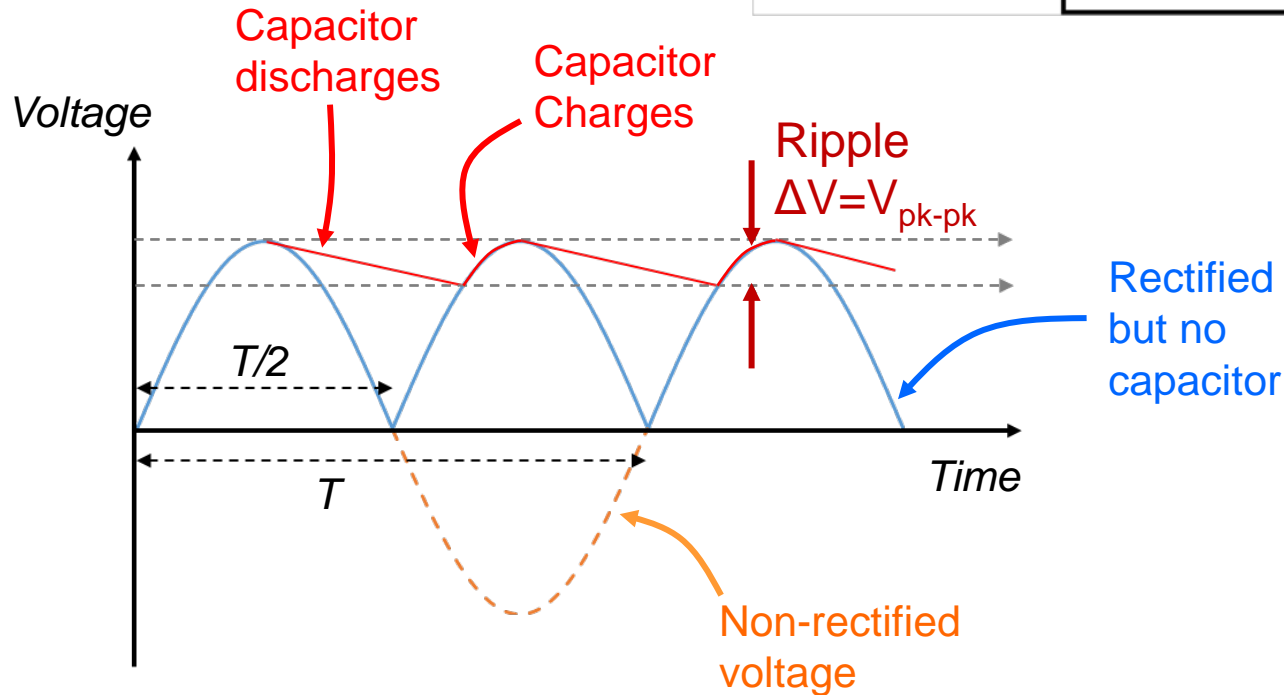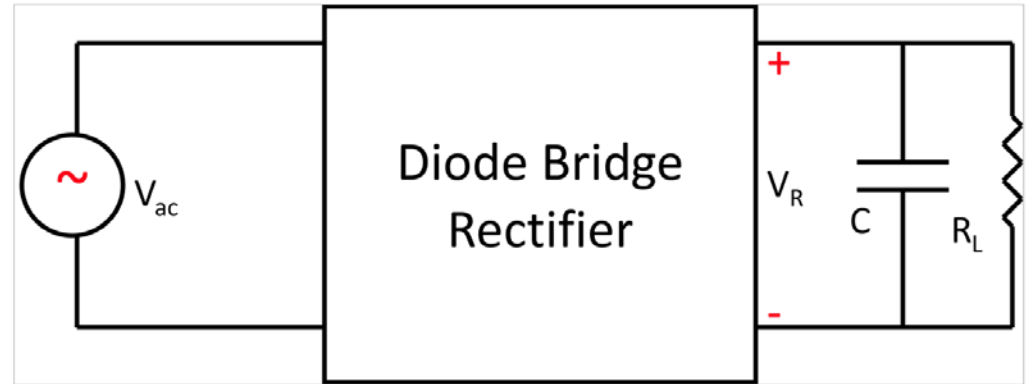


Question 1a

- Find the expression for $V_R(t)$

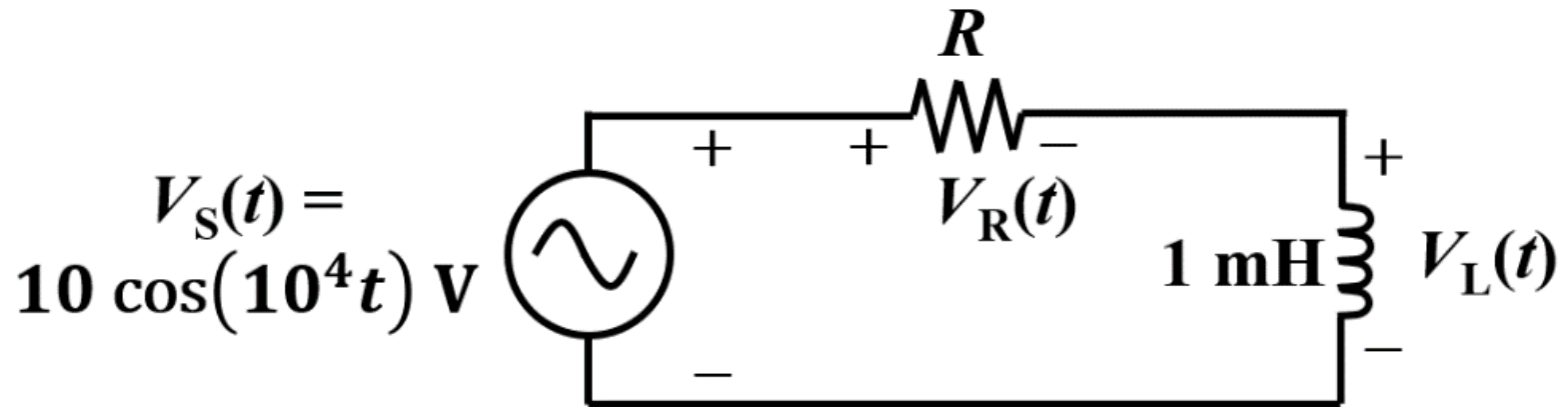


Solution to Q1a

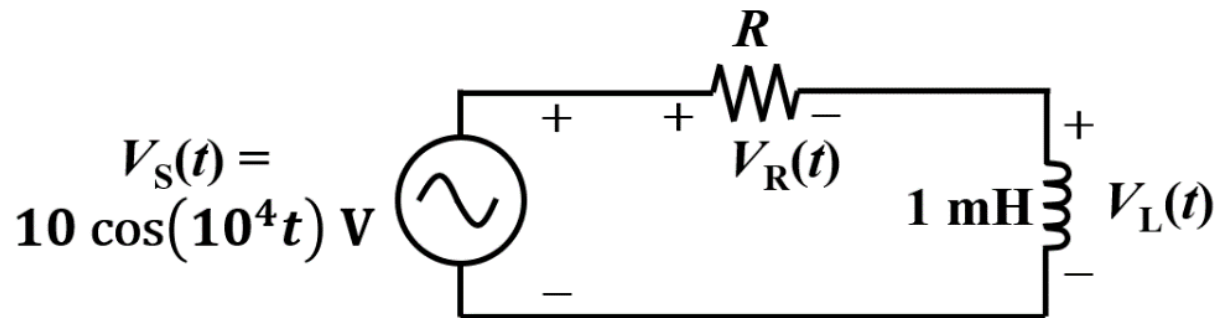- 1) Replace voltage source by phasor
- 2) Replace circuit components by impedances
- 3) Use DC circuit laws (KVL here) to solve




$$V_m = 10$$

$$\omega = 10^4$$

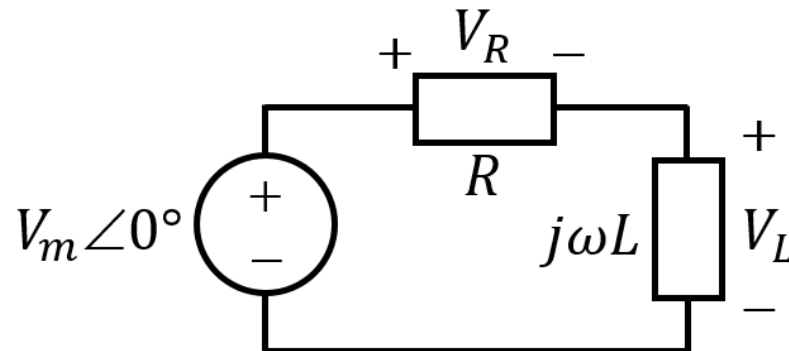

Solution to Q1a

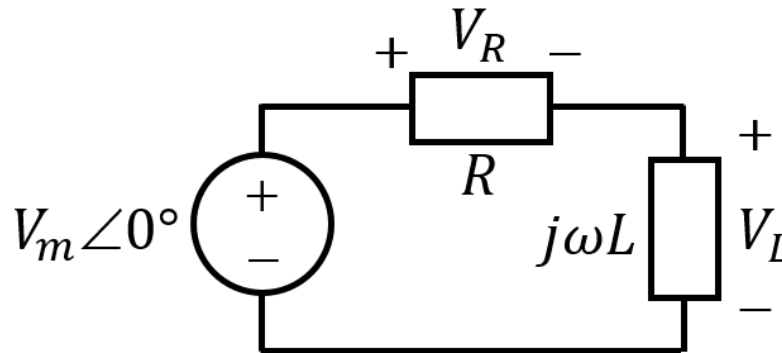

Easier to work in
phasors for
multiplication
and division

Applying voltage divider rule:

$$V_R = \frac{R}{R + j\omega L} V_m \angle 0^\circ = \frac{RV_m \angle 0^\circ}{(\sqrt{R^2 + \omega^2 L^2}) \angle \theta} = \frac{RV_m \angle -\theta}{(\sqrt{R^2 + \omega^2 L^2})}$$

where

$$\theta = \tan^{-1} \frac{\omega L}{R}$$

Therefore,

$$V_R(t) = \frac{RV_m}{(\sqrt{R^2 + \omega^2 L^2})} \cos(\omega t - \theta)$$

Question/Solution Q1b

- What is the R that would cause the phase difference between $V_S(t)$ & $V_R(t)$ to be 45° ?

Phasors of $V_S(t)$ & $V_R(t)$:

$$V_S = V_m \angle 0^\circ, \quad V_R = \frac{RV_m \angle -\theta}{(\sqrt{R^2 + \omega^2 L^2})}$$

where

$$\theta = \tan^{-1} \frac{\omega L}{R}$$

From $\theta = 45^\circ$,

$$\frac{\omega L}{R} = \tan 45^\circ = 1 \Rightarrow R = \omega L = 10^4 \times 0.001 = 10 \, \Omega$$



Question/Solution Q1c

- Draw the phasor diagram for V_S , V_R & V_L

$$V_R = \frac{R \times V_m \angle 0^\circ}{(\sqrt{R^2 + \omega^2 L^2}) \angle 45^\circ} = \frac{10 \times 10 \angle (0^\circ - 45^\circ)}{(\sqrt{10^2 + 10^8 10^{-6}})} = 7.07 \angle -45^\circ$$


$$V_L = \frac{\omega L \angle 90^\circ \times V_m \angle 0^\circ}{(\sqrt{R^2 + \omega^2 L^2}) \angle 45^\circ} = \frac{10^4 \times 10^{-3} \times 10 \angle (90^\circ - 45^\circ)}{(\sqrt{10^2 + 10^8 10^{-6}})} = 7.07 \angle 45^\circ$$

$$V_S = V_m \angle 0^\circ = 10 \angle 0^\circ$$

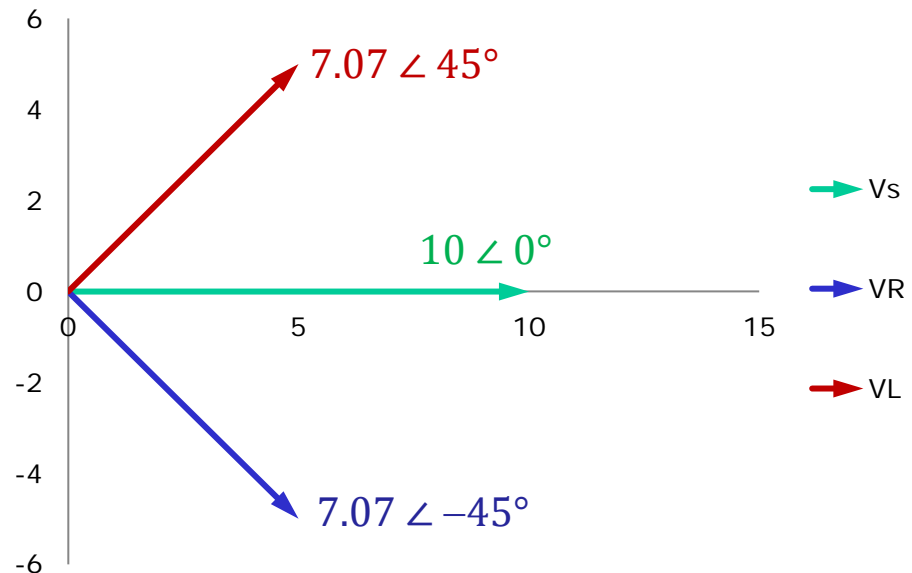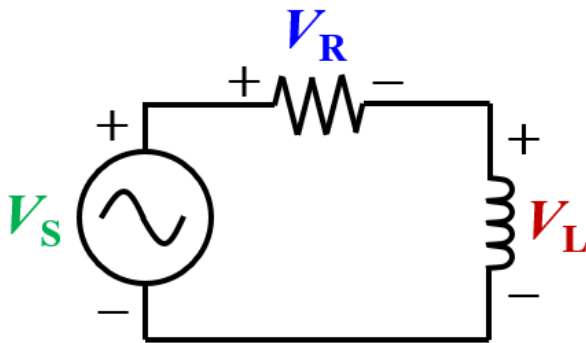


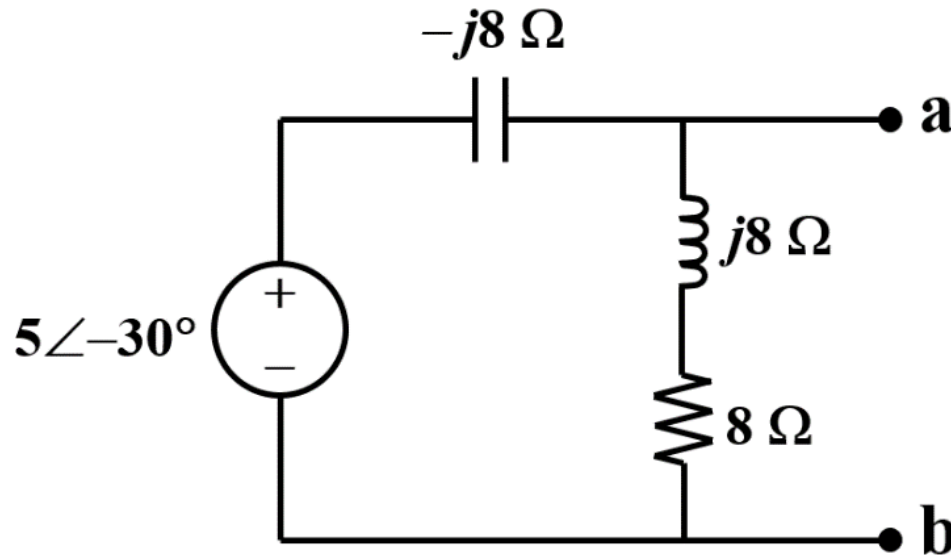Question 2

- Find the Thevenin equivalent seen across terminals **a** and **b**:



Solution to Q2

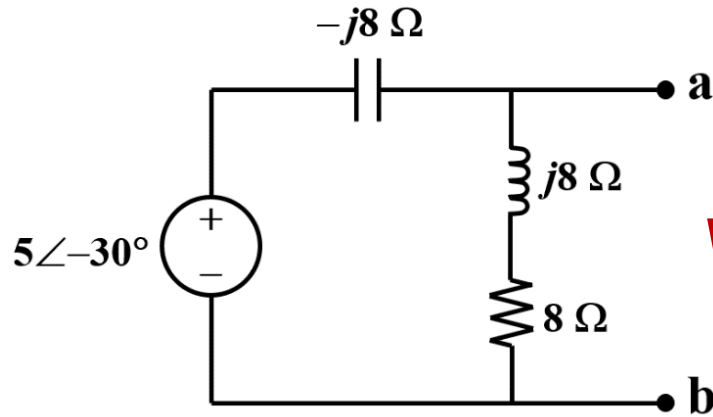

V_{Th} = Open-circuit voltage
across a & b


Applying voltage divider rule:

$$V_{Th} = \frac{8 + j8}{8 + j8 - j8} \times 5 \angle -30^\circ = (1 + j) \times 5 \angle -30^\circ$$

$$= \left[\sqrt{1^2 + 1^2} \angle \tan^{-1} \left(\frac{1}{1} \right) \right] \times 5 \angle -30^\circ$$

$$= 5\sqrt{2} \angle (45^\circ - 30^\circ) = 5\sqrt{2} \angle 15^\circ$$

Solution to Q2

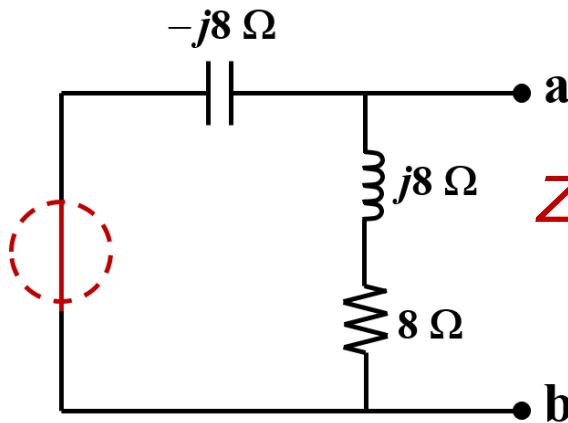

Z_{Th} = Impedance seen across a & b after putting voltage source to 0


$$Z_{Th} = \frac{(-j8) \times (8 + j8)}{(-j8) + (8 + j8)} = \frac{(-j8) \times (8 + j8)}{8}$$

$$= (-j) \times (8 + j8)$$

$$= -j8 - j^2 8 = -j8 + 8 \Omega$$


Question 3a

- Find the voltage $v(t)$

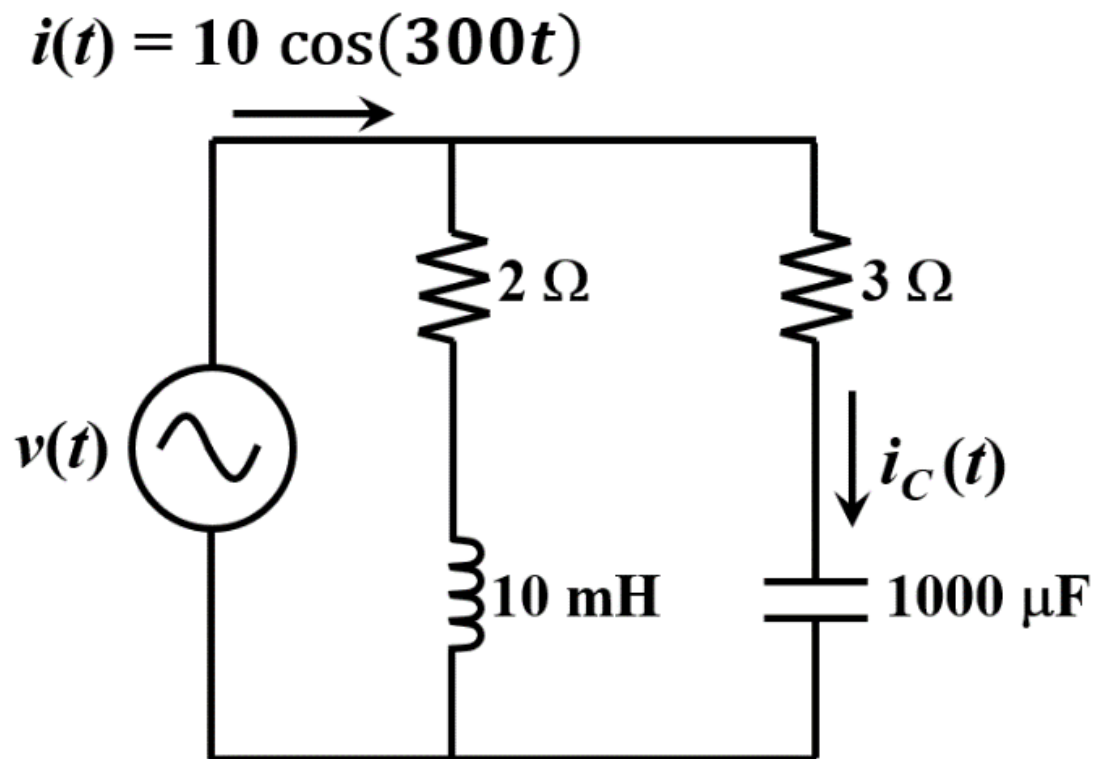


Solution to Q3a

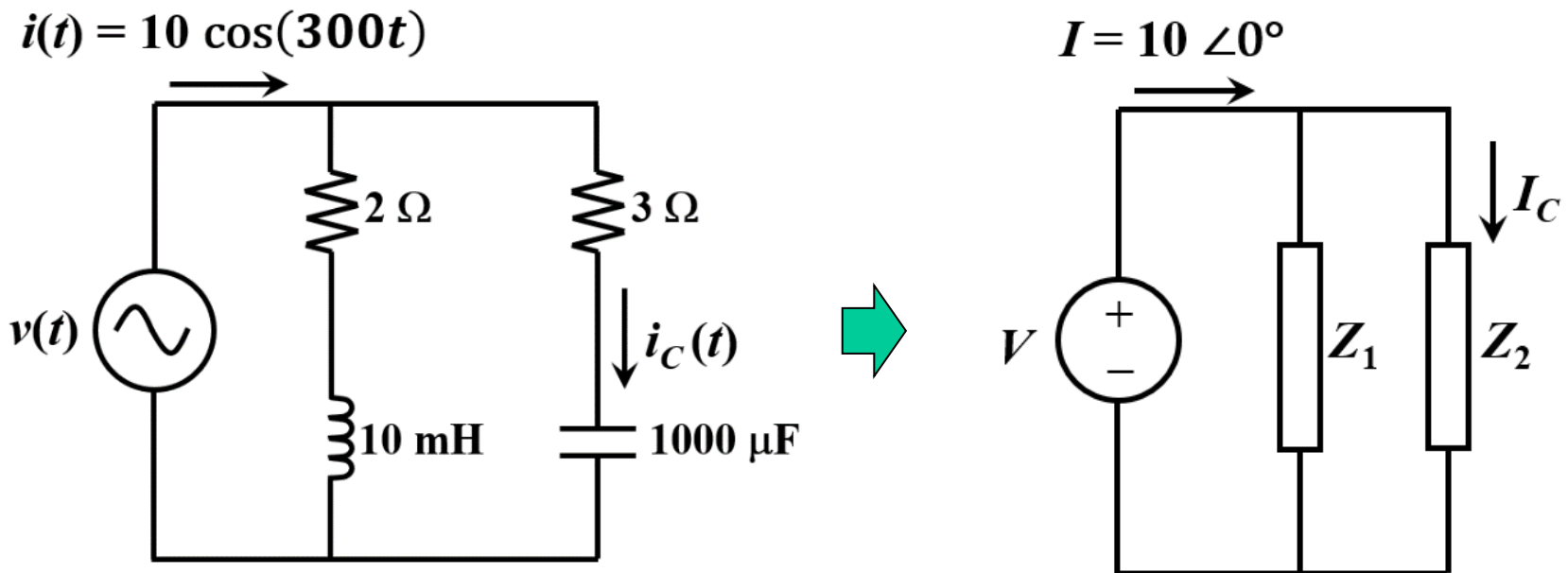- 1) Replace current by phasor
- 2) Replace circuit components by impedances
- 3) Use DC circuit laws (Ohms Law here) to solve



Solution to Q3a

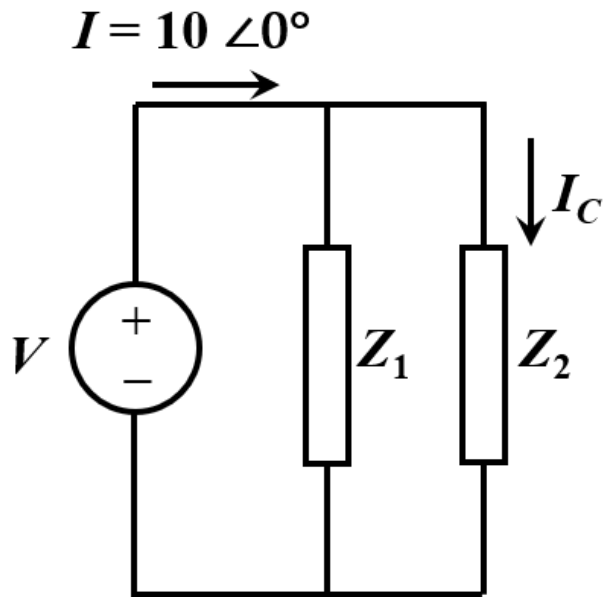

$$\omega = 300 \text{ rad/s}$$

$$Z_1 = 2 + j\omega L = 2 + j(300)(0.01) \\ = 2 + j3$$


$$Z_2 = 3 - \frac{j}{\omega C} = 3 - \frac{j}{300(1000 \times 10^{-6})} \\ = 3 - j\frac{10}{3}$$

$$Z_1 // Z_2 = \frac{Z_1 Z_2}{Z_1 + Z_2} = 3.23 \angle 12.1^\circ \quad (\text{parallel impedances})$$

$$V = 3.23 \angle 12.1^\circ \times 10 \angle 0^\circ = 32.3 \angle 12.1^\circ \quad (\text{Ohm's Law})$$

$$v(t) = 32.3 \cos(300t + 12.1^\circ) \text{ V}$$

Question/Solution to Q3b

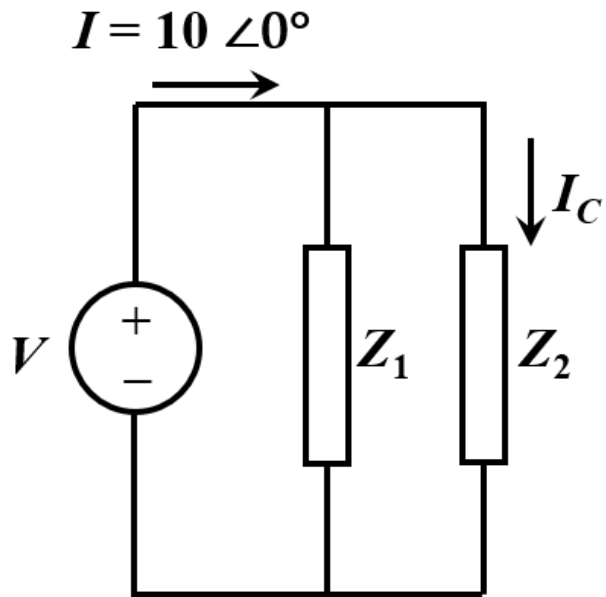

- Find the current $i_C(t)$
- Use current division principle!


$$I_C = \frac{Z_1}{Z_1 + Z_2} \times I = \frac{(2 + j3) \times 10}{2 + j3 + 3 - j\frac{10}{3}} = 7.2 \angle 60.1^\circ$$

$$i_C(t) = 7.2 \cos(300t + 60.1^\circ) \text{ A}$$

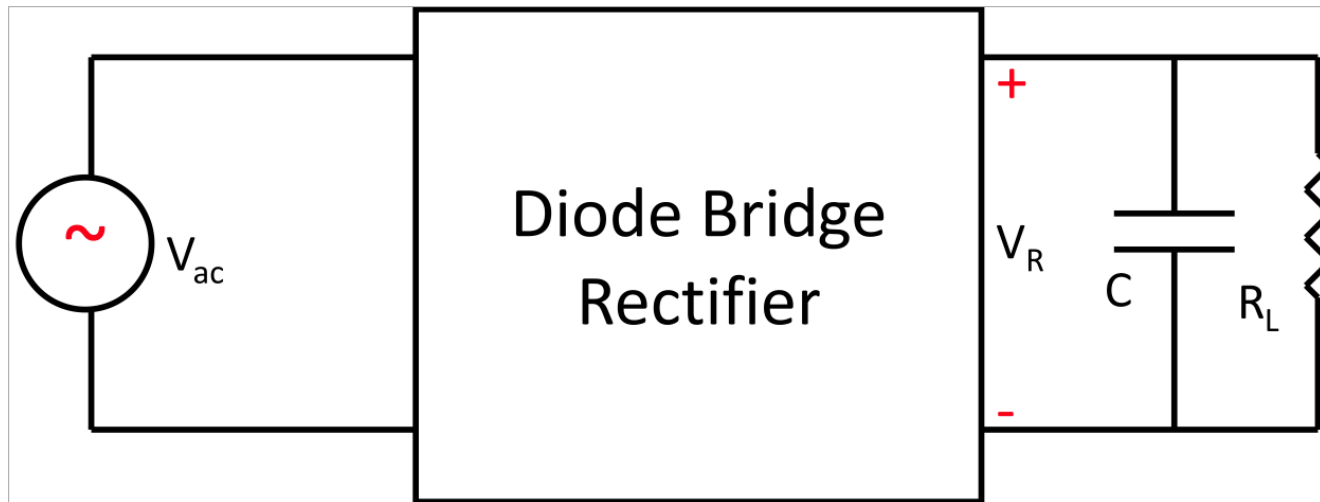
Question 4

Derive an expression for the voltage ripple at load R_L , given that:

- Average load voltage is V_{Load}
- AC power supply's frequency is f_s .



Solution to Q4

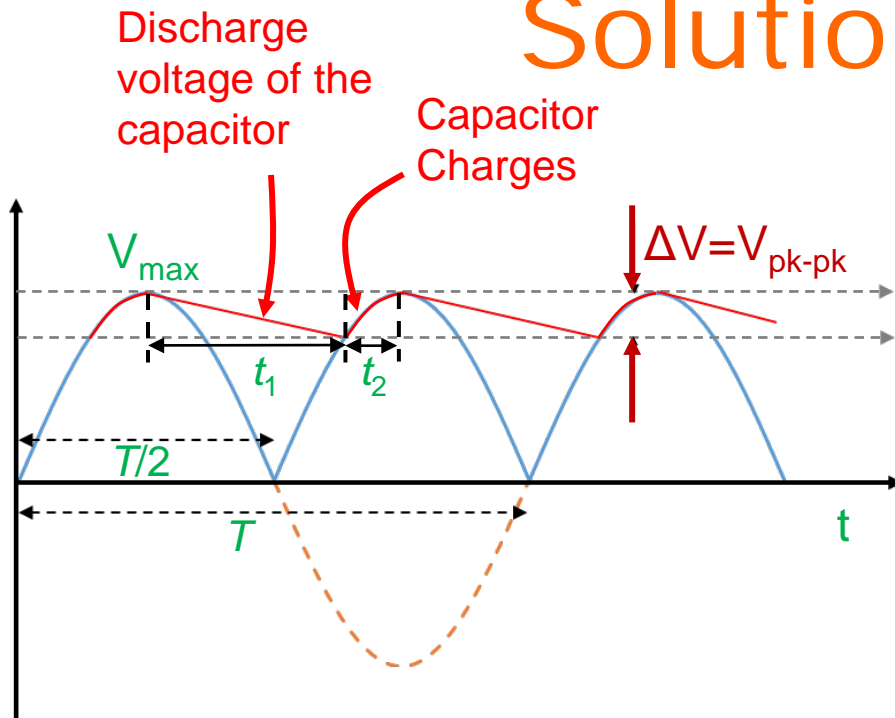

- Let V_{Load} : average load voltage
- Average load current is given by

$$I_L = \frac{V_{Load}}{R_L}$$

- Since it is a full-wave diode bridge rectifier, the pattern repeats **every $T/2$**

- Let ΔV be the peak-to-peak ripple voltage
- $\Delta V = \frac{\Delta Q}{C}$ (from capacitance's definition)
- For small ΔV , $t_1 \approx T/2$. Since $i(t) = \frac{dQ}{dt}$, average current $I_L \approx \frac{\Delta Q}{T/2}$.
- Hence $\Delta V \approx \frac{I_L * T/2}{C} = \frac{V_{Load}}{R_L} * \frac{1}{2f_s} * \frac{1}{C}$

Question 5

- Average current: 0.2 A
- Average voltage: 15 V
- AC source's frequency: 50 Hz
- Required peak-to-peak ripple $\Delta V \leq 0.5 \text{ V}$
- Assume: Ideal diodes with no voltage drop
- Find the minimum value of the filter capacitor needed

Solution to Q5

- $\Delta V = \frac{V_{Load}}{2f_s R_L C} = \frac{I_L}{2f_s C}$
- $I_L = 0.2 \text{ A}$, $f_s = 50 \text{ Hz}$, and we need $\Delta V \leq 0.5 \text{ V}$

Therefore,

$$0.5 \geq \frac{I_L}{2f_s C}$$

$$C \geq \frac{I_L}{2f_s (0.5)} = \frac{0.2}{2 * 50 * 0.5} = 4 \text{ mF}$$