CG1111 - Solution for Additional Practice Questions on DC Motors

1) 
$$K_{t} = 15 \text{ mNm/A}$$
 $R = 2.7 \Omega$ 
 $V_{m} = 12 V$ 

(a) Maximum speed possible = no-load speed

Assuming zero friction, 
$$I_{no-load} = 0 A$$

Since  $V_m = RI + E_6$ 
 $V_m = E_b = k_b CV = k_e CV$ 
 $V_m = V_m = V_m$ 

(b) Maximum torque occurs at zero speed.

At 
$$w = 0$$
, Back emf  $E_b = 0$ 

$$V_m = R I_{max}$$

$$T_{max} = K_{\ell} I_{max} = K_{\ell} \left(\frac{V_m}{R}\right) = \frac{15 \times 10^{-3} \times 12}{2.7}$$

(c)  $P_{med} = T_{cv}$ ,  $T = K_{\ell} I$ ,  $I = \frac{V_m}{R} - \frac{K_{cv}}{R}$ 

$$P_{mech} = K_{\ell} V_m w - K_{\ell} w^2$$

I hnech = 
$$\frac{K_{\ell} V_{m} w}{R} - \frac{K_{\ell} w}{R}$$
  
i  $\frac{d P_{mech}}{d w} = \frac{K_{\ell} V_{m}}{R} - \frac{2K_{\ell} w}{R}$   
When  $\frac{d V_{mech}}{d w} = 0$ ,  $V_{m} = \frac{2K_{\ell} w}{2K_{\ell} w} \Rightarrow w = \frac{V_{m}}{2K_{\ell}}$ 

in Max Prech =  $\frac{1}{R} \left[ k_t V_m \left( \frac{V_m}{2k_t} \right) - k_t^2 \left( \frac{V_m}{2k_t} \right) \right]$  $= \frac{1}{R} \left[ \frac{V_m}{2} - \frac{V_m}{4} \right]$  $= \frac{V_{m}}{4R} = \frac{12}{4\times2.7} = [3.3]$ When max Prech is produced  $\omega = \frac{V_{m}}{2K_{+}} \Rightarrow E_{b} = \frac{V_{m}}{2}$ ic,, when Back emf ? I Vm This is similar to the maximum power transper's condition for Therenin equivalent circuit, where I the spply voltage is across the theren's resistance while the other half is across the load.

2) 
$$V_{m} = 15V$$
 $N_{no-load} = 3750 \text{ RPM} \Rightarrow W_{no-load} = 392.7 \text{ rad/s}$ 
 $I_{spall} = 0.75A$ 

(a) At no load,  $V_{m} = E_{b} = K_{t} W_{no-load}$ 

if  $K_{t} = \frac{V_{m}}{W_{no-load}} = \frac{15}{392.7} = \frac{38.2 \text{ ml/m/A}}{392.7}$ 
 $V_{m} = R I_{spall} = \frac{15}{0.75} = \frac{20 \text{ s}}{20.75}$ 

(b) With unknown load,  $N_{load} = 2500 \text{ RPM}$ 
 $\Rightarrow W_{load} = 261.9 \text{ rad/s}$ 
 $E_{b} = K_{b} W_{load} = K_{c} W_{load} = 10 \text{ V}$ 
 $I = V_{m} - E_{b} = \frac{15 - 10}{20} = 0.25 \text{ A}$ 
 $I = K_{c} I = \frac{3.55 \text{ mN/m}}{20.55}$ 
 $I = I_{load} = I_{l$ 

3) 
$$V_{m} = 12V$$
,  $C_{2500} = 10 \text{ mNm}$ 
 $C_{1200} = 20 \text{ mNm}$ 
 $C$ 

4) 
$$V_{m} = 24V$$
,  $C^{2} = 60 \text{ mNm/A}$ ,  $R = 50 \text{ n}$ 
 $N = 2500 \text{ RPM} \Rightarrow W = 261 - 8 \text{ rad/s}$ 

(a)  $I = \frac{V - kW}{R} = 0.166 \text{ A}$ 
 $C = \frac{V - kW}{R} = 0.166 \text{ A}$ 
 $C = \frac{V - kW}{R} = 0.166 \text{ A}$ 

: Who-load = \frac{\frac{1}{r}}{r} = \frac{397.4 \tag{7}}{1}

(b) At 60% duty cycle,  $V_{60}$  = 0.6 × 24 = 14.4 V

Same load => same torque => same correct W = V - IR = 101-8 rad/s