

CG1111: Engineering Principles and Practice I

Summary of Key Points
for Week 2 to 5



Energy, Power & Efficiency

- Instantaneous power:

$$P = \frac{dW(t)}{dt}$$

- Efficiency

$$\eta = \frac{P_{out}}{P_{in}} = \frac{P_{out}}{P_{out} + P_{Total Loss}}$$

- C-rate of battery

–A “1C” **rate** means that the discharge current will discharge the entire battery in 1 hour

Series vs Parallel Batteries


Two Batteries connected in Series:
Double the voltage but same capacity

Two Batteries connected in Parallel:
Double the capacity but same voltage

Power Requirements


- Subsystems in Series
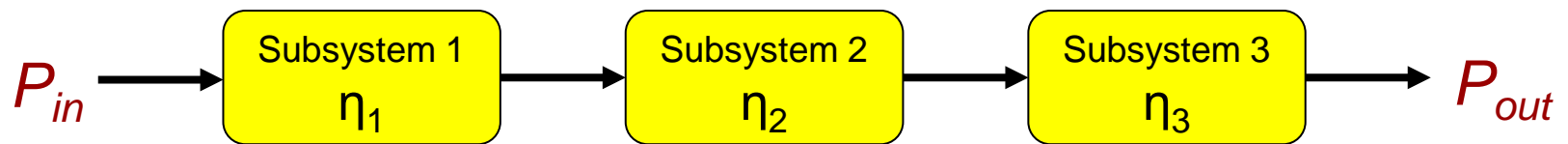
$$P_{in} = \frac{P_{out}}{\eta_1 \cdot \eta_2 \cdot \eta_3}$$




- Subsystems in Parallel

$$P_{in} = P_{in1} + P_{in2} + P_{in3}$$

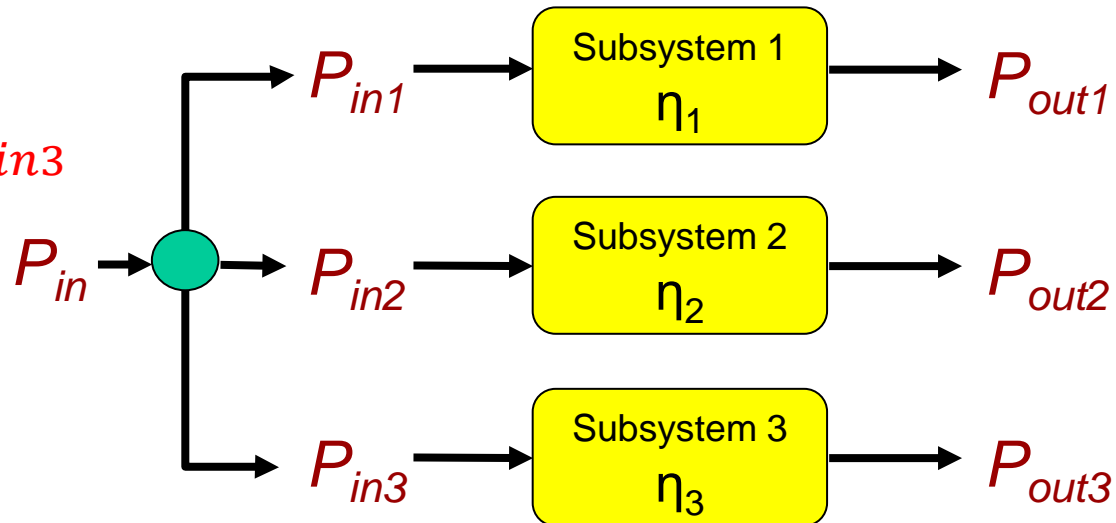

Battery Discharging Characteristics

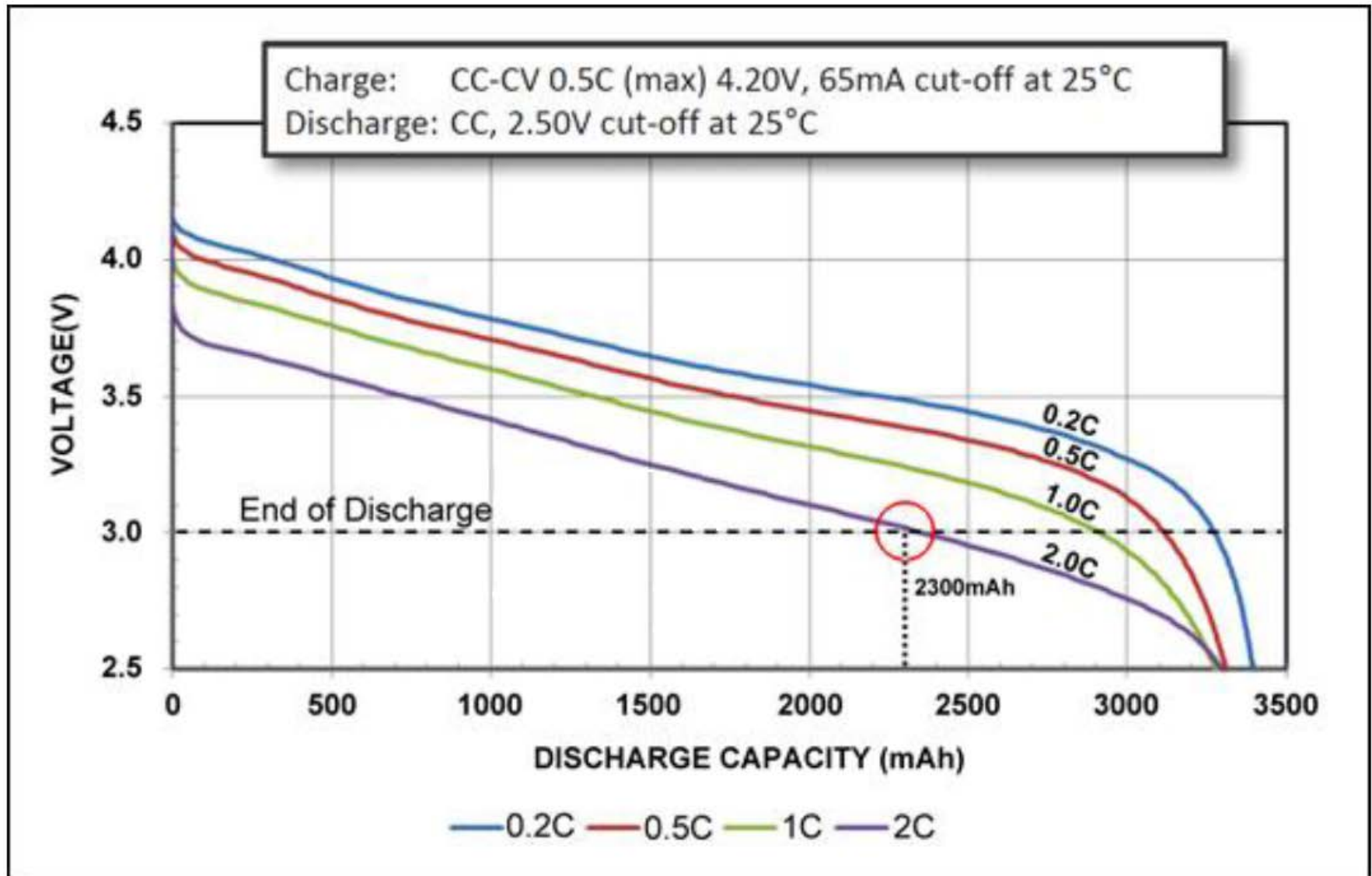

Battery Design Steps

1. Find mid-point voltage (V_{mp}) for given instantaneous C-rate
2. No. of batteries in series: $n_s = \lceil V_{op} / V_{mp} \rceil$, where
 V_{op} = desired operating voltage
3. Power requirements, $P_{in} = \Sigma (P_{out,i} / \eta_i)$ (parallel)
or $P_{in} = P_{out} / (\Pi \eta_i)$ (series)
4. Load Capacity (Ah) = Load Energy / V_{BB} , where
Load Energy (Wh) = $P_{in} \times$ (No. of operating hrs)
Battery bank's voltage $V_{BB} = n_s \times V_{mp}$
5. Find single battery's capacity from given C-rate and allowed depth of discharge (usually corresponding to V_{eod} (knee))
6. No. of batts in parallel: $n_p = \lceil \text{Load Capacity} / \text{Battery Capacity} \rceil$
7. Total No. of batteries = $n_s * n_p$
8. Conclude design by calculating the actual Load Capacity of the battery pack.

Fundamentals of Electricity

- Ohm's Law
 - Empirical observation that $V \propto I$ for purely resistive element, and resistance is defined as V/I
- How is electrical power calculated?
 - $P = VI$ (always true regardless of type of element)
 - For resistors, we have $P = I^2R$ because $V = IR$
 - ✓ Never, never use $P = I^2R$ for non-resistive elements (e.g., LEDs)!!

KVL & KCL

- KCL (conservation of mass/charge)
 - The sum of all currents entering the node must be equal to the sum of all currents leaving the node
 - ✓ The “node” can be any enclosed surface drawn in any part of the circuit
- KVL (conservation of energy & power)
 - Around any closed loop, the sum of voltage drops must equal the sum of voltage rises

Series/Parallel Resistances

- **Series:** $R_{eq} = R_1 + R_2 + \dots + R_N$

$$R_{eq} > R_i$$


Resistances in **series** lead to **increased resistance**

- **Parallel:** $1/R_{eq} = 1/R_1 + 1/R_2 + \dots + 1/R_N$

$$R_{eq} < R_i$$

Resistances in **parallel** lead to **reduced resistance**

Voltage Division Principle

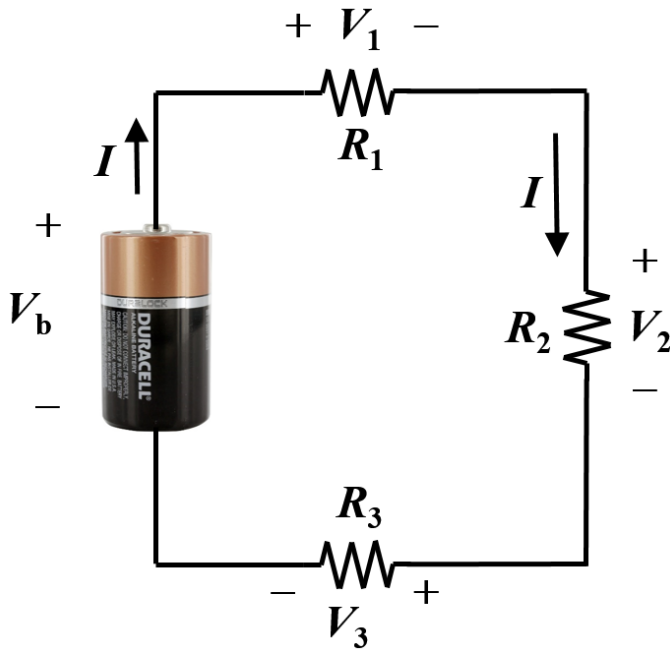


$$V_1 = \frac{R_1}{R_1 + R_2 + R_3} V_b$$

$$V_2 = \frac{R_2}{R_1 + R_2 + R_3} V_b$$

$$V_3 = \frac{R_3}{R_1 + R_2 + R_3} V_b$$

Works for any number of series resistors

Current Division Principle

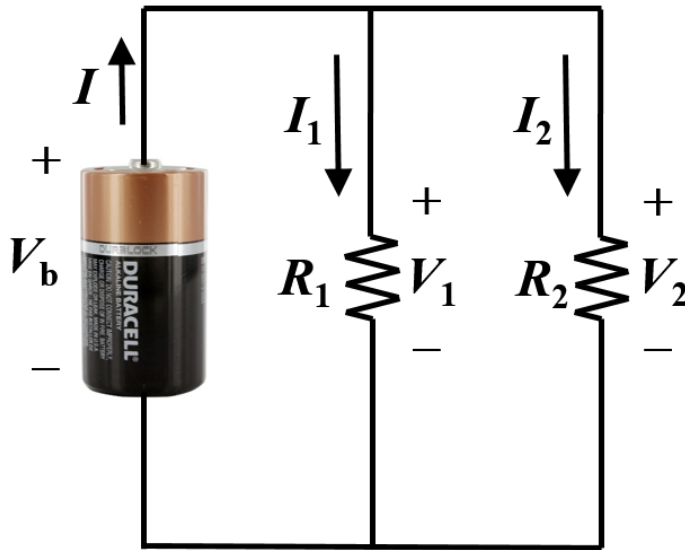

$$I_1 = \frac{R_2}{R_1 + R_2} I$$


$$I_2 = \frac{R_1}{R_1 + R_2} I$$

Only works for **two** parallel branches

Passive vs Active Elements


- Voltage has polarity, current has direction
 - Passive elements (**consumes** power):
voltage (potential) **drops** in the direction of the current

Note: Resistors are always passive

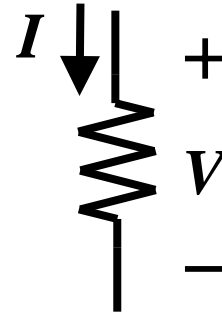


- Active elements (**delivers** power):
voltage (potential) **risers** in the direction of the current

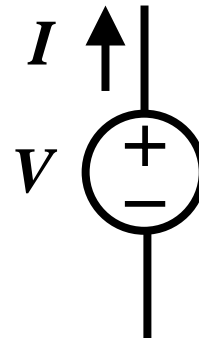Current comes out from the '+' polarity
and the voltage is positive




Passive Sign Convention

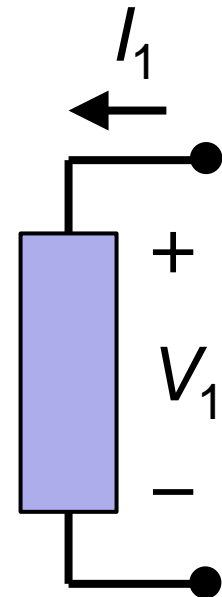- Adopted when it is not clear whether an unknown element is active or passive
- Assumes all unknown elements are passive
 - Reference direction for current is assumed to enter the positive voltage terminal of the element
 - Significance:
 - ✓ If power is calculated to be positive, the element is passive (a load)
 - ✓ If power is calculated to be negative, the element is active (a source)




How to Label V & I for Resistors?

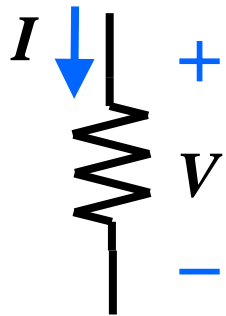- A resistor consumes power:
 - Principle: In a resistor, the voltage (potential) must drop in the direction of the current




If the current's true direction or the voltage's true polarity is not obvious in the circuit, just **pick & label either the current or the voltage**, and then **label the other one** by following the **above principle**

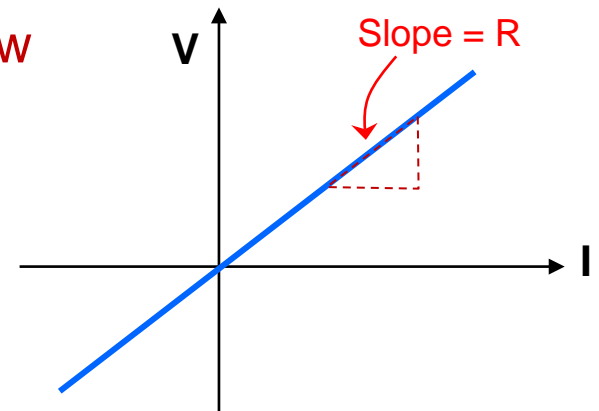You can only **apply Ohm's Law** if you label them this way!



Thevenin Equivalent Circuit

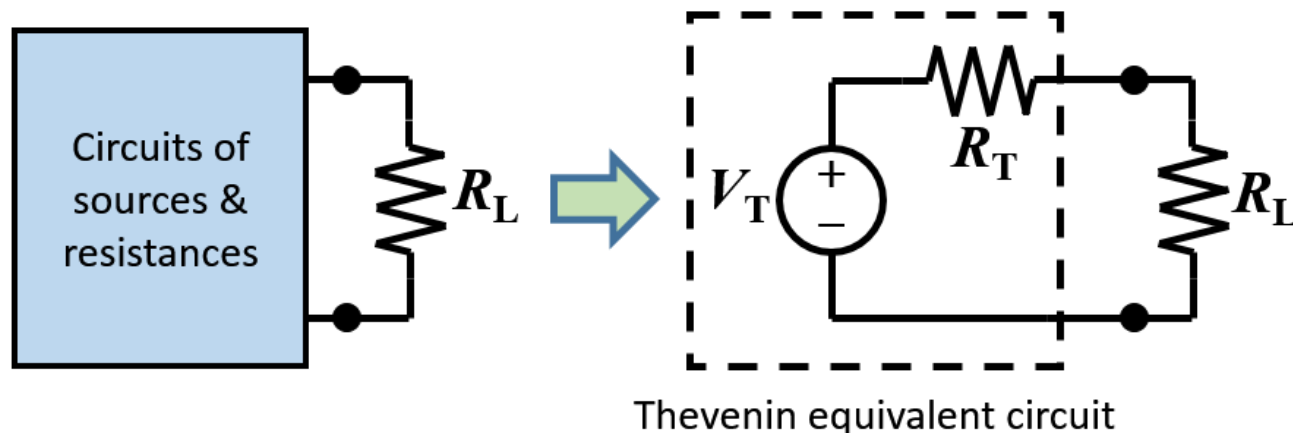
- Any circuit consisting of sources and resistances can be replaced by a Thevenin equivalent circuit



The **I-V behaviour** of the Thevenin equivalent circuit is the **same** as that of the more complex circuit
→ **Very useful for circuit analysis!**

Finding Thevenin Voltage

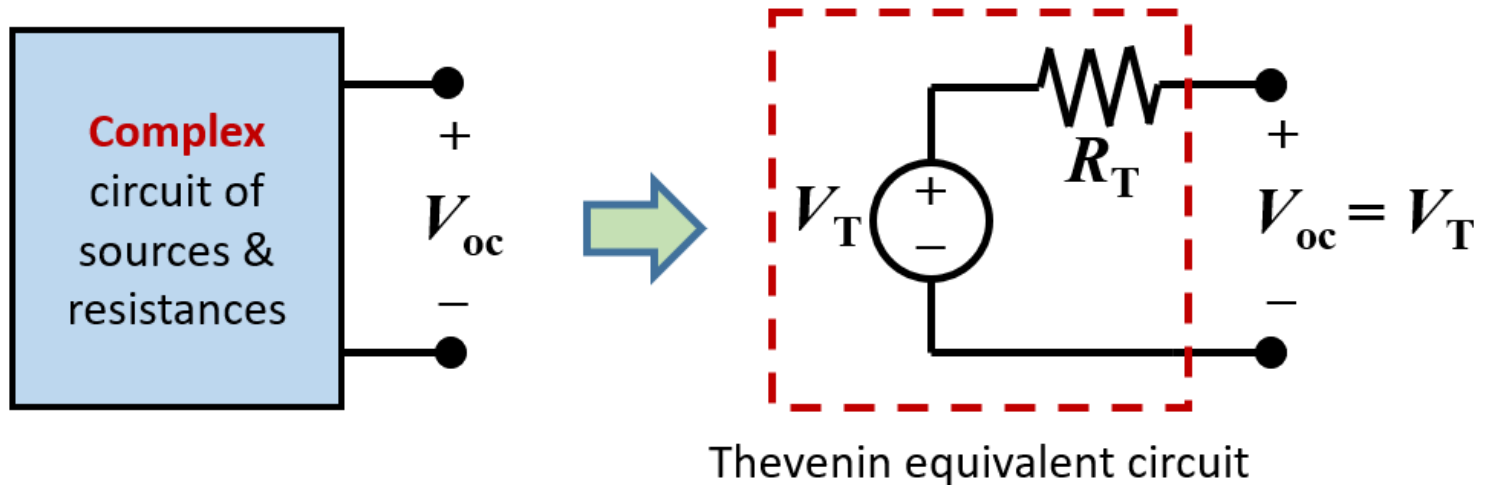
V_T can be obtained by finding V_{oc} across the 2 terminals of the complex circuit



Finding Thevenin Resistance

R_T can be obtained using Ohm's Law after finding I_{sc} across the 2 terminals of the complex circuit


$$R_T = \frac{V_T}{I_{sc}}$$

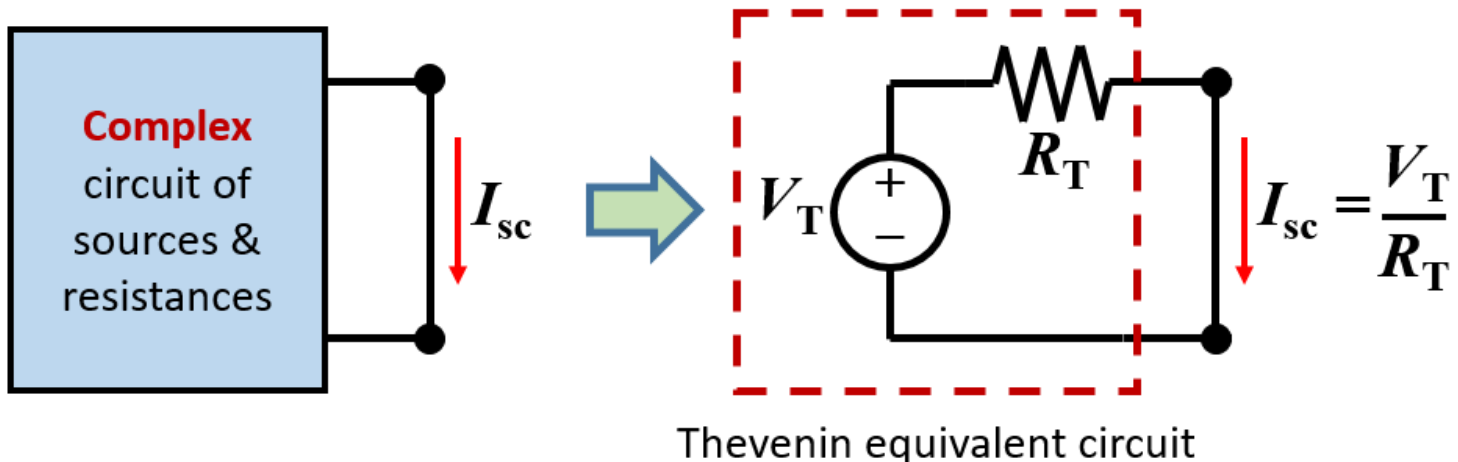


Experimental Method to Find R_T

- There is a risk that I_{sc} may be large

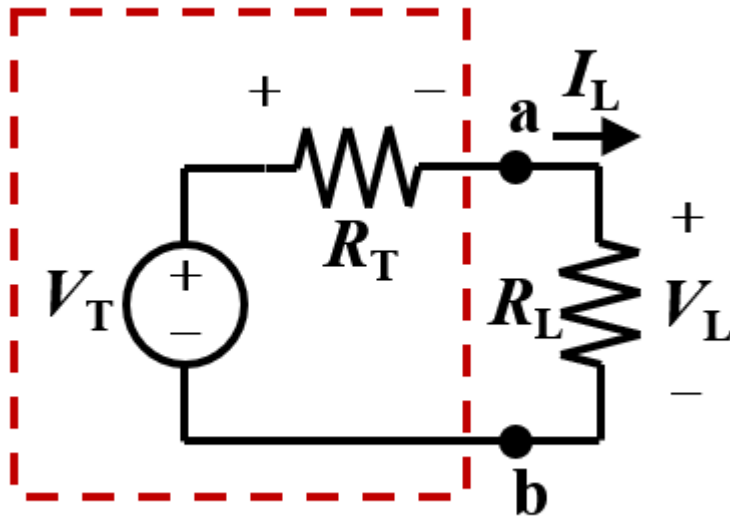It is safer to connect the circuit to multiple resistive loads and then use graphical approach




Thevenin equivalent circuit

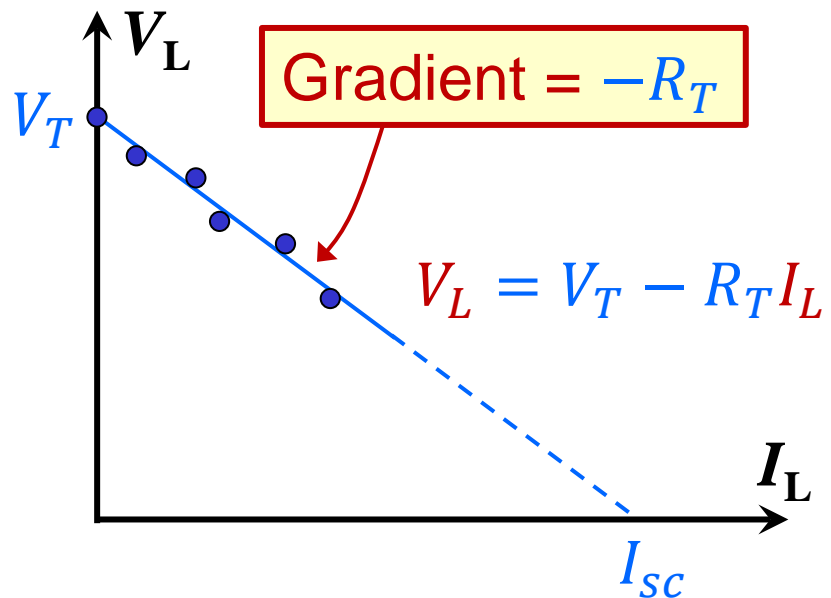


Another Analytical Method to Find R_T (Usually Easiest!)

- If the original electrical circuit consists of independent voltage sources only,
 - Replace all voltage sources with a short-circuit (0 V); this results in a purely resistive network

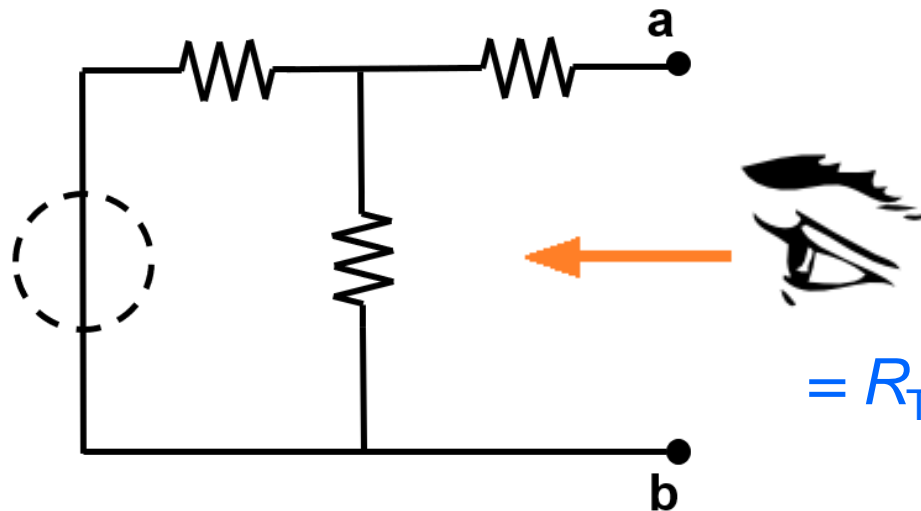Then, find the equivalent resistance between the two terminals



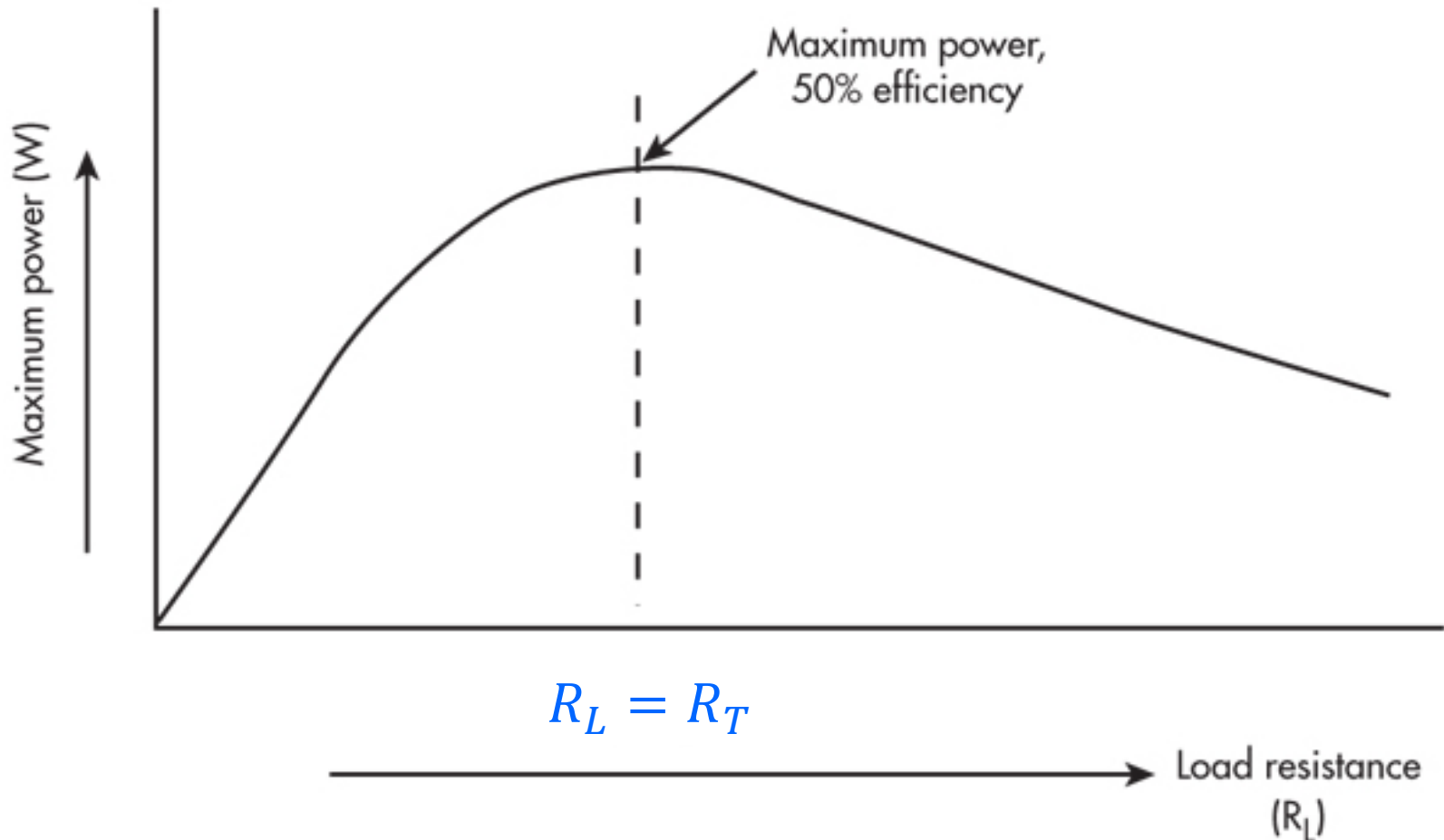Maximum Power Transfer from Thevenin Equivalent Circuit



Node Voltage Analysis Method

- Node voltage analysis
 - Most general method for analyzing circuits
- Basic idea:
 - Solve for all the unknown node voltages w.r.t. a reference node
 - Use them to calculate the voltage across any element, & the current passing through it


Node Voltage Analysis Method

- Identify the nodes with unknown voltages, & minimize number of unknowns
- Apply KCL at the nodes, to obtain as many equations as the number of unknown variables


Note: The node must be adjacent to resistive branches only

$$\frac{V_b - V_a}{R_1} + \frac{V_c - V_a}{R_2} + \frac{0 - V_a}{R_3} = 0$$

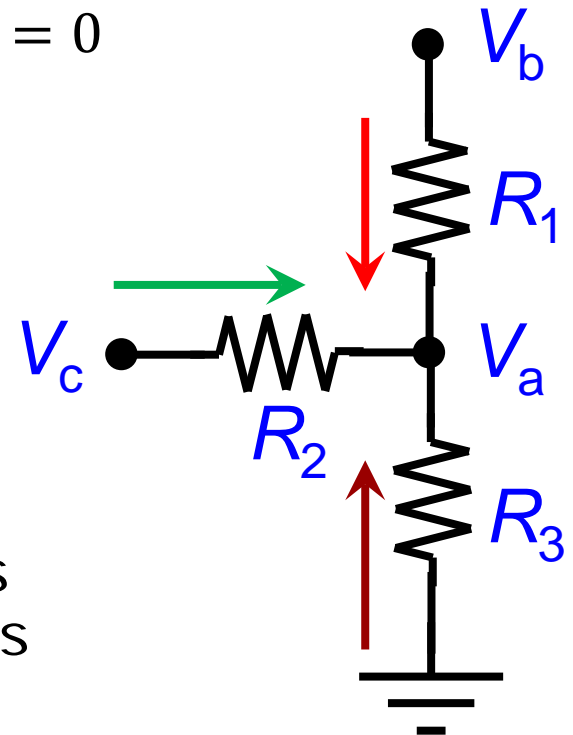- Rearrange the equations to consolidate the coefficients (via visual inspection) for each unknown
- Solve the linear system of equations to obtain the unknown node voltages



Duality of Capacitors & Inductors

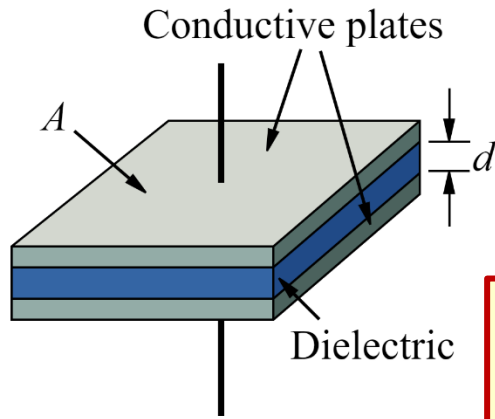

ϵ : Permittivity of the dielectric
 A : Cross-sectional area of the plate
 d : Distance between the plates

$$C = \frac{\epsilon A}{d}$$

$$C = \frac{Q}{V}$$

$$i(t) = C \frac{dv(t)}{dt}$$


$$E = \frac{1}{2} CV^2$$

$$L = \frac{\mu_r \mu_0 N^2 A}{l}$$

$$L = \frac{\Phi}{I}$$

$$v(t) = L \frac{di(t)}{dt}$$

$$E = \frac{1}{2} LI^2$$

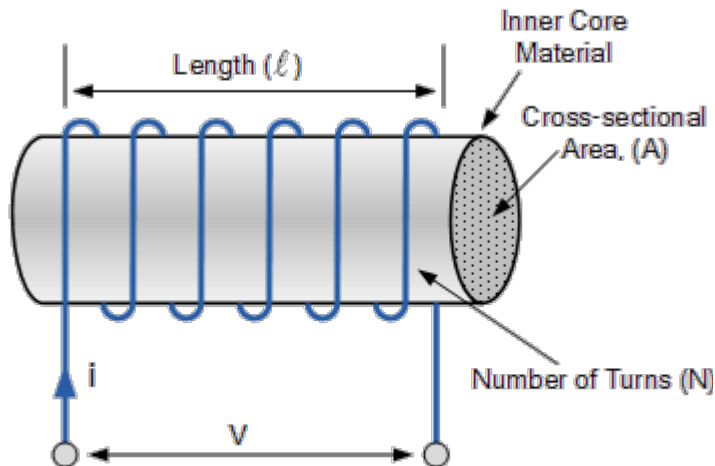

μ_r : Relative permeability of core material
 μ_0 : Permeability of free space ($4\pi \times 10^{-7}$ Wb.A/m)
 N : Number of turns in the coil
 A : Cross-sectional area of core
 l : Length of the core

Duality of Capacitors & Inductors

$$i(t) = C \frac{dv(t)}{dt}$$

Capacitor voltage cannot change instantaneously,
and must be **continuous**

$$v_c(0^-) = v_c(0^+)$$

Capacitors in DC circuits behave as
open-circuit at **steady state**


$$v(t) = L \frac{di(t)}{dt}$$

Inductor current cannot change instantaneously,
and must be **continuous**


$$i_c(0^-) = i_c(0^+)$$

Inductors in DC circuits behave as
short-circuit at **steady state**


Duality of Capacitors & Inductors

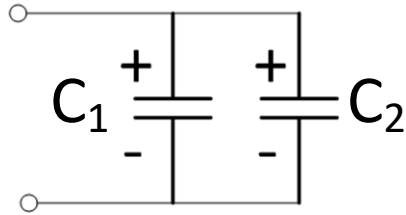


$$C_{eq} = C_1 + C_2$$

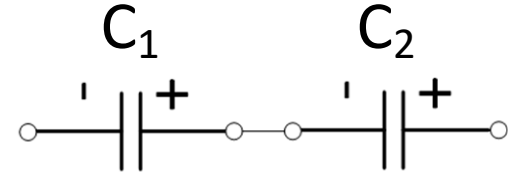
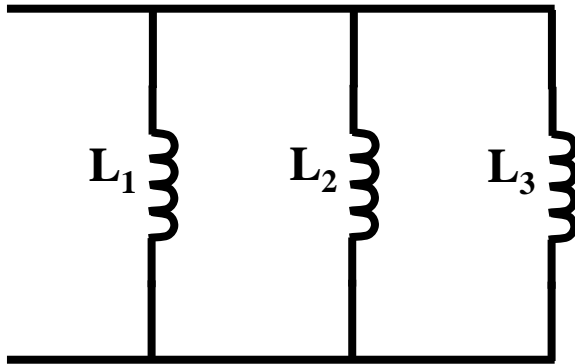
$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2}$$


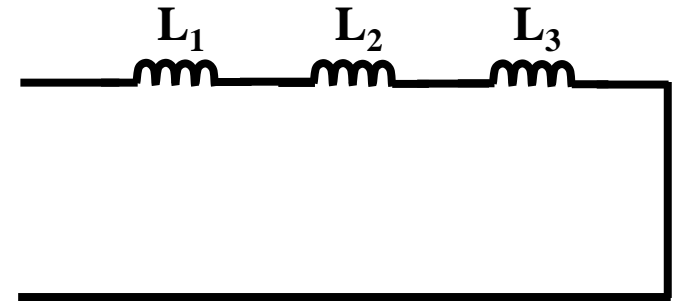
$$\frac{1}{L_{eq}} = \frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3}$$



$$L_{eq} = L_1 + L_2 + L_3$$

Duality of Capacitors & Inductors

- A capacitor's **transient voltage** in a **series RC circuit** can be expressed as

$$v_c(t) = v_c(0)e^{-\frac{t}{\tau}} + v_c(\infty)[1 - e^{-\frac{t}{\tau}}], \tau = RC$$

- An inductor's **transient current** in a **series RL circuit** can be expressed as

$$i_L(t) = i_L(0)e^{-\frac{t}{\tau}} + i_L(\infty)[1 - e^{-\frac{t}{\tau}}], \tau = L/R$$

