


CG1111 Engineering Principles and Practice I

Tutorial for Week 9


Operational Amplifiers and Filters

1. Show that if $R_{in} = R_L$, then the power gain in dB for an amplifier circuit is given by

$$\text{Power gain (dB)} = 20 \log_{10} \left| \frac{V_{out}}{V_{in}} \right| \text{ dB}$$

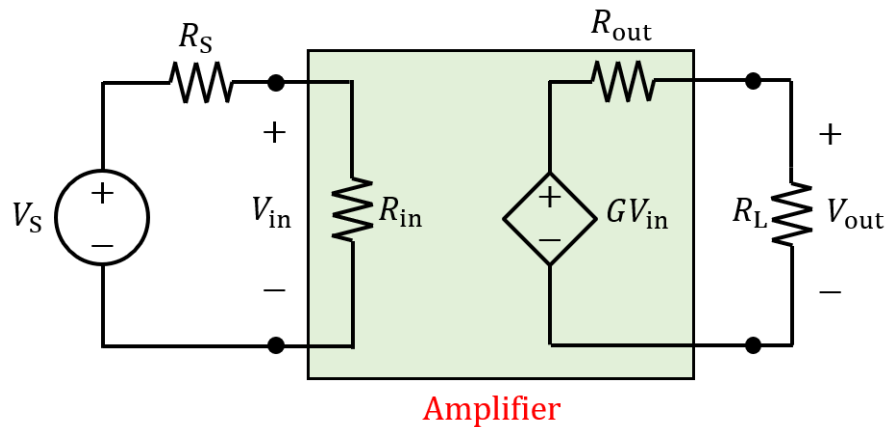


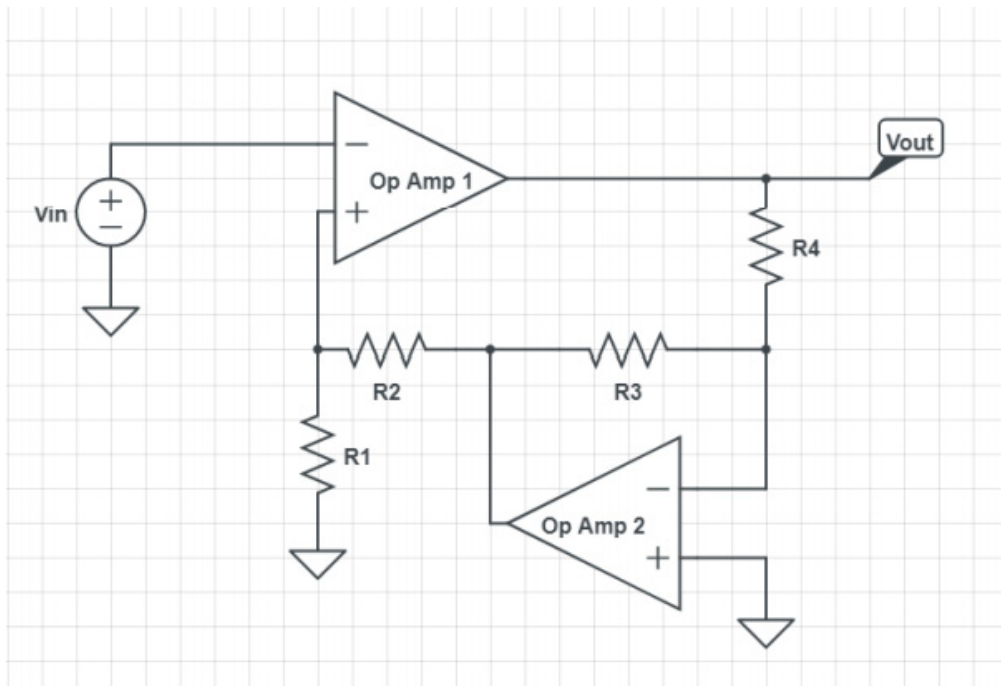2. Calculate the voltage gain (V_{out}/V_{in}) of Op Amp 1 in the figure below:



Ans: $\frac{V_{out}}{V_{in}} = -\left(1 + \frac{R_2}{R_1}\right) \times \frac{R_4}{R_3}$

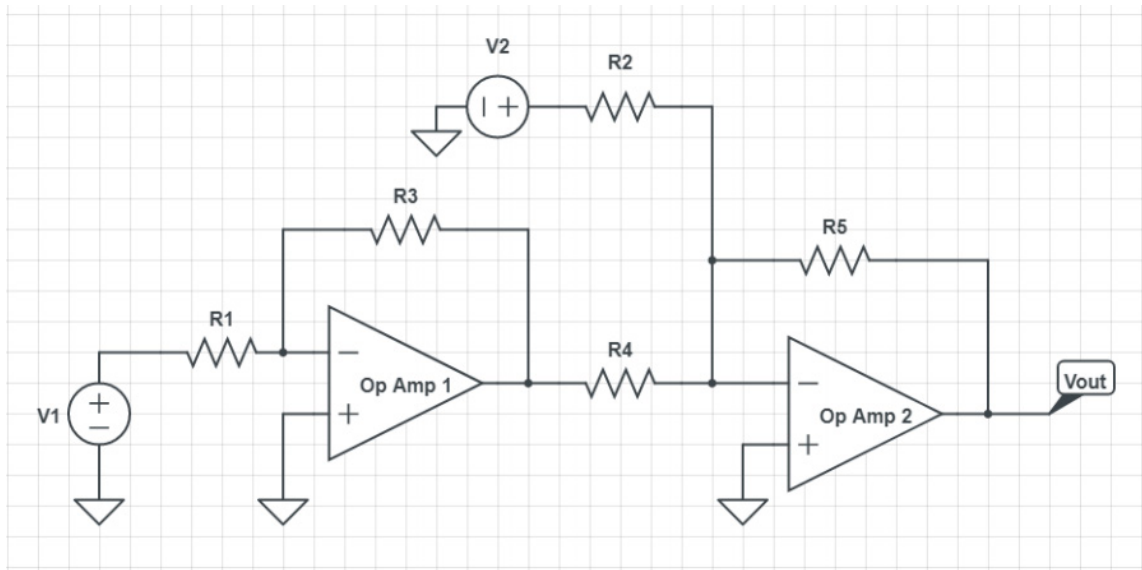3. Derive the expression relating V_{out} and the two input voltages, V_1 and V_2 .



After obtaining the expression relating the output to the inputs for the configuration, can you design the resistance values such that V_{out} is the difference between the two input signals amplified by a gain factor?

Ans:
$$V_{out} = \left(\frac{R_5}{R_4} \times \frac{R_3}{R_1} \times V_1 \right) - \left(\frac{R_5}{R_2} \times V_2 \right)$$

4. An audio song has frequencies in the range of 100-3000 Hz. It is corrupted with a high frequency noise of 10 kHz. You need to design a low-pass filter to suppress the 10 kHz noise by 20 dB relative to the passband gain. What should be the cut-off frequency of the low-pass filter?

Ans:
$$f_c = 1 \text{ kHz}$$