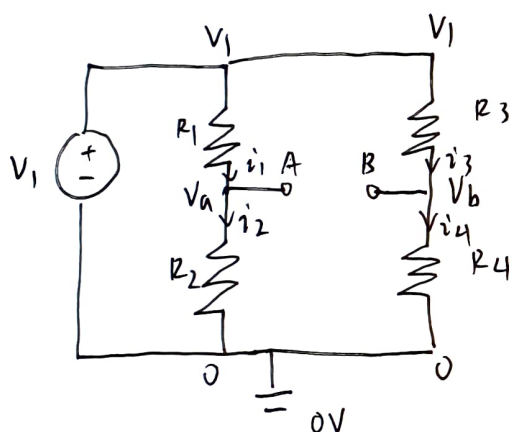


Week 3 Studw 2

Node Method

- ① select a reference node, ground, defined to be 0V potential
- ② label potential of remaining nodes wrt ground node. nodes connected to ground via an independent source is labelled with the voltage of the source (with appropriate polarity)
- ③ Remaining unknowns labelled
- ④ write KCL for nodes with unknown voltage applying element laws / KVL
- ⑤ solve for unknown potentials and back solve / substitute for branch voltage / current

Activity 1



Applying KCL at node V_a : $i_1 = i_2$

$$\frac{V_1 - V_a}{R_1} = \frac{V_a - 0}{R_2}$$

$$V_a \left(\frac{1}{R_2} + \frac{1}{R_1} \right) = \frac{V_1}{R_1}$$

$$V_a = \frac{R_2}{R_1 + R_2} V_1$$

Applying KCL at node V_b : $i_3 = i_4$

$$\frac{V_1 - V_b}{R_3} = \frac{V_b - 0}{R_4}$$

$$V_b = \frac{R_4}{R_3 + R_4} V_1$$

OR by quoting voltage divider principle :

$$V_a = \frac{R_2}{R_1 + R_2} V_1$$

$$V_b = \frac{R_4}{R_3 + R_4} V_1$$

not equivalent
reverse
polarity.

$$V_{AB} = V_a - V_b = V_1 \left(\frac{R_2}{R_1 + R_2} - \frac{R_4}{R_3 + R_4} \right)$$

$$V_{BA} = V_b - V_a = V_1 \left(\frac{R_4}{R_3 + R_4} - \frac{R_2}{R_1 + R_2} \right)$$

Suppose $R_1, R_2, R_3 = R$

$$R_4 = R + \Delta R$$

$$V_{A13} = V_1 \left(\frac{R}{R+R} - \frac{R+\Delta R}{R+R+\Delta R} \right)$$

$$= V_1 \left(\frac{1}{2} - \frac{1 + \frac{\Delta R}{R}}{1 + 1 + \frac{\Delta R}{R}} \right)$$

↓ divide both numerator and denominator by R

$$= V_1 \left(\frac{1}{2} - \frac{1+x}{2+x} \right)$$

let $\frac{\Delta R}{R}$ be x

$$= \left(\frac{-x}{4+2x} \right) V_1$$

$$4V_{A13} + 2xV_{A13} = -xV_1$$

$$x(2V_{A13} + V_1) = -4V_{A13}$$

$$x = \frac{\Delta R}{R} = \frac{-4V_{A13}}{2V_{A13} + V_1}$$

Supernodes


treat the group of elements as a black box / super node

current going into the supernode = current coming out of super node (KCL)



$$i_1 + i_2 = i_3 + i_4$$

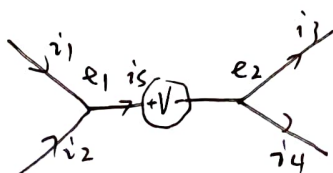supernodes are usually used when node analysis fails due to a floating independent voltage source



$$e_2 = e_1 - V$$

Activity 2

$$V_1 = 5.12 \text{ V}$$

from activity 1 :

$$\frac{\Delta R}{R} = \frac{-4V_{AB}}{2V_{AB} + V_1}$$

$$\Delta R = \frac{-4V_{AB}}{2V_{AB} + V_1} \cdot R$$

At reference value $R_1, R_2, R_3, R_4 = 500$

$$V_{AB} = 1 \text{ mV}$$

* minimise as best as you can

$$\Delta R \propto K V_{AB} \quad K = -390.625 \text{ (see derivation)}$$

Resistance R_4 / Ω	Voltage V_{AB} / mV	ΔR using precise equation $/ \Omega$	ΔR using linear approximation $/ \Omega$
480 Ω	53	-20.28	-20.70
490 Ω	26	-10.05	-10.16
510 Ω	-25	9.86	9.77
520 Ω	-52	20.73	20.31

~ see source of error in discussion behind ~

Linear approximation

when $\Delta R \ll R$, $\frac{\Delta R}{R} \approx 0$

from activity 1 : $V_{AB} = \left(\frac{-x}{4+2x} \right) V_1$ where $x = \frac{\Delta R}{R}$

If we allow the x in the denominator to $\rightarrow 0$, we can obtain a linear approximation of ΔR

* we cannot let the numerator in the equation to $\rightarrow 0$ as the equation $V_{AB} = 0 \cdot V_1$ would have no useful meaning

$$V_{AB} \approx \frac{-\frac{R}{4}}{V_1} V_1$$


$$\Delta R \approx \frac{-4V_{AB} \cdot R}{V_1}$$

$$\Delta R \approx k V_{AB}$$

$$\text{where } k = -\frac{4R}{V_1} = -\frac{4 \cdot 500 \Omega}{5.12 V} = -390.625 \Omega/V$$

~ fill in the table ~

Analysis and Observations

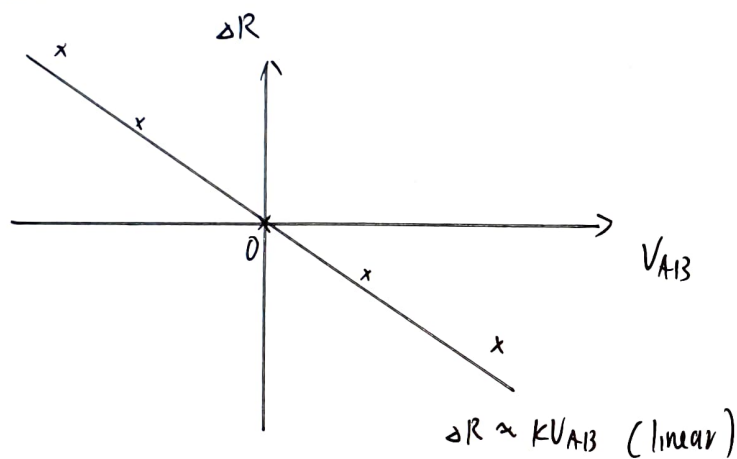

The equation from activity 1 is non linear, with values of ΔR coming away from the linear approximation as V_{AB} gets larger

comparing ΔR values obtained using the linear approx and precise equation, they follow closely for smaller values for $|V_{AB}|$ but diverge more when $|V_{AB}|$ is larger.

However, assuming we are operating in the range where ΔR is relatively small compared to R , using a linear approximation is very much appropriate

Source of error

- ① getting each variable resistor to exactly 500Ω / same value was challenging and there might be uncertainty in the reading
- ② even if the readings on the ohmmeter read 500Ω , there might be uncertainty in the equipment measurement
- ③ Initial V_{AB} for reference was not exactly 0 $\approx 1mV$ which would affect later measurements of V_{AB} when $|\Delta R|$ increases