
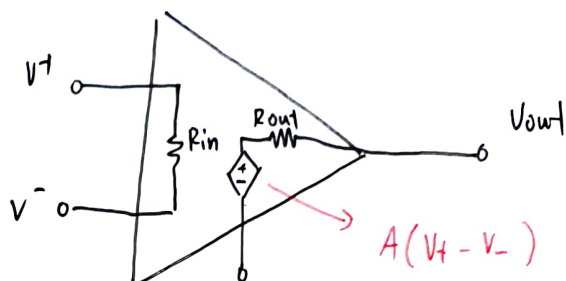
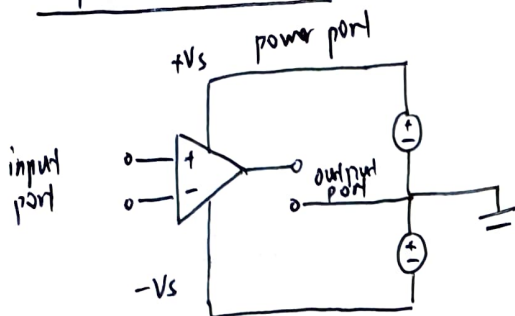


Operational Amplifier

Ideally, input resistance  $R_{in} \rightarrow \infty$   
 output resistance  $R_{out} \rightarrow 0$

$A$  (open loop voltage gain)  $\rightarrow \infty$  ( $10^5$ )

No saturation

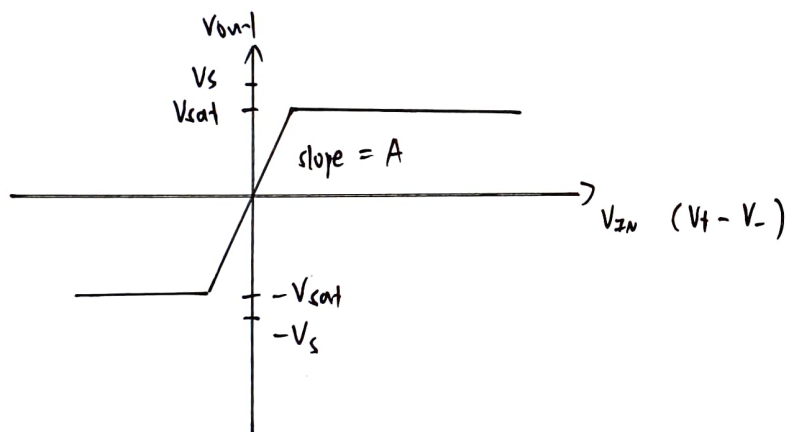



$$V_{out} = A(V_+ - V_-)$$

$V_{sat}$  is determined by the power supply voltage and is usually  $\sim 1V$  lower than  $V_s$

Op Amp Golden Rules

- ① output always tries to make voltage difference  $(V_+ - V_-)$  between the inputs 0 (negative feedback?)
- ② inputs draw no current as ideal op-amp has input resistance  $\rightarrow \infty$

## Non-Inverting Amplifier

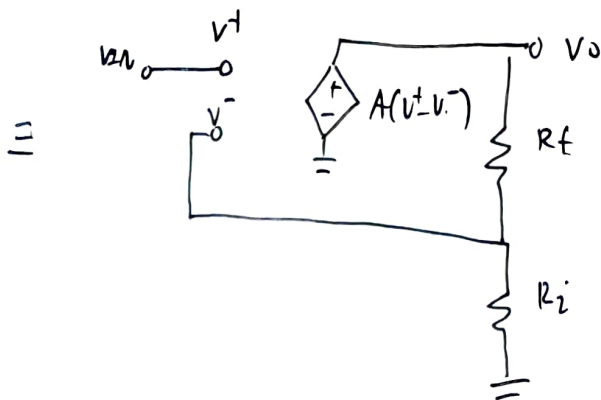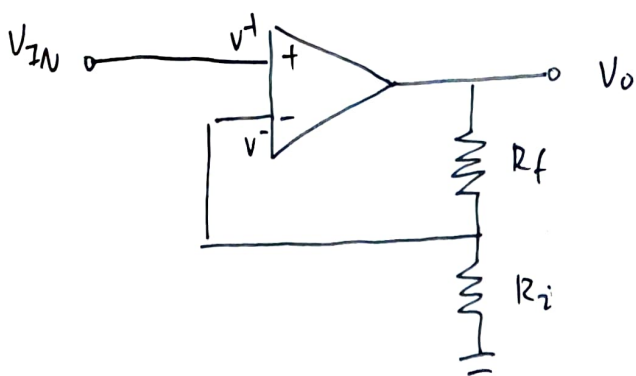

$$V_O = A(V^+ - V^-)$$

$$= A\left(V_{IN} - \frac{R_i}{R_i + R_f} V_O\right)$$

$$V_O \left(1 + \frac{AR_i}{R_i + R_f}\right) = AV_{IN}$$


$$V_O = \frac{AV_{IN}}{1 + \frac{AR_i}{R_i + R_f}}$$

$1 \ll \frac{AR_i}{R_i + R_f}$   
for large A

$$\approx \frac{AV_{IN}}{\frac{AR_i}{R_i + R_f}} \approx \frac{R_i + R_f}{R_i} V_{IN}$$

$$\approx \boxed{1 + \frac{R_f}{R_i}} V_{IN} \quad \text{gain}$$

## Negative feedback

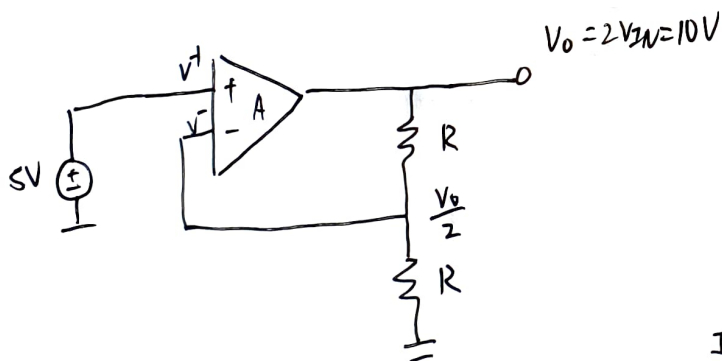

let  $R_f = R_i = R$   
and  $V_{IN} = 5V$

$$V_O = \left(1 + \frac{1}{1}\right) V_{IN} = 10V$$

If we perturb the circuit,  $\uparrow V_O$  to 12V

then  $V^- = \frac{V_O}{2} = 6V$

$$V_O = A(5 - 6) \Rightarrow \downarrow V_O$$

free to oppose  
change and  
self correct

This negative feedback is due to a portion of output being fed back into  $V^-$  input

Under negative feedback


$$V^+ - V^- = \frac{V_o}{A} = \frac{\frac{R_i + R_f}{R_i} V_{in}}{A} \rightarrow 0 \quad \text{when } A \text{ is large}$$

$$V^+ \approx V^- \quad (\text{golden rule 1})$$

$$\left. \begin{array}{l} i^+ \approx 0 \\ i^- \approx 0 \end{array} \right\} (\text{golden rule 2})$$

yields easier analysis  
method under negative feedback

Inverting Amplifier

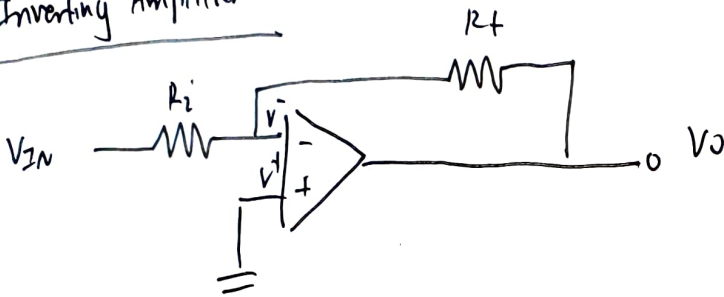

easier analysis

$$V^+ \approx V^- = 0, \quad i^+ \approx 0, \quad i^- \approx 0$$

$$\frac{V_{in} - 0}{R_i} = \frac{0 - V_o}{R_f} \Rightarrow \frac{V_o}{V_{in}} = -\frac{R_f}{R_i}$$


Impedance Model

At sinusoidal steady state

$$Z_R = R \quad (\text{constant})$$

$$Z_C = \frac{1}{j\omega C} \quad (\text{inverse})$$


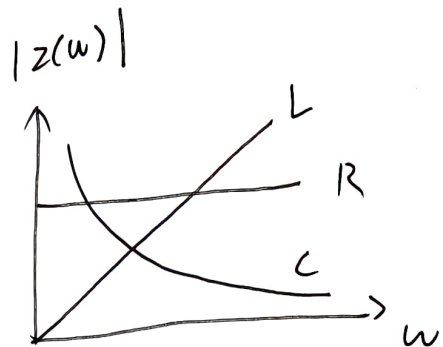
$$Z_L = j\omega L \quad (\text{linear})$$



when  $\omega = 0 \Rightarrow$  DC state


$$Z_L = 0 \quad (\text{short})$$

$$Z_C = \infty \quad (\text{open})$$

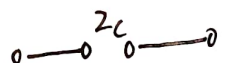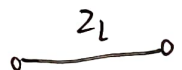

# Transfer function $H(\omega)$

take an RC circuit

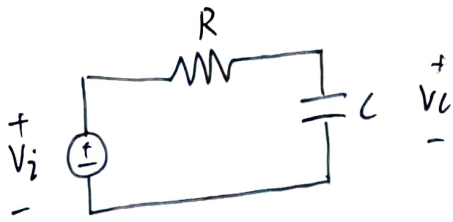

$$H(\omega) = \frac{V_C}{V_i} = \frac{1}{1 + j\omega RC}$$

$$\left| \frac{V_C}{V_i} \right| = \left| \frac{1 - j\omega RC}{1 + \omega^2 R^2 C^2} \right|$$

$$= \frac{\sqrt{1^2 + \omega^2 R^2 C^2}}{\sqrt{(1 + \omega^2 R^2 C^2)^2}}$$

$$= \frac{1}{\sqrt{1 + \omega^2 R^2 C^2}}$$

low  $\omega$ :  $\approx \frac{1}{\sqrt{1}} \approx 1$

high  $\omega$ :  $\approx \frac{1}{\omega RC}$  (inversely proportional)

$\omega = \frac{1}{RC}$ :  $\frac{1}{\sqrt{1+1}} = \frac{1}{\sqrt{2}}$  (break frequency)


By the impedance model:

$$V_C = \frac{Z_C}{Z_C + Z_R} V_i$$

$$= \frac{\frac{1}{j\omega C}}{\frac{1}{j\omega C} + R} V_i$$

$$= \frac{1}{1 + j\omega RC} V_i$$

multiply both sides by  $j\omega C$

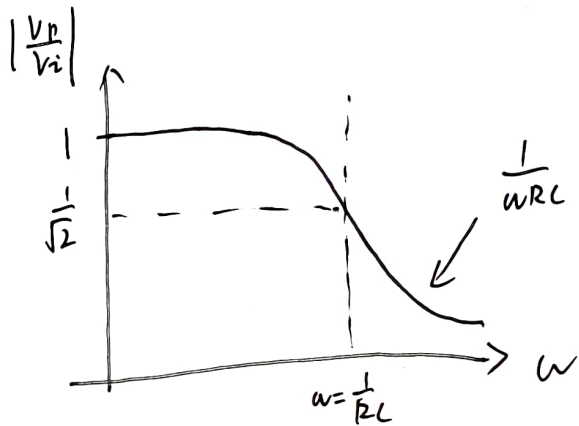

**LOW PASS FILTER**



$$\omega = 2\pi f = \frac{1}{RC}$$

$$f = \frac{1}{2\pi RC}$$

## Filters

we can build other filters by combining impedances.

$$|H(\omega)| = \left| \frac{V_R}{V_i} \right|$$

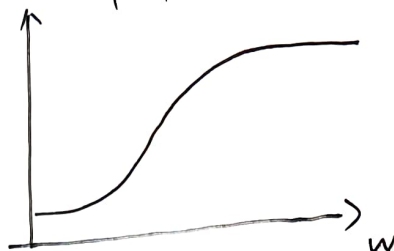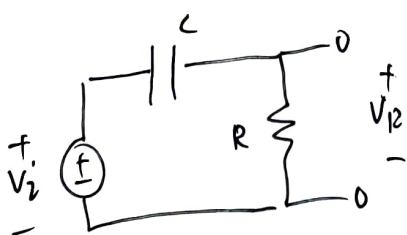

**high pass filter**

Intuitively (without equations)

low  $\omega$ : capacitor acts as open


$$\left| \frac{V_R}{V_i} \right| \approx 0$$

high  $\omega$ : capacitor acts as short

$$\left| \frac{V_R}{V_i} \right| \approx 1$$

In first order circuit, time constant is of interest  $\omega = \frac{1}{RC}$

## RLC circuit (2nd order)

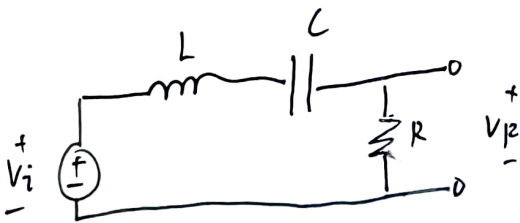

$$\frac{V_R}{V_i} = \frac{R}{j\omega L + \frac{1}{j\omega C} + R}$$


$$= \frac{j\omega C R}{1 + j\omega C R - \omega^2 L C}$$

$$\left| \frac{V_R}{V_i} \right| = \frac{\omega R C}{\sqrt{(1 - \omega^2 L C)^2 + (\omega R C)^2}}$$


low  $\omega$ :  $\approx \frac{\omega R C}{\sqrt{(1 - 0)^2 + 0^2}} \approx \omega R C$  (linear)

high  $\omega$ :  $\approx \frac{\omega R C}{\omega^2 L C} \approx \frac{R}{\omega L}$  (inversely proportional)

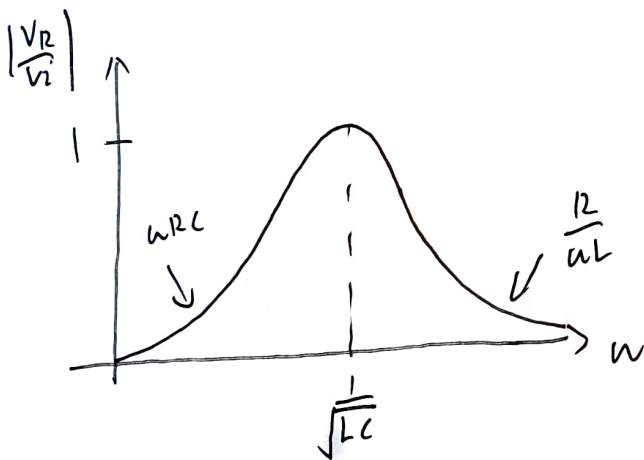$\omega = \frac{1}{\sqrt{LC}}$ :  $\frac{\omega R C}{\sqrt{(\omega R C)^2}} \approx 1$  (resonance)



Band Pass Filter

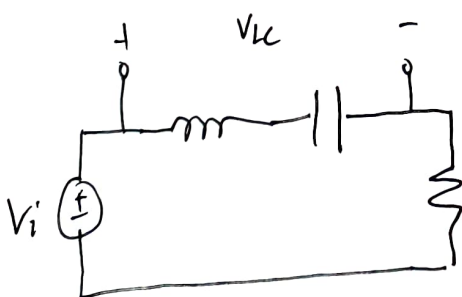

just swap terminal across L & C


### Intuitively

low  $\omega \Rightarrow$  capacitor acts as open (blocks low freq)

high  $\omega \Rightarrow$  inductor acts as open (blocks high freq)

At resonance  $\Rightarrow Z_L + Z_C \approx 0$

$V_i$  only sees  $R$ !

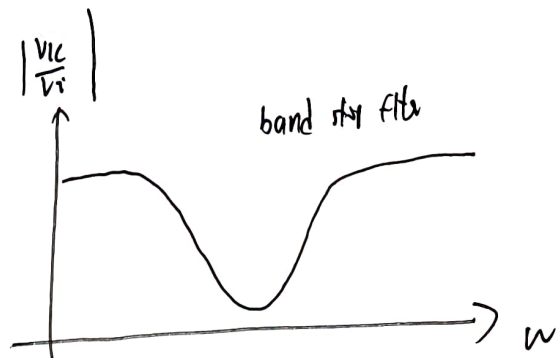

# Activity 1

1.

$V_{in}$	$V_{ref}$	$V_{out}$
+2.5V	0V	5V
+3.5V	+3.75V	0V
+1.25V	-0.5V	5V
-3V	-1V	0V
-2.5V	+2.5V	0V

For ideal comparator with no feedback resistor


$$V^+ > V^- \Rightarrow V_{CC} \text{ (ideal op-amp)}$$

$$V^+ < V^- \Rightarrow V_{EE} \text{ (ideal op-amp)}$$

since there is only a single 5V source

$$V_{CC} = 5V$$

$$V_{EE} = 0V$$

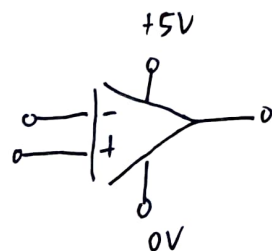

2. If a dual power supply of +5V and -5V is used the output voltage values would be
- $$\begin{cases} +5V & \text{if } V^+ > V^- \\ -5V & \text{if } V^+ < V^- \end{cases}$$

6.  $V_{ref} = \frac{R_2}{R_1 + R_2} 5V$

setting  $R_1$  to be  $1k\Omega$ ,  $1 + \frac{R_1}{R_2} = \frac{5}{1.6}$

$$R_2 \approx 470\Omega \text{ (use a variable resistor)}$$

9. A square waveform is observed as the output, when  $V_{in}$  generated from the bit scope exceeds  $V_{ref} \approx 1.6V$ , output =  $+V_{sat} \approx 3.9V$  else,  $V_{out} = -V_{sat}$  which is consistent with the behaviour of a comparator where the output is either HIGH or LOW depending on the difference between the input

10. still using  $R_1$  as a  $1k\Omega$  resistor

when  $V_{ref} = 0.7V \Rightarrow R_2 \approx 160\Omega$

when  $V_{ref} = 2.5V \Rightarrow R_2 \approx 1000\Omega$



11. When  $V_{ref}$  is small, the time when  $V_{in} > V_{ref}$  is much longer  
 when  $V_{ref}$  is closer to the 3.3V peak to peak voltage of  $V_{in}$ , the time  
 when  $V_{in} > V_{ref}$  is much shorter  
 The output is similar to pulse width modulation

## Activity 2

1. derive the voltage gain  $\left(\frac{V_{out}}{V_{in}}\right)$  equation

By applying the op-amp golden rules  $\Rightarrow V^+ \approx V^-$   
 or analysis method under negative feedback and input draws no current

$$\frac{0 - V^+}{1000} = 0 + \frac{V^+ - V_{out}}{1000}$$

$$\frac{V_{out}}{1000} = \frac{2V^+}{1000} \Rightarrow \frac{V_{out}}{V^+} = \boxed{2} \rightarrow \text{gain with current resistance value,}$$


9.

Frequency (Hz)	$V_{in}$ (V)	$V_{out}$ (V)	Gain $\left(\frac{V_{out}}{V_{in}}\right)$	Gain mdB
200	1.60	3.23	2.02	6.11
500	1.60	3.21	2.01	6.06
1000	1.60	3.09	1.93	5.71
1500	1.60	2.93	1.86	5.39
2000	1.60	2.82	1.76	4.91
3000	1.60	2.49	1.56	3.86
5000	1.60	1.88	1.18	1.44
10000	1.60	1.09	0.68	-3.35
20000	1.60	0.58	0.36	-8.87
50000	1.60	0.25	0.16	-15.92

10. plot gain in dB vs frequency

11. cut-off frequency when  $\frac{V_{out}}{V_{in}} = \frac{1}{\sqrt{2}}$  maximum gain = -3dB from initial gain  
 is somewhere between 3000 to 5000 Hz  
 From the excel plot, the cut off frequency is around 4000Hz.

12.

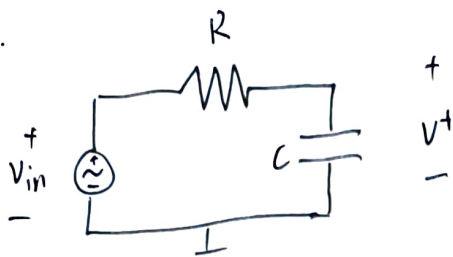

from 1.)  $V_{out} = 2V^+$

By impedance model:

$$V^+ = \frac{Z_C}{Z_C + Z_R} V_{in}$$

$$= \frac{\frac{1}{j\omega C}}{\frac{1}{j\omega C} + R} V_{in}$$

$$\frac{V^+}{V_{in}} = \frac{1}{1 + Rj\omega C}$$

$$\left| \frac{V^+}{V_{in}} \right| = \left| \frac{1(1 - j\omega RC)}{(1 + j\omega RC)(1 - j\omega RC)} \right|$$

$$= \left| \frac{1 - j\omega RC}{1 + \omega^2 R^2 C^2} \right|$$

$$= \sqrt{\left( \frac{1}{1 + \omega^2 R^2 C^2} \right)^2 + \left( \frac{-\omega RC}{1 + \omega^2 R^2 C^2} \right)^2}$$

$$= \sqrt{\frac{1 + \omega^2 R^2 C^2}{(1 + \omega^2 R^2 C^2)^2}} = \frac{1}{\sqrt{1 + \omega^2 R^2 C^2}}$$

$$\left| \frac{V_{out}}{V_{in}} \right| = 2 \left| \frac{V^+}{V_{in}} \right| = \frac{2}{\sqrt{1 + \omega^2 R^2 C^2}}$$

low  $\omega$ :  $\approx \frac{2}{\sqrt{1+0}} \approx 2$


high  $\omega$ :  $\approx \frac{2}{\sqrt{\omega^2 R^2 C^2}} \approx \frac{2}{\omega RC}$

when  $\omega = \frac{1}{RC}$ :  $\frac{2}{\sqrt{1+1}} = \frac{1}{\sqrt{2}} \cdot 2$  (cut off point)

$$\omega_c = 2\pi f_c \Rightarrow f_c = \frac{1}{2\pi RC}$$

comparing with the theoretical value obtained using  $f_c = \frac{1}{2\pi RC} = 4080\text{Hz}$ ,  
 the cut off frequency from the excel plot of around 4000Hz, the 2 values agree strongly.

$$a+bi \Rightarrow r = \sqrt{a^2+b^2}$$

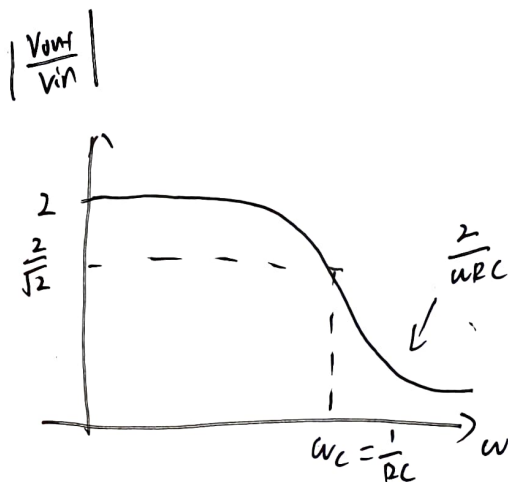




$$13. \quad 2000 = \frac{1}{2\pi R C}$$

$$C = \frac{1}{2\pi (2000) (390\Omega)}$$

$$= 204 \text{ pF}$$

challenge

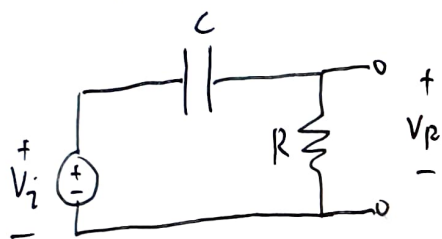2. Design a high pass filter with an RC circuit



$$\frac{V_R}{V_i} = \frac{R}{R + \frac{1}{j\omega C}}$$

$$= \frac{j\omega RC}{j\omega RC + 1}$$

$$\left| \frac{V_R}{V_i} \right| = \left| \frac{(j\omega R)(1 - j\omega RC)}{1 + \omega^2 R^2 C^2} \right|$$

$$= \left| \frac{\omega^2 R^2 C^2 + j\omega RC}{1 + \omega^2 R^2 C^2} \right|$$


$$= \sqrt{\frac{(\omega^2 R^2 C^2)^2 + \omega^2 R^2 C^2}{(1 + \omega^2 R^2 C^2)^2}}$$

$$= \sqrt{\frac{\omega^2 R^2 C^2}{1 + \omega^2 R^2 C^2}}$$


$$\text{low } \omega: \approx \sqrt{\frac{0}{1+0}} \approx 0$$

$$\text{high } \omega: \approx \sqrt{\frac{\omega^2 R^2 C^2}{\omega^2 R^2 C^2}} \approx 1$$
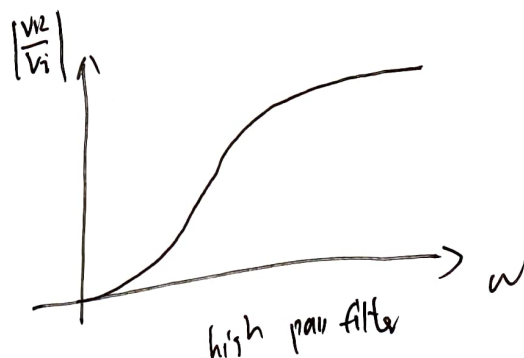
$$\omega = \frac{1}{RC} : \approx \sqrt{\frac{1}{1+1}} = \frac{1}{\sqrt{2}} \text{ (cut-off)}$$



# FUNCTION GENERATOR

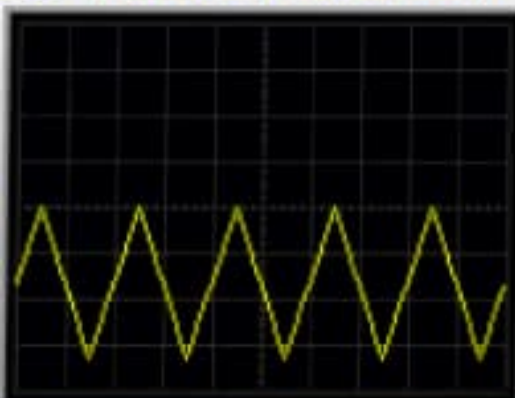


RAMP	ENABLED
1 kHz	50 %
3.3 V	0 V
2.5 ms	3.273 V
TRIGGER	1.575 mV
2.5 ms	3.271 V
400 Hz	1.31 mV/us

POST ZOOM

AUTO FOCUS

500 us/Div

REPEAT TRACE

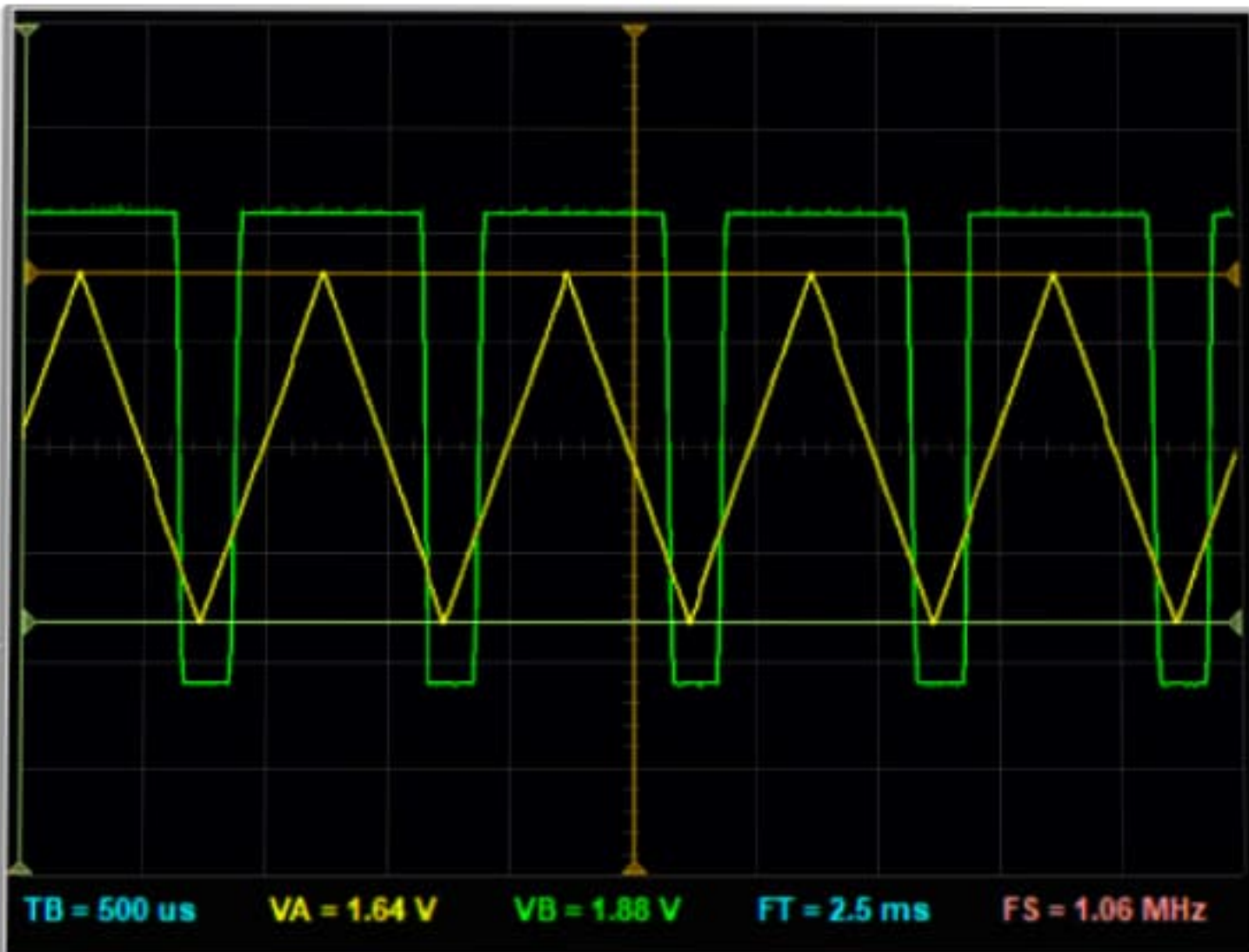

CHA PRB

9.2 V 1.64 V

1 V/Div

ON ZERO

CHB PRB

9.2 V -537.4 mV

2 V/Div

ON ZERO


OSCILLOSCOPE

10 mS 1.14 MHz

NORMAL SMOOTH

RECORDER WIDE BAND

# FUNCTION GENERATOR

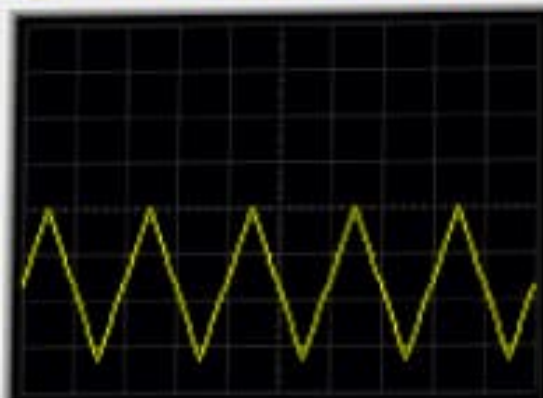


RAMP	ENABLED
1 kHz	50 %
3.3 V	0 V
2.5 ms	3.27 V
TRIGGER	-1.683 mV
2.5 ms	3.272 V
400 Hz	1.31 mV/us

POST ZOOM

AUTO FOCUS

500 us/Div

REPEAT TRACE

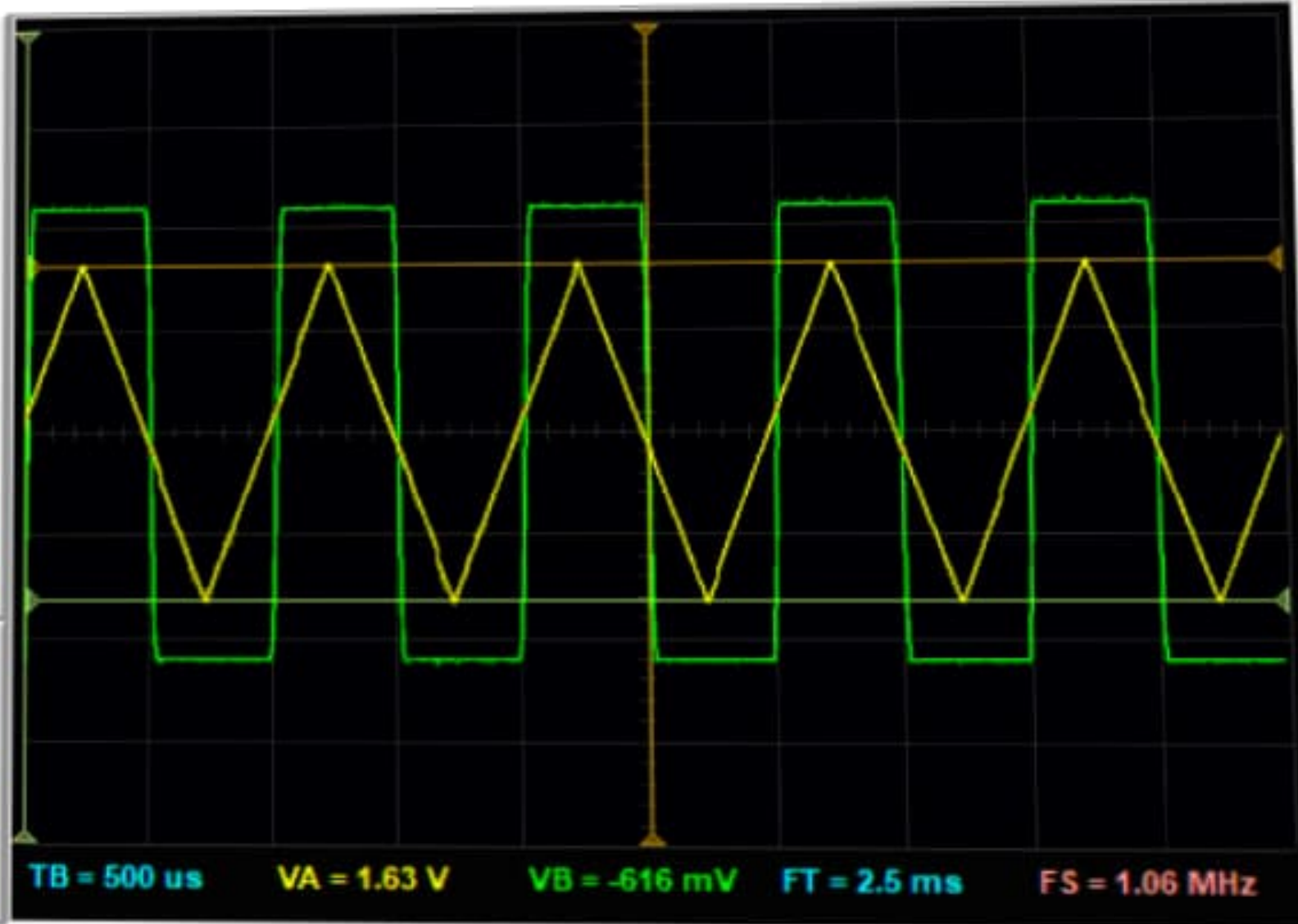

CHA PRB

9.2 V 1.63 V

1 V/Div

ON ZERO

CHB PRB

9.2 V -541.7 mV

2 V/Div

ON ZERO

OSCILLOSCOPE


10 mS 1.14 MHz

NORMAL SMOOTH

RECORDER WIDE BAND



## FUNCTION GENERATOR

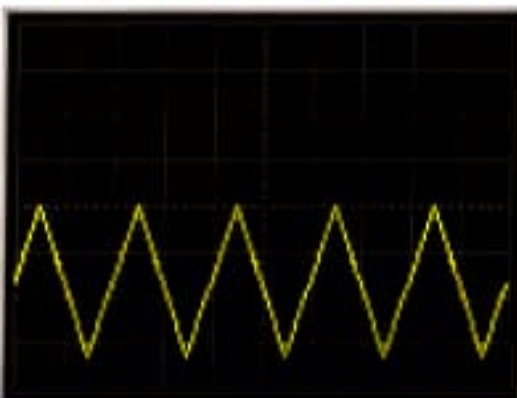

RAMP

ENABLED

1 kHz

50 %

3.3 V

0 V

2.5 ms

3.28 V

TRIGGER


-8.371 mV

2.5 ms

3.288 V

400 Hz

1.32 mV/us

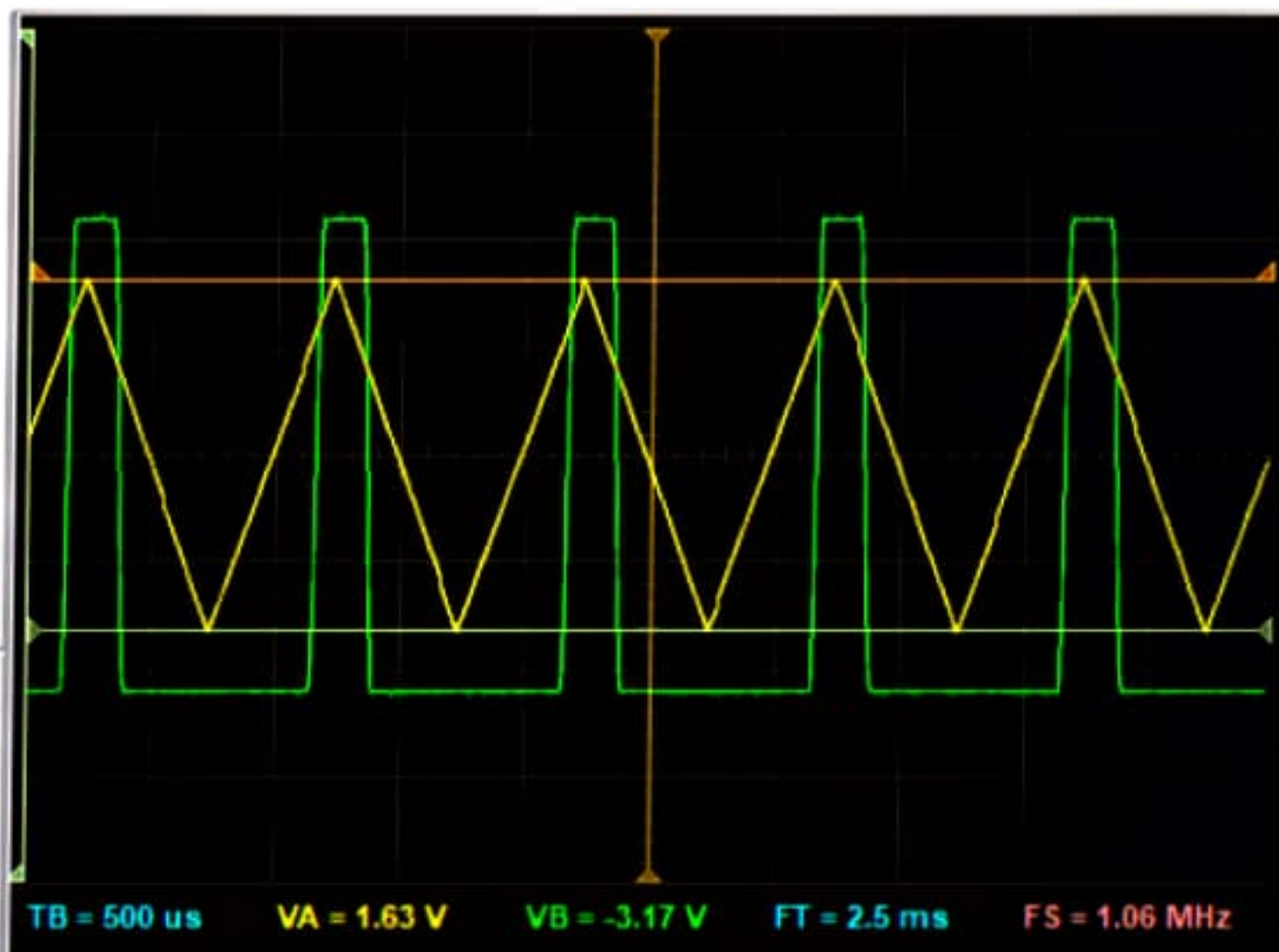

TB = 500 us

VA = 1.63 V

VB = -3.17 V

FT = 2.5 ms

FS = 1.06 MHz

POWER

SETUP

SCOPE

DUAL

MIXED

LOGIC

MACRO

CURSOR

GRID

SAVE

WAVE

POST

ZOOM

AUTO FOCUS

500 us/Div

REPEAT

TRACE

CHA

PRB

9.2 V

1.63 V

1 V/Div

ON

ZERO

CHB

PRB

9.2 V

-542.2 mV

2 V/Div

ON

ZERO

OSCILLOSCOPE

10 mS

1.14 MHz

NORMAL

SMOOTH

RECORDER

WIDE BAND

Gain in Db

6.11

6.06

5.71

5.39

4.91

3.86

1.44

-3.35

-8.87

-15.92

