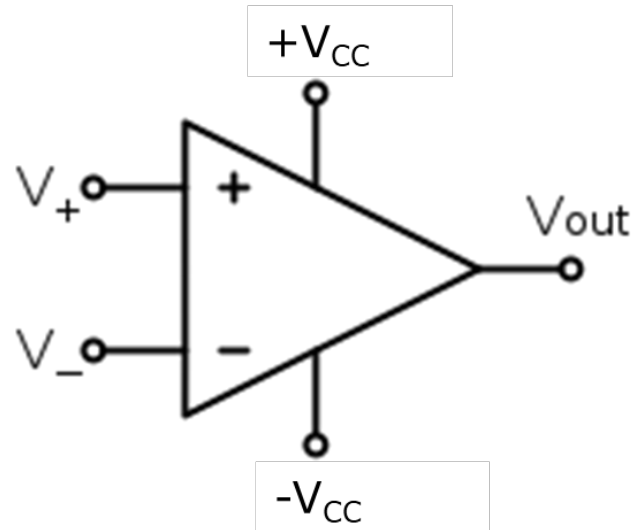


CG1111: Engineering Principles and Practice I

Debrief and Tutorial for Week 9



Comparator




- The comparator is an electronic **decision-making** circuit that makes use of an op-amp's very high gain in its **open-loop state** (i.e., there is no feedback resistor)

Op-Amp as a Comparator

– How It Works

Recall that for op-amp:

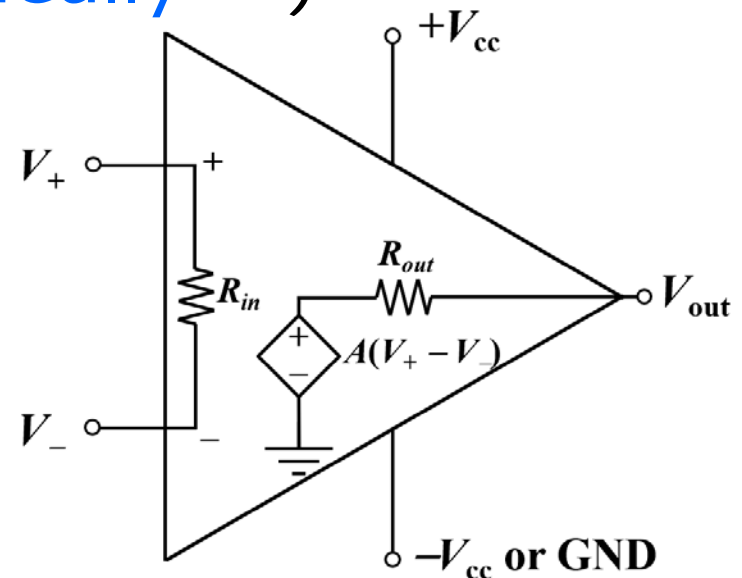- The difference between the two inputs is amplified as ' $A(V_+ - V_-)$ ' at the output
- The **open-loop** voltage gain ('A') of the op-amp is very high (**ideally ∞**)
- Even if there is a very small difference between the inputs, the high 'A' will pull the output to "**saturation**"



Op-Amp as a Comparator


– How It Works

- If $V_+ > V_-$:

$$V_{\text{out}} = +V_{\text{sat}}$$


- If $V_- > V_+$:
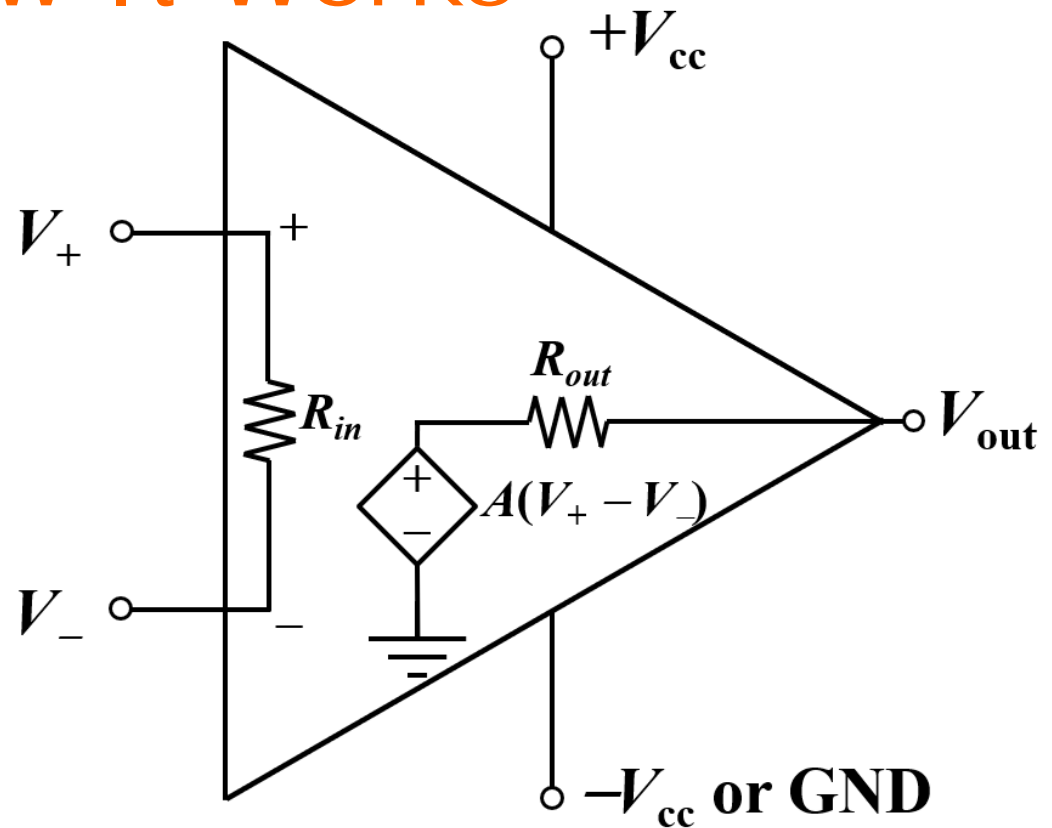
$$V_{\text{out}} = \begin{cases} -V_{\text{sat}} & \text{if dual power supply} \\ 0 & \text{if single power supply} \end{cases}$$



Common Application of Comparator

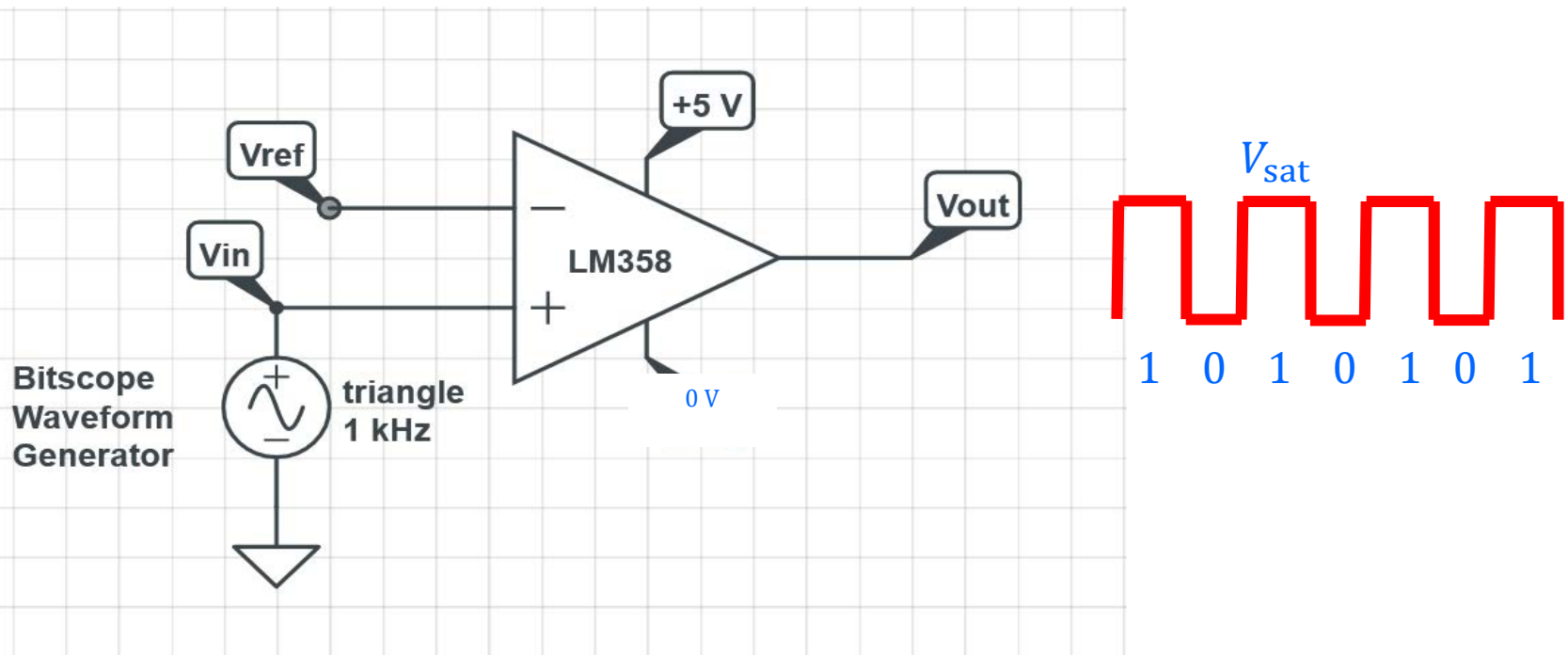- The comparator is ideal for converting analog signals to **digital signals** at certain threshold values




Filter

- A filter is a device or process that removes some unwanted components or features from a signal
- Examples:
 - Removing the noise from measured ECG signal using a filter to help a doctor understand the heart better




- Removing some frequencies or frequency bands from an audio signal

Passive Low-Pass Filter

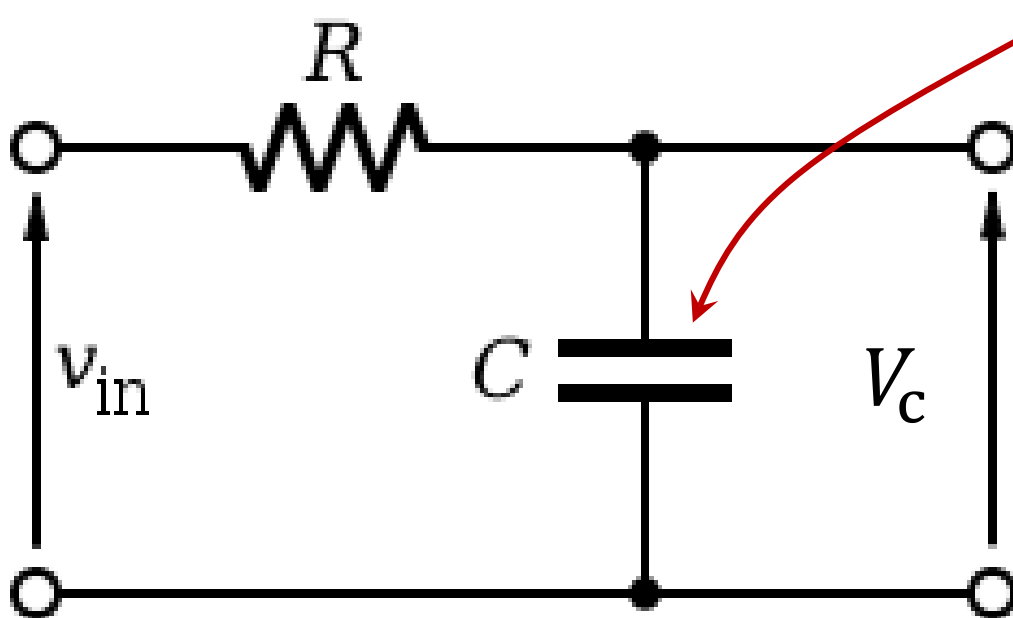

Voltage divider:
The capacitor's impedance decreases as the frequency increases, hence V_c decreases

Gain $\frac{V_c}{V_{in}}$ in dB

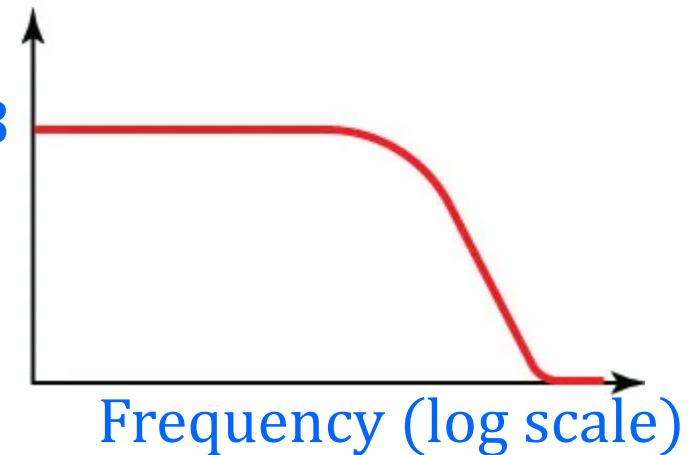

Power Gain in decibels (dB)

- The **Voltage Amplification (A_v)** or **Gain** of a voltage amplifier/filter is given by:

$$A_v = \frac{V_{\text{out}}}{V_{\text{in}}}$$

- The voltage gain is commonly expressed in terms of the resulting **power gain** in **dB**:

$$\begin{aligned}\text{Power Gain (dB)} &= 10 \log_{10} \left(\frac{V_{\text{out}}}{V_{\text{in}}} \right)^2 \text{ dB} \\ &= 20 \log_{10} \left| \frac{V_{\text{out}}}{V_{\text{in}}} \right| \text{ dB}\end{aligned}$$

Frequency Response

- It is the quantitative measure of the output spectrum of a system or device in response to a stimulus, and is used to characterize the dynamics of the system
 - Frequency in logarithmic Scale: horizontal x-axis




- Power Gain in decibels (dB): vertical y-axis
 - To describe a change in output power over the whole frequency range

$$\text{Power Gain in dB } (f) = 20 \log_{10} |A_v(f)|$$

Cut-off Frequency

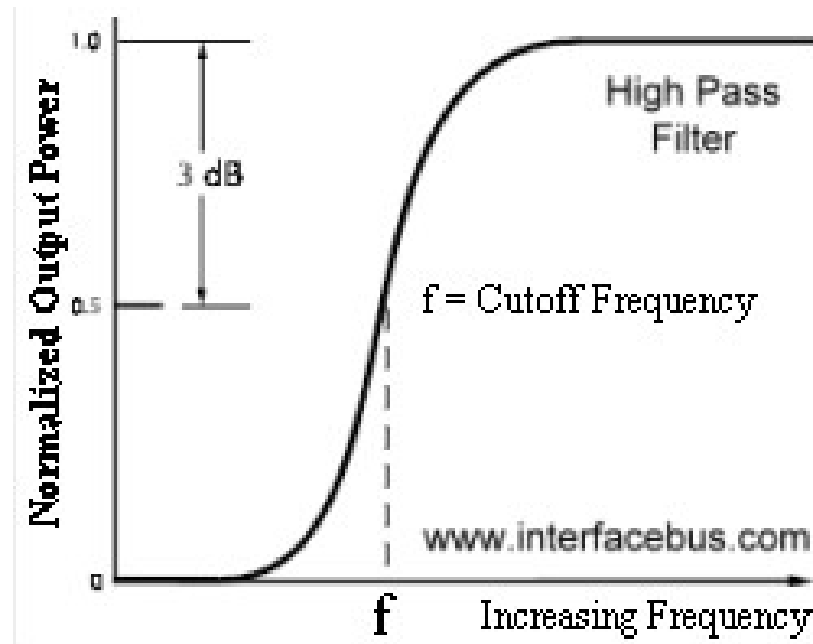
- In filters, the cut-off frequency characterizes a **boundary** between a **passband** and a **stopband**
- The cut-off frequency is taken as the frequency at which the output of the circuit is **-3 dB** (corresponding to **half the power**) of the nominal passband value



Cut-off Frequency: -3 dB Point (i.e., Half-power Point)

■ Graphical approach:

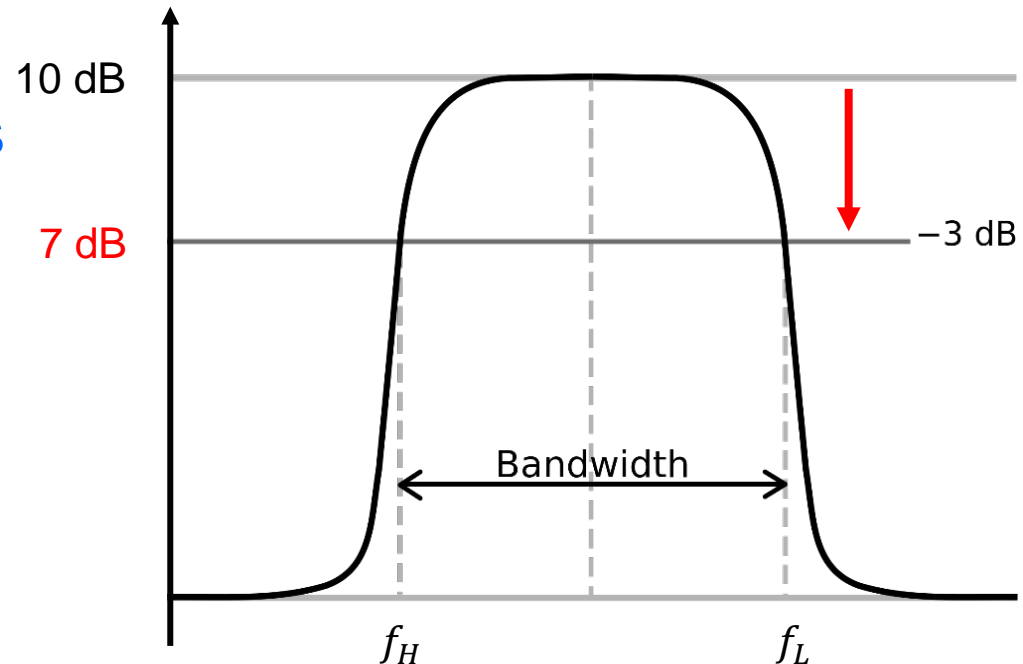- Find the passband gain from the magnitude vs frequency plot
- Subtract 3 dB from the passband gain and draw a line on the plot
- The points where this line cuts the plot corresponds to the cut-off frequency(s)




Cut-off Frequency: -3 dB Point (i.e., Half-power Point)

- Quantitative approach
(for first-order filters):

$$f_H = \frac{1}{2\pi R_H C_H}, \quad f_L = \frac{1}{2\pi R_L C_L}$$

First-order Low-Pass Filter


- Slope after cut-off frequency
 $\approx -20 \text{ dB/decade}$

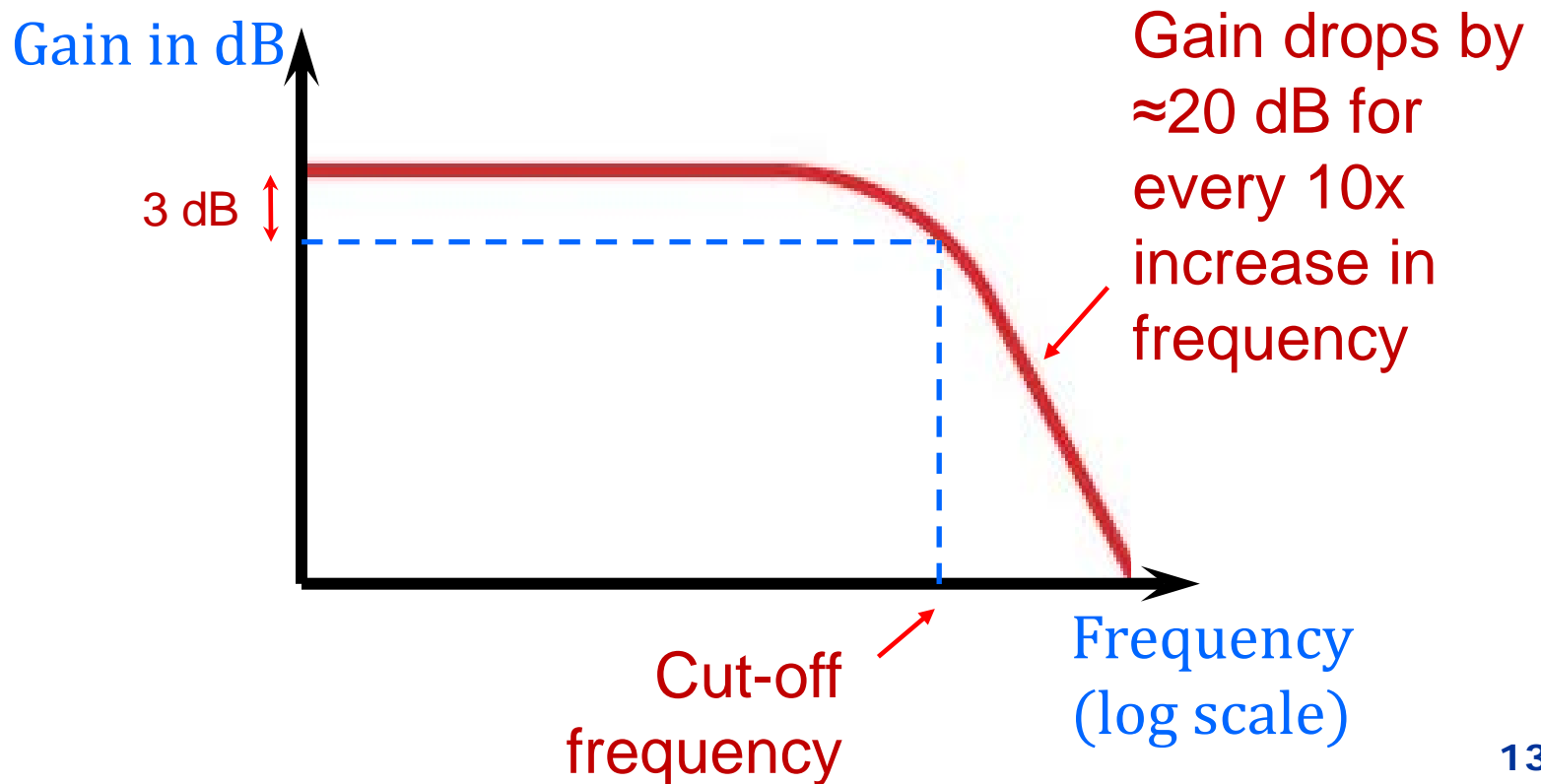

Question 1

Show that if $R_{in} = R_L$, then the power gain in dB for an amplifier circuit is given by

$$\text{Power gain (dB)} = 20 \log_{10} \left| \frac{V_{out}}{V_{in}} \right| \text{ dB}$$

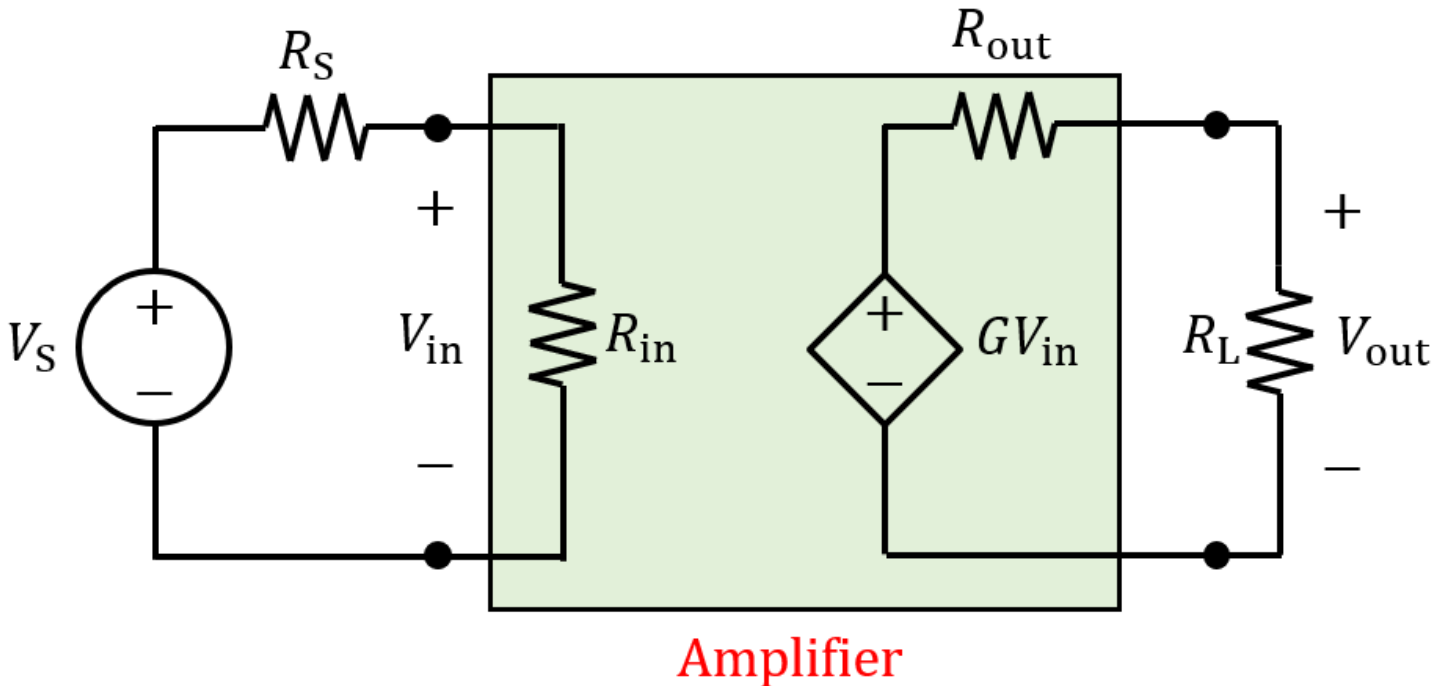


Solution to Q1

- Power at amplifier's input: $P_{\text{in}} = \frac{V_{\text{in}}^2}{R_{\text{in}}}$
- Power delivered to load: $P_{\text{out}} = \frac{V_{\text{out}}^2}{R_L}$
- Power Gain in dB

$$\begin{aligned} &= 10 \log_{10} \left(\frac{P_{\text{out}}}{P_{\text{in}}} \right) \\ &= 10 \log_{10} \left(\frac{V_{\text{out}}}{V_{\text{in}}} \right)^2 + \underbrace{10 \log_{10} \left(\frac{R_{\text{in}}}{R_L} \right)}_{\substack{\text{Equals 0 if} \\ R_{\text{in}} = R_L}} \\ &= 20 \log_{10} \left| \frac{V_{\text{out}}}{V_{\text{in}}} \right| \end{aligned}$$

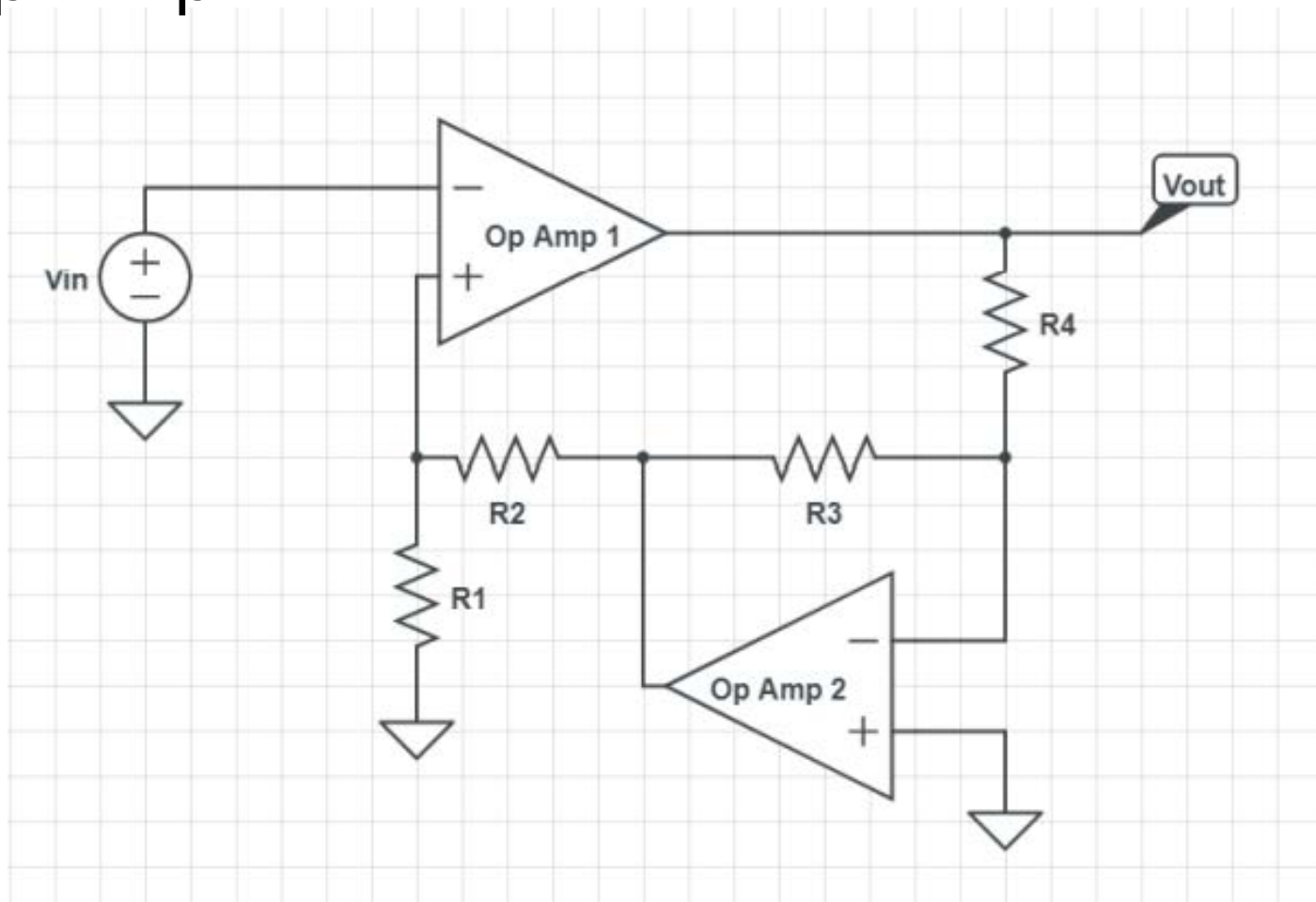
Question 2

- Calculate the voltage gain (V_{out}/V_{in}) of Op Amp 1



Solution to Q2

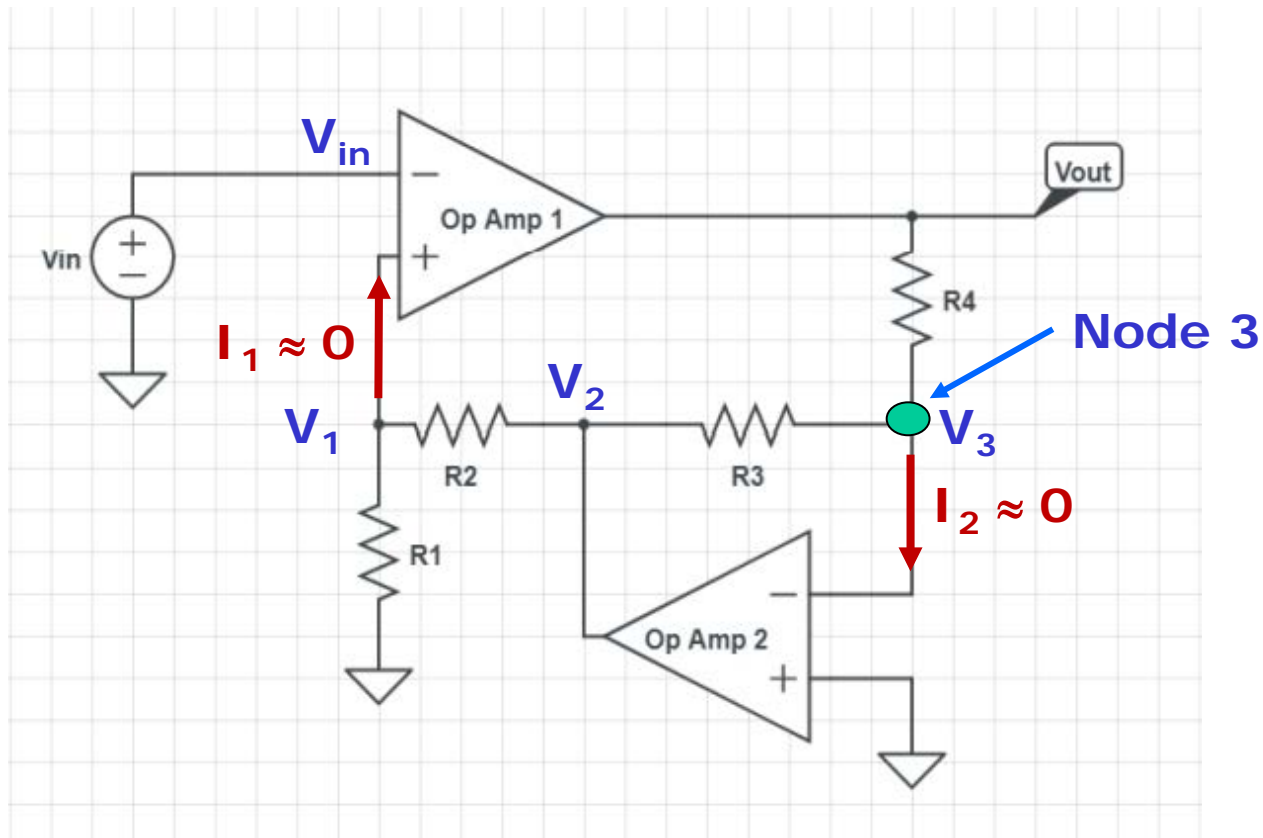- Using op amp Golden rules,
 - For Op amp 1, $V_+ = V_- = V_{in}$. Hence, $V_1 = V_{in}$
 - For Op amp 2, $V_- = V_+ = 0$. Hence, $V_3 = 0$



Solution to Q2

- Current through R_1 (downwards)

$$I_{R1} = \frac{V_{\text{in}}}{R_1}$$

- Current through R_2 (right to left)

$$I_{R2} = I_{R1} = \frac{V_{\text{in}}}{R_1}$$

$$V_2 = V_1 + (I_{R2} \times R_2)$$

$$= V_{\text{in}} + \frac{V_{\text{in}}}{R_1} \times R_2 = \left(1 + \frac{R_2}{R_1}\right) \times V_{\text{in}}$$

$$\rightarrow V_2 = \left(1 + \frac{R_2}{R_1}\right) \times V_{\text{in}} \text{ -----} > \text{Equation 1}$$

Solution to Q2

Applying KCL at Node 3,

$$\frac{V_2 - 0}{R_3} + \frac{V_{\text{out}} - 0}{R_4} = 0$$


Applying expression for V_2 from Equation 1,

$$\left(1 + \frac{R_2}{R_1}\right) \times \frac{V_{\text{in}}}{R_3} = \frac{-V_{\text{out}}}{R_4}$$

$$\frac{V_{\text{out}}}{V_{\text{in}}} = - \left(1 + \frac{R_2}{R_1}\right) \times \frac{R_4}{R_3}$$

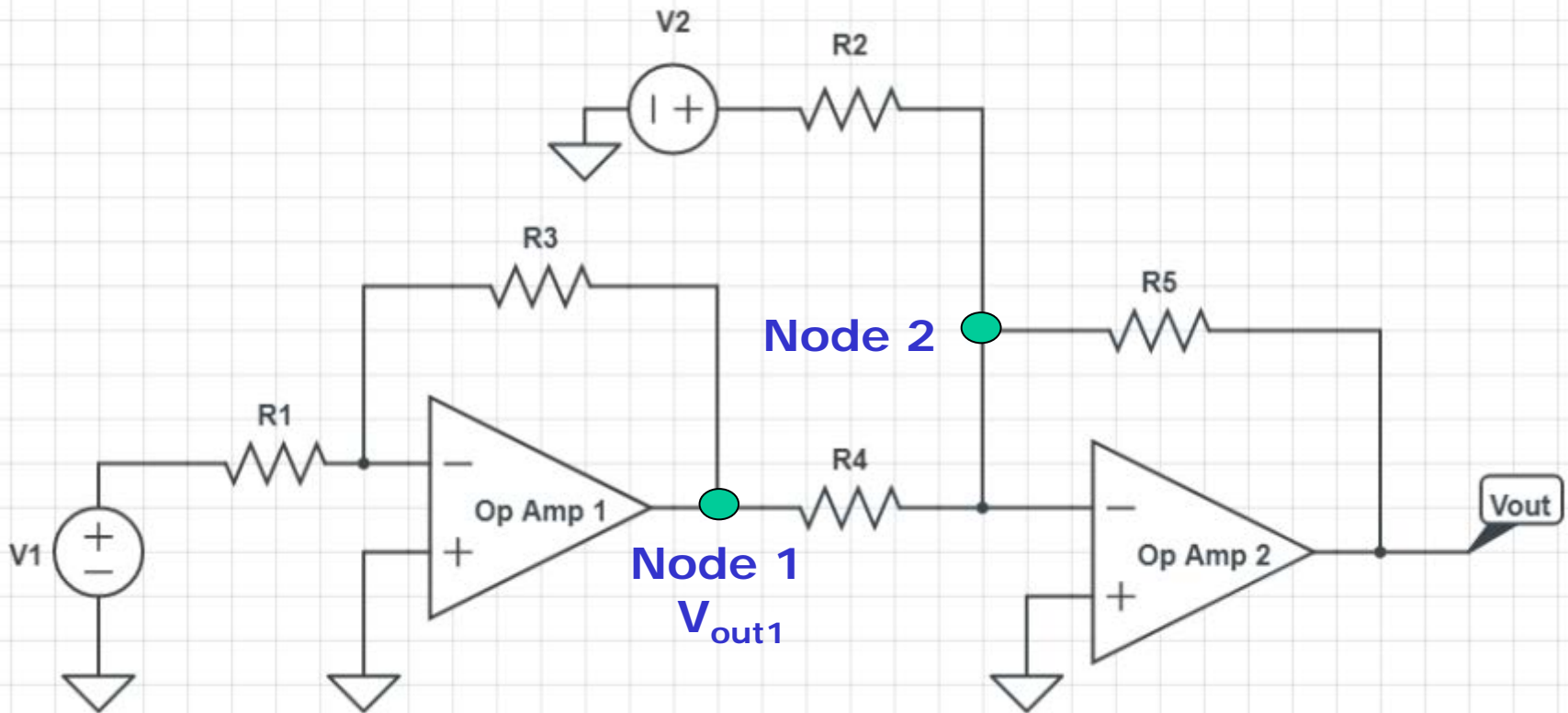Question 3

- Derive the expression relating V_{out} and the two inputs, V_1 and V_2
- Design R values such that $V_{out} \propto (V_1 - V_2)$



Solution to Q3

- For both op amps, $V_- = V_+ = 0$
(op amp golden rules)

$$\frac{V_1 - 0}{R_1} + \frac{V_{\text{out1}} - 0}{R_3} = 0 \rightarrow V_{\text{out1}} = -\frac{R_3}{R_1} V_1$$

Applying KCL at Node 2,

$$\frac{V_2 - 0}{R_2} + \frac{V_{\text{out1}} - 0}{R_4} + \frac{V_{\text{out}} - 0}{R_5} = 0$$

$$V_{\text{out}} = \left(\frac{R_5}{R_4} * \frac{R_3}{R_1} * V_1 \right) - \left(\frac{R_5}{R_2} * V_2 \right)$$

Solution to Q3

If $\frac{R_5 R_3}{R_4 R_1} = \frac{R_5}{R_2}$, which gives $\frac{R_3}{R_4 R_1} = \frac{1}{R_2}$, then

$$V_{\text{out}} = \frac{R_5}{R_2} (V_1 - V_2)$$

$$= K (V_1 - V_2)$$

Question 4

- Audio song frequencies: 100-3000 Hz
- Corrupted with 10 kHz noise
- Design a low-pass filter to suppress the 10 kHz noise by 20 dB relative to the passband gain
- What is the cut-off frequency of the low-pass filter?

A Note About –20 dB in Power

- Suppressing the noise by 20 dB is equivalent to reducing its **power** to just **1%** compared to no filtering
- Also equivalent to reducing its **voltage** to just **10%** compared to no filtering

- $10 \log_{10} \left(\frac{P_{\text{noise(filtered)}}}{P_{\text{noise(no filter)}}} \right) = 10 \log_{10}(0.01) = -20 \text{ dB}$

- $20 \log_{10} \left(\frac{V_{\text{noise(filtered)}}}{V_{\text{noise(no filter)}}} \right) = 20 \log_{10}(0.1) = -20 \text{ dB}$

Solution to Q4


Suppose we take an active low-pass filtering approach (i.e., filtering noise + amplifying entire signal)

Blue:

Active gain
(= 2) due to
non-inverting
amplifier

Red:

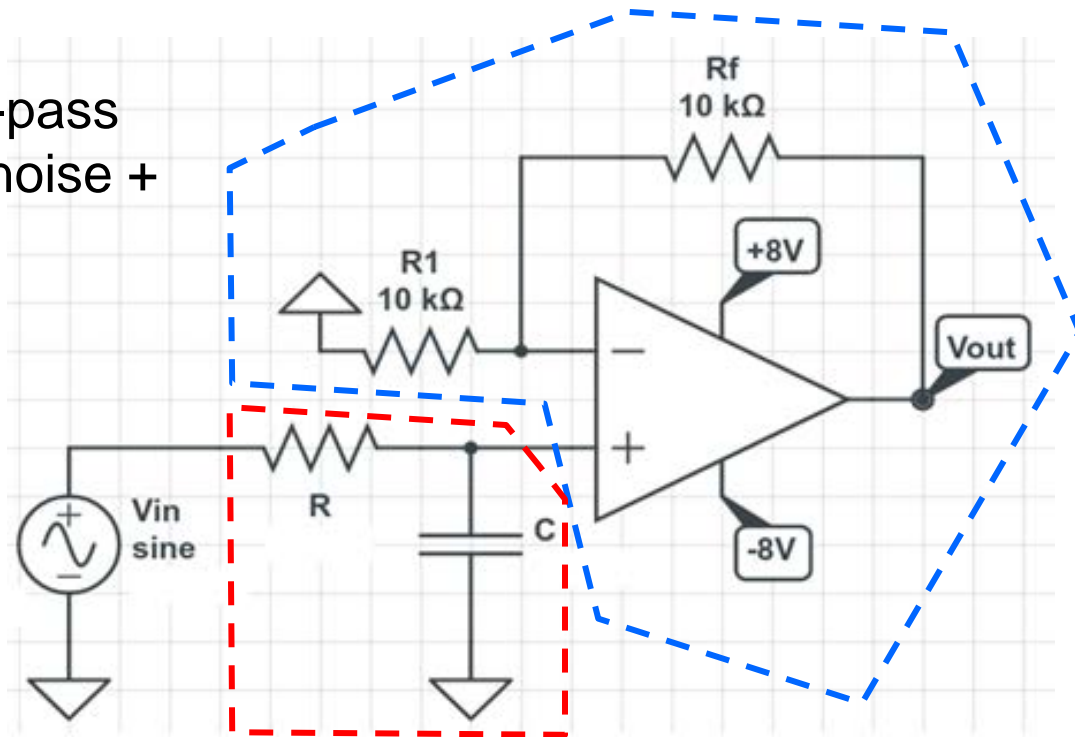Passive filter's
gain (< 1) due
to RC potential
divider
(ω -dependent)



$$\frac{V_{\text{out}}}{V_{\text{in}}} = \frac{V_{\text{out}}}{V_{+}} \times \frac{V_{+}}{V_{\text{in}}} = \left(1 + \frac{R_f}{R_1}\right) \frac{V_{+}}{V_{\text{in}}} = 2 \left[\frac{\frac{1}{j\omega C}}{\frac{1}{j\omega C} + R} \right] = \frac{2}{1 + j\omega CR}$$

Hence, gain's magnitude w.r.t. $\omega = \left| \frac{V_{\text{out}}}{V_{\text{in}}} \right| = \frac{2}{\sqrt{1 + (\omega CR)^2}}$

Solution to Q4

$$\text{Gain in dB} = \overbrace{20 \log_{10} 2}^{\text{Passband gain}} - \overbrace{20 \log_{10} \sqrt{1 + (\omega CR)^2}}^{\text{Change in gain with } \omega}$$

A gain reduction of 20 dB at $f = 10$ kHz means:

$$\left. -20 \log_{10} \sqrt{1 + (\omega CR)^2} \right|_{f = 10 \text{ kHz}} = -20 \text{ dB}$$

Hence, $\sqrt{1 + (\omega CR)^2} = 10$ when $f = 10$ kHz

Our low-pass filter needs to have:

$$RC = \frac{\sqrt{10^2 - 1}}{2\pi \times 10000} = 1.584 \times 10^{-4} \text{ s}$$

Solution to Q4

- Cutoff frequency is the frequency at which the gain decreases by 3 dB from passband gain
- A gain reduction of 3 dB at $f = f_c$ means:
$$-20 \log_{10} \sqrt{1 + (\omega CR)^2} \Big|_{f = f_c} = -3 \text{ dB}$$
- Hence, $\sqrt{1 + (\omega CR)^2} = 10^{3/20} = \sqrt{2}$ when $f = f_c$


$$\omega CR = 1 \text{ when } f = f_c$$

$$f_c = \frac{1}{2\pi RC} = \frac{1}{2\pi \times 1.584 \times 10^{-4}} \approx 1 \text{ kHz}$$

Graphical Visualization for Q4

- First-order low-pass filter: -20 dB/decade
- Each horizontal box is "1 decade" ↗

DC gain ↗

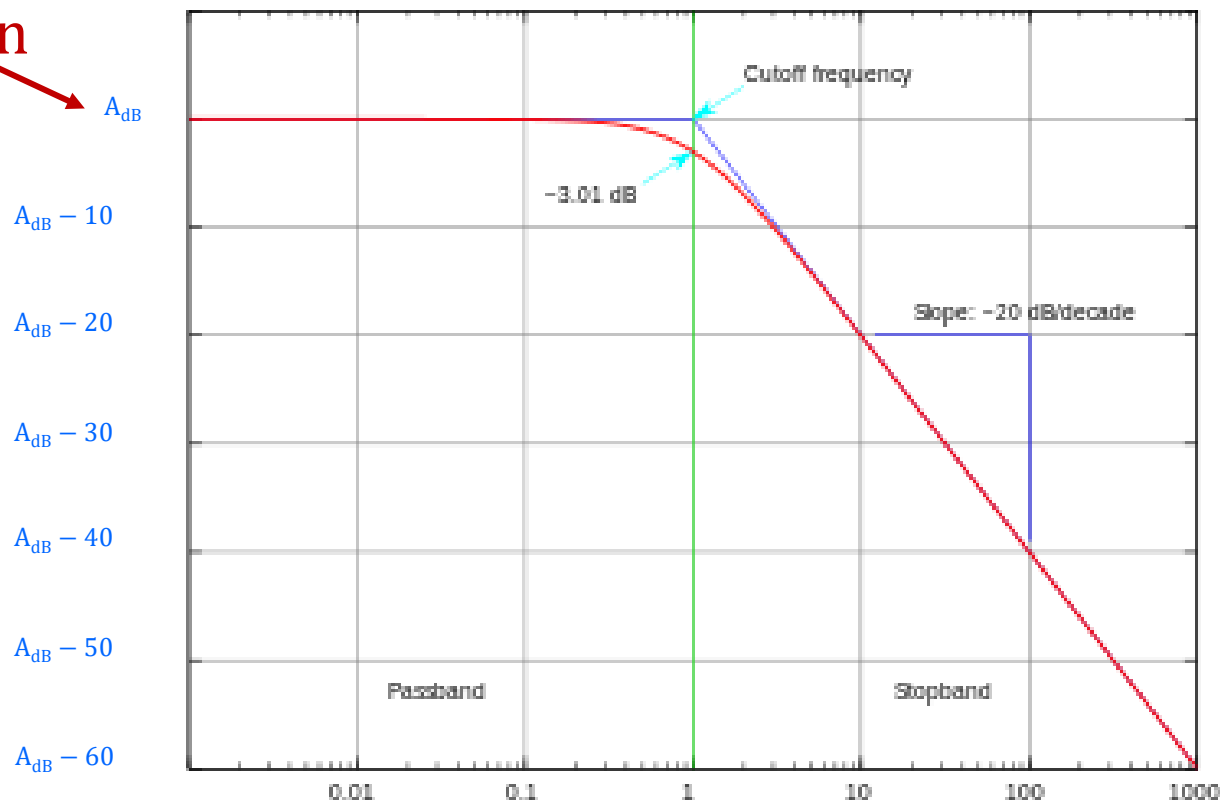


i.e.,
frequency
changes by
10 times

Frequency

Why -20 dB/decade?


f	$-20 \log_{10} \sqrt{1 + (\omega CR)^2}$
f_c	≈ -3 dB
$10 \times f_c$	≈ -20 dB
$100 \times f_c$	≈ -40 dB
$1000 \times f_c$	≈ -60 dB

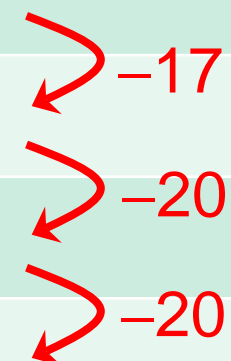

Graphical Visualization for Q4


- We need to reduce the **gain at 10 kHz** by 20 dB (always relative to passband gain)

DC gain

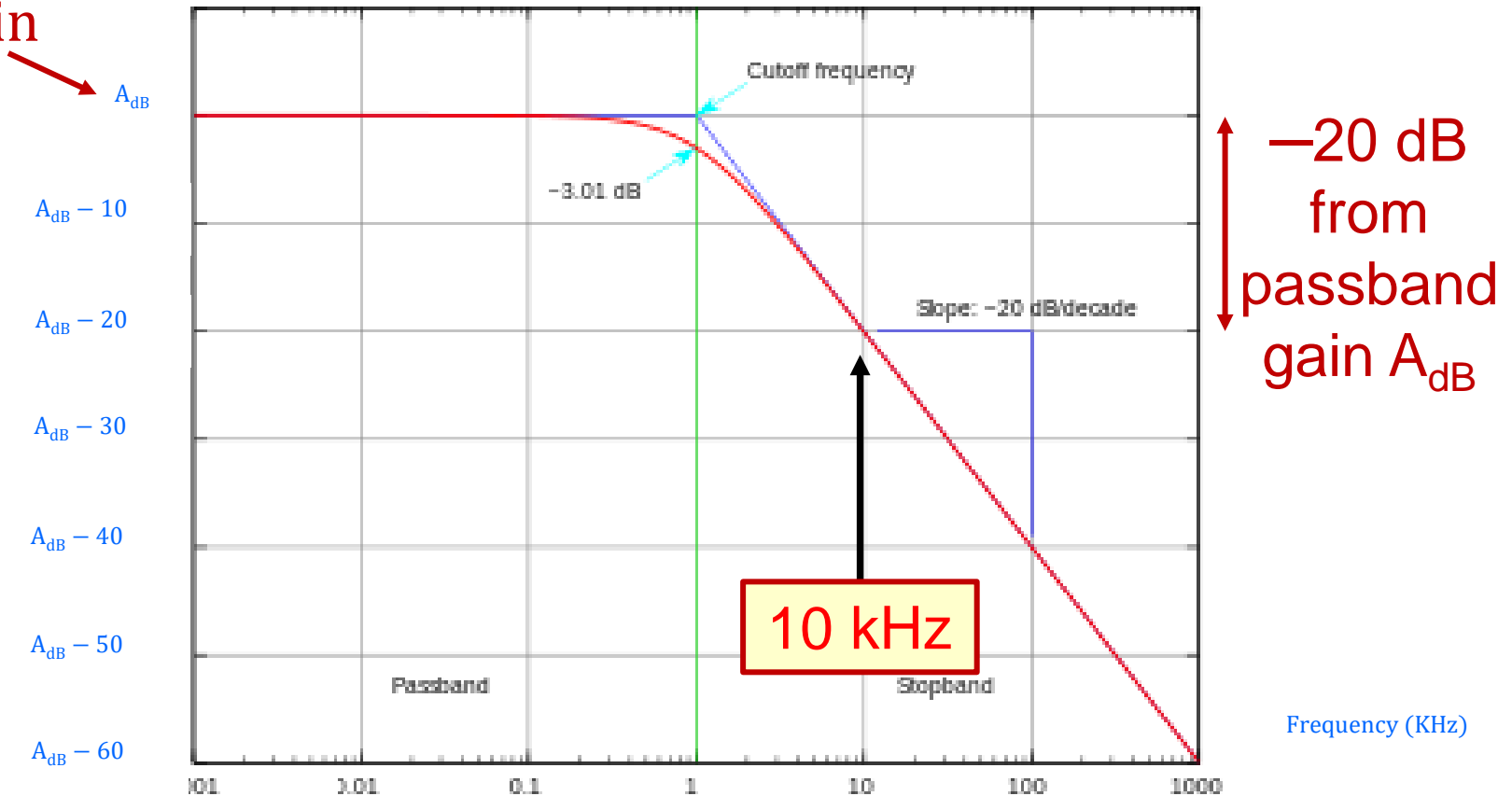

Graphical Visualization for Q4

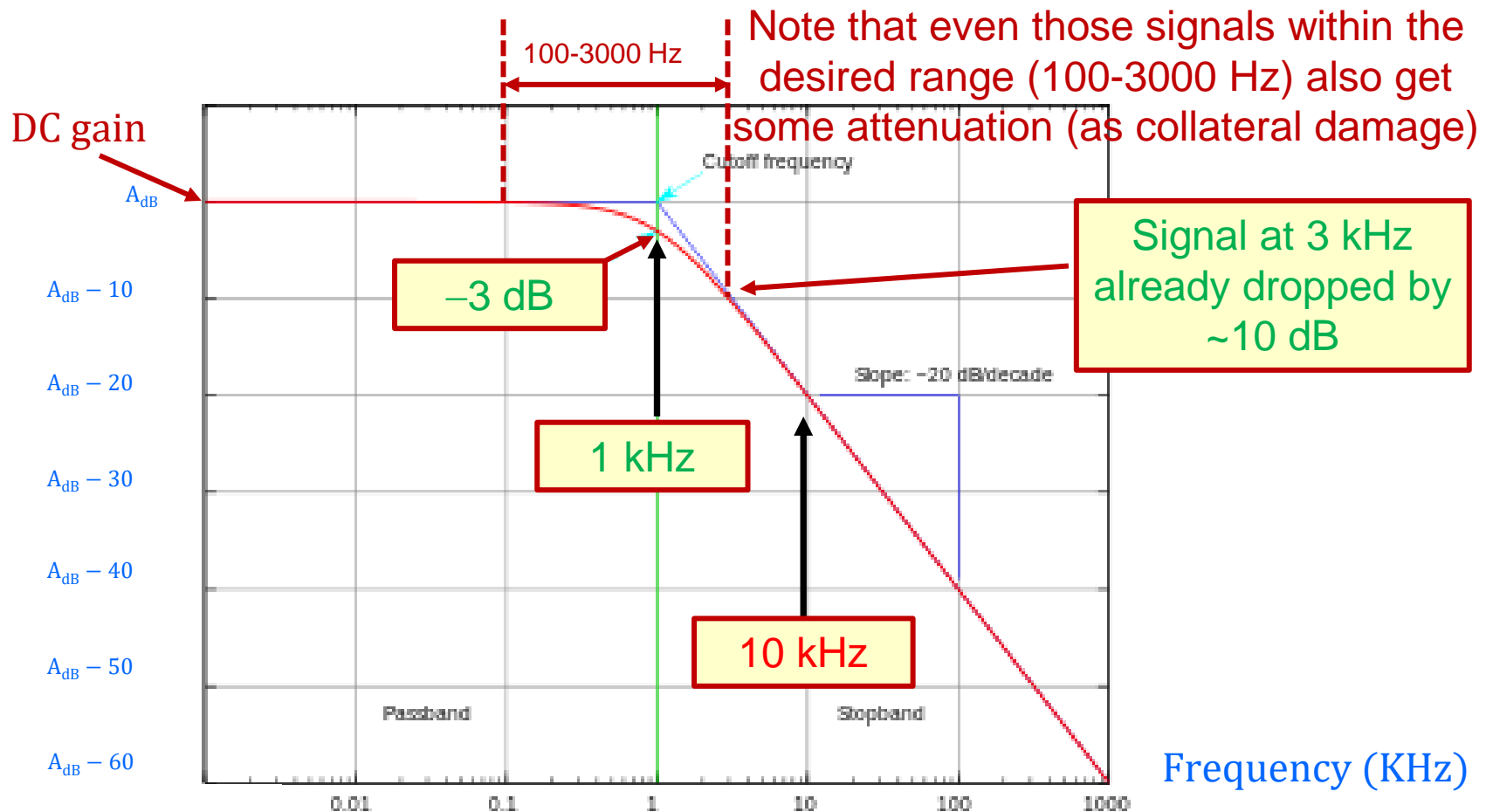- If 10 kHz noise has to be reduced by 20 dB, we need to have the cutoff frequency at **1 kHz**



Extra Points to Note for Q4

For your curiosity only:

As can be seen, with a first-order filter, we also **lose some audio signals** that we desire. How do we improve this?

We can use **higher-order** filters! This allows us to have sharper attenuation slope, so that our desired passband is not attenuated too much!

- **2nd** order: **40 dB/decade**
 - <http://www.electronics-tutorials.ws/filter/second-order-filters.html>
- **3rd** order: **60 dB/decade**
 - <http://www.circuitstoday.com/higher-order-filters>

