

CG1111: Engineering Principles and Practice I


Debrief and Tutorial for Week 11
(Filters and Signal Processing Basics)



Spectral Analysis


- Any function of time can be described as a **sum of sine waves**, each with **different amplitudes and frequencies**
- **Spectral analysis** investigates the distribution of a signal's **frequency components**
- The plot of a signal's **frequency components** and their corresponding **magnitudes** is called "**frequency spectrum**"

Example of Frequency Spectrum

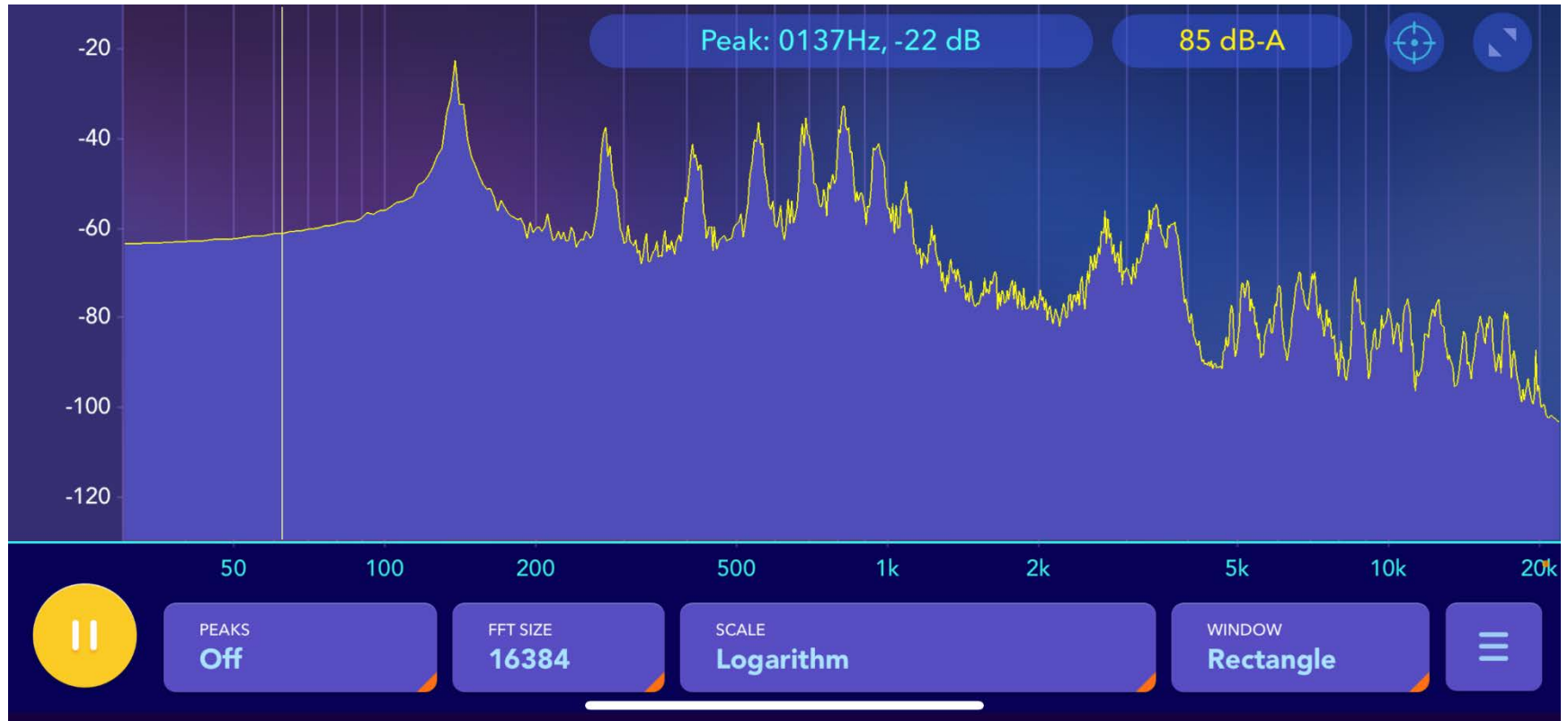


The frequency spectrum of a particular audio tone

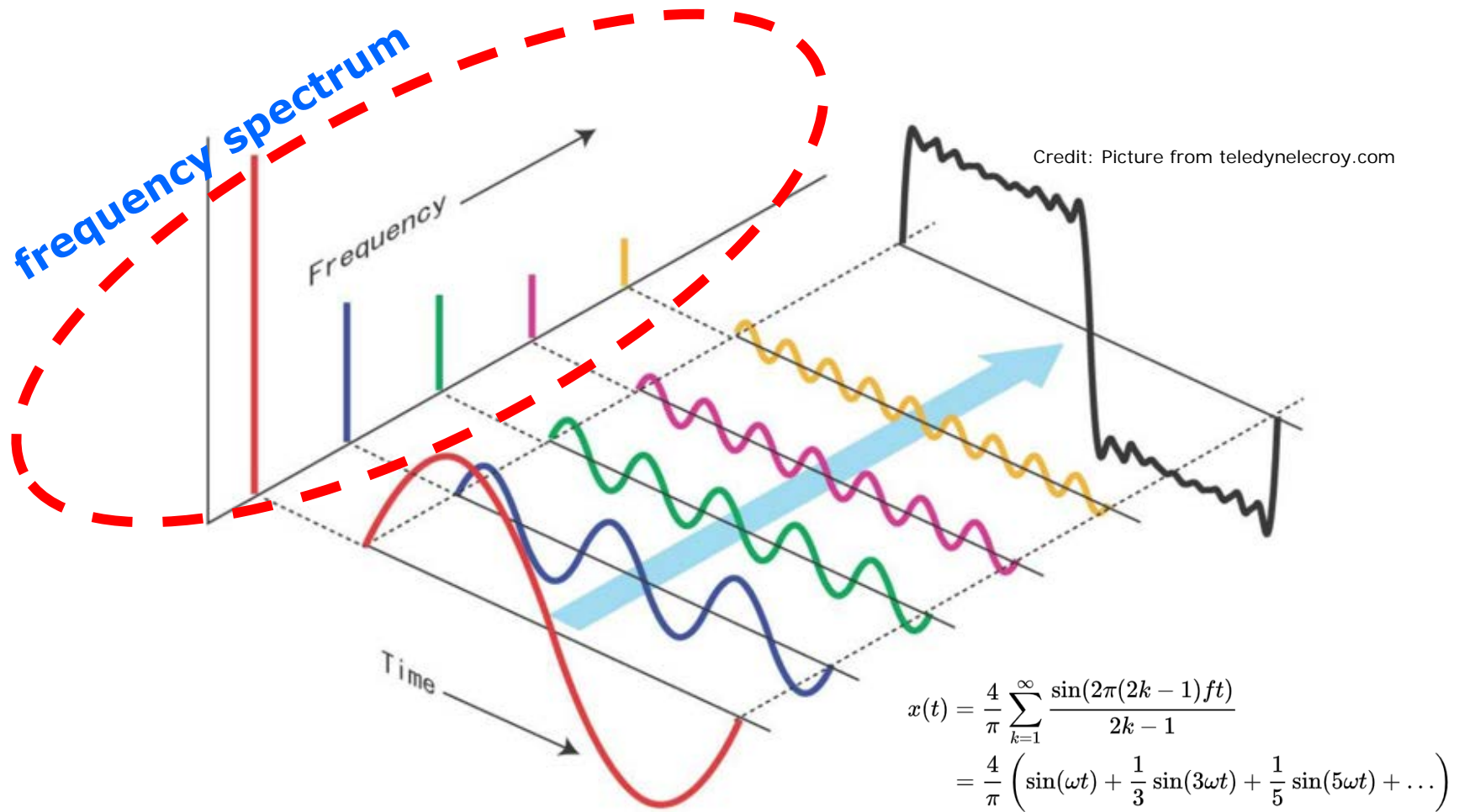Oscilloscope Can Help Us Perform Spectral Analysis



- A square wave (triangular waveform too) can be decomposed into an infinite sum of sinusoidal waves

Filters Can Help Suppress (Attenuate) Undesirable Frequencies

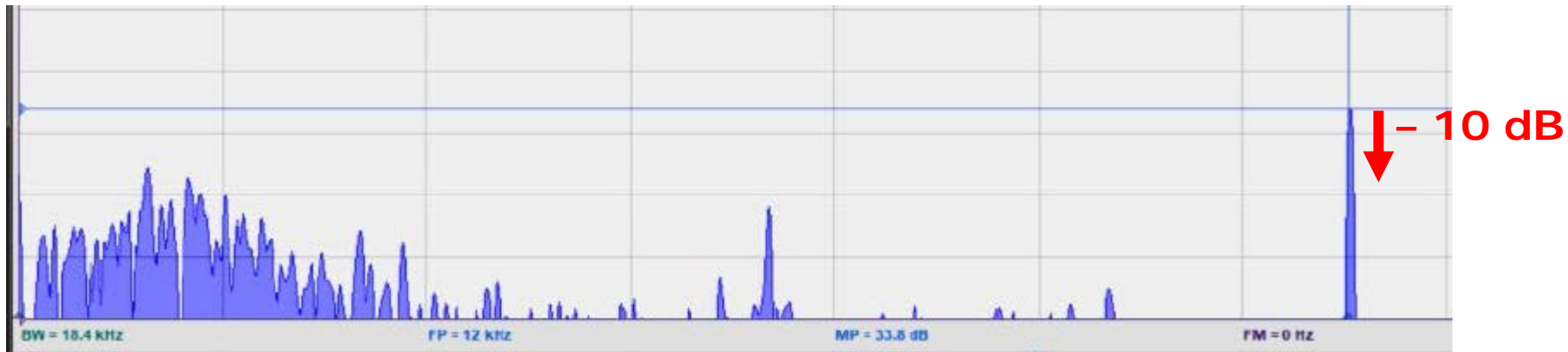

Question 1

- An audio song from a CD is passed through a low-pass filter with cut-off frequency of 4000 Hz to obtain the signal $Y(t)$.
- What is the minimum sampling rate that we can use to sample $Y(t)$ without degrading its quality significantly?

Solution to Q1

- The audio spectrum ranges from 20 Hz to 20 kHz
- After applying low-pass filter with 4 kHz cut-off frequency, the frequencies beyond 4 kHz are attenuated considerably (they are now less than 50% of their original power)
- The **minimum** sampling rate is **8 kHz** (although it is still better to sample at higher frequencies, e.g., 16 kHz, to minimize **aliasing effects**)

Aliasing can still occur from the attenuated frequencies, creating random noise which might fall within the desired 20 Hz - 4 kHz range

Question 2

A microphone is recording an audio song with a frequency range of the 5th octave.

The song is corrupted by a 12 kHz noise.

This recording needs to be sampled by an Arduino Uno for controlling the loudness of the speaker connected to the audio system.


Solution to Q2a

- a) Design an analog low-pass filter to suppress the **12 kHz noise** by at least **15 dB**

Since it is **not mentioned** if the filter has to be **active** or **passive**, we can design either one. The design for the RC circuit will be the same.

The active filter (e.g., using an additional non-inverting amplifier) will have an additional gain factor associated with it.


Let us design a **passive filter**

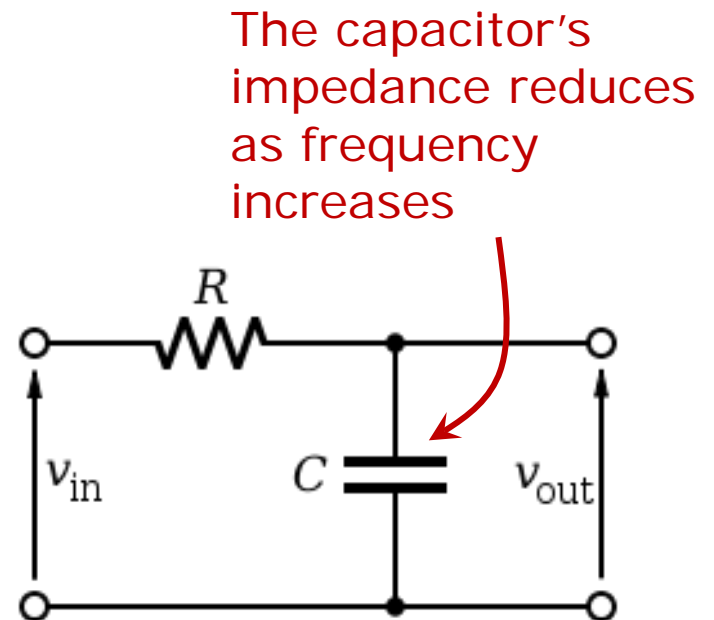

Solution to Q2a

- Here V_{out} = Voltage across the capacitor
- We can use the **voltage divider rule** to find the **voltage gain**
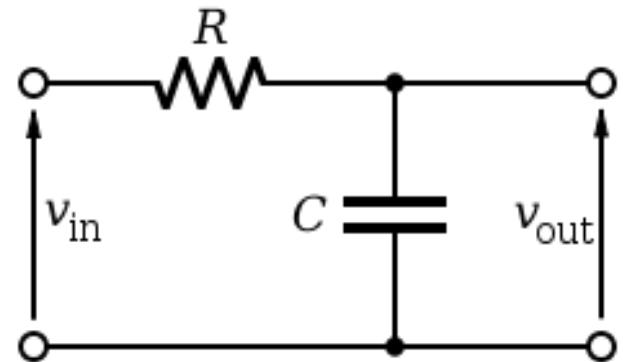
$$\rightarrow V_{\text{out}} = \left[\frac{\frac{1}{j\omega C}}{\frac{1}{j\omega C} + R} \right] V_{\text{in}}$$



$$\rightarrow \frac{V_{\text{out}}}{V_{\text{in}}} = \left[\frac{\frac{1}{j\omega C}}{\frac{1}{j\omega C} + R} \right] = \left[\frac{1}{1 + jR\omega C} \right] = \frac{1 \angle 0^\circ}{\sqrt{1^2 + (R\omega C)^2} \angle \theta^\circ}$$

$$\rightarrow \left| \frac{V_{\text{out}}}{V_{\text{in}}} \right| = \left[\frac{1}{\sqrt{1 + (R\omega C)^2}} \right] = \underbrace{20 \log_{10} 1}_{\text{Passband gain}} - \underbrace{20 \log_{10} \sqrt{1 + (R\omega C)^2}}_{\text{Change in gain with } \omega} \text{ dB}$$

Magnitude

Passband gain
(= 0 dB)

Change in gain with ω
(we want -15 dB at 12 kHz) 10

Solution to Q2a

A gain reduction of 15 dB at $f=12$ kHz means:

$$\left. -20 \log_{10} \sqrt{1 + (\omega CR)^2} \right|_{f = 12 \text{ kHz}} = -15 \text{ dB}$$

Hence, $\sqrt{1 + (\omega CR)^2} = 10^{15/20}$ when $f = 12$ kHz

Our low-pass filter needs to have:

$$RC = \frac{\sqrt{10^{(15/20)^2} - 1}}{2\pi \times 12000} = 73.4 \text{ } \mu\text{s}$$

If we choose $C = 10$ nF, we get $R = 7.34$ k Ω

Solution to Q2b

b) What is the **minimum sampling rate** required for processing the audio song?

- 5th Octave: 523 Hz to 987 Hz (C5 to B5)
(not required to remember)
- The **maximum frequency** in this octave is **987 Hz**
- ➔ The **minimum sampling frequency** will be $2 \times 987 \text{ Hz} = \mathbf{1974 \text{ Hz}}$

Solution to Q2c

c) If we need to design a digital low-pass filter to suppress the 12 kHz noise (instead of an analog low-pass filter), what is the minimum sampling rate required?


If the low-pass filter is digital, we need to consider that the maximum frequency in the signal is 12 kHz

→ The minimum sampling frequency will be
 $2 \times 12 \text{ kHz} = 24 \text{ kHz}$

(Otherwise the noise will have aliasing after sampling, and end up as some other frequencies which may be difficult to suppress)

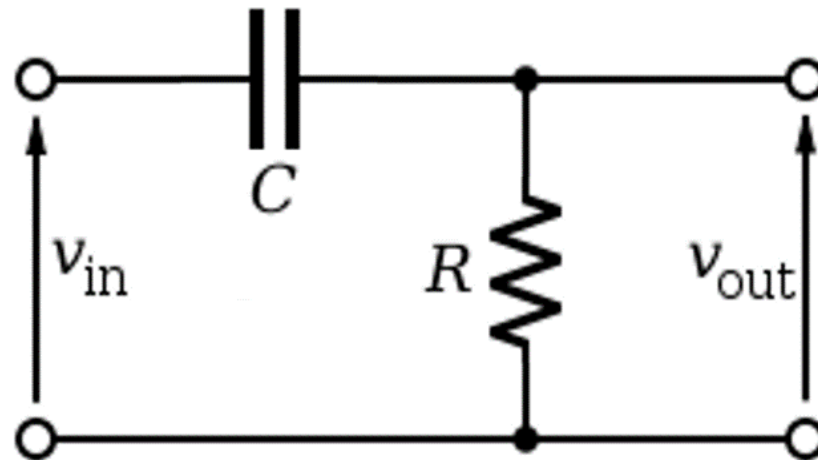Question 3


For the following passive first-order **high-pass filter**, show that its **cutoff frequency** is given by $f_H = \frac{1}{2\pi CR}$



Solution to Q3

- Using **voltage divider rule** to find the **voltage gain**:
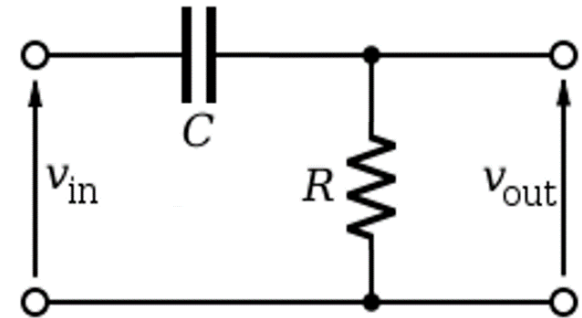
$$\rightarrow V_{\text{out}} = \left[\frac{R}{R + \frac{1}{j\omega C}} \right] V_{\text{in}}$$



$$\rightarrow \frac{V_{\text{out}}}{V_{\text{in}}} = \left[\frac{R}{R + \frac{1}{j\omega C}} \right] = \left[\frac{1}{1 - \frac{j}{\omega CR}} \right] = \frac{1 \angle 0^\circ}{\sqrt{1^2 + \left(\frac{1}{\omega CR} \right)^2} \angle \theta^\circ}$$

$$\rightarrow \left| \frac{V_{\text{out}}}{V_{\text{in}}} \right| = \left[\frac{1}{\sqrt{1 + \left(\frac{1}{\omega CR} \right)^2}} \right] = \underbrace{20 \log_{10} 1}_{\text{Passband gain (} = 0 \text{ dB)}} - \underbrace{20 \log_{10} \sqrt{1 + \left(\frac{1}{\omega CR} \right)^2}}_{\text{Change in gain with } \omega \text{ (-3 dB occurs at } f_H \text{)}} \text{ dB}$$

Magnitude

Solution to Q3

A gain reduction of 3 dB at $f = f_H$ means:

$$\left. -20 \log_{10} \sqrt{1 + \left(\frac{1}{\omega CR} \right)^2} \right|_{f=f_H} = -3 \text{ dB}$$

Hence, $\sqrt{1 + \left(\frac{1}{\omega CR} \right)^2} = 10^{3/20}$ when $f = f_H$,

which gives $\frac{1}{\omega CR} = \frac{1}{2\pi f_H CR} = 1 \rightarrow f_H = \frac{1}{2\pi CR}$