
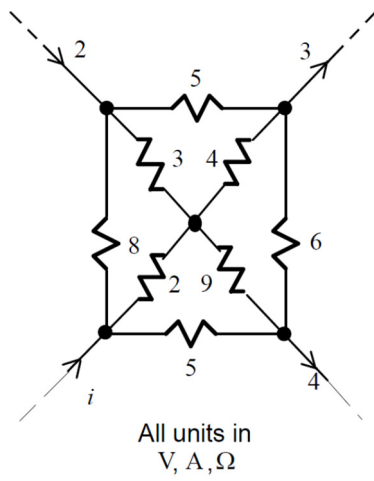


Practice Questions for DC Circuit Analysis

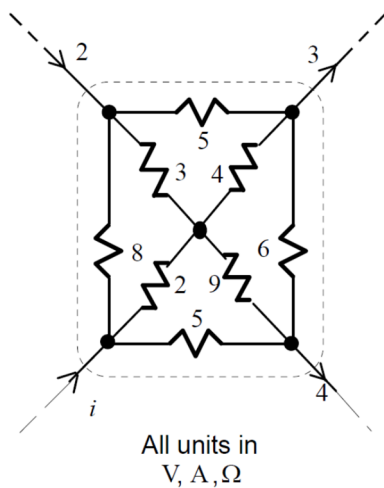1. Determine the current i in the following circuit:




Ans:




Applying KCL to the dotted surface:

$$i + 2 = 3 + 4 \Rightarrow i = 5$$


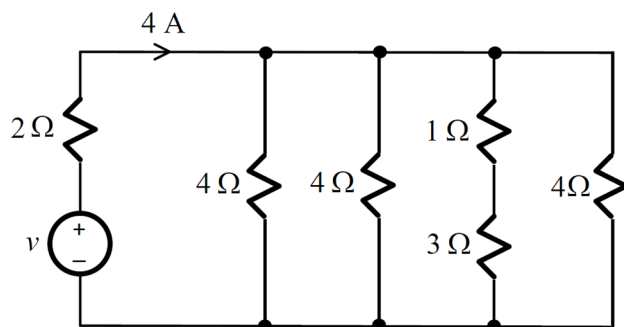
2. Determine the source voltage v and the voltage across the 3Ω resistor in the following circuit.



Ans:

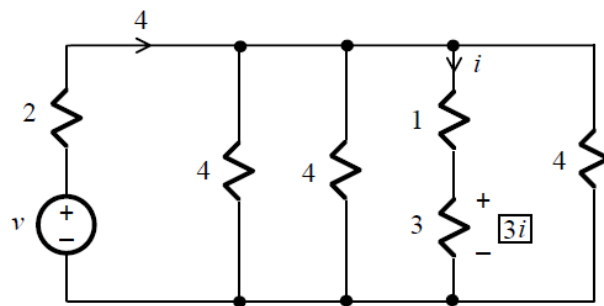


All units in
V, A, Ω

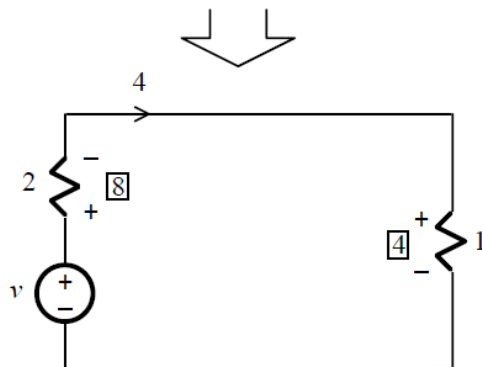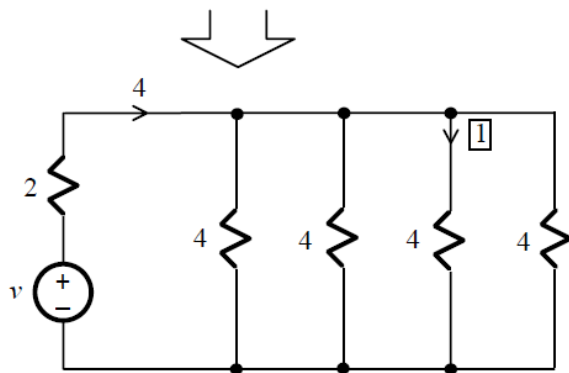


$v = 8 + 4 = 12 \text{ V}$; $i = 1$; voltage across 3Ω resistor $= 3i = 3 \text{ V}$

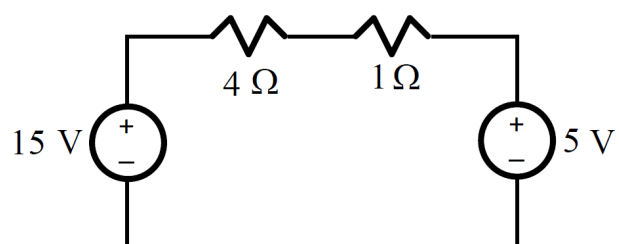3. Determine the current in the following circuit. How much power is each voltage source consuming or supplying?



Ans:

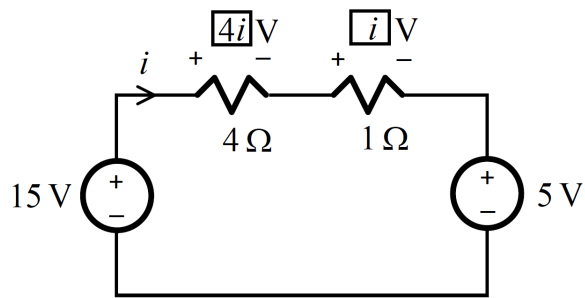


Applying KVL:

$$15 = 4i + i + 5 \Rightarrow i = 2$$

Using “passive sign convention”, power consumed/supplied:

- Power consumed by 5 V source = $5 \times i = 10$ W
- Power consumed by 15 V source = $15 \times (-i) = -30$ W
 \Rightarrow Since it is negative, therefore the 15 V source is supplying a power of 30 W.

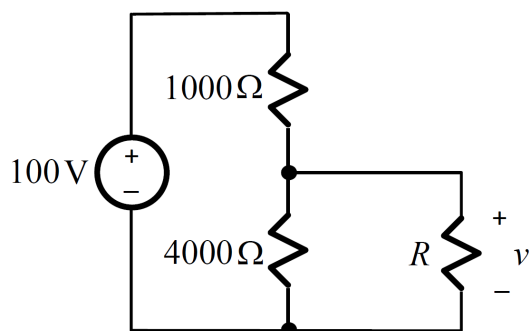4. The following circuit shows a common voltage divider for obtaining a certain voltage v across a load resistor R .




A novice may forget to include the loading effects of R . To understand these effects, determine v and the current in R when


- (a) $R = \infty$ (open-circuit)
- (b) $R = 8000 \Omega$
- (c) $R = 200 \Omega$
- (d) $R = 0$ (short-circuit)

Ans:

(a) $R = \infty$ (open-circuit)

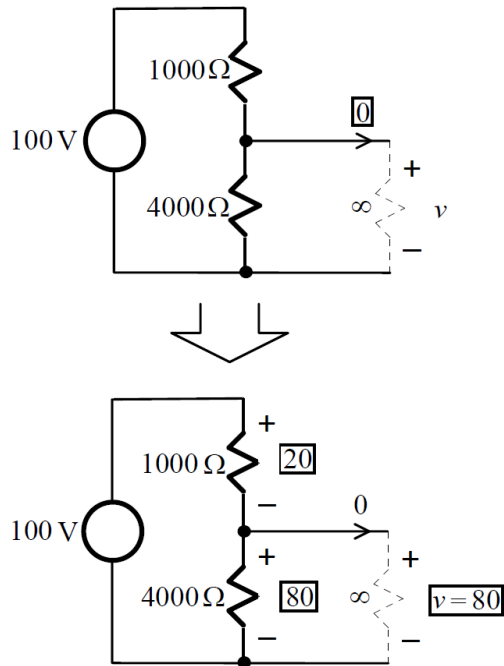



(b) $R = 8000 \Omega$

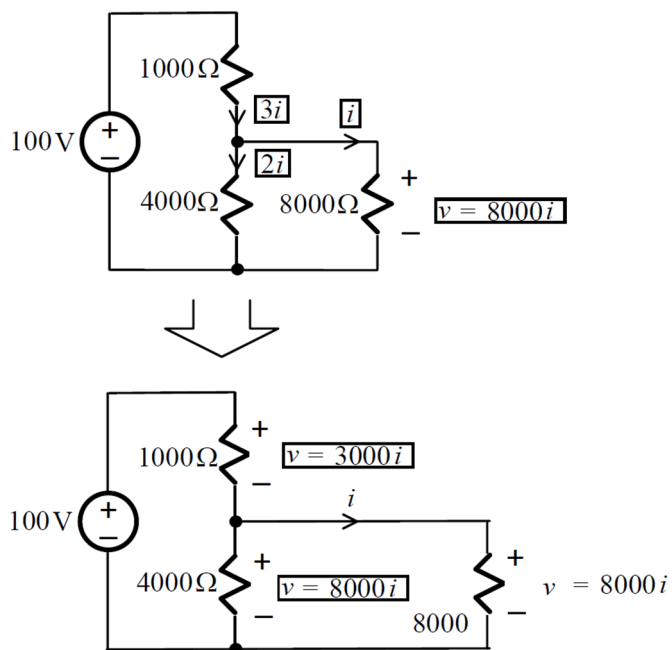

$$100 = 3000i + 8000i \Rightarrow i = \frac{1}{110} \text{ A}$$

$$v = 8000i = 72.73 \text{ V}$$



(c) $R = 200\ \Omega$

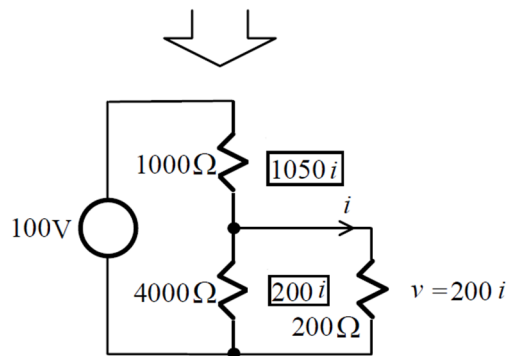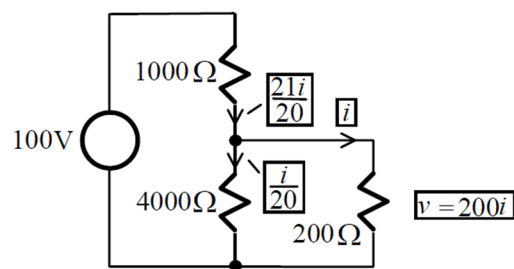

$$100 = 1050i + 200i \Rightarrow 100 = 1250i \Rightarrow i = \frac{2}{25}\text{ A}$$

$$v = 200i = 16\text{ V}$$


(d) $R = 0$ (short-circuit)

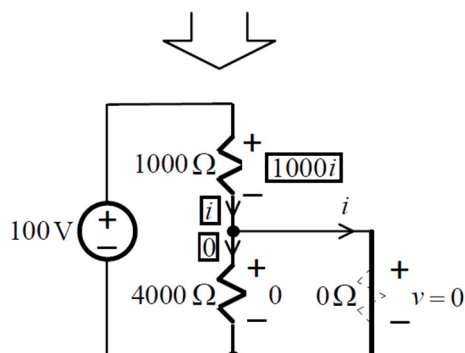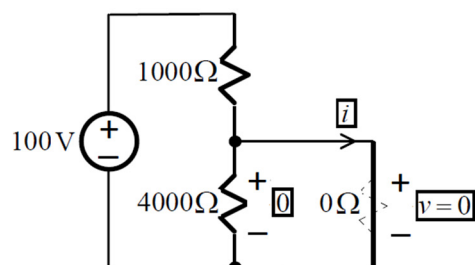

$$100 = 1000i \Rightarrow i = 0.1\text{ A}$$


It may be slightly faster to derive two general formulas for v and i and then substitute the values for R .

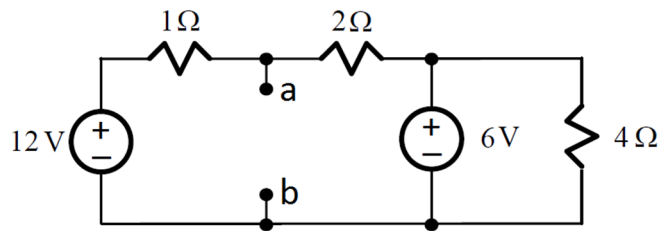5. Determine the maximum power that can be obtained from terminals **a** and **b** of the following circuit.



Ans:


Open circuit voltage

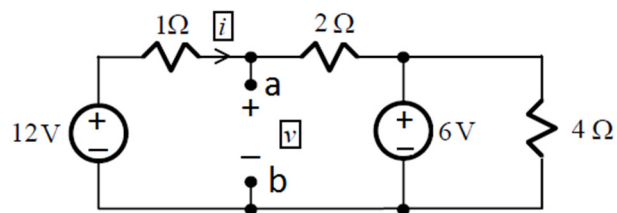

$$i = \frac{12 - 6}{1 + 2} = 2$$


$$v = 12 - i = 10 \text{ V}$$

Equivalent resistance

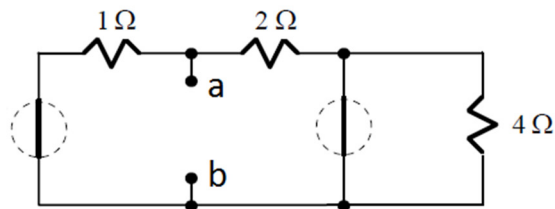


$$\text{Resistance across terminals} = 1 \parallel 2 = \frac{1}{1 + \frac{1}{2}} = 0.667 \Omega$$

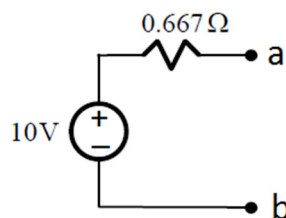Thevenin's equivalent circuit and maximum power




$$\text{Maximum power transferable (with a } 0.667 \Omega \text{ load)} = \left(\frac{10}{2 \times 0.667} \right)^2 0.667 = 37.5 \text{ W}$$

6.

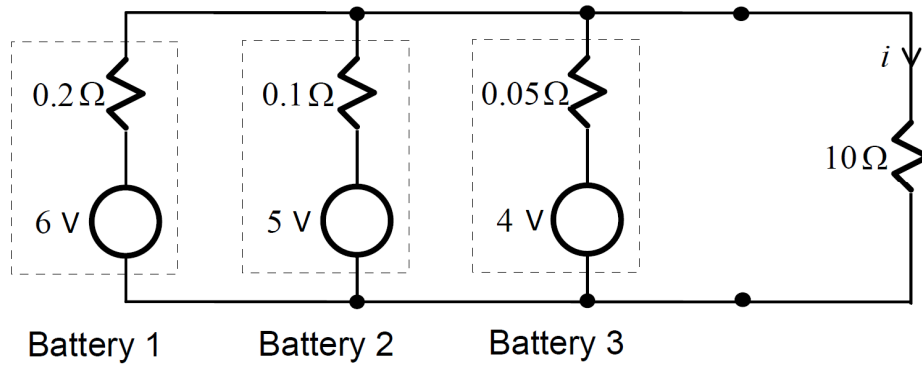

The circuit above shows a $10\ \Omega$ load connected to three batteries in parallel. Using node voltage analysis method, determine the voltage across the $10\ \Omega$ load, and also its current i .

Ans:

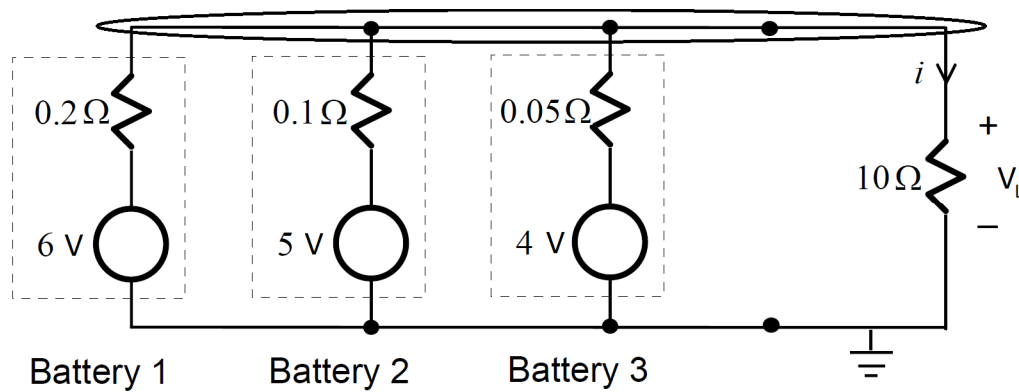

First, we assign the bottom wire as the reference node (earthed, with voltage 0).

We only need to have one unknown voltage variable for the above circuit, V_L .

Writing the KCL equation for the top node enclosed by the ellipse (equate the sum of currents leaving the node to zero):

$$\frac{V_L - 6}{0.2} + \frac{V_L - 5}{0.1} + \frac{V_L - 4}{0.05} + \frac{V_L}{10} = 0$$

Solving the above equation, we get $V_L = 4.56\text{ V}$, and $i = 0.456\text{ A}$.