


CG1111: Engineering Principles and Practice I

Debrief and Tutorial for Week 4




How to Label V & I for Resistors?

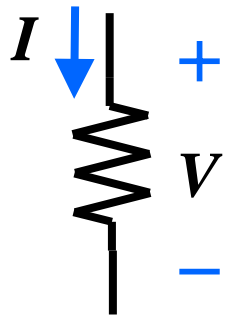- A resistor consumes power:
 - Principle: In a resistor, the voltage (potential) must drop in the direction of the current




If the current's true direction or the voltage's true polarity is not obvious in the circuit, just **pick & label either the current or the voltage**, and then **label the other one** by following the **above principle**

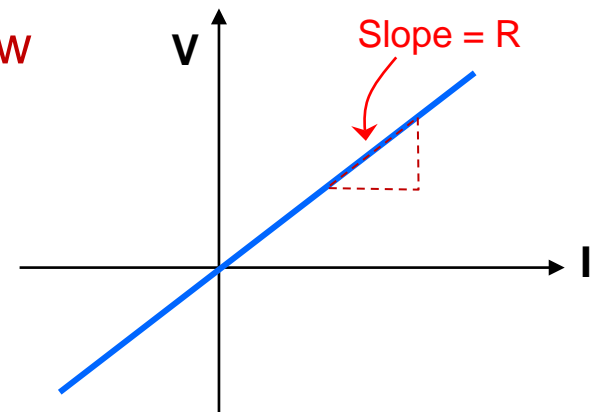You can only **apply Ohm's Law** if you label them this way!



Thevenin Equivalent Circuit


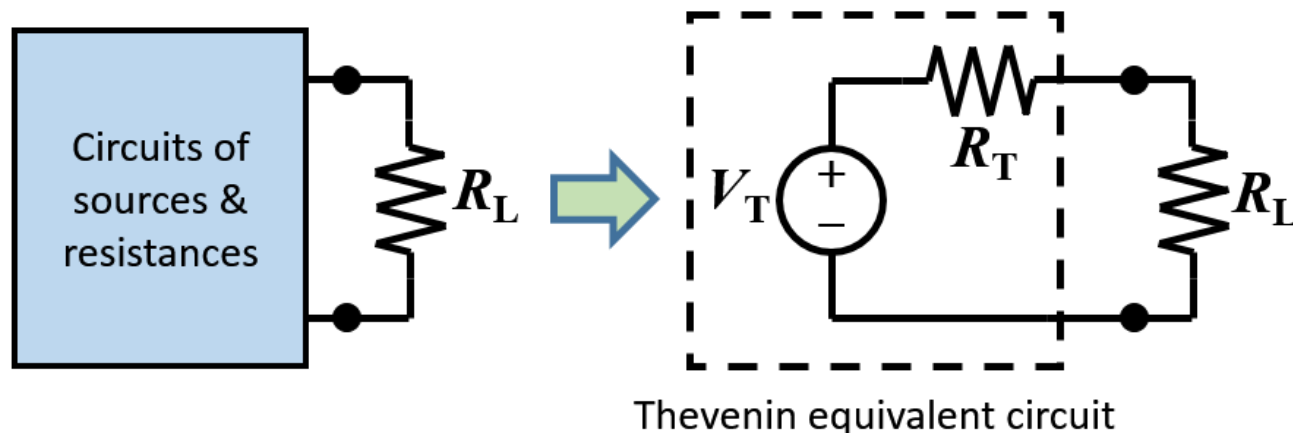
- Any circuit consisting of sources and resistances can be replaced by a Thevenin equivalent circuit



The **I-V behaviour** of the Thevenin equivalent circuit is the **same** as that of the complex circuit
→ **Very useful for circuit analysis!**

Battery's Equivalent Circuit

It is just a model!!

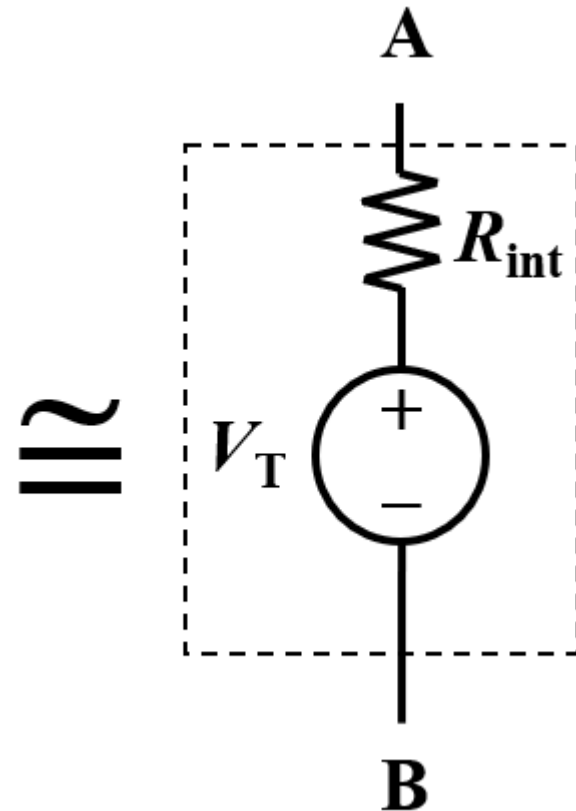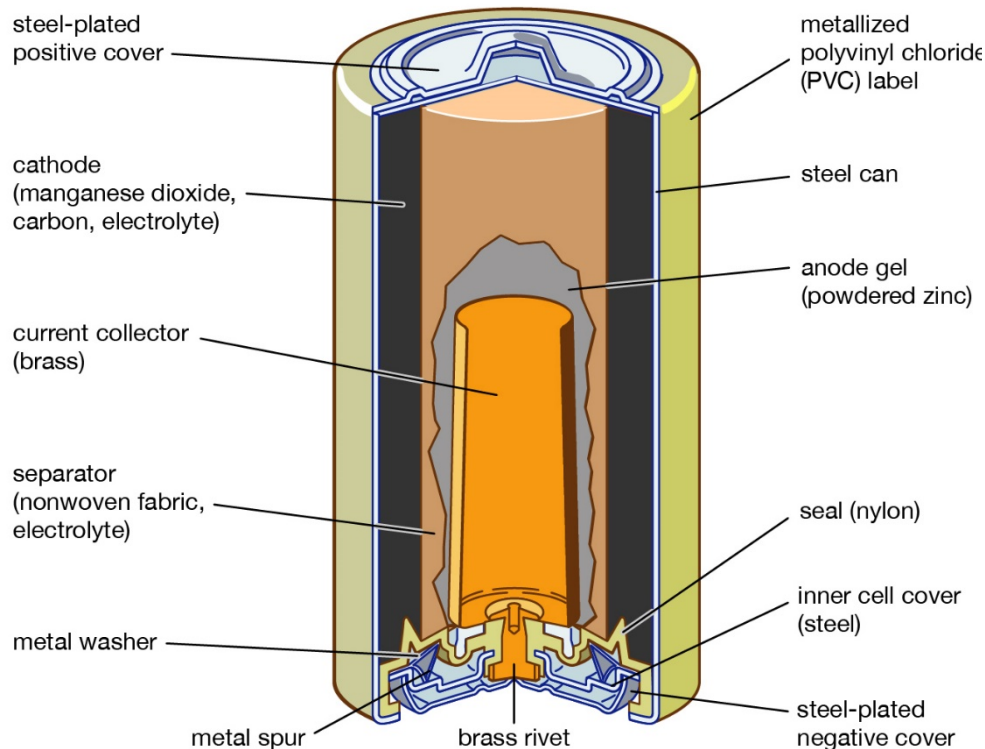


© Encyclopædia Britannica, Inc.

- Battery's equivalent circuit is actually a Thevenin equivalent circuit!

Finding Thevenin Voltage

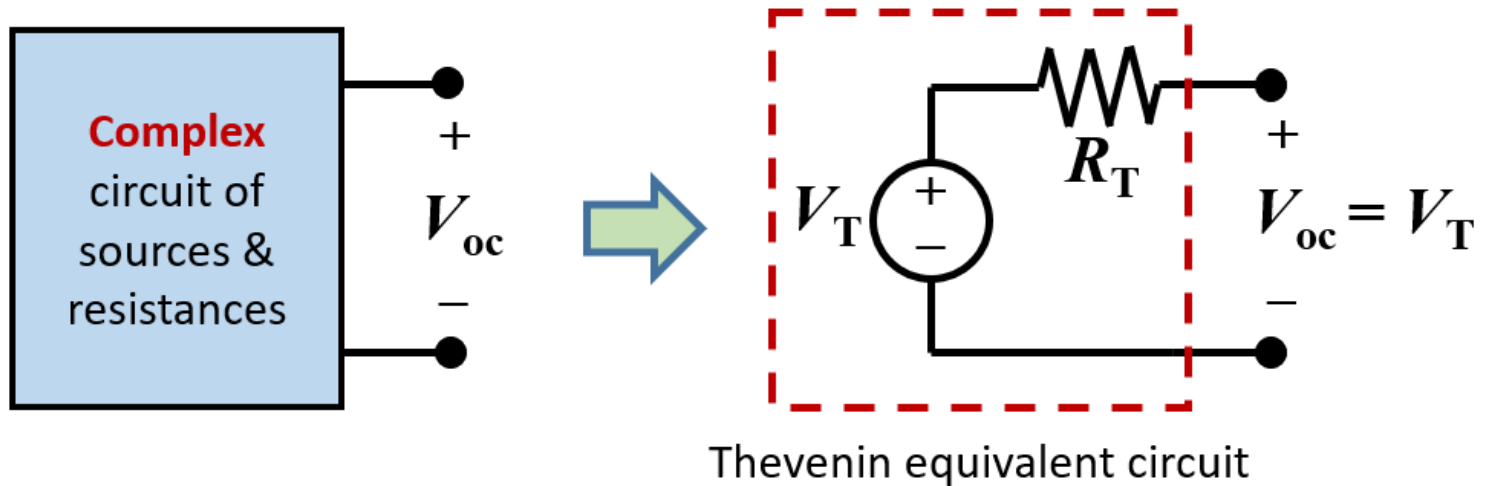
V_T can be obtained by finding V_{oc} across the 2 terminals of the complex circuit



Finding Thevenin Resistance

R_T can be obtained using Ohm's Law after finding I_{sc} across the 2 terminals of the complex circuit



$$R_T = \frac{V_T}{I_{sc}}$$

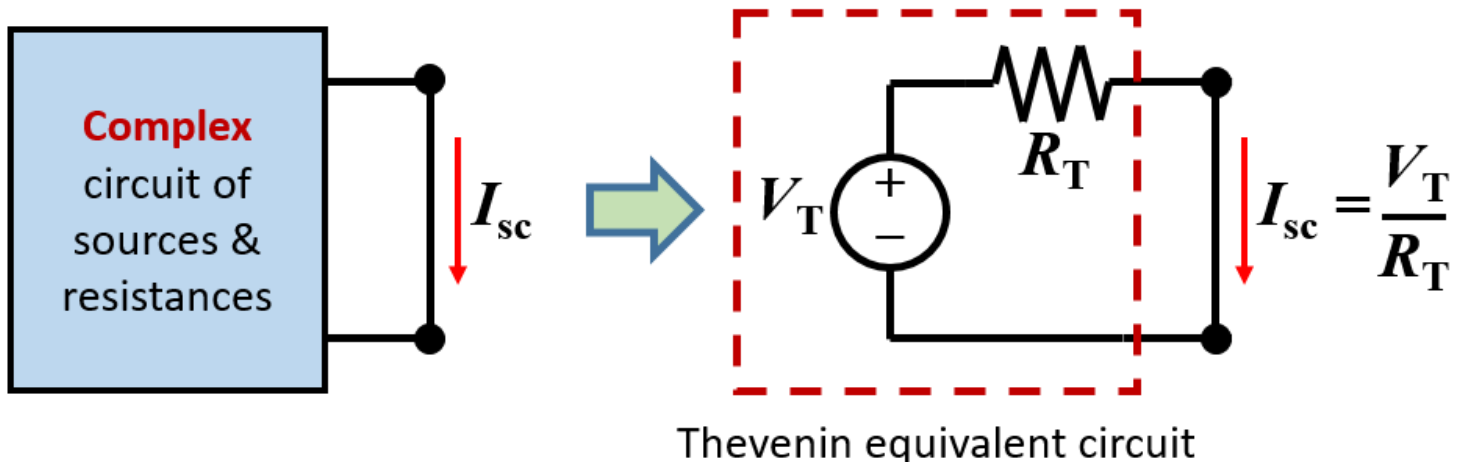

Experimental Method to Find R_T

- There is a risk that I_{sc} may be large

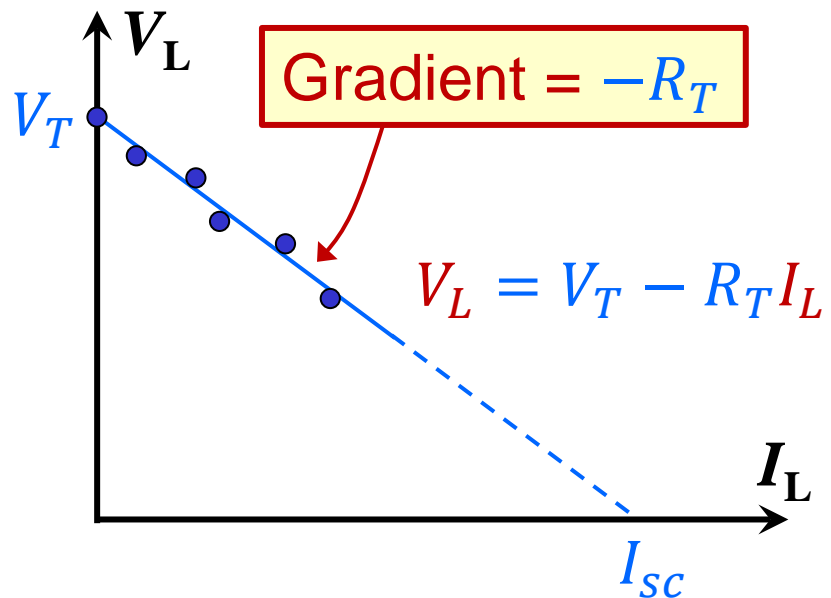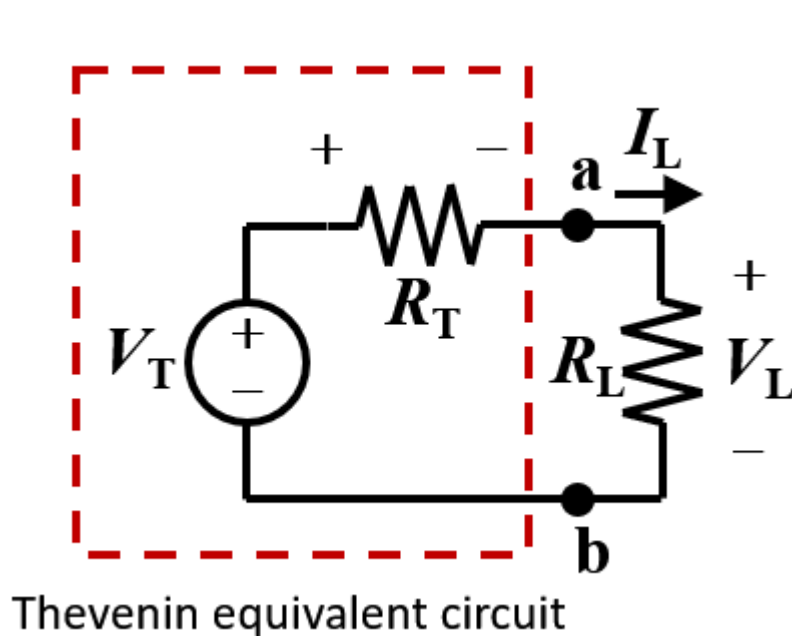
It is safer to connect the circuit to multiple resistive loads and then use graphical approach



Another Analytical Method to Find R_T (Usually Easiest!)


- If the original electrical circuit consists of independent voltage sources only,
 - Replace all voltage sources with a short-circuit (0 V); this results in a purely resistive network

Then, find the equivalent resistance between the two terminals

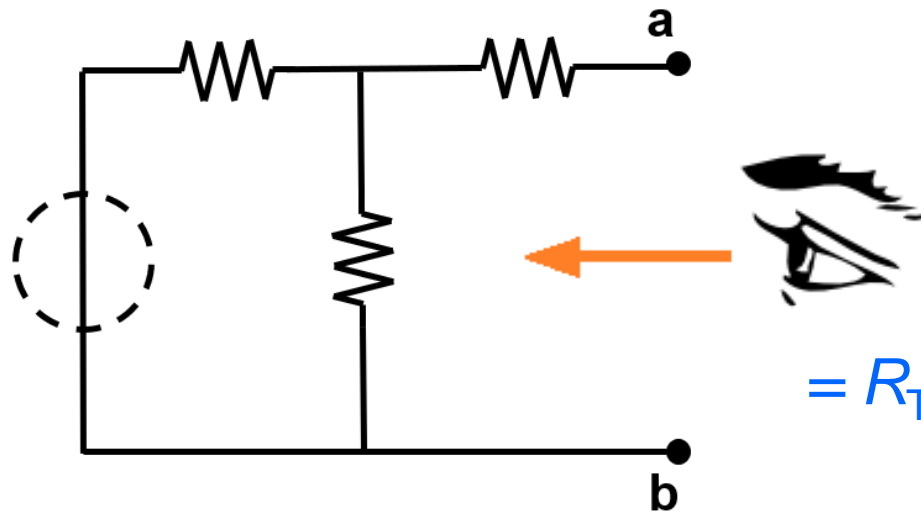


Question 1

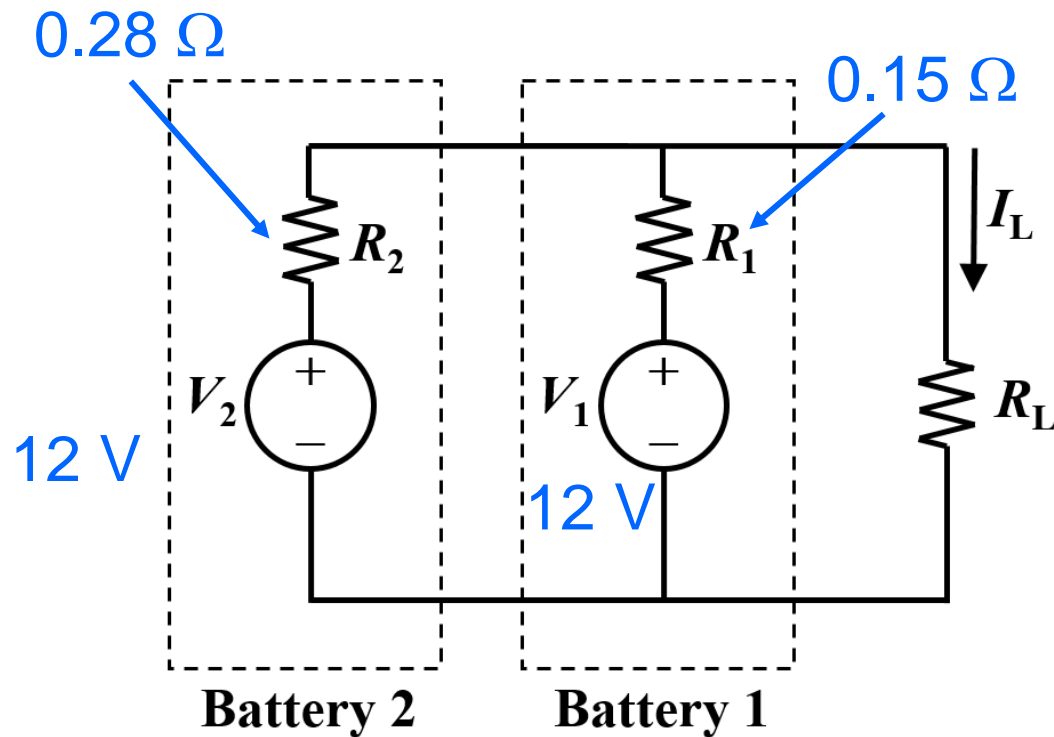(i) Find Thevenin equivalent circuit seen by R_L



Solution to Q1 (i)

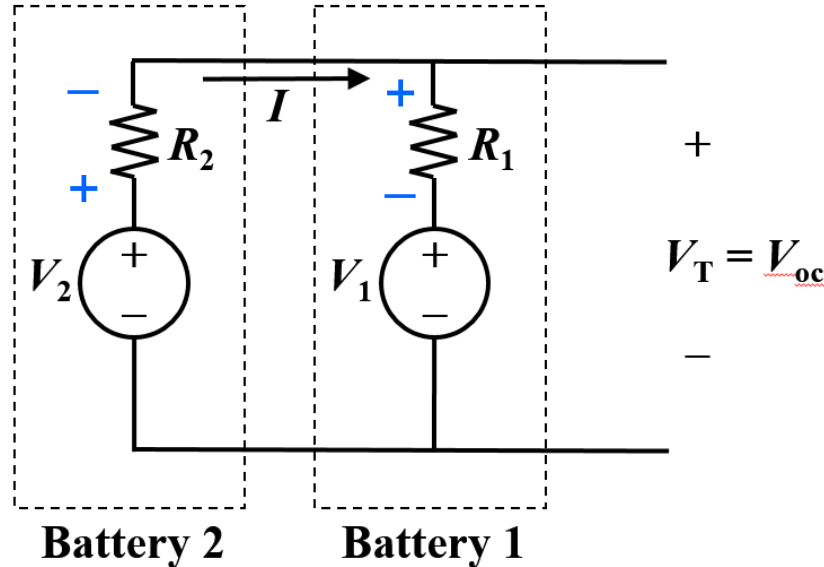

- Using KVL in the loop without load:

$$V_2 = R_2 I + R_1 I + V_1$$

$$12 = (0.28 + 0.15)I + 12$$


$$I = 0$$

- Therefore, $V_T = 12 \text{ V}$


Solution to Q1 (i)

To find R_T , put V_1 and V_2 to 0, and calculate resistance as seen across the two terminals:
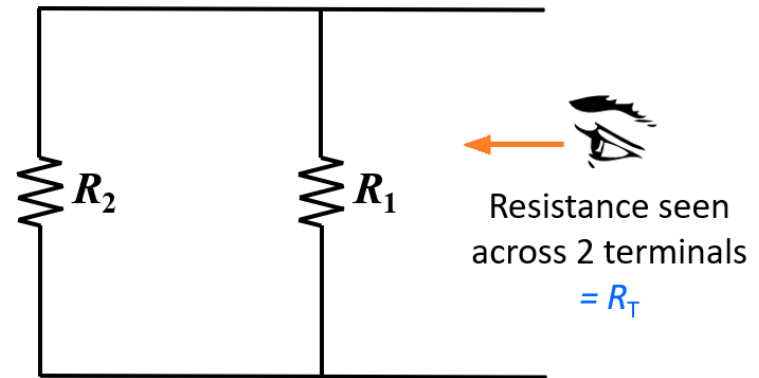
$$\begin{aligned} R_T &= R_1 // R_2 \\ &= 0.15 // 0.28 \\ &= 0.098 \, \Omega \end{aligned}$$



Hence,

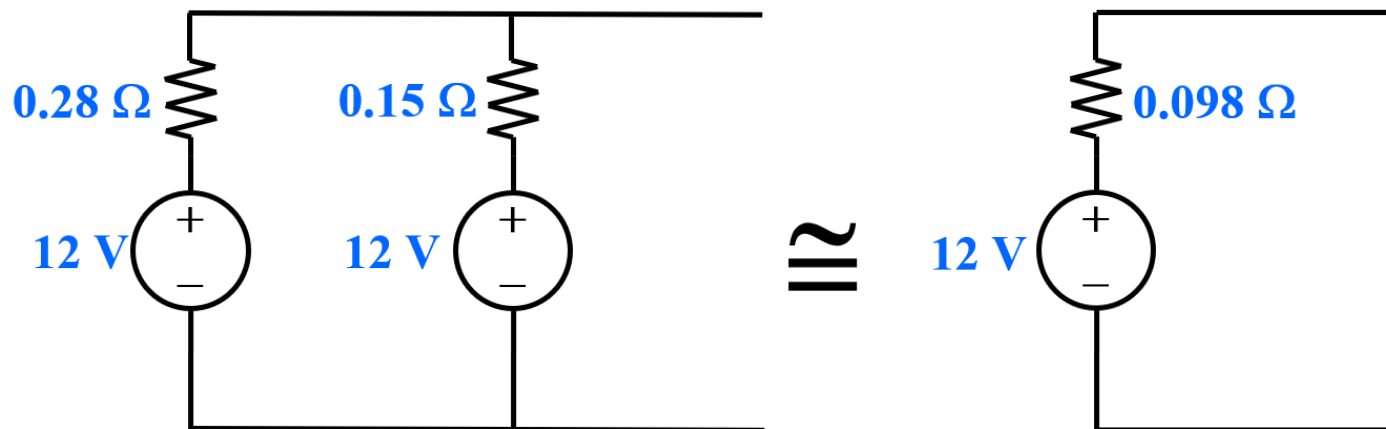


Solution to Q1 (ii)

If load $R_L = 2.5 \Omega$, find I_L and V_L

$$I_L = \frac{12}{0.098 + 2.5} = 4.62 \text{ A}$$
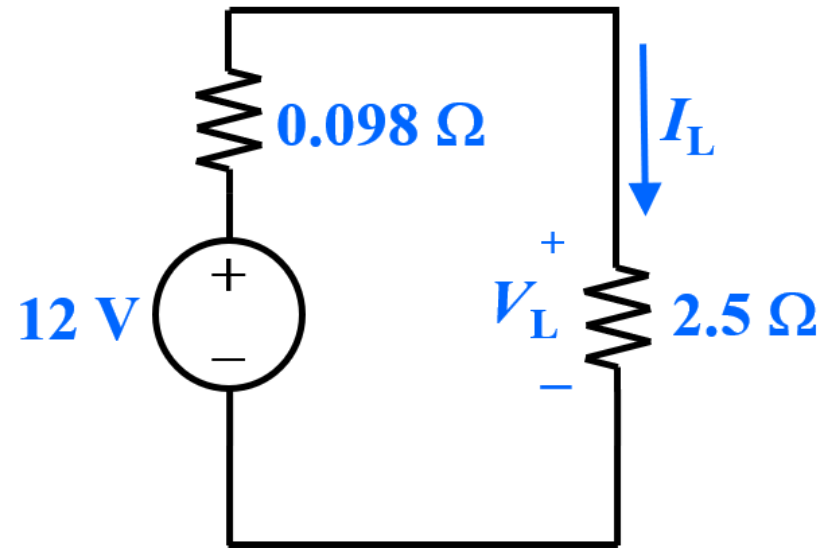
$$V_L = \frac{2.5}{0.098 + 2.5} \times 12 = 11.5 \text{ V}$$



Solution to Q1 (iii)

- Is load voltage V_L higher or lower compared to using just one of the two batteries alone?

- Using battery 1 alone:

$$V_L = \frac{2.5}{0.15 + 2.5} \times 12 = 11.3 \text{ V}$$


- Using battery 2 alone:

$$V_L = \frac{2.5}{0.28 + 2.5} \times 12 = 10.8 \text{ V}$$



- Load voltage V_L is **higher** compared to using any one of the two batteries alone

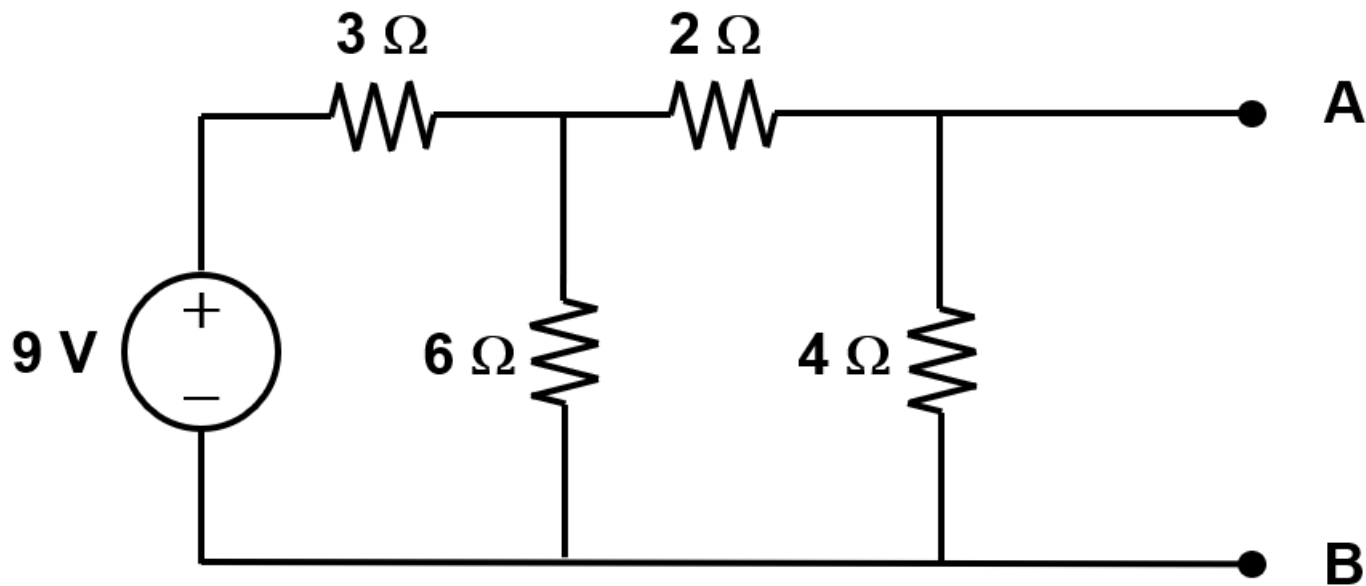Question 2

Find Thevenin equivalent circuit seen across A & B:



Solution to Q2

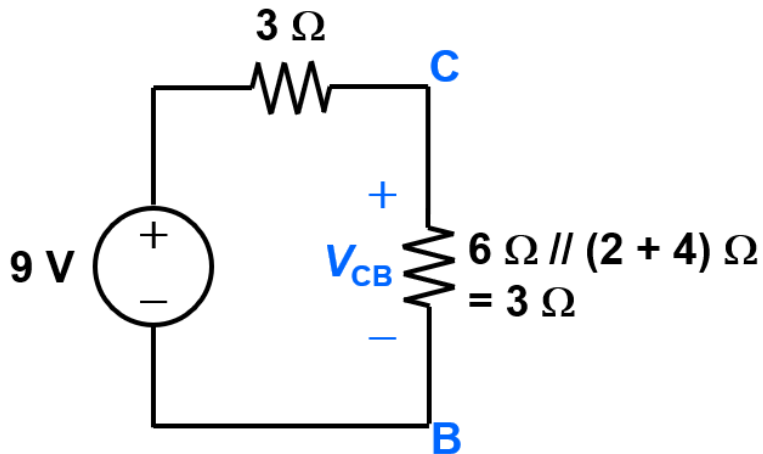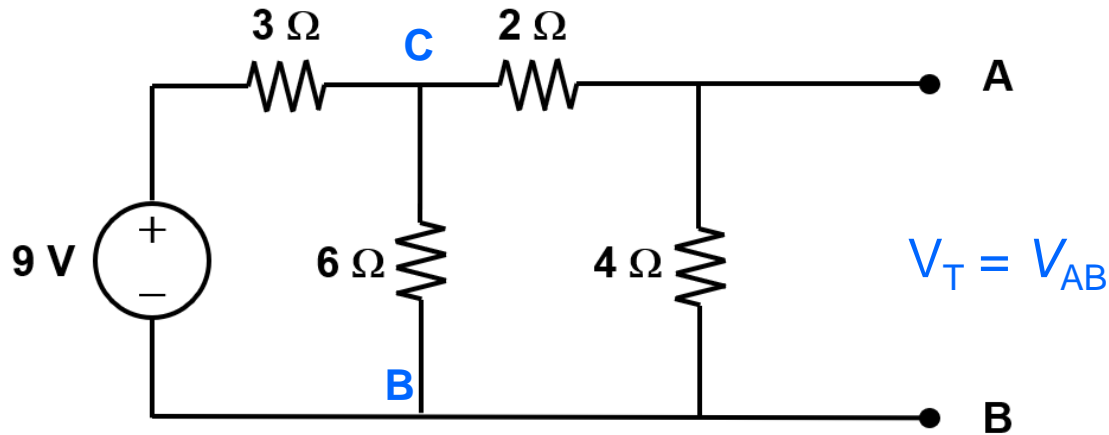


- $V_{CB} = \frac{3}{3+3} \times 9 = 4.5\ V$



- Hence,

$$V_T = V_{AB} = \frac{4}{4+2} \times 4.5 = 3\ V$$

Solution to Q2

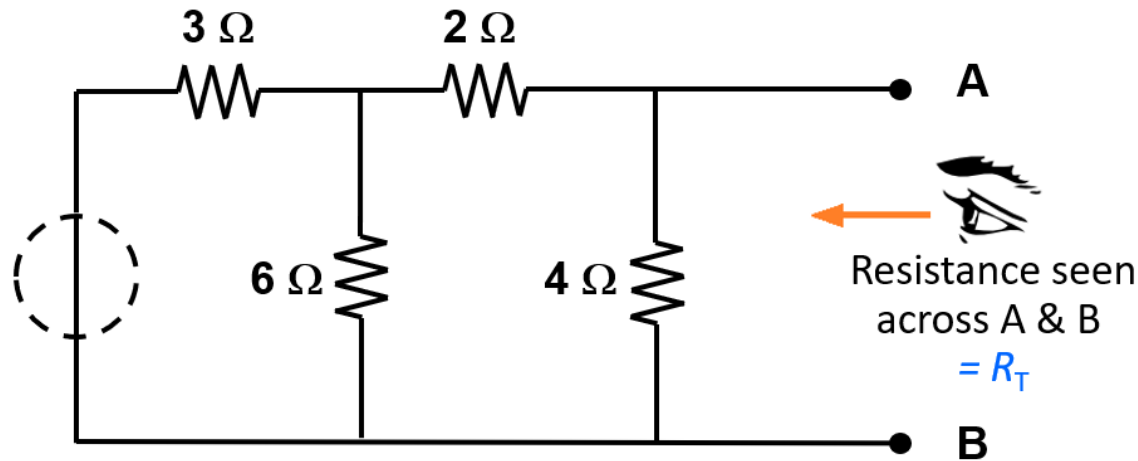

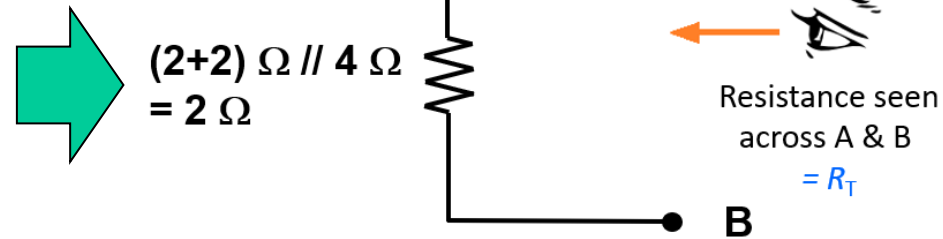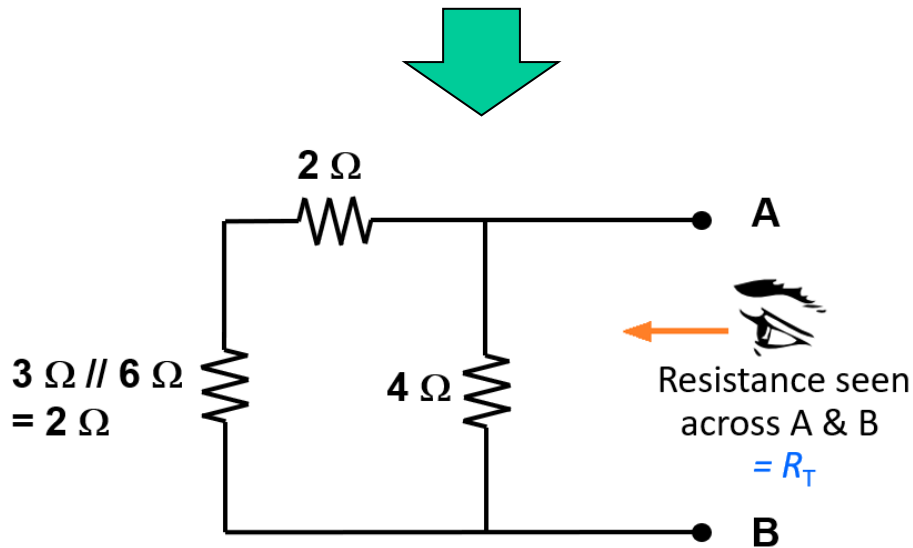
Put the voltage source to 0 V (becomes essentially just a wire)



Hence, $R_T = 2\ \Omega$

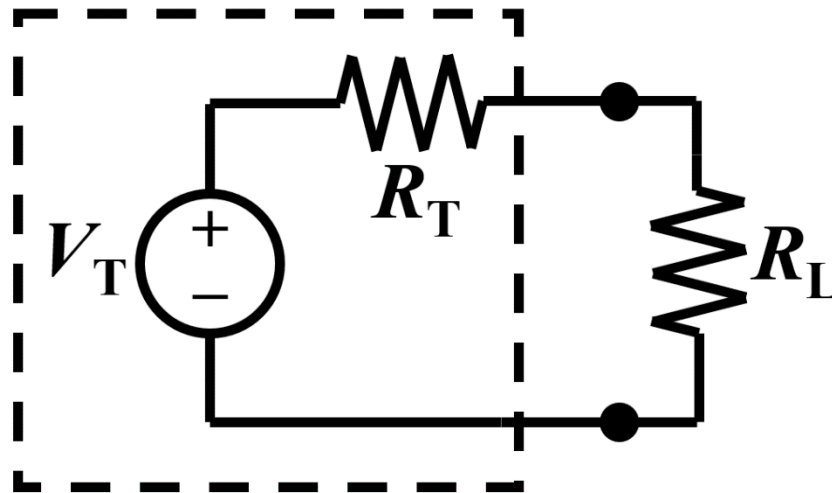Question 3

- For the Thevenin equivalent circuit shown below, derive the value of R_L that causes **maximum power transfer** from the **source** to the **load** R_L .




Thevenin equivalent circuit

Solution to Q3


- $i = \frac{V_T}{R_T + R_L}$
- $P_L = i^2 R_L = \left(\frac{V_T}{R_T + R_L} \right)^2 R_L$
- The value of R_L which gives maximum P_L is the value for which $\frac{dP_L}{dR_L} = 0$
- $\frac{dP_L}{dR_L} = \frac{V_T^2 (R_T + R_L)^2 - 2V_T^2 R_L (R_T + R_L)}{(R_T + R_L)^4} = 0$
- $V_T^2 (R_T + R_L)^2 - 2V_T^2 R_L (R_T + R_L) = 0$
- The above equation is true when $R_L = R_T$

Solution to Q3

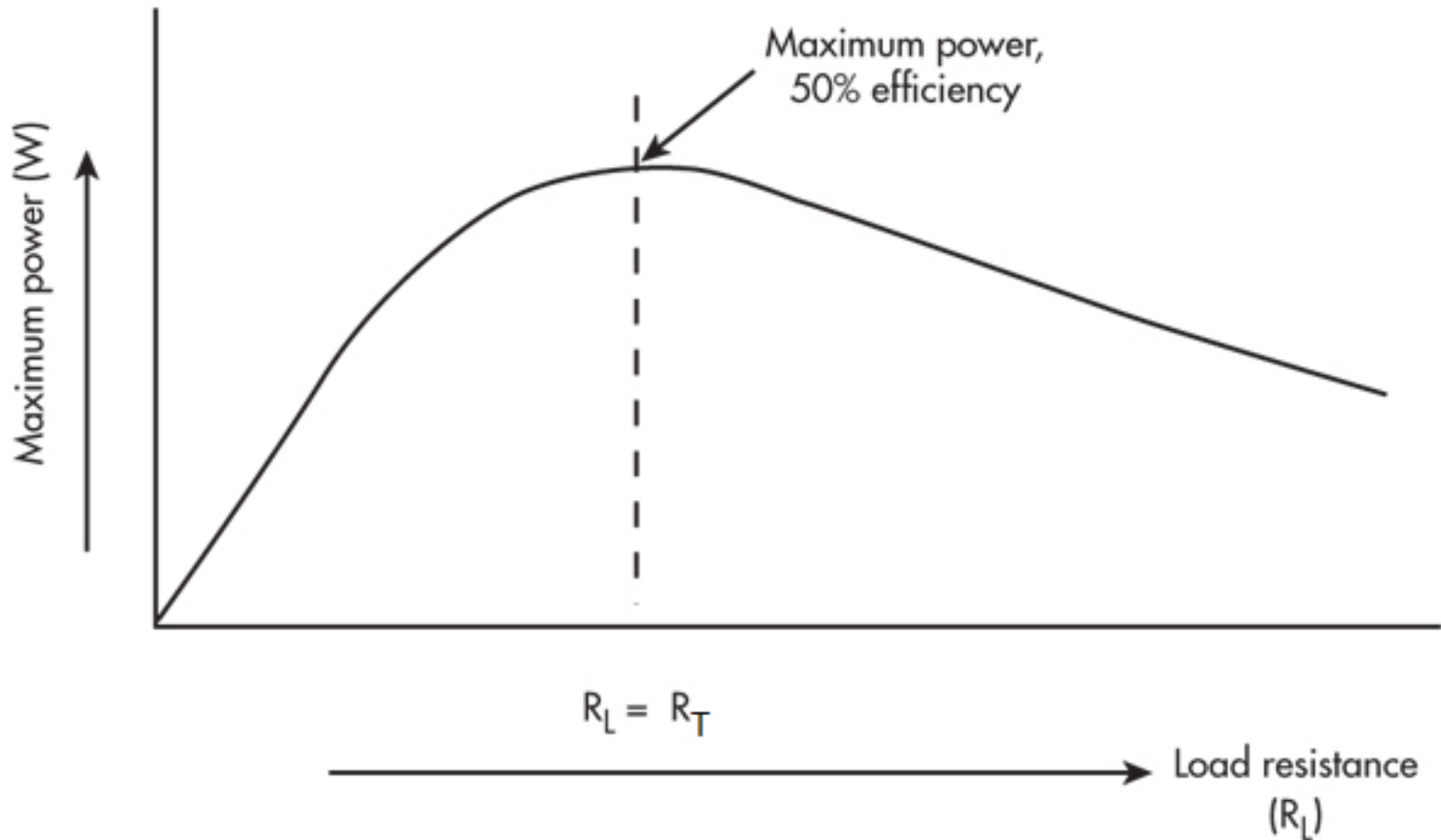

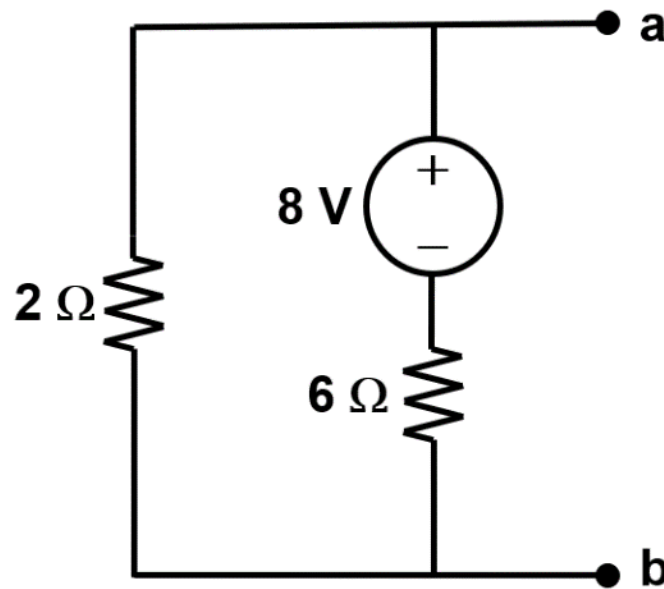
Question 4

Determine the value of R_L to be placed across nodes a and b, in order for it to draw maximum power. Calculate this power.



Solution to Q4

- Find Thevenin equivalent circuit!

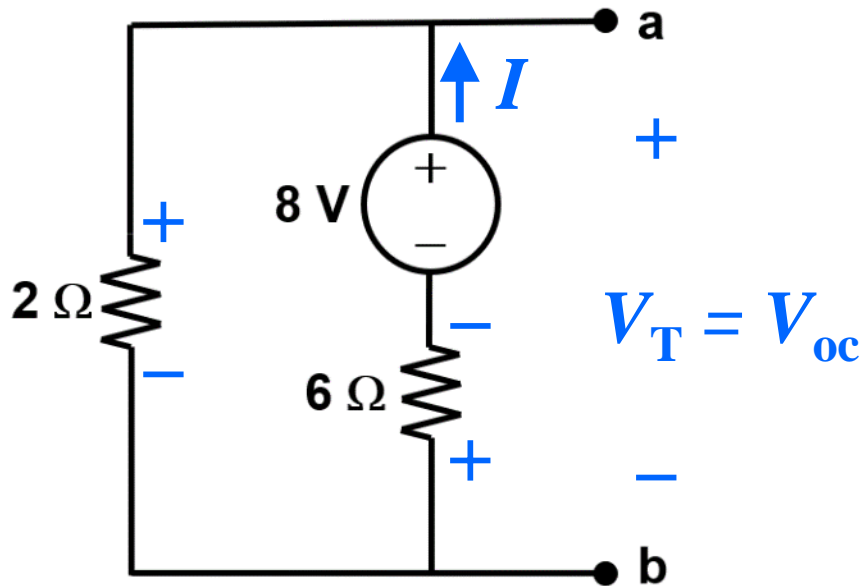

$$I = \frac{8}{2 + 6} = 1 \text{ A}$$


$$\begin{aligned} V_T &= V_{oc} \\ &= 8 - (6 \times 1) \\ &= 2 \text{ V} \end{aligned}$$

How do we label the voltage polarity across a resistor (a passive element)?

Label it in such a way that the potential decreases in the labeled direction of current.

$$\begin{aligned} R_T &= 6 // 2 \\ &= 1.5 \Omega \end{aligned}$$

Solution to Q4

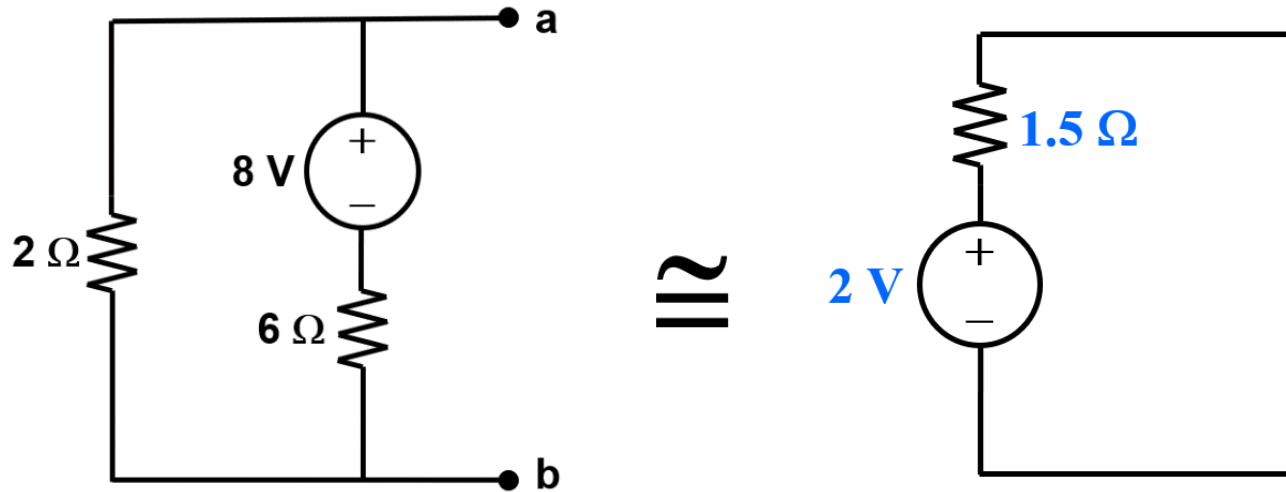

Load R_L that draws maximum power:

$$R_L = R_T = 1.5\ \Omega$$

Maximum power:

$$P = (I_L)^2 R_L = \left(\frac{2}{1.5 + 1.5} \right)^2 \times 1.5 = 0.67\text{ W}$$