

NATIONAL UNIVERSITY OF SINGAPORE

CG1111 – ENGINEERING PRINCIPLES AND PRACTICE I

QUIZ #1

05 OCTOBER 2019


INSTRUCTIONS:

1. This paper contains **15** multiple-choice questions (MCQs), with only a **SINGLE** correct answer each.
 2. Answer **ALL** questions.
 3. Use only **2B pencils** to shade the bubble sheet.
 4. This is an **OPEN-BOOK** test.
 5. There is no restriction on the use of programmable calculators.
 6. There is **no penalty (i.e., no negative marks) for wrong answers**. Please attempt all questions.
 7. You are **NOT ALLOWED** to use your **mobile phone, tablet or computer** during the test.
 8. **DO NOT READ** the questions until you are told to do so.
 9. Time allowed: **75 MINUTES**
 10. After the quiz, please remain seated while we tally the number of submitted scripts.
-

1. What is the discharge current of a 14.4 Wh battery operating at 2.4 V and 1.6C?
 - (A) 3750 mA
 - (B) 23.04 A
 - (C) 9600 mA
 - (D) 9 A

2. Calculate the number of batteries in series and the number of parallel branches required in a battery pack for a wireless Bluetooth speaker consisting of Lithium Ion batteries, to last a period of 7 hours. The mid-point voltage per battery for the required maximum instantaneous C rate is 3.65 V. Single battery capacity at the maximum allowable 80% depth of discharge (same as end of discharge) is 5000 mAh. The required operating voltage is 13 V. The Bluetooth speaker consists of 3 subsystems working in parallel with the following power efficiencies: $\eta_1 = 90\%$, $\eta_2 = 85\%$, $\eta_3 = 94\%$, and each subsystem's output power is 20 W.
 - (A) 4 batteries in series, 7 branches in parallel
 - (B) 3 batteries in series, 8 branches in parallel
 - (C) 4 batteries in series, 8 branches in parallel
 - (D) 3 batteries in series, 7 branches in parallel


3.

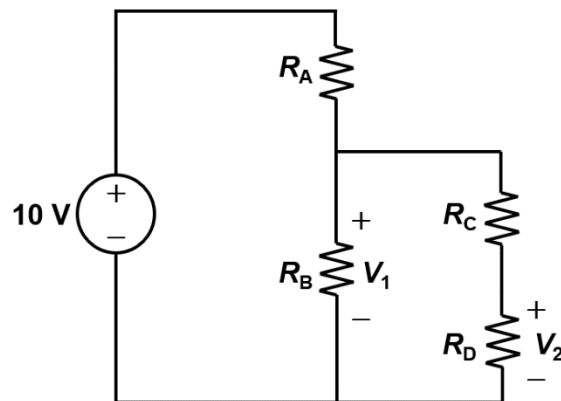

Benedict, who'd just learnt about the voltage divider principle, is excited about applying it to build a circuit shown in the figure above. He wishes to obtain $V_1 = 6\text{ V}$, and $V_2 = 2\text{ V}$. However, he does not realize that he cannot apply the principle directly to R_A and R_B , as resistors R_C and R_D have a “loading effect”. Which one of the following sets of resistor values would allow him to get V_1 and V_2 to be closest to his desired voltages of 6 V and 2 V, respectively?

| | R_A | R_B | R_C | R_D |
|-----|----------------|----------------|----------------|----------------|
| (A) | $40\ \Omega$ | $60\ \Omega$ | $400\ \Omega$ | $200\ \Omega$ |
| (B) | $40\ \Omega$ | $60\ \Omega$ | $4000\ \Omega$ | $2000\ \Omega$ |
| (C) | $400\ \Omega$ | $600\ \Omega$ | $40\ \Omega$ | $20\ \Omega$ |
| (D) | $4000\ \Omega$ | $6000\ \Omega$ | $40\ \Omega$ | $20\ \Omega$ |


4.

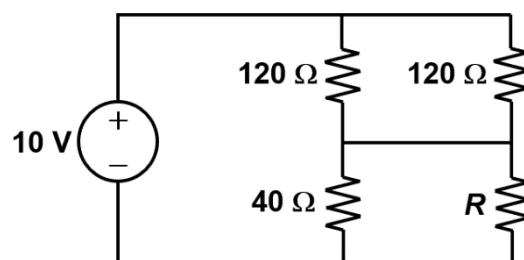

What is the value of R that will result in a current of 0.1 A passing through R ?
(Hint: Use Thevenin equivalent circuit)

- (A) $56\ \Omega$
- (B) $24\ \Omega$
- (C) $40\ \Omega$
- (D) $16\ \Omega$


5.

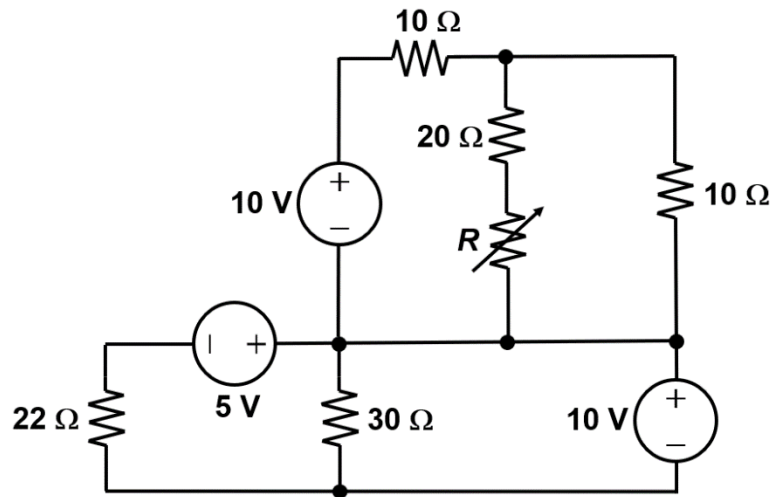

What is this maximum power that can be utilized by the load R ?

- (A) 0.25 W
- (B) 1 W
- (C) 1.56 W
- (D) 6.25 W


6.

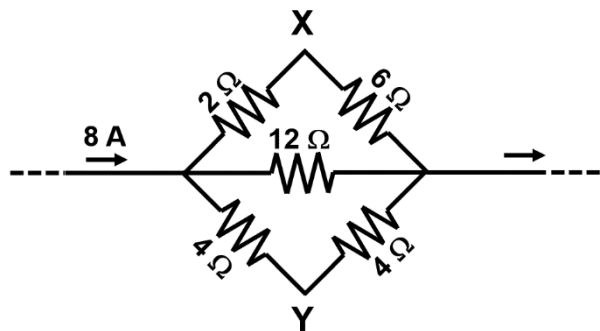

A current of 8 A flows through a resistor network as shown in the figure above. The voltage difference V_{XY} (given by $V_X - V_Y$) is

- (A) 12 V
- (B) 6 V
- (C) 4.57 V
- (D) 11.4 V


7.

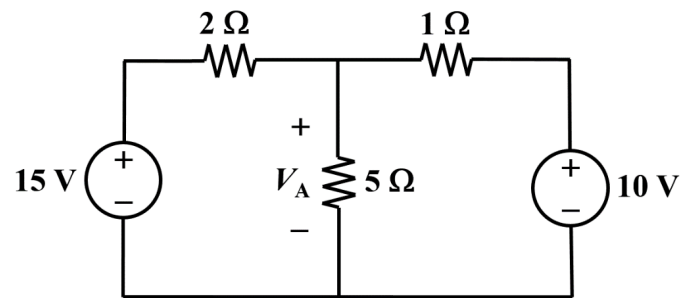

For the circuit shown in the figure above, what is the voltage V_A ?

- (A) 12.1 V
- (B) 11.7 V
- (C) 11.3 V
- (D) 10.3 V


8.

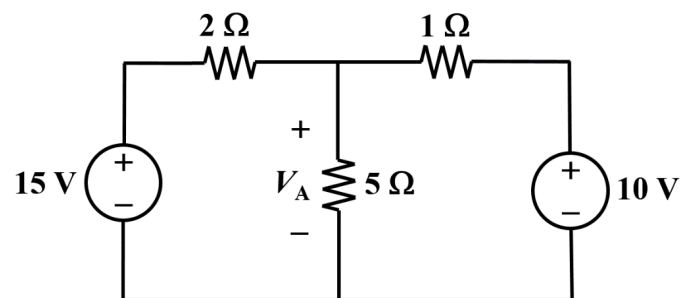

For the circuit shown in the figure above, the 10 V voltage source is

- (A) supplying a power of about 28 W.
- (B) consuming a power of about 21 W.
- (C) consuming a power of about 3 W.
- (D) consuming a power of about 13 W.


9.

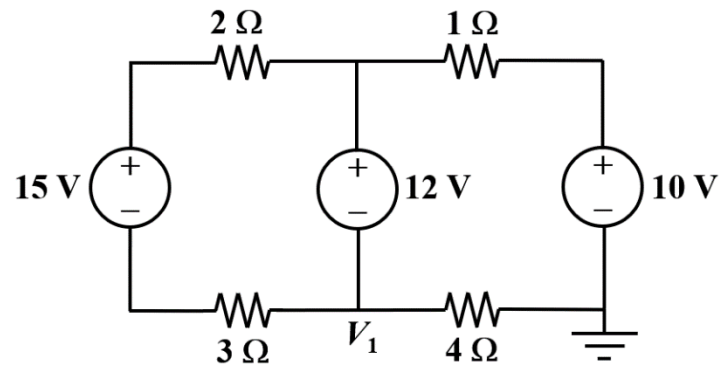

For the circuit shown in the figure above, what is the voltage V_1 with respect to ground?

- (A) 3.4 V
- (B) -3.4 V
- (C) 1.6 V
- (D) -1.6 V


10.

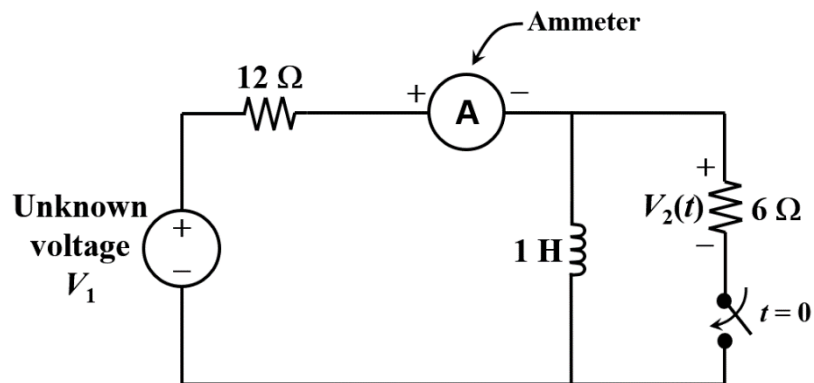

For the circuit shown in the figure above, the switch has been opened for a long time, and the current measured by the ammeter was 1 A before time $t = 0$. At time $t = 0$, the switch is closed. What would be the voltage $V_2(t)$ at time $t = 0^+$ s?

- (A) 0 V
- (B) -6 V
- (C) 4 V
- (D) 6 V


11.

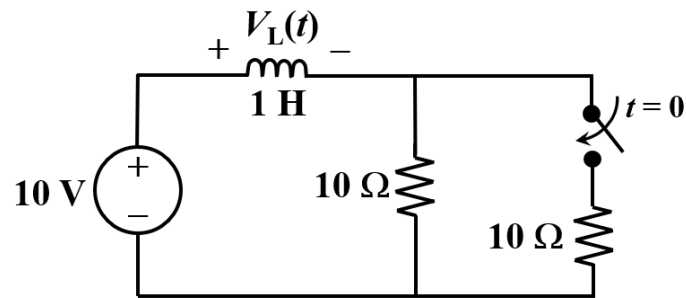

In the circuit shown in the figure above, the switch was initially OPEN for a long time. At time $t = 0$, the switch is closed. What is the inductor's voltage $V_L(t)$ at time $t = 0.2$ s?

- (A) 8.16 V
- (B) 1.84 V
- (C) 6.32 V
- (D) 3.68 V


12.

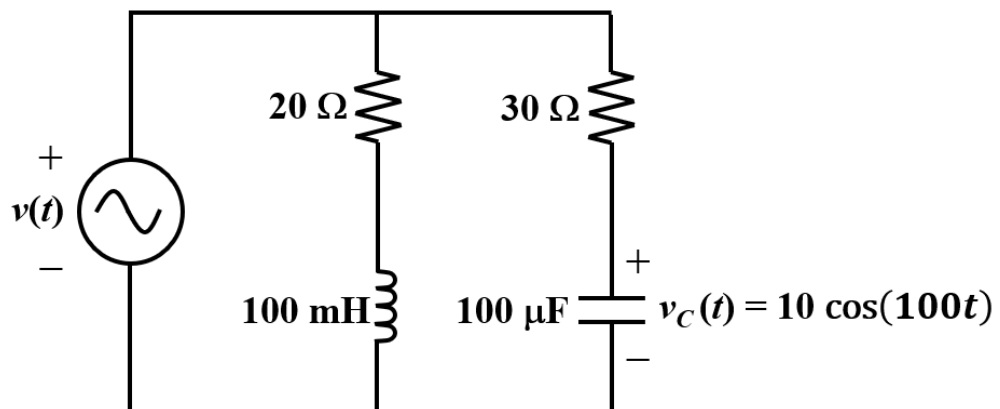

In the circuit shown in the figure above, the voltage $v(t)$ is

- (A) $9.58 \cos(100t - 16.7^\circ)$ V
- (B) $9.58 \cos(100t + 16.7^\circ)$ V
- (C) $10.4 \cos(100t + 16.7^\circ)$ V
- (D) $10.4 \cos(100t - 16.7^\circ)$ V


13.

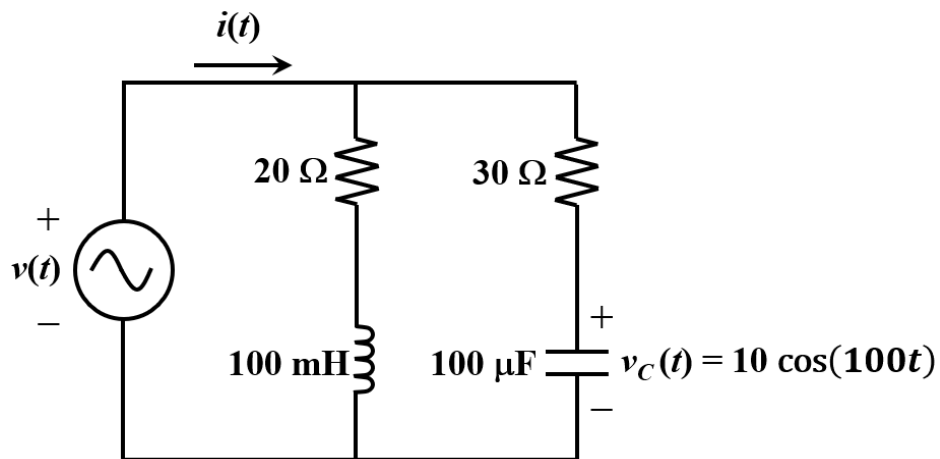

In the circuit shown in the figure above, the current $i(t)$ is

- (A) $237 \cos(100t + 30.9^\circ)\text{ A}$
- (B) $2.17 \cos(100t - 2.5^\circ)\text{ A}$
- (C) $0.46 \cos(100t + 2.5^\circ)\text{ A}$
- (D) $0.54 \cos(100t - 17.6^\circ)\text{ A}$


14.

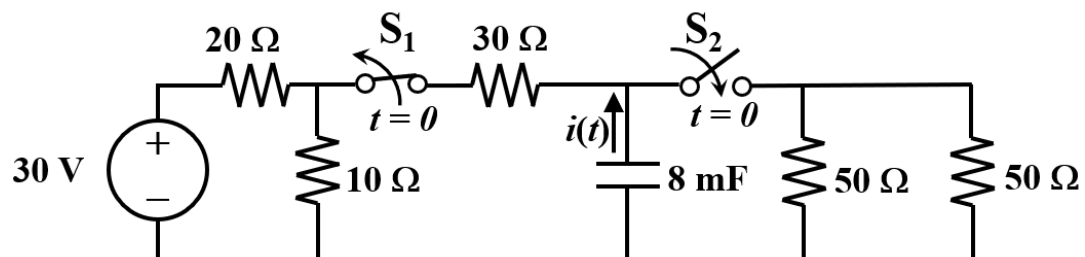

In the circuit shown in the figure above, switch S_1 was CLOSED and switch S_2 was OPEN for a long time before time $t = 0$. At time $t = 0$, both switches are flipped (i.e., S_1 becomes OPEN, and S_2 becomes CLOSED). What is the capacitor's current $i(t)$ at time $t = 0.2$ second?

- (A) 0.147 A
- (B) 0.253 A
- (C) 3.68 A
- (D) 73.6 mA

15.

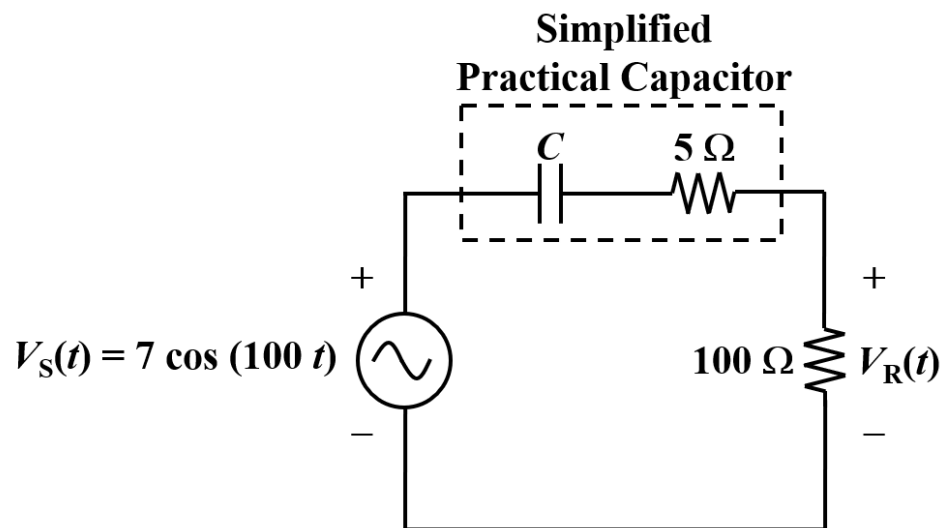

In the circuit shown in the figure above, a $100\ \Omega$ resistor is connected in series with a practical capacitor. The practical capacitor has a series resistance of $5\ \Omega$, and an unknown capacitance C . Suppose the phase angle of the voltage $V_R(t)$ is found to be 43.6° with respect to the source voltage $V_s(t)$, the capacitance C can be obtained as:

- (A) $10\ \mu\text{F}$
- (B) $100\ \mu\text{F}$
- (C) $1\ \text{mF}$
- (D) $10\ \text{mF}$

END OF PAPER