

CG1111: Engineering Principles and Practice I

Debrief and Tutorial for Week 3



Main Concepts & Topics

- Energy, Power & Efficiency:

- Instantaneous power:

- ✓ $P = \frac{dW(t)}{dt}$

- Efficiency

- ✓ $\eta = \frac{P_{out}}{P_{in}} = \frac{P_{out}}{P_{out} + P_{Total Loss}}$

- C-rate of battery

- ✓ A "1C" **rate** means that the discharge current will discharge the entire battery in 1 hour


Main Concepts & Topics

- Series vs Parallel Connection of Batteries


Two Batteries connected in Series: double the voltage but have the same capacity

Two Batteries connected in Parallel: double the capacity but have the same voltage

Battery Discharging Characteristics

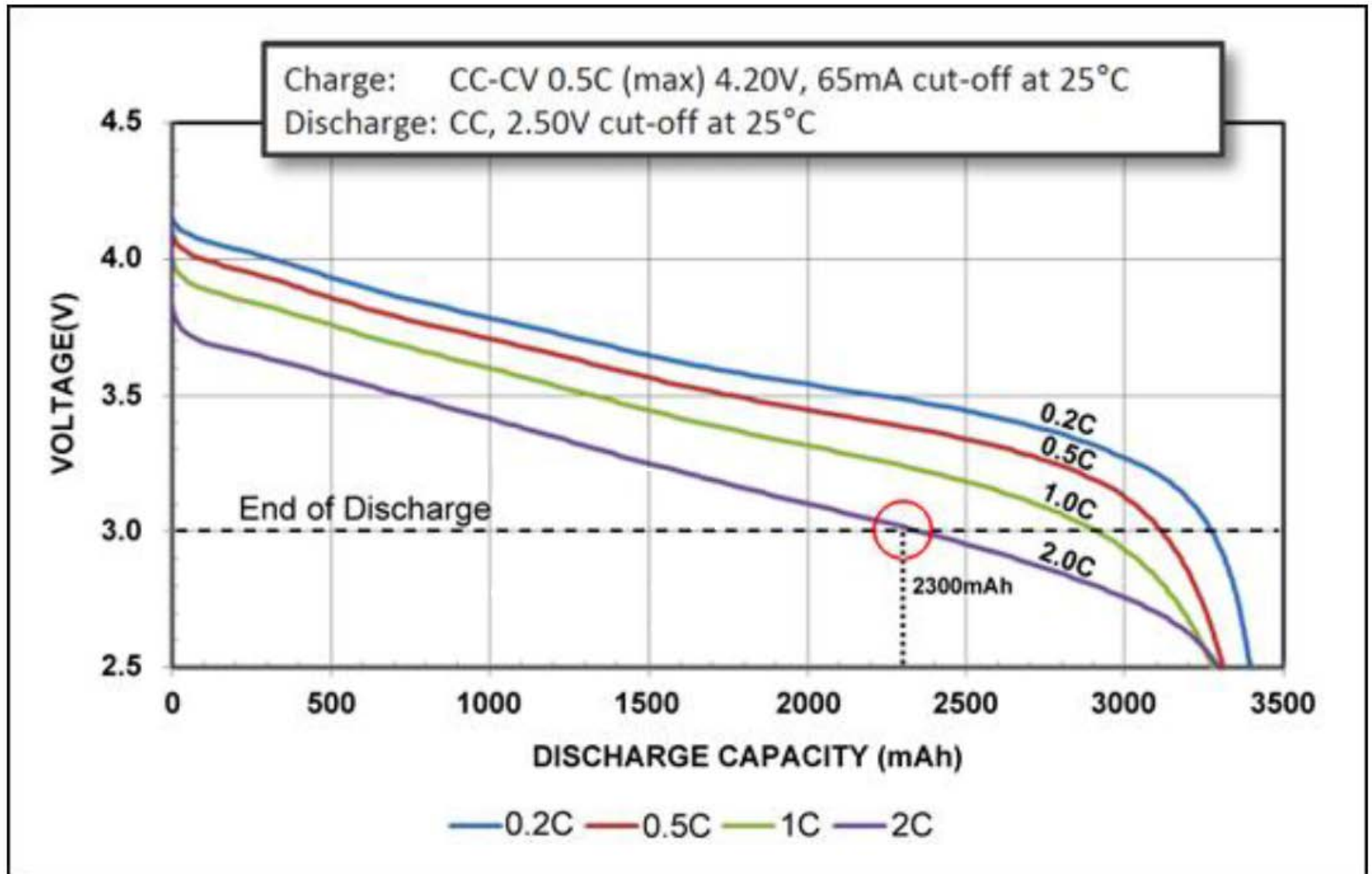

Battery Design

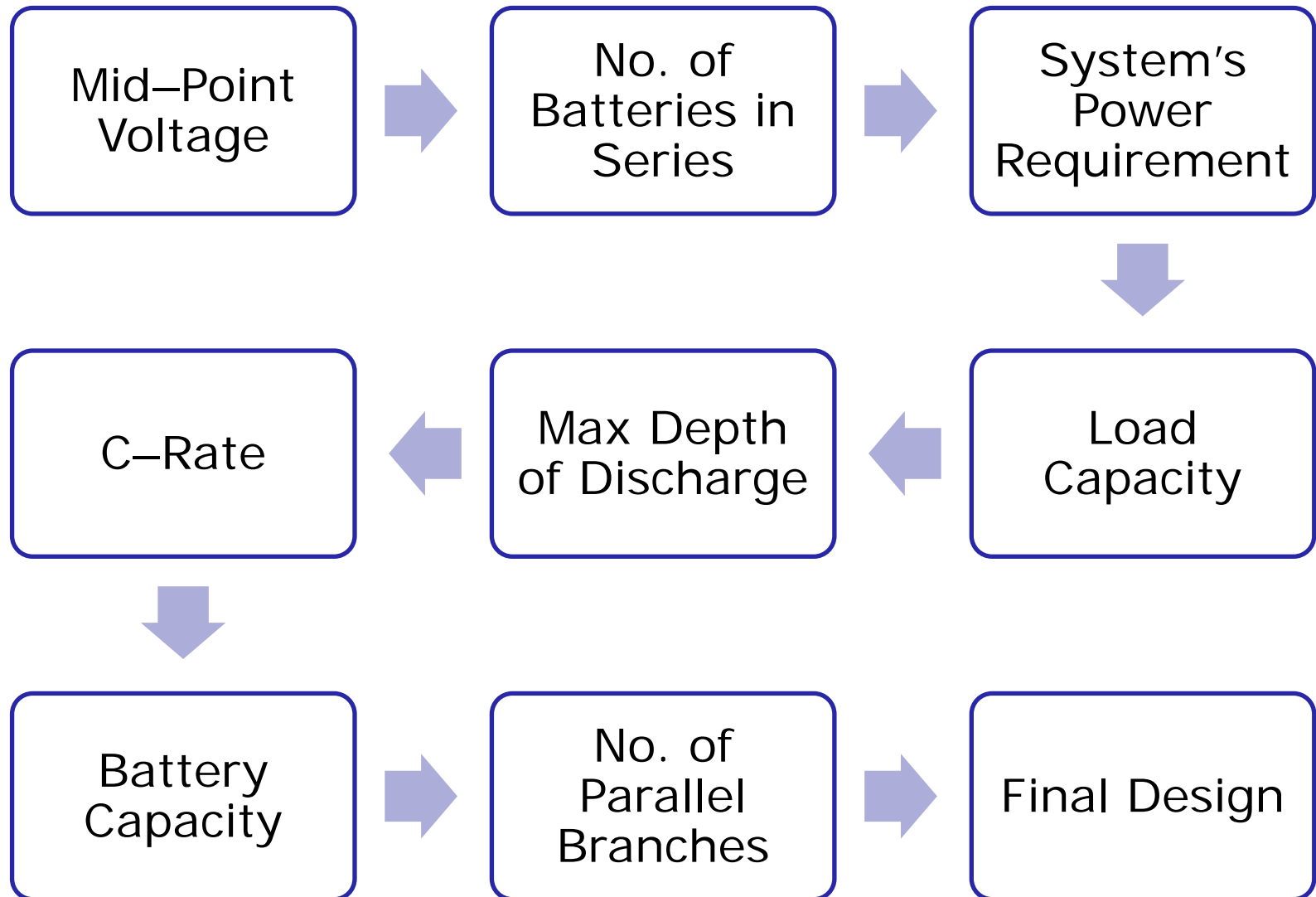

Main Concepts & Topics

- Fundamentals of electricity:

- What is Resistance?

- ✓ All materials present some opposition to electric current

- Ohm's Law

- ✓ Empirical observation that $V \propto I$ for purely resistive element, and resistance is defined as V/I


- How is electrical power calculated?

- ✓ $P = VI$ (always true regardless of type of element)
 - ✓ For resistors, we have $P = I^2R$ because $V = IR$

- Never, never use $P = I^2R$ for non-resistive elements (e.g., LEDs)!!

Main Concepts & Topics

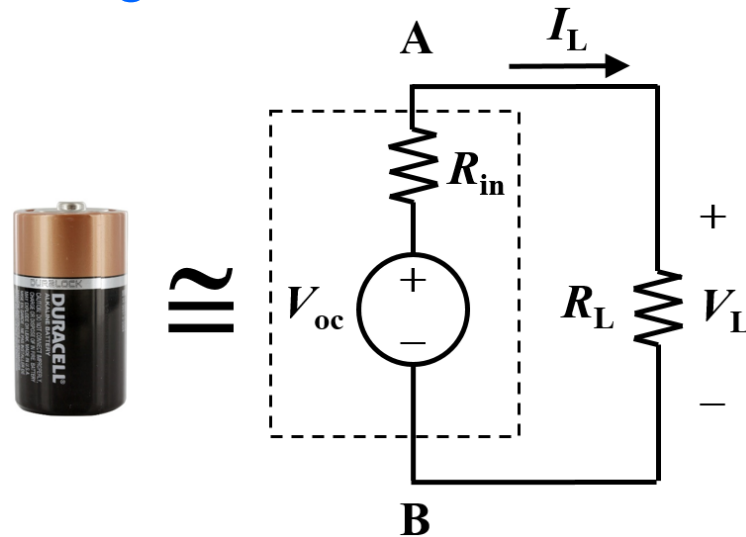- Basic circuit concepts
 - Practical voltage sources have internal resistances



- How do we go about measuring voltage & current?
 - ✓ Connect voltmeter in parallel;
ammeter in series

Main Concepts & Topics

- Principles & techniques for circuit analysis

- KCL (conservation of mass/charge)

- ✓ The sum of all currents entering the node must be equal to the sum of all currents leaving the node

- KVL (conservation of energy & power)

- ✓ Around any closed loop, the sum of voltage drops must equal the sum of voltage rises

- Resistances in series/parallel (derived from KVL/KCL)

- ✓ Series: $R_{eq} = R_1 + R_2 + \dots + R_N$
 - ✓ Parallel: $1/R_{eq} = 1/R_1 + 1/R_2 + \dots + 1/R_N$

Question 1

Calculate the total capacity of a battery given that it can provide a current of 3 A for 9 hrs

- Capacity normally calculated as:

Current x Time (in hrs)

- Hence, capacity = 3 A x 9 hrs
= 27 Ah or 27,000 mAh

Question 2

How long would a 6000 mAh battery last if it is operated at 10C rate?

- Operating time (hrs) = $1 / \text{C-rate}$
= 0.1 hrs or 6 mins

Question 3

An electric device has an input power of 100 W. The device has converted 4500 J into useful work in 1 min. Find the power efficiency of the device.

- Output power
= (work done in J)/(time in s)
= 4500 J / 60 s
= 75 W
- Hence, efficiency = $P_{\text{out}} / P_{\text{in}}$
= 75 / 100 = 75%

Question 4

What is the discharging C-rate of a battery of capacity 6000 mAh if the discharge current is 3 A?


- Remember: 1C is the current that discharges the battery in 1 hr
- Hence, in this case, 1C is 6 A
- So, 3 A is 0.5C

Question 5

Consider the following battery with open-circuit voltage $V_1 = 12\text{ V}$, and internal resistance $R_1 = 0.15\ \Omega$. Find the load current I_L and the corresponding power efficiency η_L for the following load:

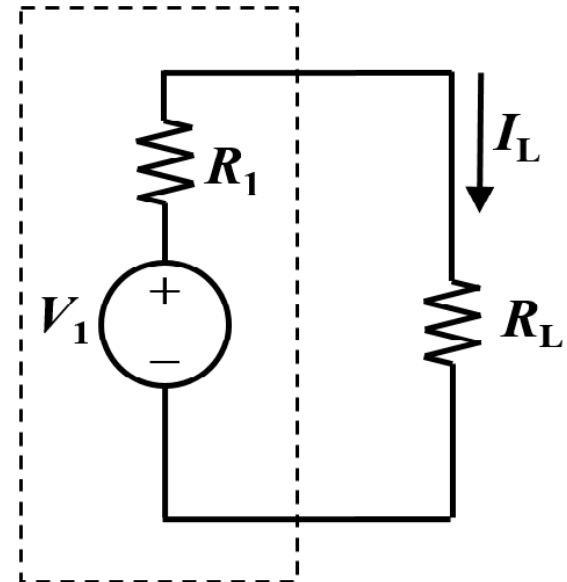(i) $R_L = 10\ \Omega$


- $I_L = 12 / (10 + 0.15)$
 $= 1.18\text{ A}$
- $\eta_L = (I_L)^2 R_L / V_1 I_L$
 $= 98.5\%$



Question 5 (Cont'd)

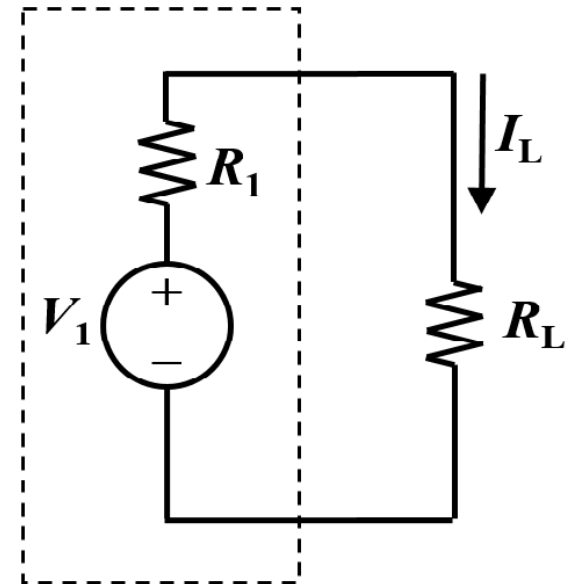(ii) $R_L = 1 \, \Omega$

- $I_L = 12 / (1 + 0.15)$
 $= 10.4 \, \text{A}$
- $\eta_L = (I_L)^2 R_L / V_1 I_L$
 $= 87.0\%$



Notice the big drop in efficiency when $I \uparrow$


A lot of power is lost in internal resistance when $I \uparrow$

Question 6


The figure below shows a loaded voltage divider circuit. Calculate the voltage difference V_{AB} (given by $V_A - V_B$).

- $150\ \Omega // 100\ \Omega$
 $= 60\ \Omega$

- $V_{AB} = 60 / (100 + 60) \times 10$
 $= 3.75\ \text{V}$

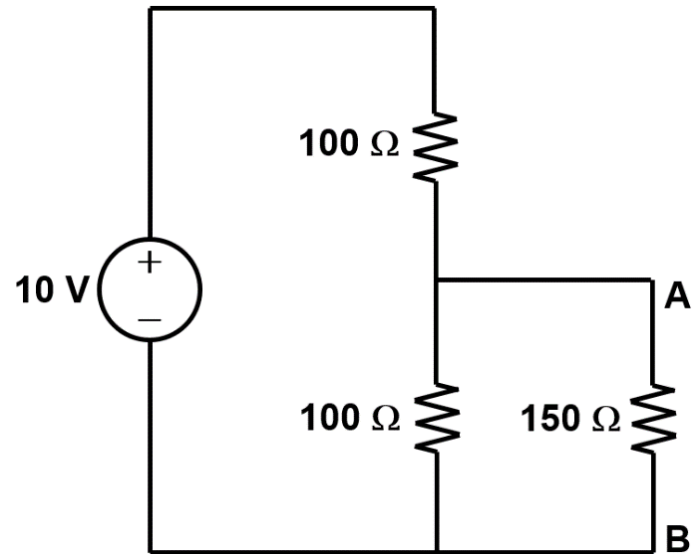

Question 7

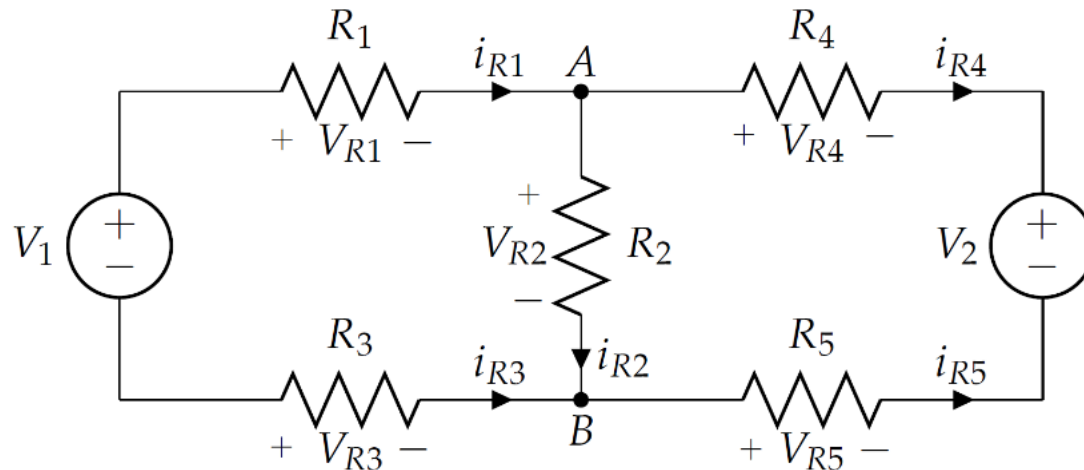

Considering the circuit diagram shown in the figure above, which one of the following correctly applies both KVL and KCL?

a) $V_1 - V_{R1} - V_{R2} - V_{R3} = 0$; ✗ $i_{R1} - i_{R2} - i_{R4} = 0$ ✓

b) $V_1 + V_{R3} - V_{R1} - V_{R2} = 0$; ✓ $i_{R1} + i_{R3} = 0$ ✓

c) $V_2 + V_{R4} + V_{R2} + V_{R5} = 0$; ✗ $i_{R4} + i_{R5} = 0$ ✓

d) $V_2 + V_{R4} - V_{R2} - V_{R5} = 0$; ✓ $i_{R3} - i_{R2} - i_{R5} = 0$ ✗