

Activity 1

Measured resistance of $2.2k\Omega$ resistor = $2.15k\Omega$

frequency = $5kHz$

$$\omega = 2\pi f = \frac{2\pi}{T}$$

$$\Rightarrow T = 0.0002s$$

peak to peak voltage = $3.3V$

$$V_{S, MAX} = 3.165V$$

$$V_{S, MIN} = 78.21mV$$

$$\Rightarrow V_{S, peak\ to\ peak} = 3.087V$$

not $3.3V$ as the source has internal resistance

$$V_{C, MAX} = 2.887V$$

$$V_{C, MIN} = 458mV$$

$$\Rightarrow V_{C, peak\ to\ peak} = 2.429V$$

CHB lagging CHA by $20\mu s$

	peak to peak (V)	Amplitude (V)	RMS (V)	measured $\Delta T (\mu s)$	phase angle	phasor
V_S	3.087	1.5435	1.0914	—	0°	$1.54 \angle 0^\circ$
V_C	2.429	1.2145	0.8588	20	-36°	$1.21 \angle -36^\circ$
V_R	1.753	0.8765	0.6198	-30	54°	$0.88 \angle 54^\circ$

V_C lagging V_S by $20\mu s$

$$\Delta T = 20\mu s$$


$$\text{phase angle} = - \frac{20\mu s}{2 \times 10^{-4}s} \times 360^\circ = -36^\circ$$

V_S lagging V_R by $30\mu s$

$$\Delta T = -30\mu s$$

$$\text{phase angle} = - \frac{-30\mu s}{2 \times 10^{-4}s} \times 360^\circ = 54^\circ$$

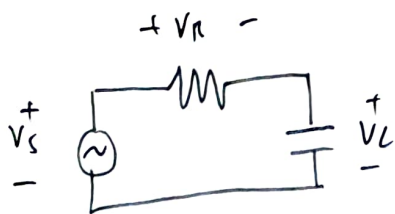11. KVL cannot be applied for RLU voltages



$$V_S - V_C - V_R = 0$$


$$1.09 - 0.85 - 0.61 \approx -0.37 \neq 0$$

violates KVL

12. $V_S = 1.54 + 0i$
 $V_C = 0.9789 - 0.7112i$
 $V_R = 0.5172 + 0.7119i$

$$V_C + V_R \approx 1.4961 \approx 1.54$$

13.

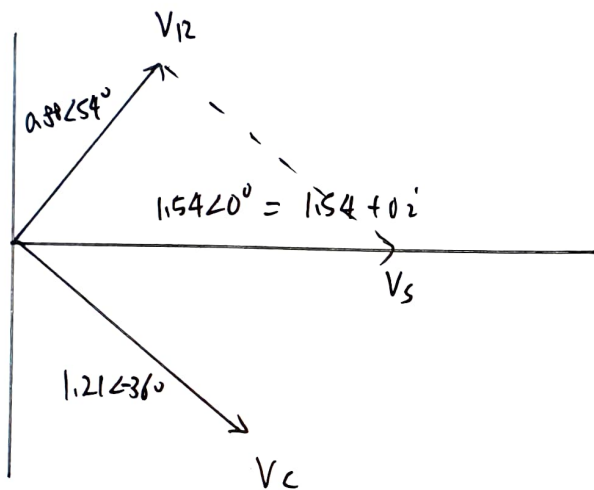

Activity 2

1. Impedance of resistor = $R \angle 0^\circ$

$$I_S = \frac{V_R}{R \angle 0^\circ} = \frac{0.88 \angle 54^\circ}{2.15 k\Omega} = 409 \mu A \angle 54^\circ$$

2. $Z_C = \frac{-j}{\omega C}$ where $\omega = 2\pi f = 10 \times 10^4 \pi$

3. $Z_C = \frac{V_C}{I_S} = \frac{1.21 \angle -36^\circ}{409 \mu A \angle 54^\circ} = 2958 \angle -90^\circ$

$$-2958j = \frac{-j}{\omega C}$$

$$C = \frac{1}{2958 \times 10 \times 10^4 \pi}$$

$$= \underline{\underline{10.7 nF}}$$